
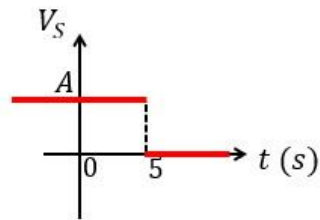


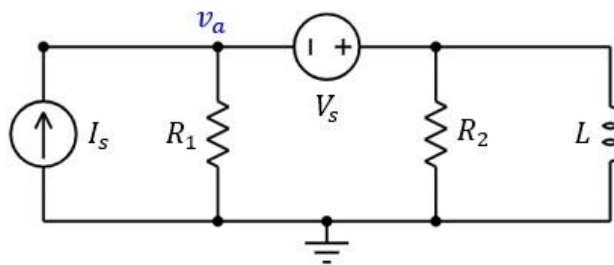Q1

The voltage source V_s changes from A to 0 at $t = 5$ s, as shown on the right. For $t < 5$ s, you may assume the system has reached steady state. The voltage v_a is a node voltage.



- (a) Find $v_a(5^-)$.
 (b) Find $v_a(t)$ for $t > 5$ s. Write the equation.



R1:	1 Ω
R2:	2 Ω
I _s :	2 A
A:	6 V
L:	2 nH

Q2


For $t < 0$ s, the switch has been opening and closing (and the capacitor may not have reached steady state).

The switch closes at time $t = 0$ s.

You are given the capacitor voltage at time $t = 4^-$ s:

$$v_C(4^-) = X$$

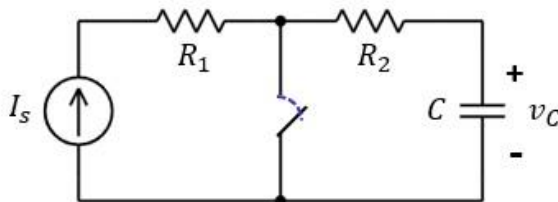- (a) Find $v_C(0^+)$. (You can leave your answer written as a function of e)
 (b) The switch opens again at time $t = 4$ s. Find $v_C(6$ s).



R1:	1 Ω
R2:	4 Ω
X:	3 V
I _s :	1 A
C:	2 F