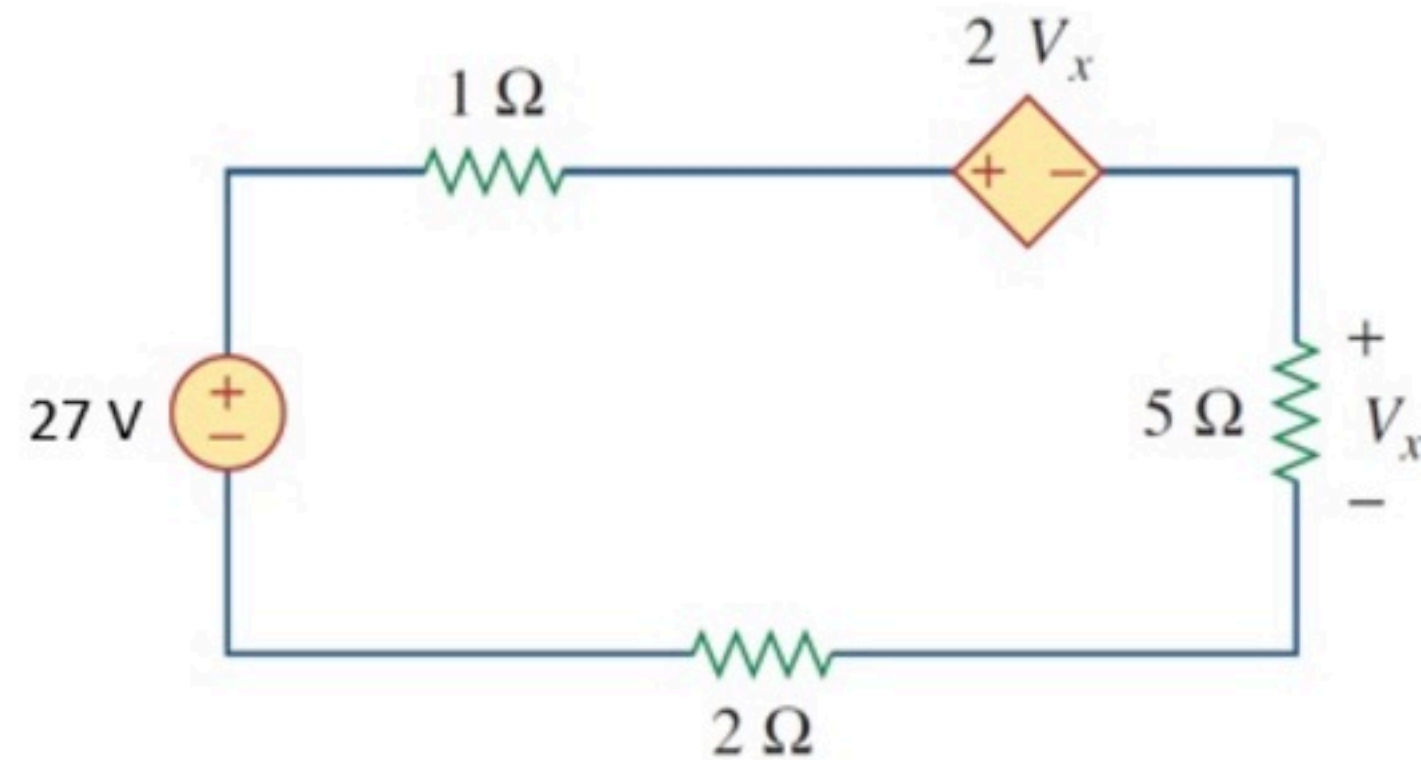


PP - Basic analysis 008

Problem has been graded.

Calculate the voltage V_x .



Given Variables:

...

Calculate the following:

V_x (V) :

7.5

