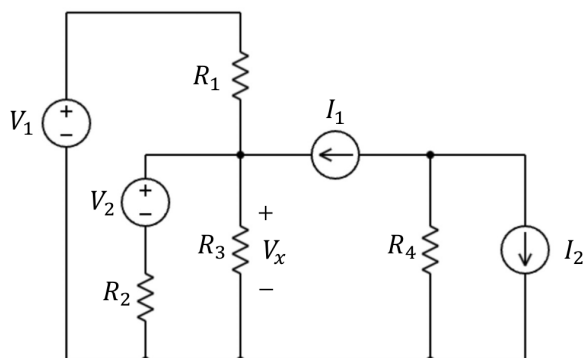


Consider the circuit below. You are not given the values of V_1 , V_2 and I_2 . However, you are told the values of the other components and that of V_x .

- (a) What is the new value of V_x when all the source values (i.e., V_1 , V_2 , I_1 and I_2) are doubled? We will call this new value V_{x1} .
- (b) What is the new value of V_x when only I_1 is doubled and the other sources are what they were originally? We will call this new value V_{x2} .

$$\begin{aligned} R_1 &= 15\Omega \\ R_2 &= 5\Omega \\ R_3 &= 15\Omega \\ R_4 &= 7\Omega \\ I_1 &= 2A \\ V_x &= 15 \end{aligned}$$



a. Generally,

$$V_x = aV_1 + bV_2 + cI_1 + dI_2 \quad \text{from linearity and superposition}$$

If all sources are doubled,

$$\begin{aligned} V_{x1} &= a(2V_1) + b(2V_2) + c(2I_1) + d(2I_2) = 2(aV_1 + bV_2 + cI_1 + dI_2) \\ &= 2V_x \\ &= 2 \cdot 15 \end{aligned}$$


$$\boxed{V_{x1} = 30V}$$

b. If only I_1 is doubled

$$\begin{aligned} V_{x2} &= aV_1 + bV_2 + c(2I_1) + dI_2 = (aV_1 + bV_2 + cI_1 + dI_2) + cI_1 \\ &= V_x + cI_1 \end{aligned}$$

find the contribution of I_1 using superposition

When only I_1 is on,

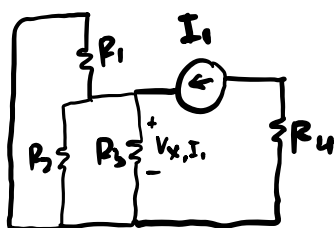

$$\begin{aligned} V_{x,I_1} &= I_1 \left(\frac{R_1 // R_2}{R_1 // R_2 + R_3} \right) R_3 \\ V_{x,I_1} &= 2 \left(\frac{\frac{15}{4}}{\frac{15}{4} + 15} \right) 15 \\ &= 2 \left(\frac{15}{15 + 60} \right) 15 \\ &= 2 \cdot \frac{1}{5} \cdot 15 \\ &= 6V \Rightarrow cI_1 \end{aligned}$$

$$\begin{aligned} V_{x2} &= V_x + cI_1 \\ &= 15 + 6 \end{aligned}$$

$$\boxed{V_{x2} = 21V}$$