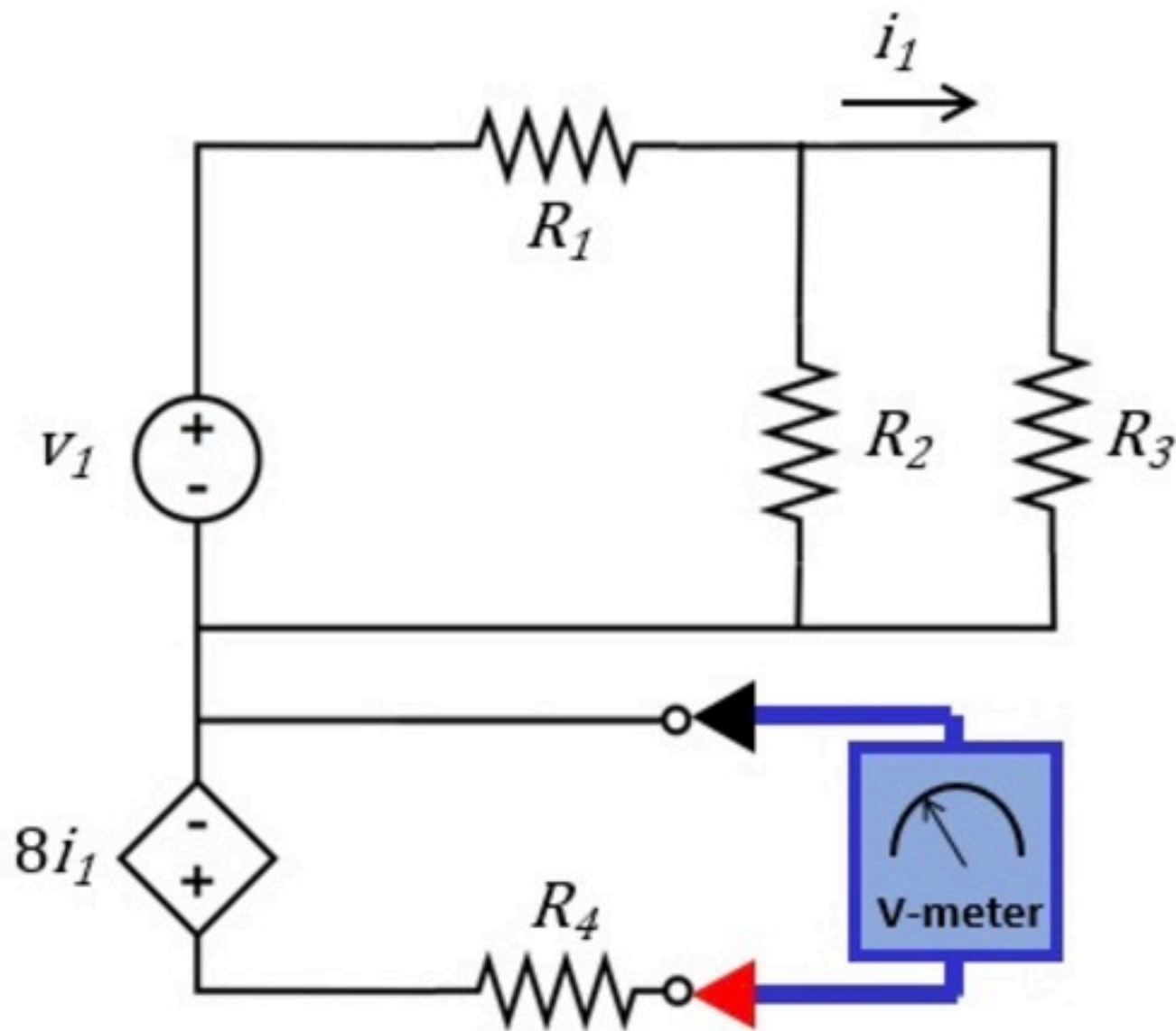


# Basic analysis 008

Problem has been graded.

Find the volt meter reading X.



Given Variables:

$v_1$  : 20 V

$R_1$  : 10 ohm

$R_2$  : 15 ohm

$R_3$  : 10 ohm

$R_4$  : 20 ohm

Calculate the following:

X (V) :

Hint: Mind the direction of the V meter