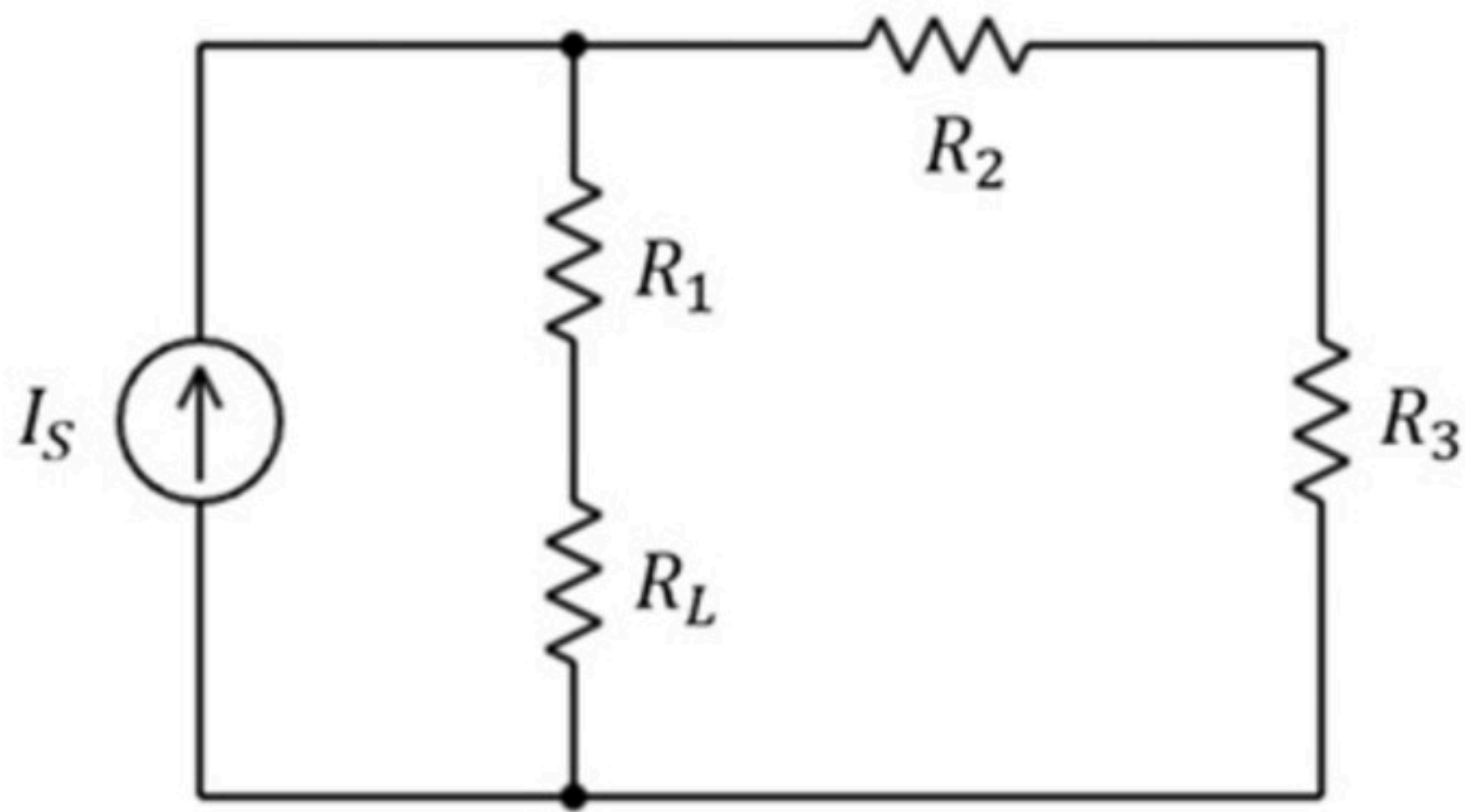


Circuit theorems 016

Problem has been graded.

Find the value of R_L such that the power received by R_L is maximized.

Find the corresponding max power received by R_L .



Given Variables:

I_S : 2 A

R_1 : 2 ohm

R_2 : 1 ohm

R_3 : 1 ohm

Calculate the following:

R_L (ohm) :

P_{\max} (W) :

Hint: Find the Thevenin equivalent model of the circuit after taking out R_L .

Find the value of R_L such that the power received by R_L is maximized.


Find the corresponding max power received by R_L .

$$I_S = 2A$$


$$R_1 = 12\Omega$$

$$R_2 = 2\Omega$$

$$R_3 = 2\Omega$$

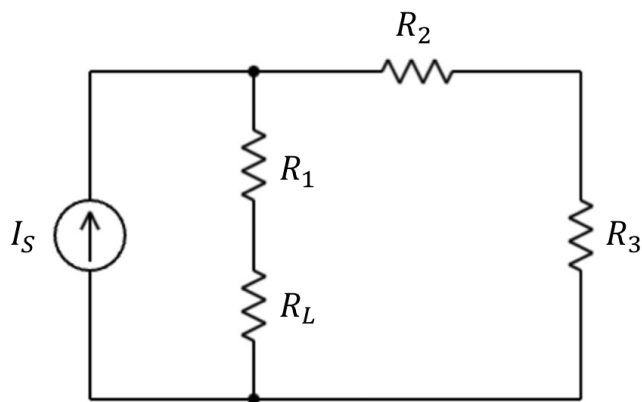

find R_{Th}

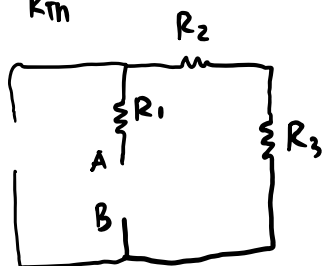


R_1, R_2, R_3 are in series

$$R_{Th} = R_1 + R_2 + R_3$$

$$= 12 + 2 + 2$$

$$R_{Th} = 16\Omega$$

find V_{Th}

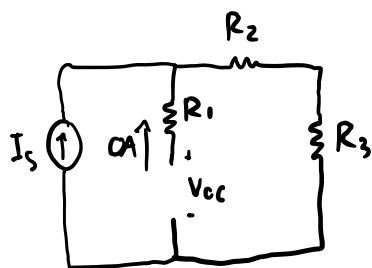

$$V_{OC} = I_S \cdot (R_2 + R_3)$$

$$= 2 \cdot (2 + 2)$$

$$V_{OC} = 8V$$

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}}$$

$$= \frac{8^2}{4(16)}$$

$$P_{max} = 1W$$