

Name

PID

**UNIVERSITY OF CALIFORNIA, SAN DIEGO**

Electrical and Computer Engineering Department

ECE 65 – Spring 2021

*Components and Circuits lab*


Final Exam

You should submit your handwritten solutions in a PDF format to Gradescope on Thursday, 6/10, by 2:30 pm (Pacific Time).

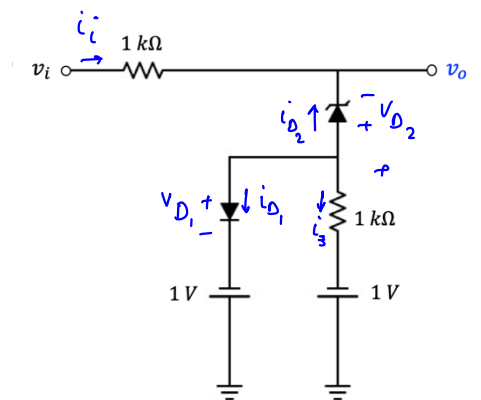**Problem 1.** (10 points)

The diodes in the below circuit have  $V_{D0} = 0.7\text{ V}$ , and  $V_Z = 5\text{ V}$ .

- Write the possible cases of the operation of the diodes.
- For each case, include the calculation of finding the relationship between  $v_o$  and  $v_i$  and the range of  $v_i$ .
- Sketch the output signal when  $v_i = \sin(\omega t)$ . You do not need to label the time axis.



**Show your work.**

Case 1:  $D_2$  in Zener &  $D_1$  is off

Case 2:  $D_2$  in Zener &  $D_1$  is on

Case 3:  $D_2$  is on &  $D_1$  is off

Case 4:  $D_1$  &  $D_2$  off

$$i_i = -i_{D_2} \quad \text{and} \quad i_{D_1} + i_{D_2} + i_3 = 0$$

Case 1 analysis:

$D_2$  in Zener &  $D_1$  is off

$$V_{D_2} = -V_Z, \quad i_{D_2} \leq 0, \quad i_{D_1} = 0, \quad v_{O_1} < V_{O_0}$$

KVL 1:


$$v_i = 1k\Omega \times i_i - V_{D_2} + 1k\Omega \times i_3 - 1$$

$$i_i = -i_{D_2} \quad \text{and} \quad i_{D_1} + i_{D_2} + i_3 = 0 \rightarrow i_3 = -i_{D_2}$$

$$v_i = 1k\Omega \times (-i_{D_2}) + 5 + 1k\Omega \times (-i_{D_2}) - 1$$

$$\rightarrow i_{D_2} = \frac{-v_i + 4}{2k\Omega} \quad i_{D_2} \leq 0 \Rightarrow v_i \geq 4V$$

$V_{D_1}$  must also be less than  $0.7V$

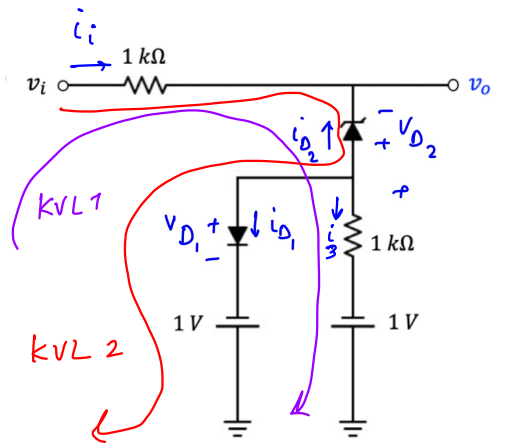

KVL 2:

$$v_i = 1k\Omega \times i_i - V_{D_2} + V_{D_1} - 1 = 1k\Omega \times (-i_{D_2}) + 4 + V_{D_1}$$

$$v_i = 1k\Omega \times \left( \frac{-v_i + 4}{2k\Omega} \right) + 4 + V_{D_1} \rightarrow \frac{1}{2}v_i - 2 = V_{D_1}$$

$$V_{D_1} < V_{O_0} \rightarrow \frac{1}{2}v_i - 2 < 0.7V \rightarrow v_i < 5.4V$$

the range of  $v_i$  for this case is  $4 \leq v_i < 5.4V$

$$v_o = -V_{D_2} + 1k\Omega \times i_3 - 1 = 5V + 1k\Omega \times (-i_{D_2}) - 1 = 4V + 1k\Omega \times \frac{v_i - 4}{2k\Omega}$$

$$v_o = \frac{1}{2}v_i + 2$$

Case 2 analysis:

$D_2$  in Zener &  $D_1$  is ON

$$V_{O_2} = -V_Z, \quad i_{D_2} \leq 0, \quad i_{D_1} \geq 0, \quad V_{O_1} = V_{O_0}$$

KVL 1:

$$V_i = 1k\Omega \times i_i - V_{D_2} + 1k\Omega \times i_3 - 1$$

$$i_i = -i_{D_2} = i_{D_1} + i_3$$

KVL 3:


$$1V - V_{D_1} + 1k\Omega \times i_3 - 1 = 0 \quad \Rightarrow \quad 1k\Omega \times i_3 = V_{D_1}$$

$$V_i = 1k\Omega \times (i_{D_1} + \frac{0.7}{1k\Omega}) + 5 + 0.7 - 1 \quad \rightarrow \quad i_{D_1} = \frac{V_i - 5.4}{1k\Omega}$$

$$i_{D_1} \geq 0 \rightarrow V_i \geq 5.4V$$

the range of  $V_i$  for this case is  $V_i \geq 5.4V$
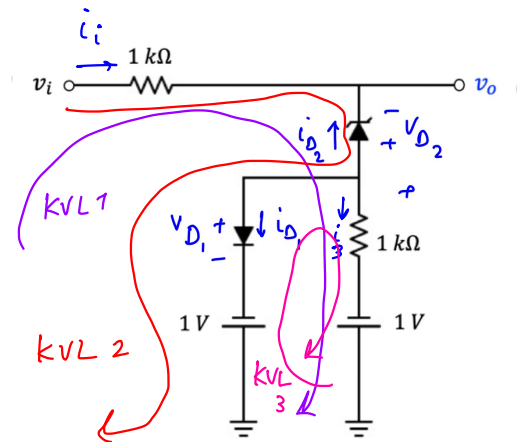
$$V_0 = -V_{D_2} + V_{D_1} - 1 = 4.7V \rightarrow V_0 = 4.7V$$



Case 3 analysis:

$D_2$  is on &  $D_1$  is off

$$V_{D_2} = V_o, \quad i_{D_2} \geq 0, \quad i_{D_1} = 0, \quad V_{D_1} < V_o$$

KVL 1:

$$V_i = 1k\Omega \times i_i - V_{D_2} + 1k\Omega \times i_3 - 1$$


$$i_i = -i_{D_2}, \quad i_3 = -i_{D_2}$$

$$V_i = 1k\Omega \times (-i_{D_2}) - 0.7 + 1k\Omega \times (-i_{D_2}) - 1$$

$$\rightarrow i_{D_2} = \frac{-V_i - 1.7}{2k\Omega} \quad i_{D_2} \geq 0 \Rightarrow V_i \leq -1.7V$$

$$V_o = 1k\Omega \times (-i_i) + V_i = 1k\Omega \times (i_{D_2}) + V_i = -\frac{V_i}{2} - \frac{1.7}{2} + V_i = \frac{1}{2} V_i - \frac{1.7}{2}$$
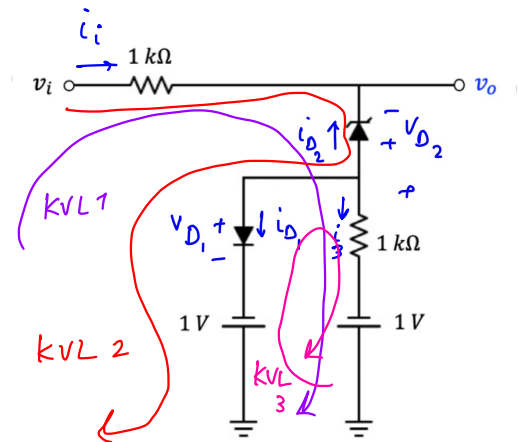
$$V_o = \frac{1}{2} V_i - \frac{1.7}{2} V$$



Case 4 analysis:



$D_2$  &  $D_1$  are off

$$-V_2 < V_{D_2} < V_{D_0}, \quad i_{D_2} = 0, \quad i_{D_1} = 0, \quad V_{D_1} < V_{D_0}$$

$$-1.7 \text{ V} < V_i < 4 \text{ V}$$

$$V_o = 1 \text{ k}\Omega \times (-i_i) + V_i = V_i \rightarrow V_o = V_i$$


c)  $V_i(t) = \sin \omega t \rightarrow$  The amplitude of  $V_i$  will change between  $-1 \text{ V}$  and  $1 \text{ V}$ . Both diodes will be off in this range.  $\Rightarrow V_o(t) = \sin \omega t$

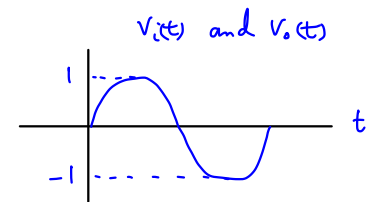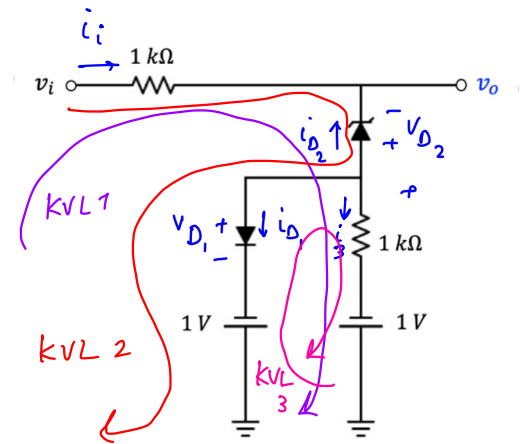

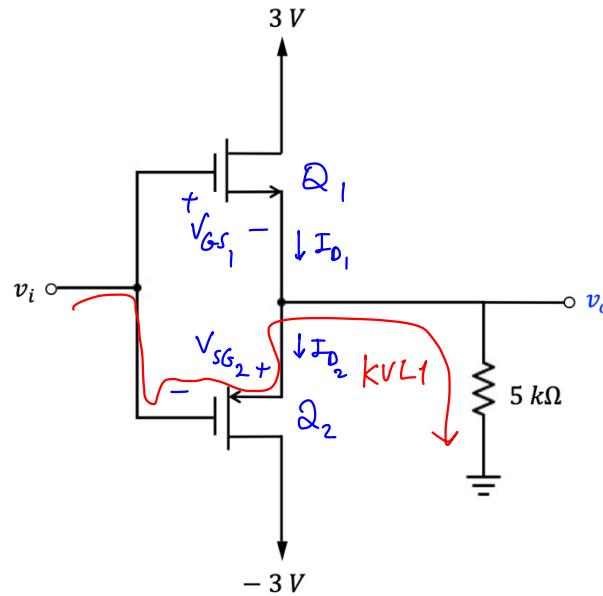**Problem 2.** (10 points)

In the following circuit,  $V_{tn} = -V_{tp} = 1\text{ V}$ ,  $k_n = k_p = 0.5\text{ mA/V}^2$ , and  $\lambda = 0$  for both transistors.

If  $v_i = -3\text{ V}$ , find the drain currents of both transistors and  $v_o$ .



**Show your work.**

Assume both  $Q_1$  &  $Q_2$  are off :  $I_{D1} = I_{D2} = 0$  &  $V_{GS1} < V_{tn}$  &  $V_{GS2} < |V_{tp}|$

KVL1 :  $V_i = -V_{SG2} + V_o = -V_{SG2} \rightarrow V_{SG2} = 3\text{ V} > 1\text{ V} \Rightarrow$  assumption is wrong.

$V_{GD2} = 0\text{ V} \Rightarrow Q_2$  is in saturation.  $I_{D2} = \frac{1}{2} k_p V_{OV2}^2 = \frac{1}{2} \times \frac{1}{2} \times V_{OV2}^2$

From KVL1 :  $V_i = -V_{SG2} - 5k\Omega \times I_{D2} \rightarrow -3\text{ V} = -V_{SG2} - 5k\Omega \times I_{D2}$

$-|V_{tp}| + V_{SG2} = 3\text{ V} - 5k\Omega \times I_{D2} - |V_{tp}| \rightarrow V_{OV2} = 2\text{ V} - 5k\Omega \times I_{D2} \rightarrow V_{OV2} = 1.73\text{ V}$

Assume  $Q_1$  is ON and  $Q_2$  is off

$$Q_1 \text{ is ON} \rightarrow V_{ov_1} \geq 0 \text{ and } I_{D_1} \geq 0 \rightarrow V_{S_1} = 5k\Omega \times I_{D_1} \geq 0$$

$$V_{G_1} = V_i = -3V, \quad V_{GS_1} = -3 - V_{S_1} \leq -3 \rightarrow V_{ov_1} = V_{GS_1} - V_{tn} = -4 - V_{S_1} \leq -4V$$

$$V_{ov_1} < 0 \rightarrow Q_1 \text{ is not ON.}$$

assumption was wrong.

Assume  $Q_1$  is off and  $Q_2$  is ON

$$V_{GD_2} = 0V \Rightarrow Q_2 \text{ is in saturation. } I_{D_2} = \frac{1}{2} k_p V_{ov_2}^2 = \frac{1}{2} \times \frac{1}{2} \times V_{ov_2}^2$$

$$\text{From KVL 1: } V_i = -V_{SG_2} - 5k\Omega \times I_{D_2} \rightarrow -3V = -V_{SG_2} - 5k\Omega \times I_{D_2}$$

$$-|V_{tp}| + V_{SG_2} = 3V - 5k\Omega \times I_{D_2} - |V_{tp}| \rightarrow V_{ov_2} = 2V - 5k\Omega \times I_{D_2}$$

$$5V_{ov_2}^2 + 4V_{ov_2} - 8 = 0$$

$$\begin{cases} I_{D_2} = \frac{1}{2} k_p V_{ov_2}^2 = \frac{1}{2} \times \frac{1}{2} \times V_{ov_2}^2 \\ V_{ov_2} = 2V - 5k\Omega \times I_{D_2} \end{cases} \rightarrow V_{ov_2} = 2V - 5 \times \frac{1}{4} V_{ov_2}^2 \rightarrow V_{ov} = 0.93V$$

$$I_{D_2} = \frac{1}{2} \times \frac{1}{2} \times V_{ov_2}^2 = \frac{1}{4} (m\cancel{A}/\cancel{V^2}) \times (1.73)^2 \rightarrow I_{D_2} = 0.216 \text{ mA}$$

$$V_o = -5k\Omega \times I_{D_2} = -1.08V$$


$$V_o = -1.08V$$



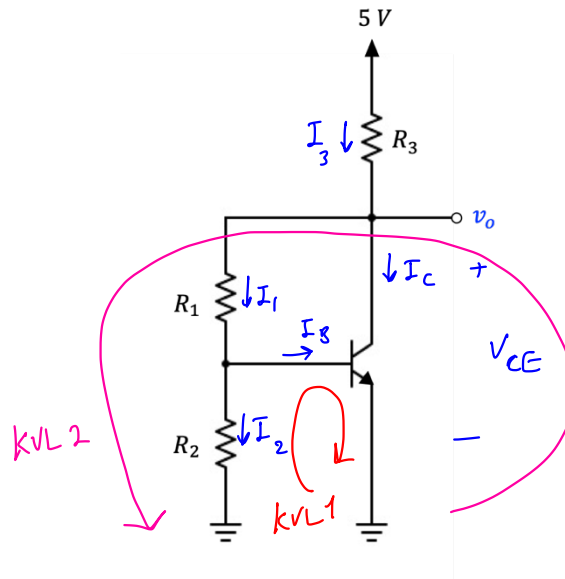**Problem 3** (5 points)

Design the following circuit (find the resistor values) to have  $I_C = 1 \text{ mA}$  and  $V_C = 2.5 \text{ V}$ . Assume  $\beta = 100$ ,  $V_D = 0.7 \text{ V}$ , and  $V_{sat} = 0.2 \text{ V}$ .

The resistors must have finite non-zero values.



Show your work.

$$I_C = 1 \text{ mA} > 0 \Rightarrow \text{BJT is ON} \Rightarrow V_{BE} = 0.7 \text{ V}$$

$$V_{CE} = V_C - V_E = V_C - 0 = V_C = 2.5 \text{ V}$$

$$V_{CE} > V_{D_0} \Rightarrow \text{BJT is in active mode.} \Rightarrow I_C = \beta I_B$$

$$\text{KVL 1: } R_2 I_2 = V_{BE} = 0.7 \text{ V}$$

$$\text{KVL 2: } V_{CE} = R_1 I_1 + R_2 I_2 = R_1 I_1 + 0.7 \text{ V} \Rightarrow R_1 I_1 = 1.8 \text{ V}$$

KVL 3:

$$5V = R_3 I_3 + V_{CE} \Rightarrow R_3 I_3 = 2.5V$$

KCL at Collector:  $I_3 = I_C + I_1 = 1mA + I_1$

KCL at Base:  $I_1 = I_B + I_2 = 0.01mA + I_2$

Choose  $R_2 = 10k \rightarrow I_2 = \frac{0.7V}{10k} = 0.07mA$


$$I_1 = I_B + I_2 = 0.08mA$$

$$R_1 I_1 = 1.8V \rightarrow R_1 = \frac{1.8V}{0.08mA} = 22.5k\Omega$$

$$R_1 = 22.5k\Omega$$

$$I_3 = I_C + I_1 = 1.08mA$$
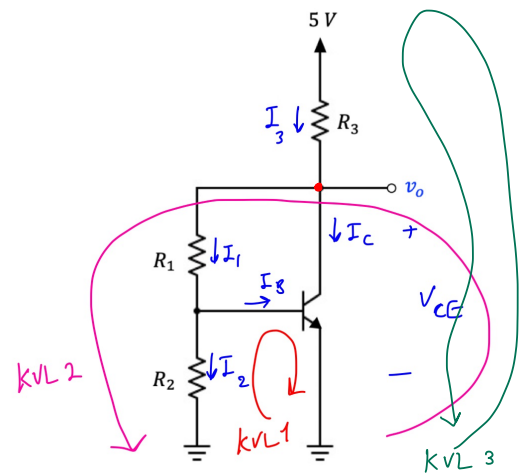
$$R_3 I_3 = 2.5V \rightarrow R_3 = \frac{2.5V}{1.08mA} = 2.32k\Omega$$



$$R_1 I_1 = 1.8V$$

$$R_2 I_2 = 0.7V$$

$$R_3 = 2.32k\Omega$$

**Problem 4**


In the below amplifier circuit,

- Find the DC emitter currents and the DC Base node voltages of  $Q_1$  and  $Q_2$
- Find the small signal parameters ( $g_m$  and  $r_\pi$ ) for  $Q_1$  and  $Q_2$ .
- Draw the small signal equivalent circuit.
- If a load resistance  $R_L = 10\text{ k}\Omega$  is connected to the output terminal, and a signal source with  $R_{sig} = 0$  is connected to the input terminal, find  $A = \frac{v_o}{v_{sig}}$ .

Assume  $Q_1$  has  $\beta_1 = 60$  and  $Q_2$  has  $\beta_2 = 100$ ,  $V_{D0} = 0.7V$ ,  $V_T = 25mV$ . Neglect the early effect in the bias and signal circuits. The capacitors are short for the signal circuit.

Hint: The input resistance of the second stage will act as the load resistor for the first stage.

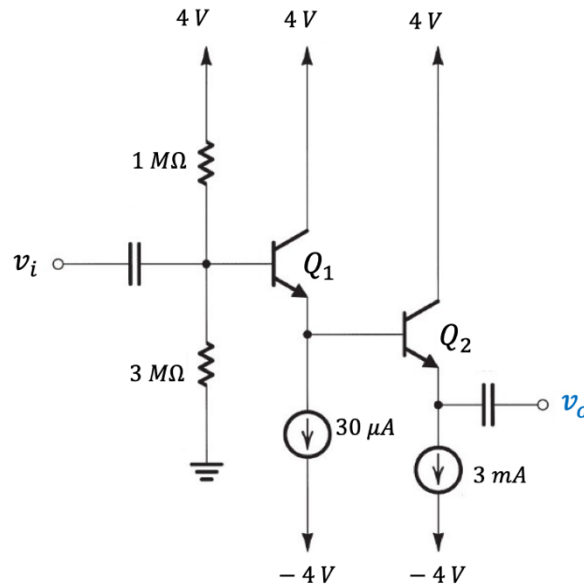For a common-collector amplifier use  $A_{vo} = \frac{(1/g_m) \parallel r_\pi \parallel R_E \parallel r_o}{(1/g_m) \parallel r_\pi}$ .



**Show your work.**

Bias circuit:

a)  $I_{E_2} = 3 \text{ mA}$


KCL at Emitter of  $Q_1$ :  $I_{E_1} = I_{B_2} + 30 \mu\text{A}$

This is an amplifier circuit so the BJTs will be in active mode.


$$I_{B_2} = \frac{I_{E_2}}{1 + \beta_2} = \frac{3 \text{ mA}}{101} = 29.7 \mu\text{A}$$

$$I_{E_1} = 29.7 \mu\text{A} + 30 \mu\text{A} = 59.7 \mu\text{A}$$

$I_{E_1} = 59.7 \mu\text{A}$

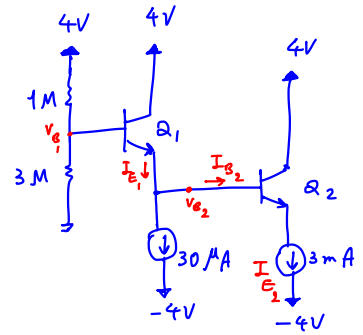

The Thevenin equivalent

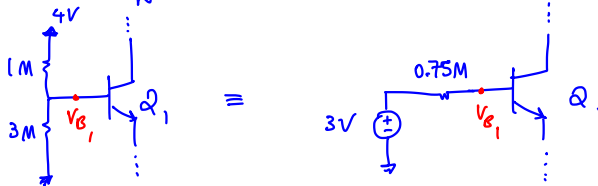

$$V_{B_1} = 3 \text{ V} - 0.75 \text{ M}\Omega \times I_{B_1}$$

$$I_{B_1} = \frac{I_{E_1}}{1 + \beta_1} = \frac{59.7 \mu\text{A}}{61} \approx 0.98 \mu\text{A}$$

$$V_{B_1} = 3 \text{ V} - 0.75 \times 0.98 = 2.265 \text{ V}$$

$V_{B_1} = 2.265 \text{ V}$

$$V_{B_2} = V_{E_1} = V_{B_1} - V_{BE_1} = 2.265 - 0.7 = 1.565 \text{ V}$$

$V_{B_2} = 1.565 \text{ V}$

b)



$$g_{m_2} = \frac{I_{C_2}}{V_T} = \frac{3 \text{ mA} \times \frac{100}{101}}{25 \text{ mV}} \approx 118.8 \text{ mA/V}$$

$$g_{m_1} = \frac{I_{C_1}}{V_T} = \frac{59.7 \mu\text{A} \times \frac{60}{61}}{25 \text{ mV}} = 2.35 \text{ mA/V}$$

$$r_{\pi_2} = \frac{\beta_2}{g_{m_2}} = 842 \Omega$$

$$r_{\pi_1} = \frac{\beta_1}{g_{m_1}} = 25.53 \text{ k}\Omega$$

small signal circuit:

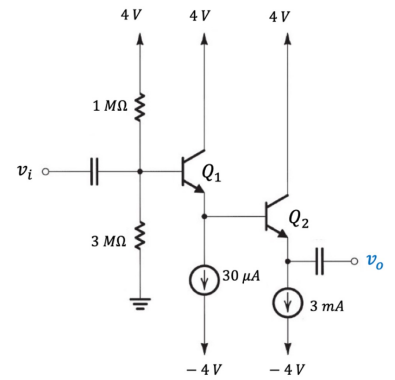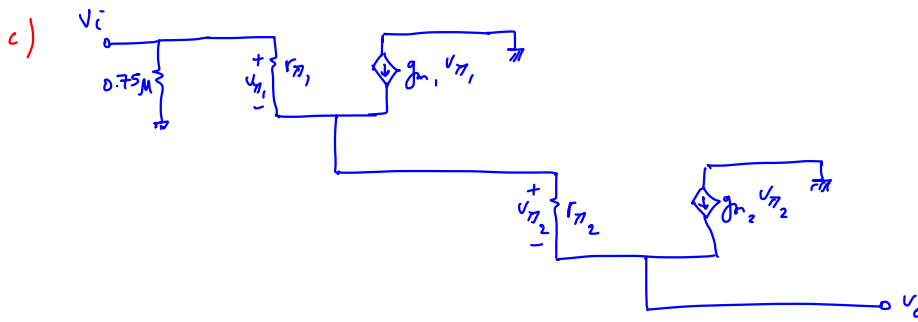

d) We will find  $R_{i1}$ ,  $R_{i2}$ ,  $R_{o1}$ ,  $R_{o2}$ ,  $A_{v_{o1}}$ ,  $A_{v_{o2}}$ , and use the voltage amplifier model to answer this question.



$$g_{m2} = 118.8 \text{ mA/V}$$

$$r_{\pi2} = 842 \Omega$$

$$R_{o2} = \frac{1}{g_{m2}} \parallel r_{\pi2} \approx 8.32 \Omega$$

$$R_{o1} = \frac{1}{g_{m1}} \parallel r_{\pi1} \approx 418 \Omega$$

$$A_{v_{o2}} = \frac{\frac{1}{g_{m2}} \parallel r_{\pi2}}{\frac{1}{g_{m2}} \parallel r_{\pi2}} = 1 \text{ V/V}$$

$$g_{m1} = 2.35 \text{ mA/V}$$

$$r_{\pi1} = 25.53 \text{ k}\Omega$$

$$R_{i2} = r_{\pi2} + (\beta_2 + 1)R_L \approx 7010.8 \text{ k}\Omega$$

$$R_{i1} = R_{B1} \parallel [r_{\pi1} + (\beta_1 + 1)R_{i2}] \approx 741 \text{ k}\Omega$$

$$A_{v_{o1}} = \frac{\frac{1}{g_{m1}} \parallel r_{\pi1}}{\frac{1}{g_{m1}} \parallel r_{\pi1}} = 1 \text{ V/V}$$



$$\frac{V_o}{V_{sig}} = \frac{R_L}{R_L + R_{o2}} \cdot A_{v_{o2}} \cdot \frac{R_{i2}}{R_{i2} + R_{o1}} \cdot A_{v_{o1}} \cdot \frac{R_{i1}}{R_{i1} + R_{sig}}$$

$$\frac{V_o}{V_{sig}} = 0.997 \quad V/V$$

