

# **ECE 65: Components & Circuits Lab**

## **Amplifier practice problems**


Reference notes: sections 6.1, 6.2

Sedra & Smith (7<sup>th</sup> Ed): section 7.3

Saharnaz Baghdadchi

# Course map
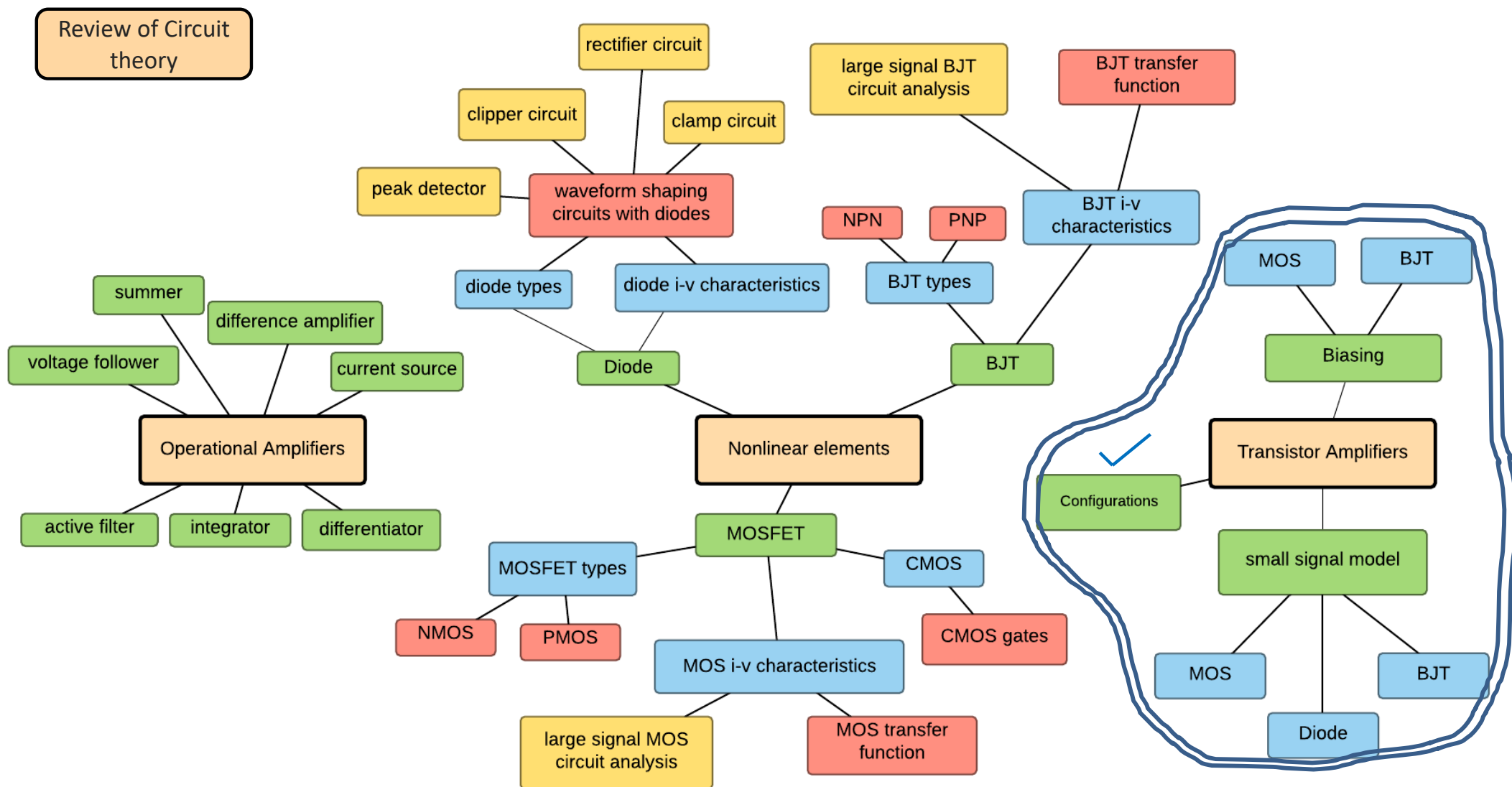
## 7. Transistor Amplifier Configurations




## Practice problem 1.

The below BJT amplifier circuit is biased with a constant current source ( $I$ ). Design the circuit (find  $I$ ,  $R_B$ , and  $R_C$ ) to meet the following specifications:


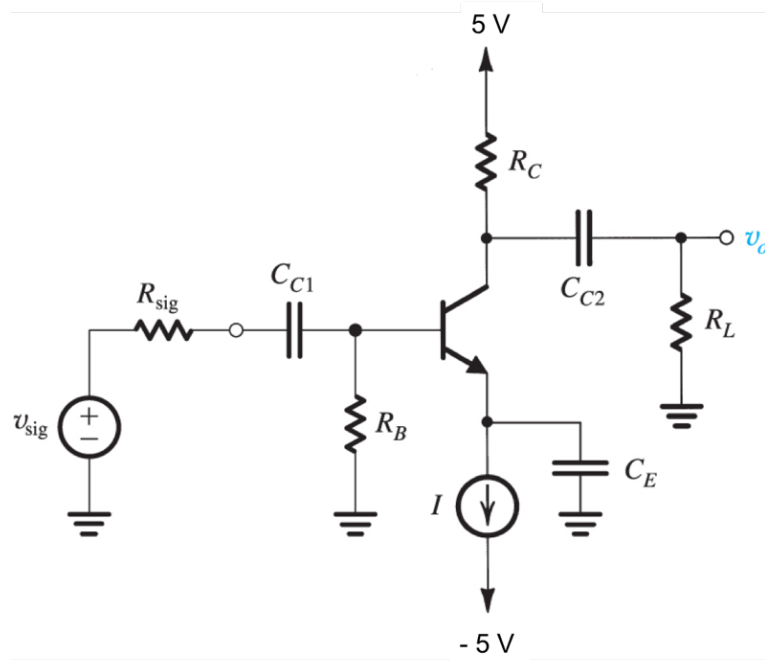
- a)  $R_i = 10\text{ k}\Omega$ .
- b) The DC voltage drop across  $R_B$  is  $0.2\text{ V}$ .
- c) The open loop voltage gain of the amplifier ( $A_{Vo}$ ) is  $-160\text{ V/V}$ .

Assume  $\beta = 100$ ,  $V_{D0} = 0.7\text{ V}$ ,  $V_A = \infty$ ,  $V_T = 25\text{ mV}$  and the capacitors are short for the signal circuit.


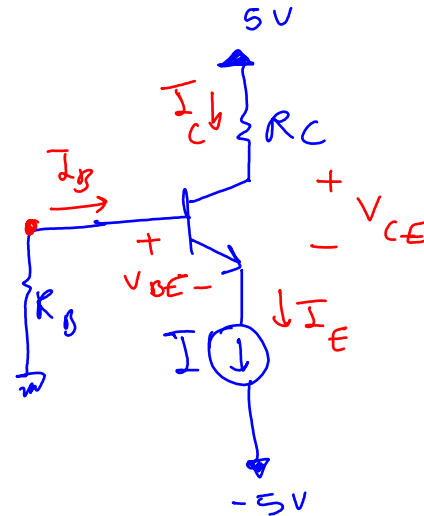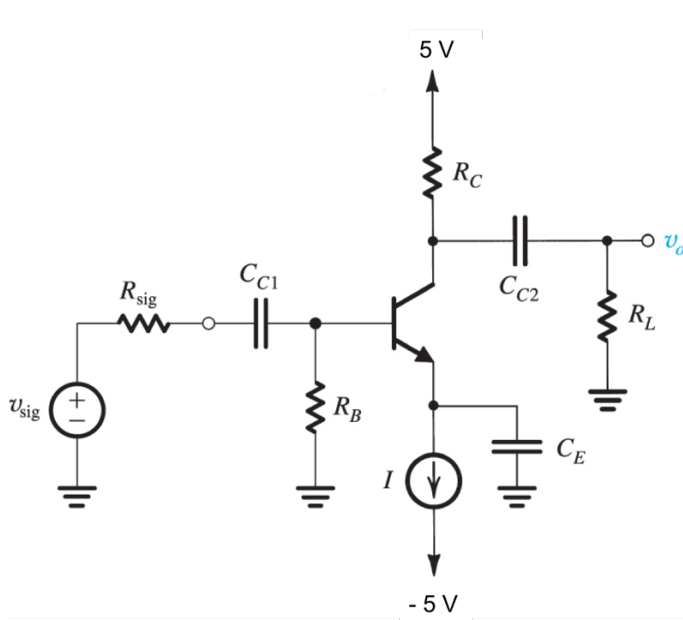
## Practice problem 1.

- $R_i = 10\text{ k}\Omega$ .  $R_i = R_B \parallel r_{\pi}$
- The DC voltage drop across  $R_B$  is 0.2 V.
- The open loop voltage gain of the amplifier ( $A_{Vo}$ ) is -160 V/V.





$$a) R_B \parallel r_{\pi} = R_B \parallel \frac{V_T}{I_B} = 10\text{ k}\Omega$$

$$b) R_B I_B = 0.2\text{ V}$$
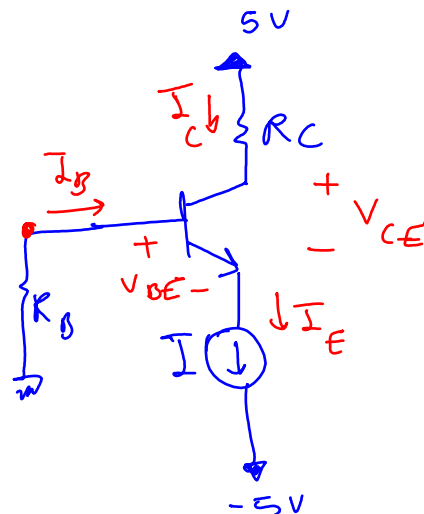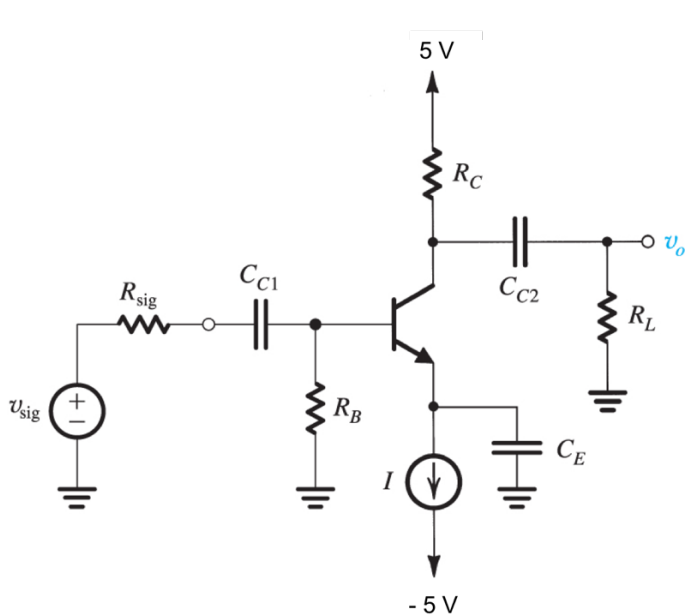
# Practice problem 1.

- $R_i = 10\text{ k}\Omega$ .  $R_i = R_B \parallel r_{\pi}$
- The DC voltage drop across  $R_B$  is 0.2 V.
- The open loop voltage gain of the amplifier ( $A_{Vo}$ ) is -160 V/V.




$$a) R_B \parallel r_{\pi} = R_B \parallel \frac{V_T}{I_B} = 10\text{ k}\Omega$$

$$b) R_B I_B = 0.2\text{ V}$$

$$\rightarrow \frac{R_B \times \frac{25\text{ mV}}{I_B}}{R_B + \frac{25\text{ mV}}{I_B}} = 10\text{ k}\Omega$$
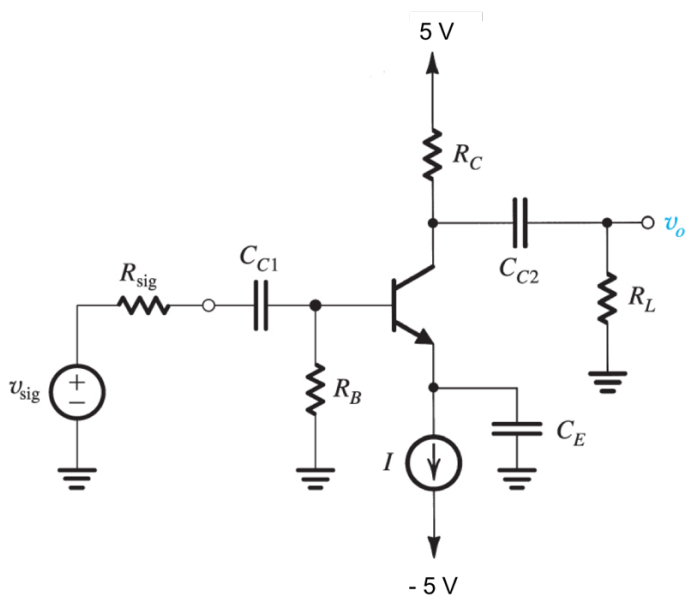
## Practice problem 1.

- $R_i = 10\text{ k}\Omega$ .
- The DC voltage drop across  $R_B$  is 0.2 V.
- The open loop voltage gain of the amplifier ( $A_{Vo}$ ) is -160 V/V.



$$a) \quad 0.025 \frac{R_B}{I_B} = 10^4 R_B + \frac{250}{I_B}$$

$$0.025 R_B = 10^4 R_B I_B + 250$$

$$b) \quad R_B I_B = 0.2\text{ V}$$

$$R_B = 90\text{ k}\Omega$$


$$I = 0.22\text{ mA}$$

$$I = I_E = (1 + \beta) I_B$$
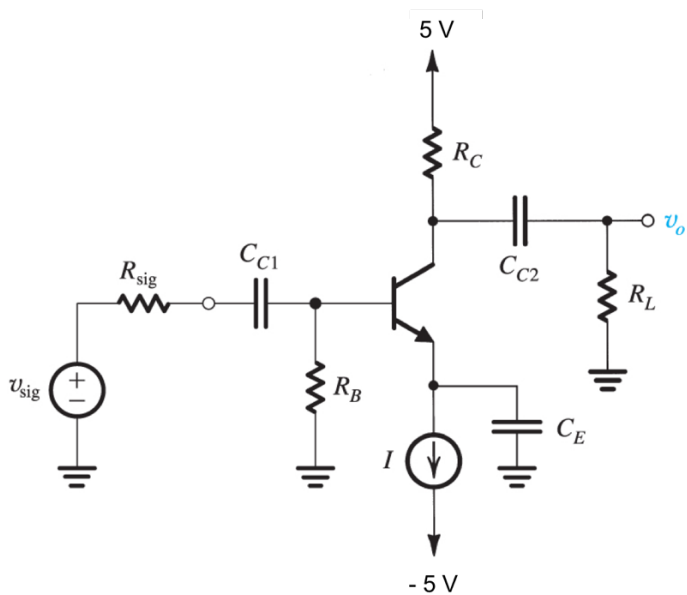
## Practice problem 1.

$$I_E = \frac{1 + \beta}{\beta} I_C$$

- $R_i = 10 \text{ k}\Omega$ .
- The DC voltage drop across  $R_B$  is 0.2 V.
- The open loop voltage gain of the amplifier ( $A_{V_o}$ ) is -160 V/V.




$$A_{V_o} = -g_m (R_C \parallel r_o)$$

$$r_o = \infty$$

$$A_{V_o} = -g_m R_C = -160 \text{ V/V}$$

$$g_m = \frac{I_C}{V_T} = \frac{0.22 \text{ mA}}{25 \text{ mV}} = 8.8 \text{ mA/V}$$

$$R_C = 18 \text{ k}\Omega$$

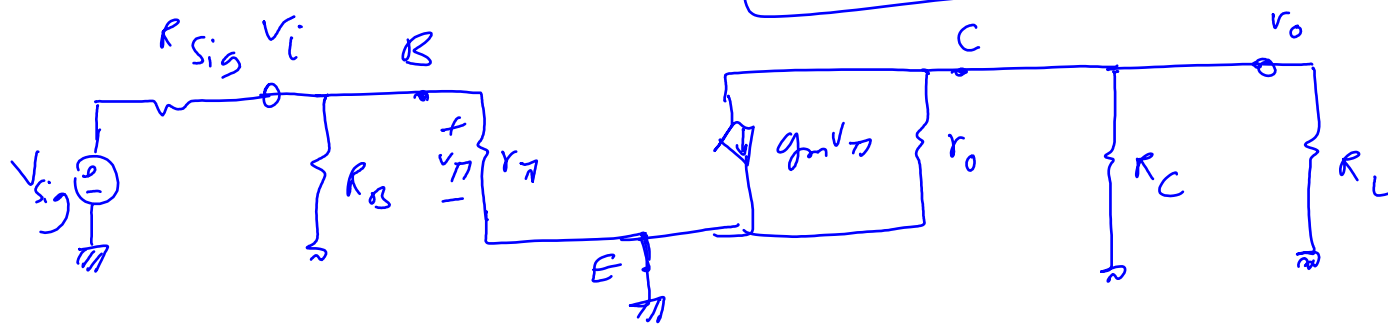


## Practice Problem 2.

## Amplifier design problem

The PMOS in the below common-source amplifier circuit has  $V_{tp} = -0.7\text{ V}$  and  $\lambda = 0$ .

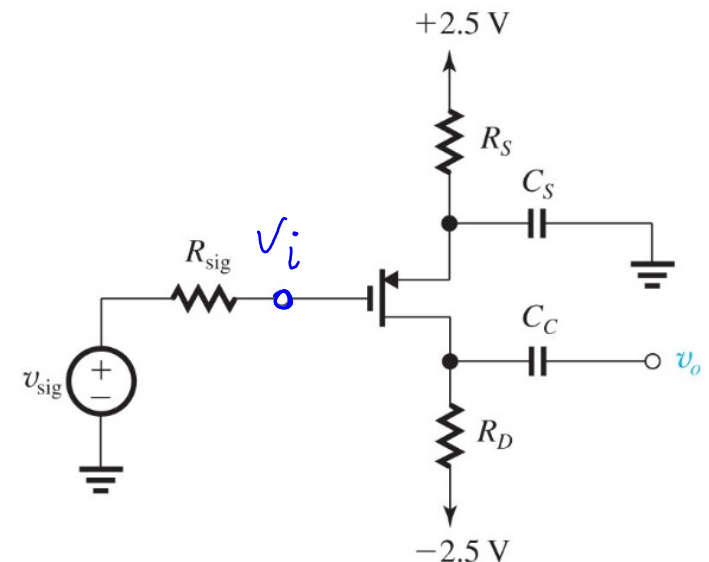1. Select a value for  $R_S$  to bias the transistor at  $I_D = 0.3\text{ mA}$  and  $V_{OV} = 0.3\text{ V}$ .
2. Select a value for  $R_D$  that results in  $A_V = -10\text{ V/V}$ .






## Practice Problem 2.

The PMOS in the below common-source amplifier circuit has  $V_{tp} = -0.7\text{ V}$  and  $\lambda = 0$ .

1. Select a value for  $R_S$  to bias the transistor at  $I_D = 0.3\text{ mA}$  and  $V_{OV} = 0.3\text{ V}$ .

Bias circuit:

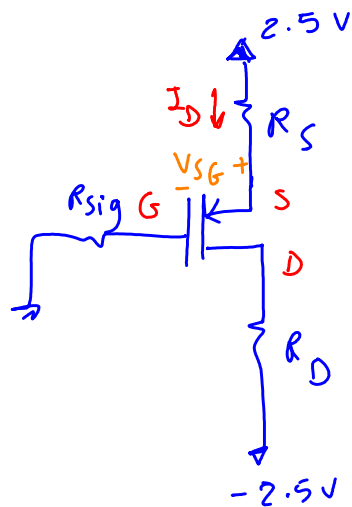


$$\text{Since } I_G = 0 \rightarrow V_G = 0$$

$$V_{OV} = V_{SG} - |V_{tp}|$$

$$V_{SG} = 0.3\text{ V} + 0.7\text{ V} = 1\text{ V}$$

$$V_{SG} = V_S - V_G = V_S = 1\text{ V}$$
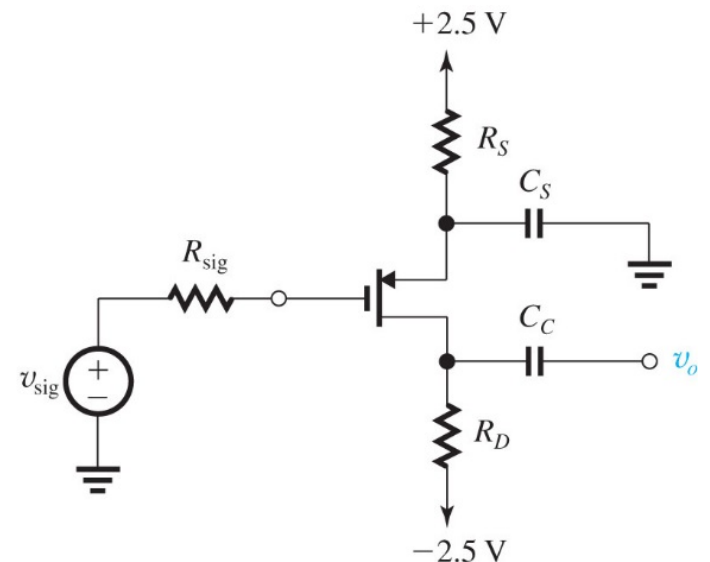
$$\boxed{V_S = 1\text{ V}} \rightarrow R_S = \frac{2.5\text{ V} - 1\text{ V}}{0.3\text{ mA}} = 5\text{ k}\Omega$$



## Practice Problem 2.


The PMOS in the below common-source amplifier circuit has  $V_{tp} = -0.7\text{ V}$  and  $\lambda = 0$ .

1. Select a value for  $R_S$  to bias the transistor at  $I_D = 0.3\text{ mA}$  and  $V_{OV} = 0.3\text{ V}$ .
2. Select a value for  $R_D$  that results in  $A_V = -10\text{ V/V}$ .

$$A_{v_o} = -g_m R_D = -10\text{ V/V}$$

$$g_m = \frac{2I_D}{V_{OV}} = \frac{2 \times 0.3\text{ mA}}{0.3\text{ V}} = 2\text{ mA/V}$$
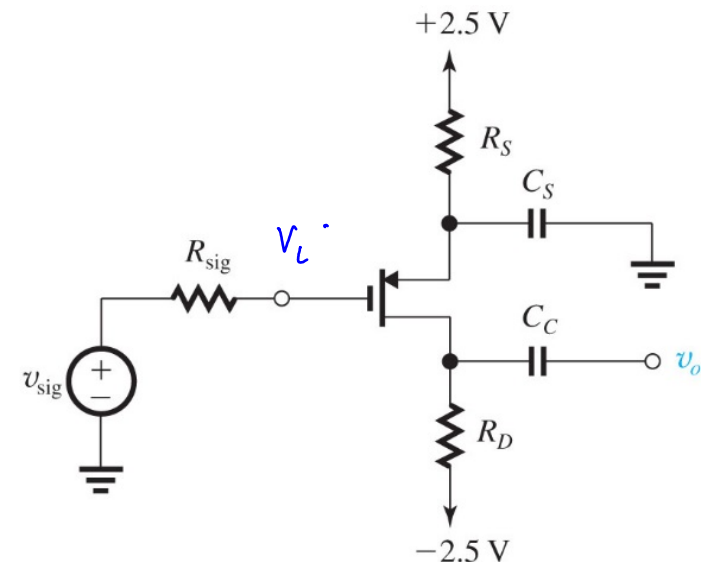
$$2\text{ (mA/V)} R_D = 10 \rightarrow R_D = 5\text{ k}\Omega$$



## Practice Problem 2.

## Amplifier design problem


The PMOS in the below common-source amplifier circuit has  $V_{tp} = -0.7\text{ V}$  and  $\lambda = 0$ .

1. Select a value for  $R_S$  to bias the transistor at  $I_D = 0.3\text{ mA}$  and  $V_{OV} = 0.3\text{ V}$ .
2. Select a value for  $R_D$  that results in  $A_V = -10\text{ V/V}$ .
3. If  $v_{sig} = 5 \sin(\omega t)\text{ (mV)}$  and  $R_{sig} = 1\text{ k}\Omega$ , find and sketch all node voltages &  $i_D$ .

DC node voltages and DC drain current:

$$V_S = 1\text{ V}, \quad V_G = 0\text{ V}, \quad I_D = 0.3\text{ mA}$$
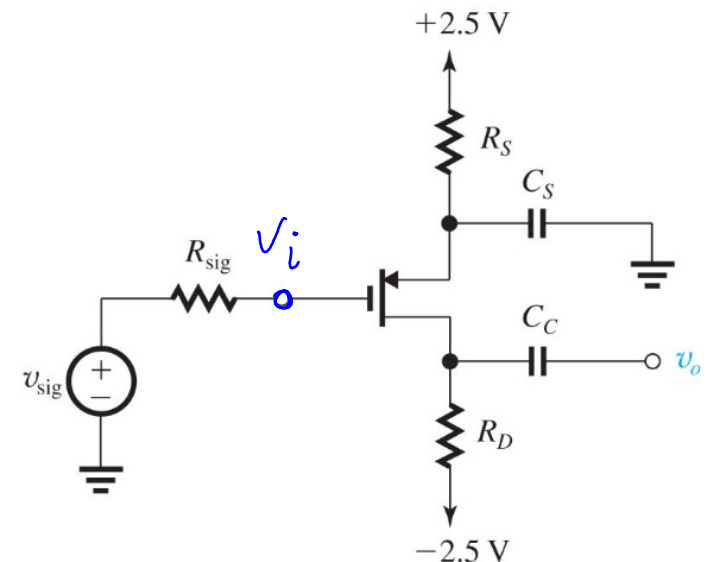
$$V_D = R_D I_D - 2.5\text{ V} = 5\text{ k}\Omega \times 0.3\text{ mA} - 2.5 = -1\text{ V}$$





## Practice Problem 2.

## Amplifier design problem

The PMOS in the below common-source amplifier circuit has  $V_{tp} = -0.7\text{ V}$  and  $\lambda = 0$ .

1. Select a value for  $R_S$  to bias the transistor at  $I_D = 0.3\text{ mA}$  and  $V_{OV} = 0.3\text{ V}$ .
2. Select a value for  $R_D$  that results in  $A_V = -10\text{ V/V}$ .
3. If  $v_{sig} = 5 \sin(\omega t)\text{ (mV)}$  and  $R_{sig} = 1\text{ k}\Omega$ , find and sketch all node voltages &  $i_D$ .

The signal node voltages & currents:

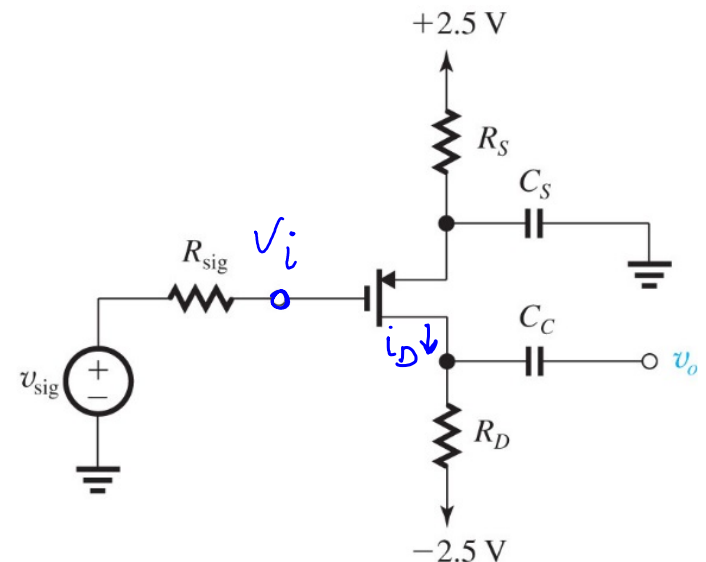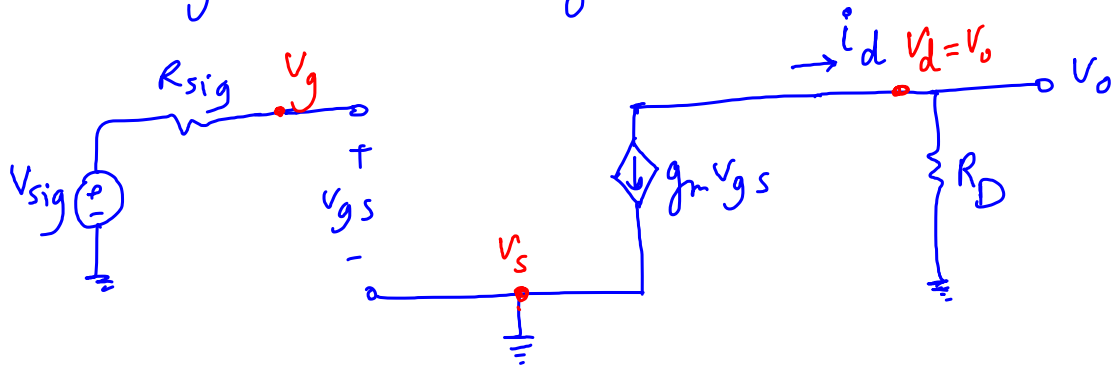


## Practice Problem 2.

## Amplifier design problem


The PMOS in the below common-source amplifier circuit has  $V_{tp} = -0.7 \text{ V}$  and  $\lambda = 0$ .

1. Select a value for  $R_S$  to bias the transistor at  $I_D = 0.3 \text{ mA}$  and  $V_{OV} = 0.3 \text{ V}$ .
2. Select a value for  $R_D$  that results in  $A_V = -10 \text{ V/V}$ .
3. If  $v_{sig} = 5 \sin(\omega t) \text{ (mV)}$  and  $R_{sig} = 1 \text{ k}\Omega$ , find and sketch all node voltages &  $i_D$ .

The signal node voltages & currents:

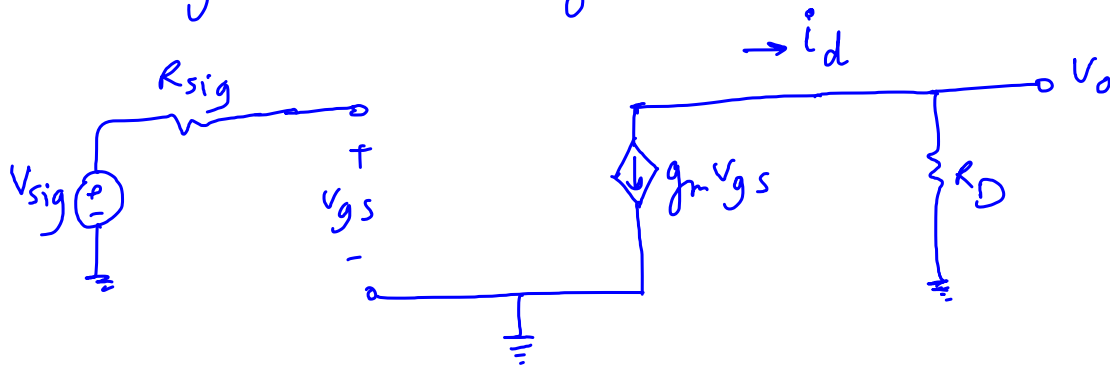
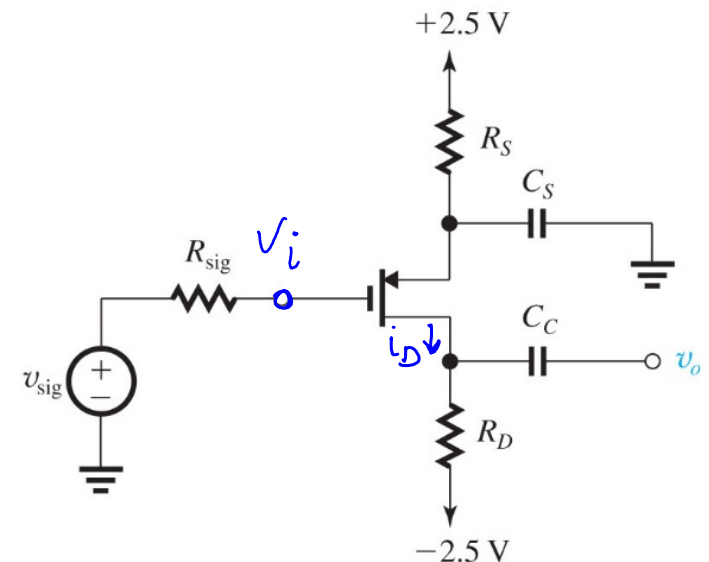
$$v_d = v_o = v_{sig} \times -10 \text{ V/V} = -10 v_{sig}$$



$$v_s = 0, \quad v_g = v_{sig}$$

$$i_d = -g_m v_{gs} = -g_m v_{sig} = -2 v_{sig} \text{ (mA)}$$

## Practice Problem 2.





## Amplifier design problem

The PMOS in the below common-source amplifier circuit has  $V_{tp} = -0.7 \text{ V}$  and  $\lambda = 0$ .

1. Select a value for  $R_S$  to bias the transistor at  $I_D = 0.3 \text{ mA}$  and  $V_{OV} = 0.3 \text{ V}$ .
2. Select a value for  $R_D$  that results in  $A_V = -10 \text{ V/V}$ .

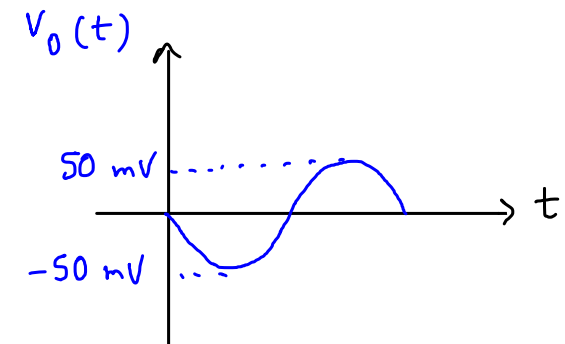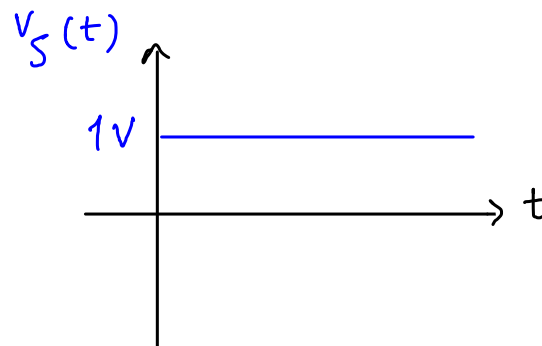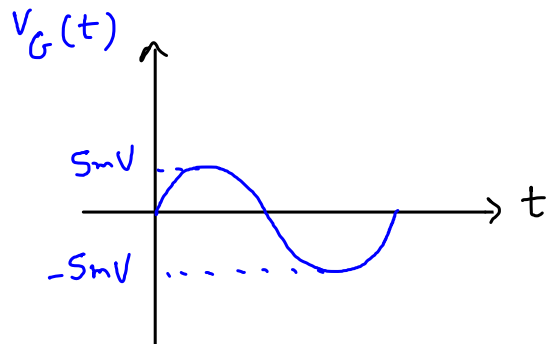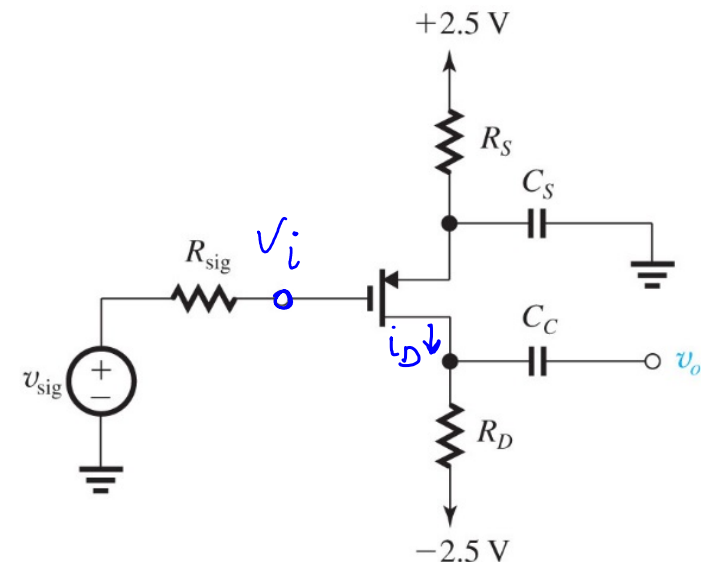3. If  $v_{sig} = 5 \sin(\omega t) \text{ (mV)}$  and  $R_{sig} = 1 \text{ k}\Omega$ , find and sketch all node voltages &  $i_D$ .

$$V_S = 0, \quad V_G = v_{sig}, \quad V_D = V_O = -10 v_{sig}, \quad i_D = -2 v_{sig} \text{ (mA)}$$



## Practice Problem 2.

## Amplifier design problem

The PMOS in the below common-source amplifier circuit has  $V_{tp} = -0.7\text{ V}$  and  $\lambda = 0$ .

1. Select a value for  $R_S$  to bias the transistor at  $I_D = 0.3\text{ mA}$  and  $V_{OV} = 0.3\text{ V}$ .
2. Select a value for  $R_D$  that results in  $A_V = -10\text{ V/V}$ .

3. If  $v_{sig} = 5 \sin(\omega t)\text{ (mV)}$  and  $R_{sig} = 1\text{ k}\Omega$ ,  
find and sketch all node voltages &  $i_D$ .

$$V_s = 0, \quad V_g = v_{sig}, \quad V_d = V_o = -10 v_{sig}, \quad i_d = -2 v_{sig} \text{ (mA)}$$

