
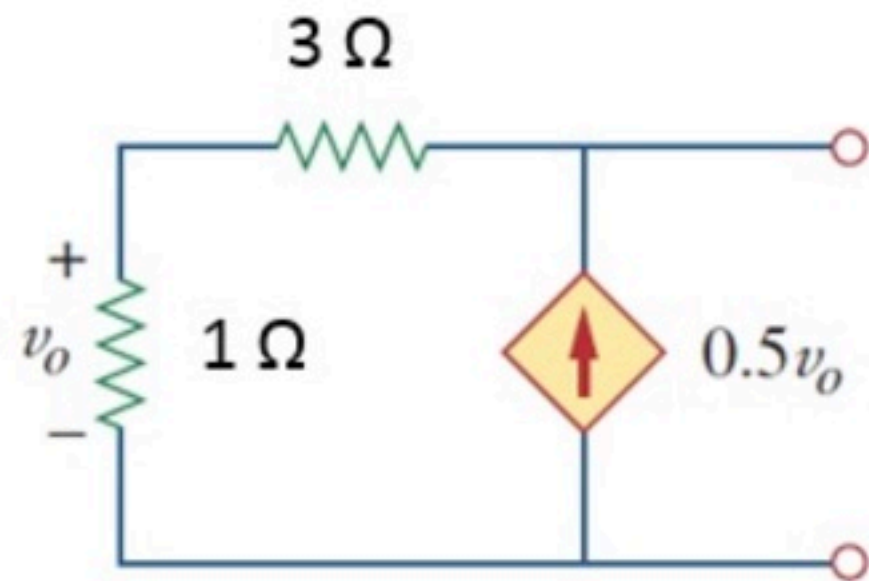


PP Circuit theorems 012

Unlimited Attempts.

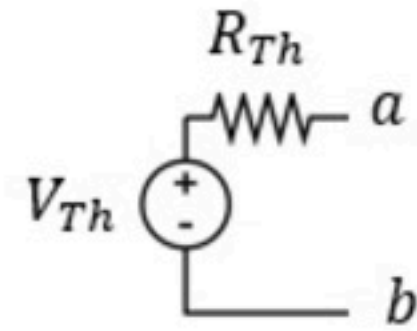Find the Thevenin equivalent model of this circuit, as seen between a and b.



Given Variables:

...

Calculate the following:

Vth (V) :

0



Rth (ohm) :

8



Hint: What do you expect Vth to be? Use test source for Rth.