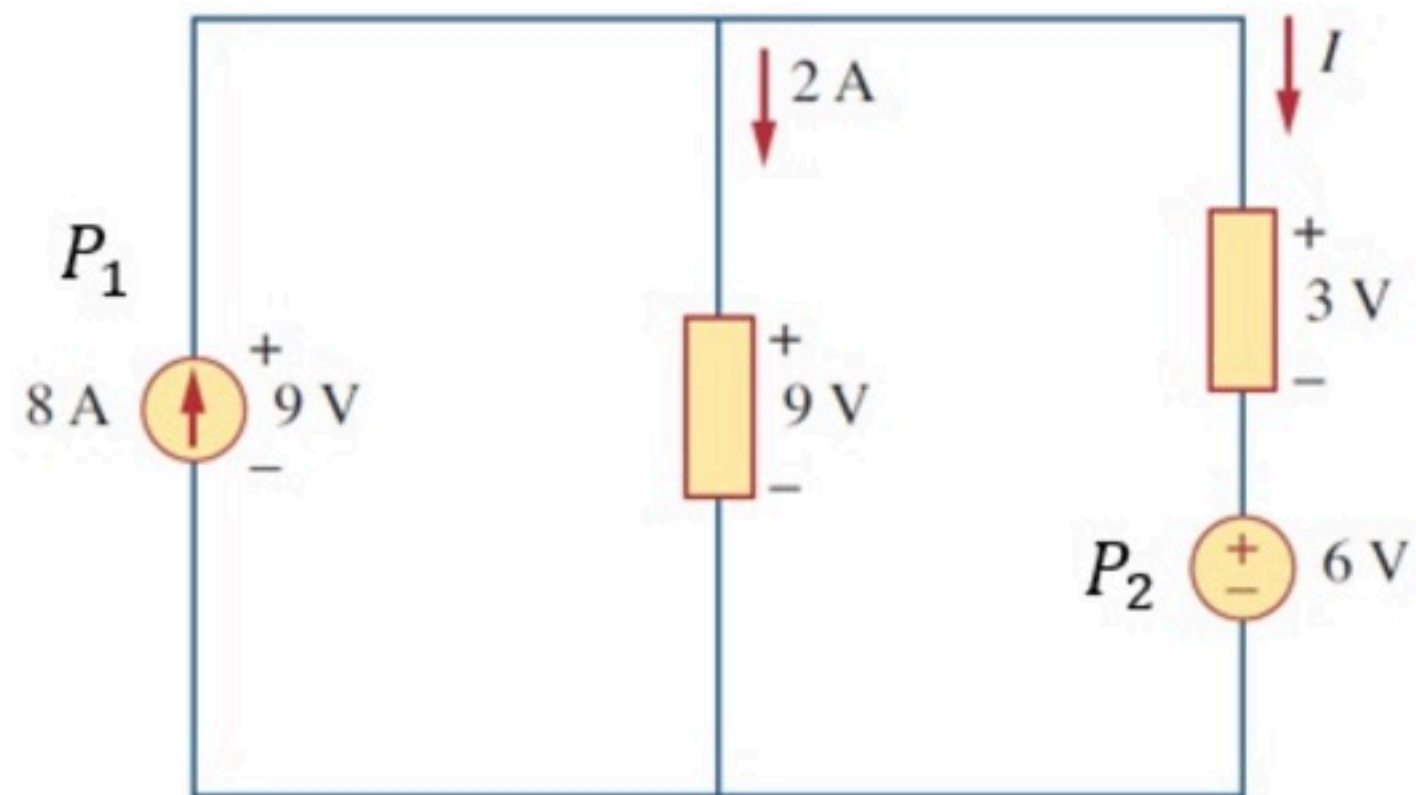


# PP - Basic concepts 009

Problem has been graded.

Find the power supplied by the current source and the voltage source.



Given Variables:

...

Calculate the following:

$P_1$  (W) :

72



$P_2$  (W) :

-36



Hint: Use KCL to find the missing current