

ECE 35, Fall 2017  
Quiz 3 - Section B

Last name

First + middle  
name(s)

PID

**Instructions:**

- Read each problem completely and thoroughly before beginning
- All calculations need to be done on these sheets
- Write your answers in the answer boxes for each question. Make sure you list units!
- Answers without supporting calculations will receive zero credit

(1) Consider the system below (it is repeated on the next page). For  $t < 0$ , the switch is closed. At  $t = 0$ , the switch is opened and it remains open. At time  $t = 0^-$ , just before the switch was opened, the system was not in steady state, but it is given that  $v_C(0^-) = 8V$  and  $i_L(0^-) = -2A$ .

(a) What is the energy in the inductor at time  $t = 0^+$ , (right after the switch is opened)?


(b) Find the expression for the capacitor current  $i_C(t)$ , for  $t > 0$ .


$i_C(t)$  in A =

(c) At time  $t = 1000$ , the switch is closed again. Find the capacitor voltage  $v_C$  and the inductor current  $i_L$  at time  $t = \infty$ .

$v_C$

$i_L$

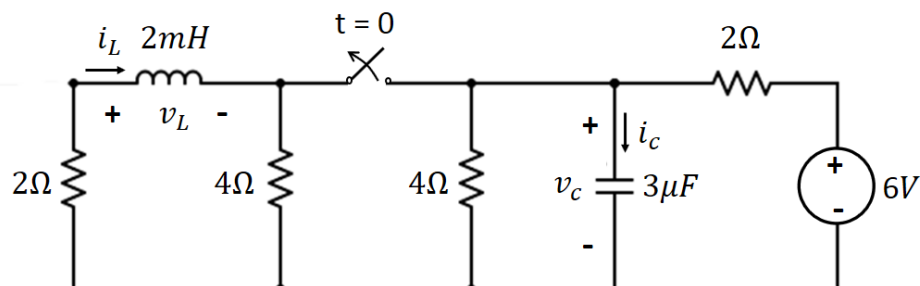

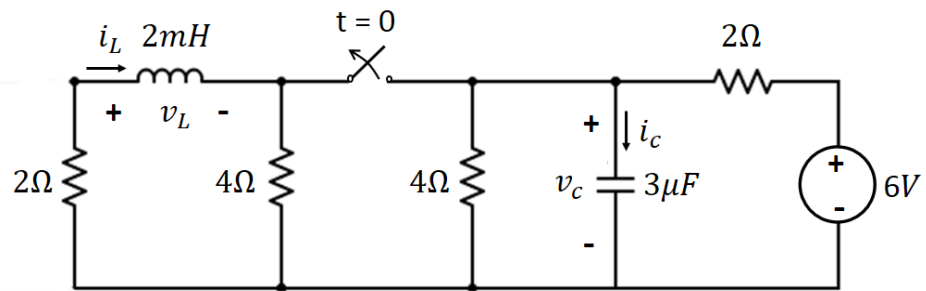

(2) Find  $v_L(t)$ . (Hint: you can use nodal analysis)

