


Basic analysis 011

Problem has been graded.

This circuit contains a capacitor (which we will cover in detail later in this course) with a voltage v_C across it. Voltage v_2 and current i_1 will satisfy the equations shown below (as we will also see later). Find the coefficients A , D and E .

$$v_C = 10 - 10 \cdot e^{-20t} \text{ V}$$
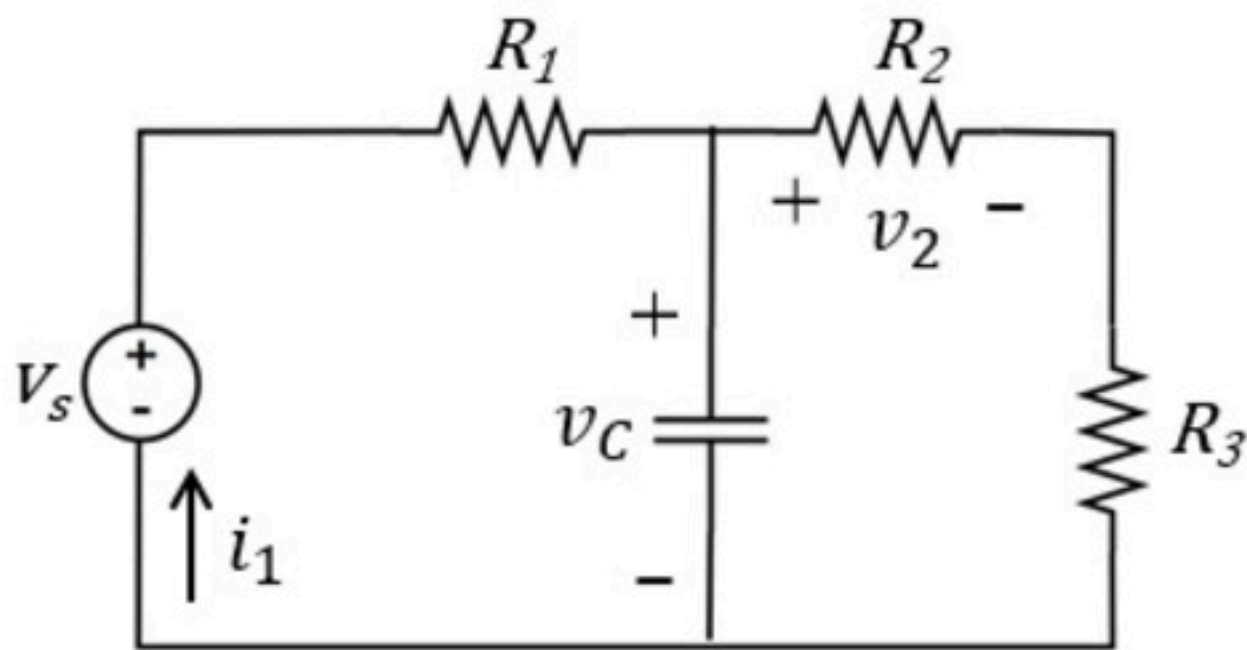
$$v_2 = A + B \cdot e^{-20t} \text{ V} \quad i_1 = D + E \cdot e^{-20t} \text{ A}$$



Given Variables:

v_s : 20 V

R_1 : 20 ohm

R_2 : 7 ohm

R_3 : 13 ohm

Calculate the following:

A (.) :

B (.) :

D (.) :

E (.) :