

ECE 65: Components & Circuits Lab

Lecture 11


BJT circuits

Reference notes: sections 3.2


Sedra & Smith (7th Ed): sections 6.1-6.3

Saharnaz Baghdadchi

3. Bipolar Junction Transistor (BJT)

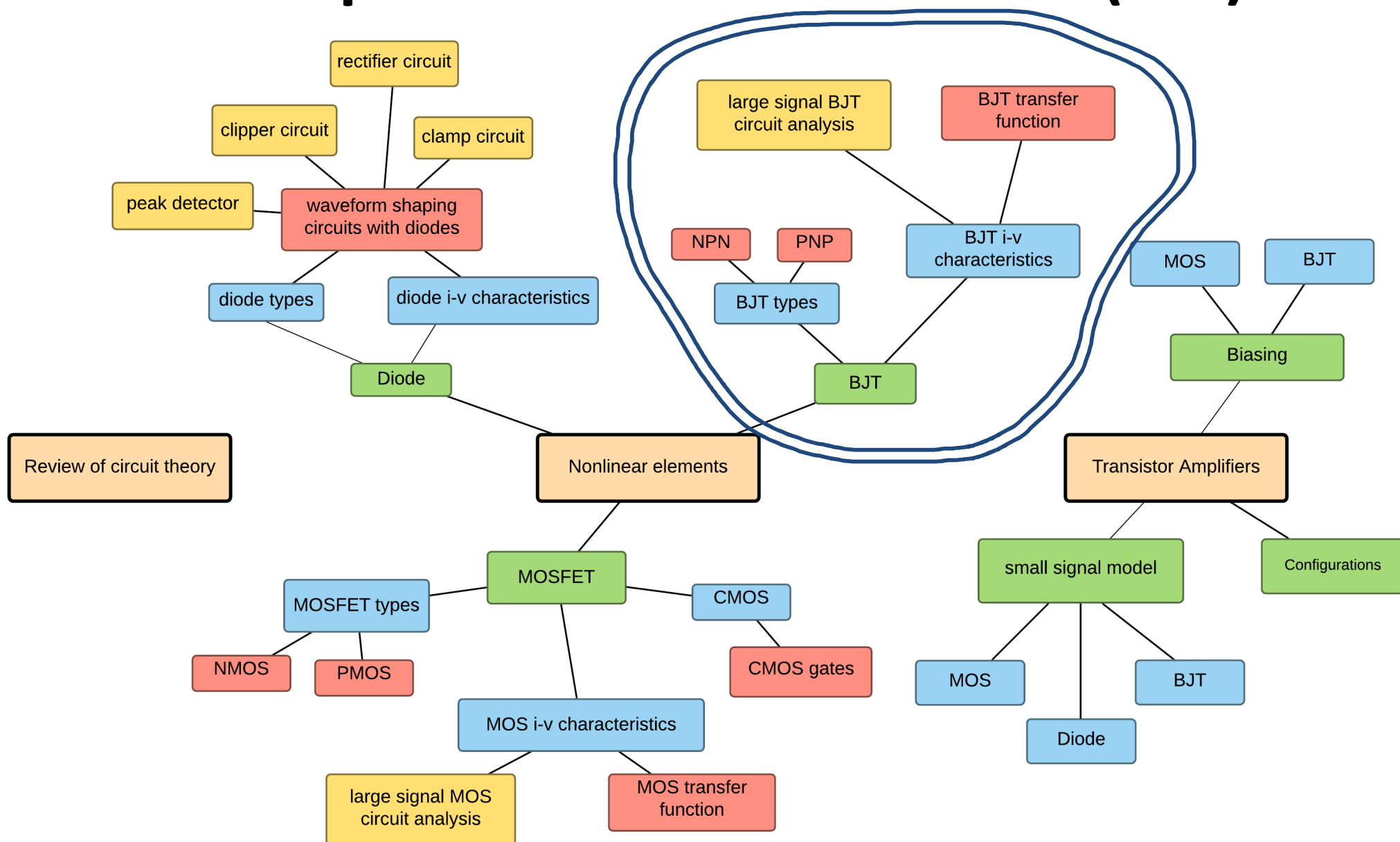

PNP Transistor Example:

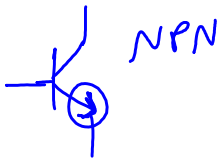

In this circuit, find the transistor parameters (Si BJT with $\beta = 100$).

EB KVL:

$$12 = V_{EB} + 40k \times i_B + 8$$


$$4 = V_{EB} + 40k \times i_B$$

EC KVL:

$$12 = V_{EC} + 1k \times i_C$$

Assume the BJT is in cut-off, $i_B = 0$, $V_{EB} < V_{D_0} = 0.7V$

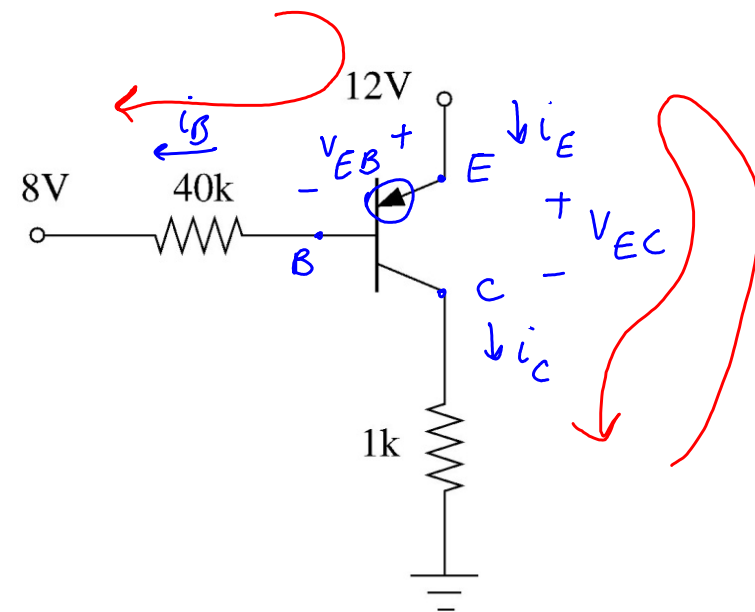EB KVL: $4 = V_{EB} + 40k \times 0 \rightarrow V_{EB} = 4V > 0.7 \rightarrow$ BJT is not in cut-off



BJT is ON, $i_B \geq 0$, $V_{EB} = V_{D_0} = 0.7 \text{ V}$

EB KVL, $4 = 40\text{k} \times i_B + 0.7 \rightarrow i_B = 82.5 \mu\text{A} > 0$


Assuming active mode:

$i_C = \beta i_B$, $V_{EC} \geq V_{D_0} = 0.7 \text{ V}$

$i_C = 100 \times 82.8 \mu\text{A} = 8.25 \text{ mA}$

EC KVL: $12 = V_{EC} + \underbrace{10^3}_{\text{resistor}} \times \underbrace{8.25 \times 10^{-3}}_{i_C} \rightarrow \underline{V_{EC} = 3.75 \text{ V}} > 0.7$


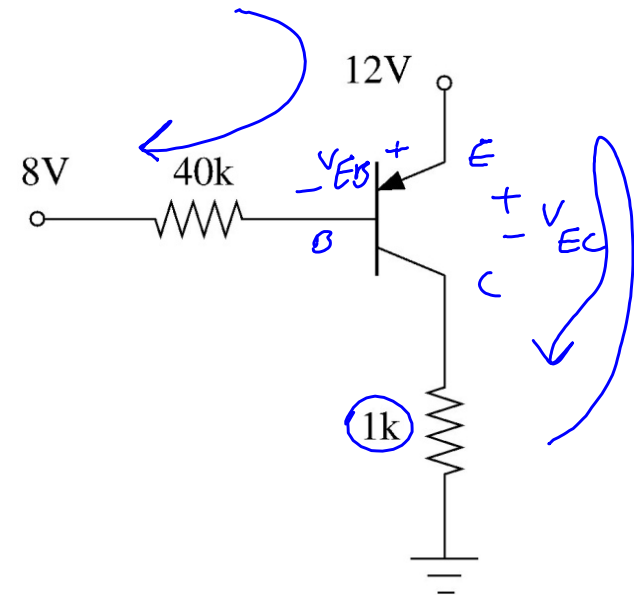
Assumption was correct, BJT is in active mode.



Note:


In the BJT and MOSFET circuits, to differentiate the applied node voltages from the measured node voltages:

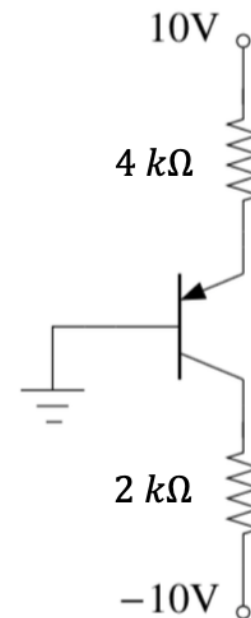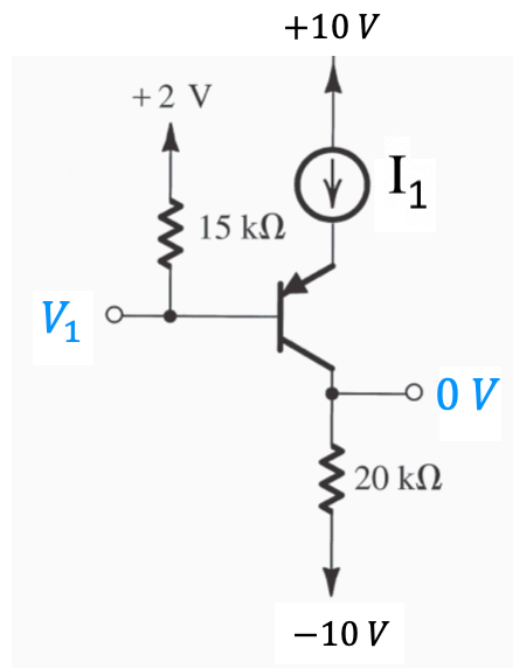We will show the measured node voltages in **blue color** and the applied DC or AS voltage sources to different nodes in **black color**.



Lecture 11 reading quiz

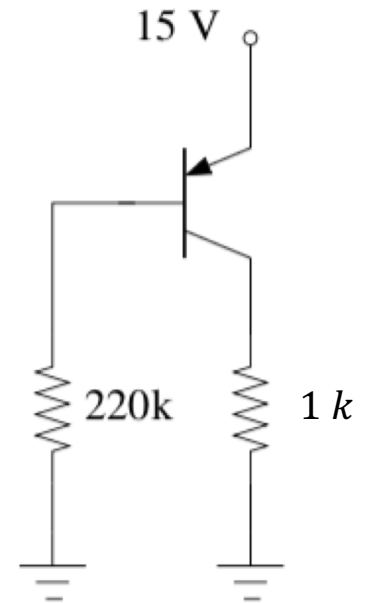
Find the transistor parameters in this BJT circuit. ($\beta = 100$, $V_{D0} = 0.7V$).



Clicker question 1:

The transistor in the following circuit has $\beta = 100$. Find the value for V_{EC} . (assume $V_{D0} = 0.7V$, $V_{sat} = 0.2 V$).

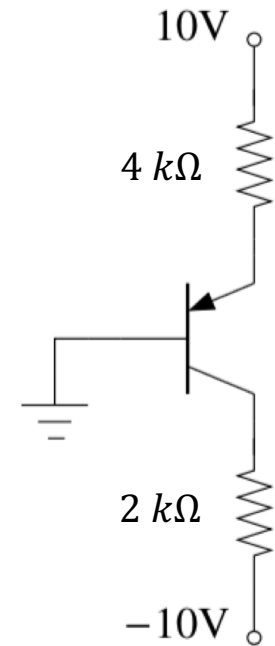- A. $V_{EC} \approx 10.5 V$
- B. $V_{EC} = 0 V$
- C. $V_{EC} \approx 6.1 V$
- D. $V_{EC} = 0.2 V$



Cut-off :

$$i_B = 0, \quad i_C = 0$$

$$v_{EB} < V_{D0}$$

Active:

$$v_{EB} = V_{D0}, \quad i_B \geq 0$$

$$i_C = \beta i_B, \quad v_{EC} \geq V_{D0}$$


Saturation:


$$v_{EB} = V_{D0}, \quad i_B \geq 0$$

$$v_{EC} = V_{sat}, \quad i_C < \beta i_B$$

Hints:


- Write the EB KVL and test if the BJT is in cut-off.
- If the BJT is ON, you can either assume active mode of operation or saturation mode of operation.
- If you assume active mode, you can use the relationship between I_C and I_B , the EC KVL, and the KCL relating the BJT currents to find V_{EC} , compare it with V_{D0} , and confirm or reject your assumption. You can replace the DC sources (10 V and -10 V with the symbol of a DC voltage source and explicitly draw the grounds.
- If you assume saturation mode, you can use $V_{EC}=V_{sat}$ and the EC KVL to find I_C . Compare I_C with I_B and confirm or reject your assumption.

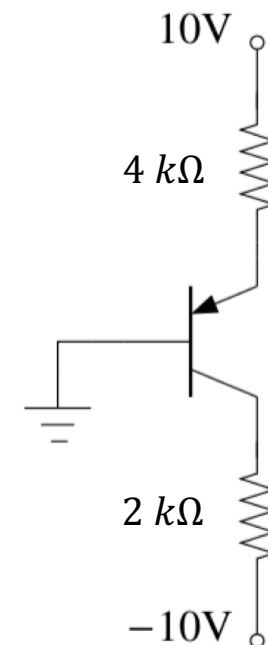

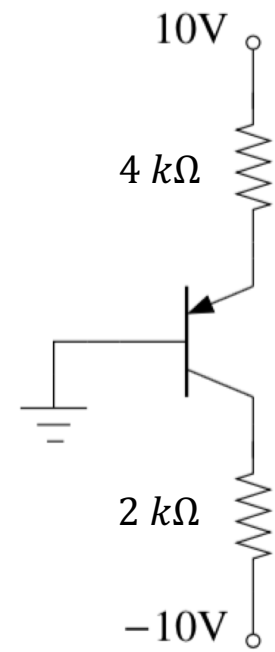

Discussion question 1:

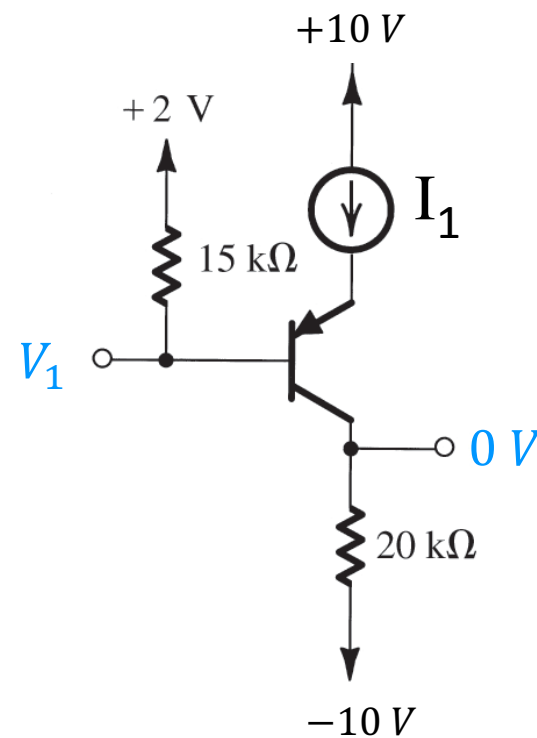In this BJT circuit find V_1 and I_1 . Assume $\beta = 100$, $V_{D0} = 0.7V$, $V_{sat} = 0.2V$.



Cut-off :

$$i_B = 0, \quad i_C = 0$$

$$v_{EB} < V_{D0}$$

Active:

$$v_{EB} = V_{D0}, \quad i_B \geq 0$$

$$i_C = \beta i_B, \quad v_{EC} \geq V_{D0}$$


Saturation:

$$v_{EB} = V_{D0}, \quad i_B \geq 0$$

$$v_{EC} = V_{sat}, \quad i_C < \beta i_B$$


Hints:

- Find the collector current and use it to determine if the BJT is ON or in Cut-off.
- If it is ON, you can assume active mode of operation, and find I_B and I_E . You will need to verify this assumption by finding V_{EC} .
- Using I_B , you can find V_B and using V_{BE} , you can find V_E . If the PNP BJT is ON, $V_{EB}=0.7$ V.
- Note that the voltage drop across the current source will be non-zero.

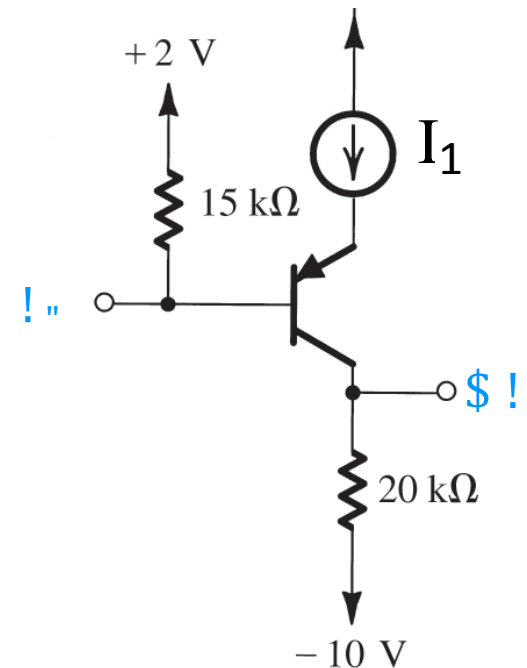

Discussion question 2:

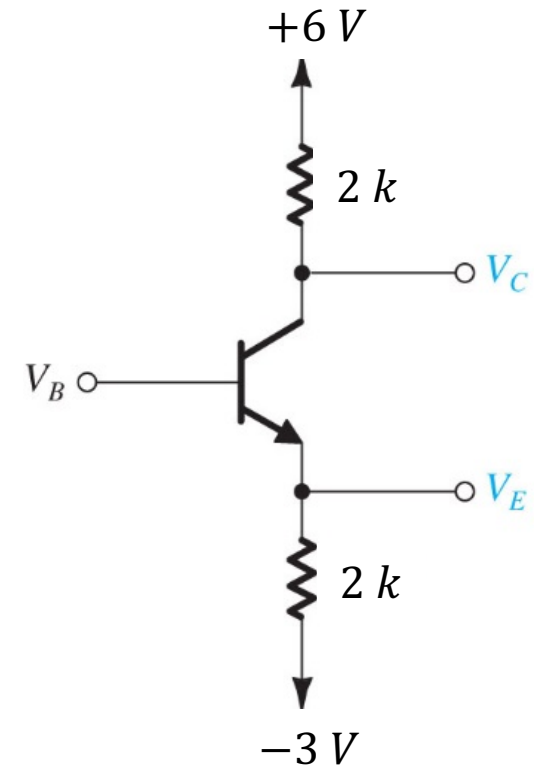Consider the operation of the below circuit for V_B at -1 V and 1V. Assume $V_{D0} = 0.7V$ and $\beta = 100$. What are the values of V_E and V_C ?



Cut-off :

$$i_B = 0, \quad i_C = 0$$

$$v_{BE} < V_{D0}$$

Active:

$$v_{BE} = V_{D0}, \quad i_B \geq 0$$

$$i_C = \beta i_B, \quad v_{CE} \geq V_{D0}$$

Saturation:

$$v_{BE} = V_{D0}, \quad i_B \geq 0$$

$$v_{CE} = V_{sat}, \quad i_C < \beta i_B$$