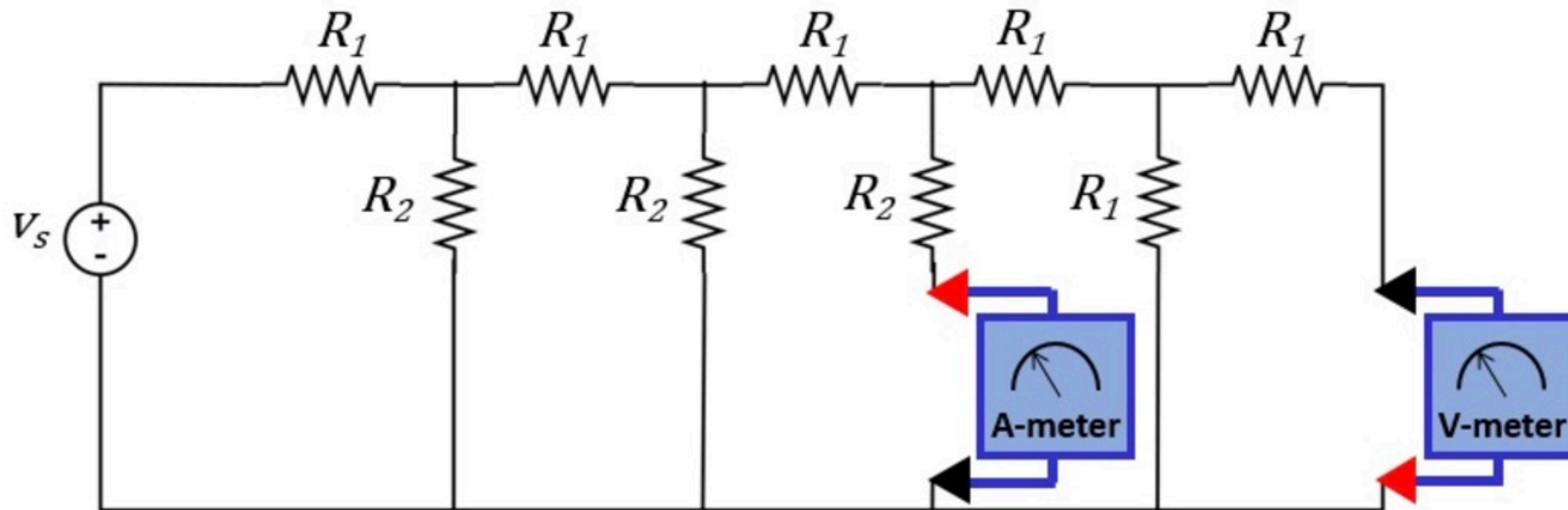


# Basic Analysis 010b

No more attempts left.

Find the ammeter reading  $X$  and the volt-meter reading  $Y$ .



Given Variables:

$v_s$  : 32 V

$R_1$  : 2 ohm

$R_2$  : 4 ohm





Calculate the following:

$X$  (A) :

$Y$  (V) :

Hint: First find the current through  $V_s$ . Use series/parallel. Then find  $X$  with current divider.

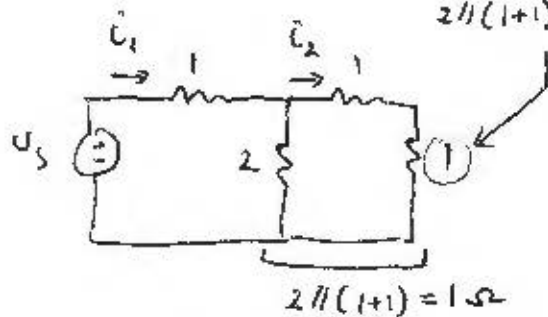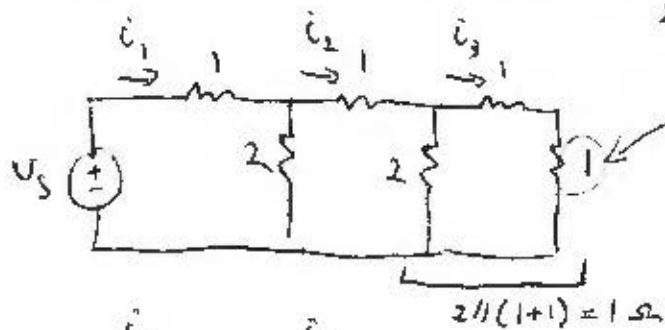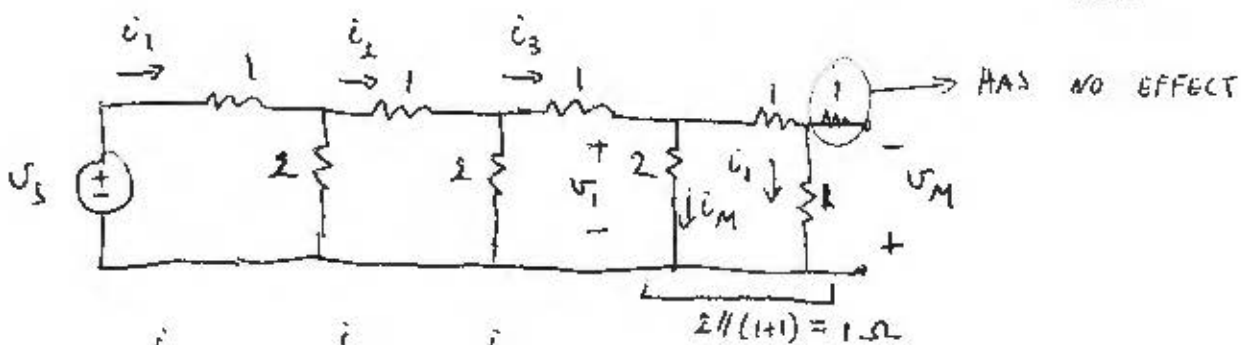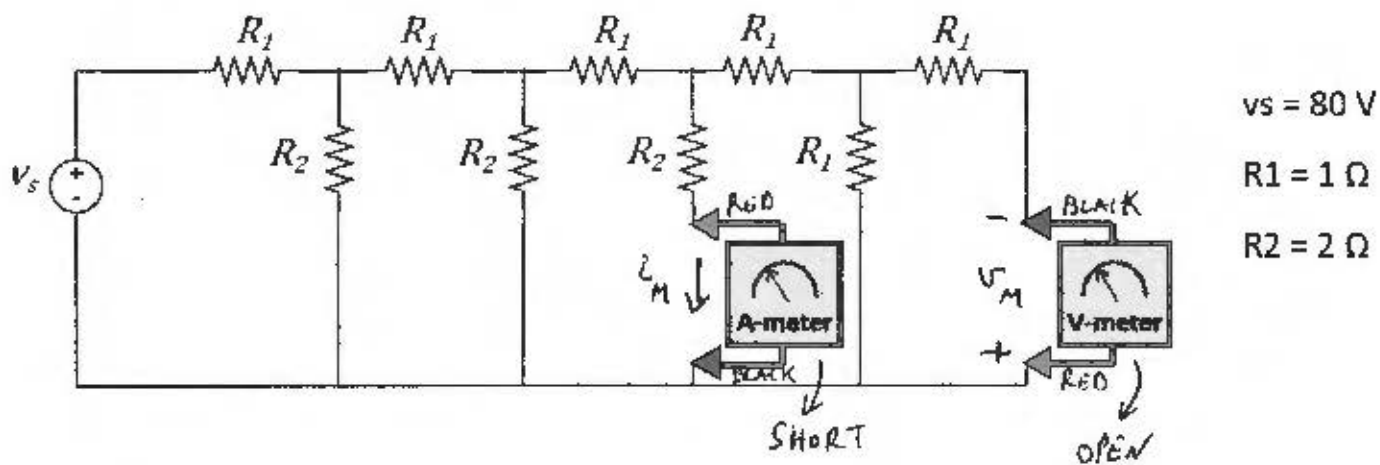Find the ammeter reading  $X$  and the volt-meter reading  $Y$ .



$$L_1 = \frac{55}{1+1} = 40$$

$$I_1 = I \frac{2}{2+2} = 20 \quad (\text{CURRENT DIVIDER})$$

$$C_3 = C_2 \frac{2}{2+2} = 10 \quad (\text{CURRENT DIVIDER})$$

$$I_M = I_3 \cdot \frac{2}{2+2} = 5 \quad (\text{CURRENT DIVIDER})$$

$$\boxed{X = 5A}$$

$$v_1 = 2, \quad C_M = 10$$

~~1.~~  $C_1 = C_M = 5 \Rightarrow -U_M = 1 \cdot C_1 = 5$

$$y = -5V$$