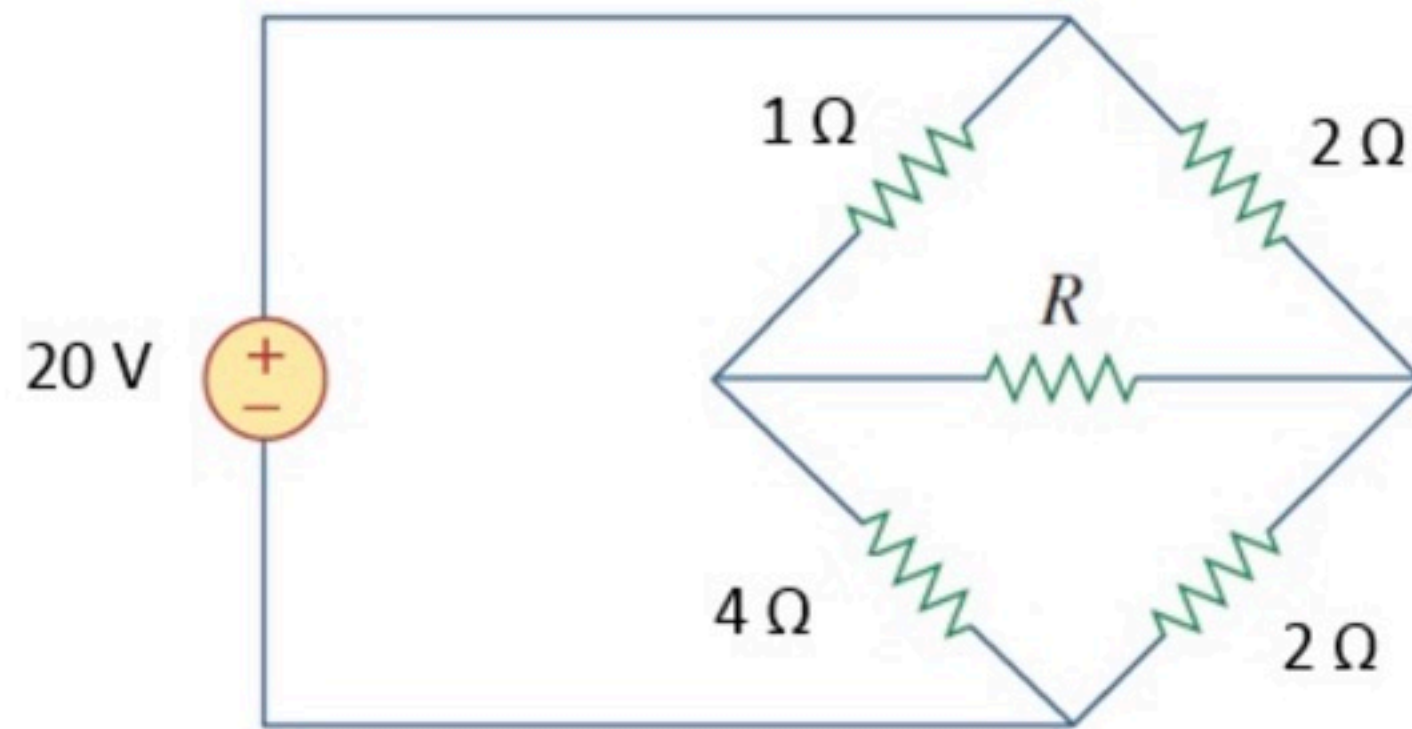


PP Circuit theorems 015

Unlimited Attempts.

What is the maximum power P that can be delivered to the variable resistor R ?
[Do not look up the equation for power.]



Given Variables:

...

Calculate the following:

P (W) :

5

