

ECE 35, Fall 2018

Quiz 3

/ 20

Last name

First + middle
name(s)

PID

Instructions:


- Read each problem completely and thoroughly before beginning
- All calculations need to be done on these sheets
- Write your answers in the answer boxes for each question. Make sure you list units!
- Answers without supporting calculations will receive zero credit


(1) For $t < 2$ s, the switch is closed and you may assume the system has reached steady state.
The switch opens at time $t = 2$ s.

(a) Find $i_b(2^-)$. (1 point)

 $i_b(2^-)$

(b) Find $i_b(t)$ for $t > 2$ s. (6 points)

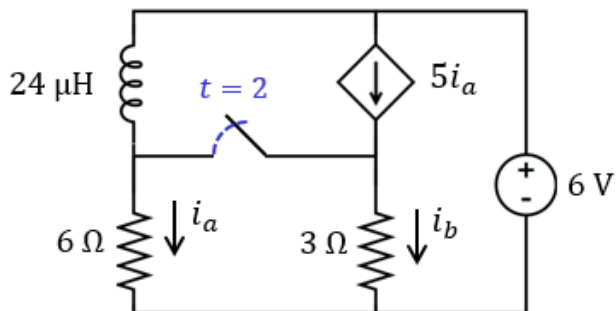 $i_b(t)$ 

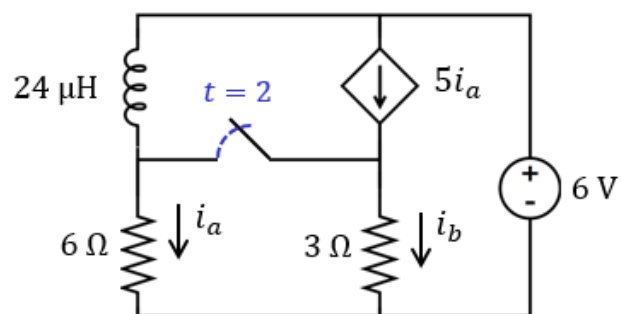


- (2) For an RC system, we found $i_1(t) = -4 \cdot e^{-t/4s} + 1$ A. Draw this waveform. Indicate where you can find the time constant on the graph. (2 points)



- (3) The system is in steady state. Find $i_a(t)$. (In your answer, combine cosines/sines with the same frequency. So for each frequency, there should be only one cosine wave.) (6 points)

$i_a(t)$

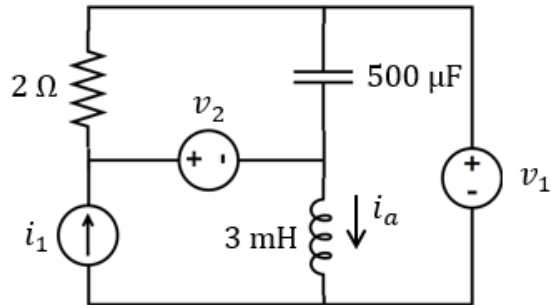

$$i_1(t) = \sin(1000t) \quad \text{A}$$

$$v_1(t) = 2 \cdot \cos(1000t + \pi) \quad \text{V}$$

$$v_2(t) = 4 \quad \text{V}$$

- (4) In the circuit below, the switch moves from position A to position B at time $t = 0$ s. For $t < 0$ s (switch in position A), you may assume the system is in steady state. The voltage source is sinusoidal with $\omega = 1000$. The diagram shows two phasors, **A** and **B** (not to scale). One of them represents the capacitor voltage and the other the resistor voltage (but you are not told which one is which). (5 points)

$$i_R(0^-) \quad \boxed{}$$

$$i_R(0^+) \quad \boxed{}$$

(a) Find i_R at time $t = 0^-$ (i.e. just before the switch moves to B).

(b) Find i_R at time $t = 0^+$ (i.e. immediately after the switch moves to B).

