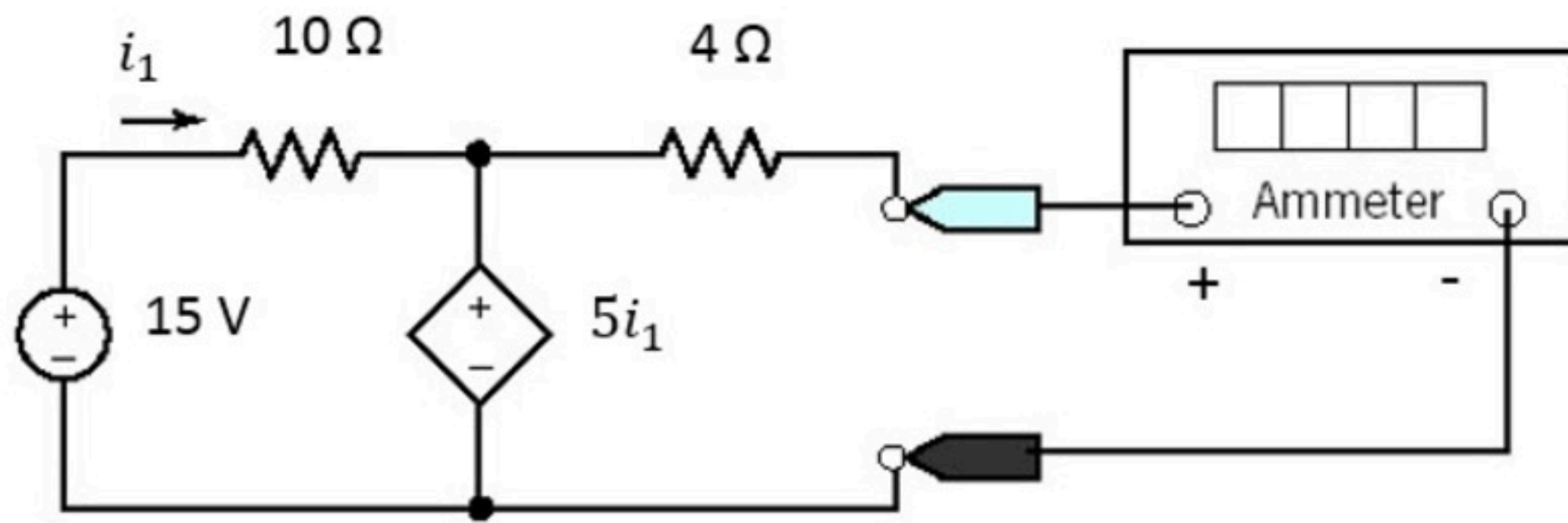


PP - Basic analysis 004

Unlimited Attempts.

What is the reading X from the ammeter?

What would be the reading Y if I replaced the ammeter by a volt-meter?



Given Variables:

...

Calculate the following:

X (A) :

1.25



Y (V) :

5



Hint: Ammeters and volt meters behave as short and open circuits respectively