


PP Capacitors Inductors 001

Unlimited Attempts.

Below is the current through a $5\text{ }\mu\text{H}$ inductor.

What is the voltage v_1 across the inductor at time $t = 3\text{ ms}$?

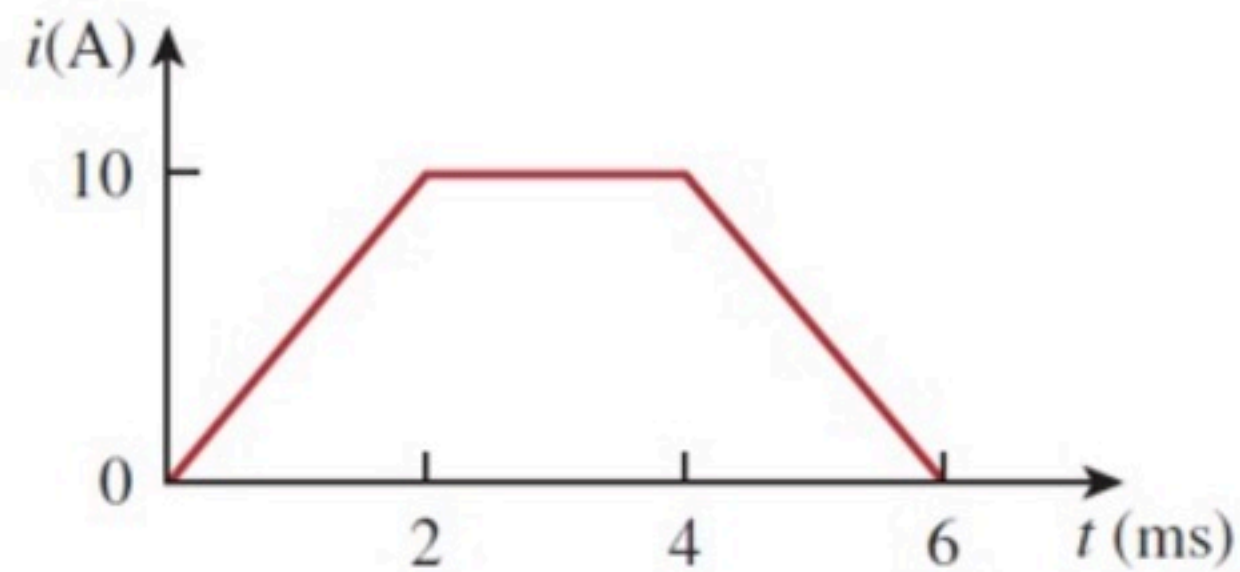What is the voltage v_2 across the inductor at time $t = 5\text{ ms}$?



Given Variables:

...

Calculate the following:

v_1 (V) :

0



v_2 (V) :

-0.025



Hint: Check the units.


PP Capacitors Inductors 002

Unlimited Attempts.

Below is the current through a $400\ \mu\text{F}$ capacitor. The voltage across the capacitor at time $t = 0$ is $5\ \text{V}$.

What is the voltage v_1 across the capacitor at time $t = 3\ \text{s}$?

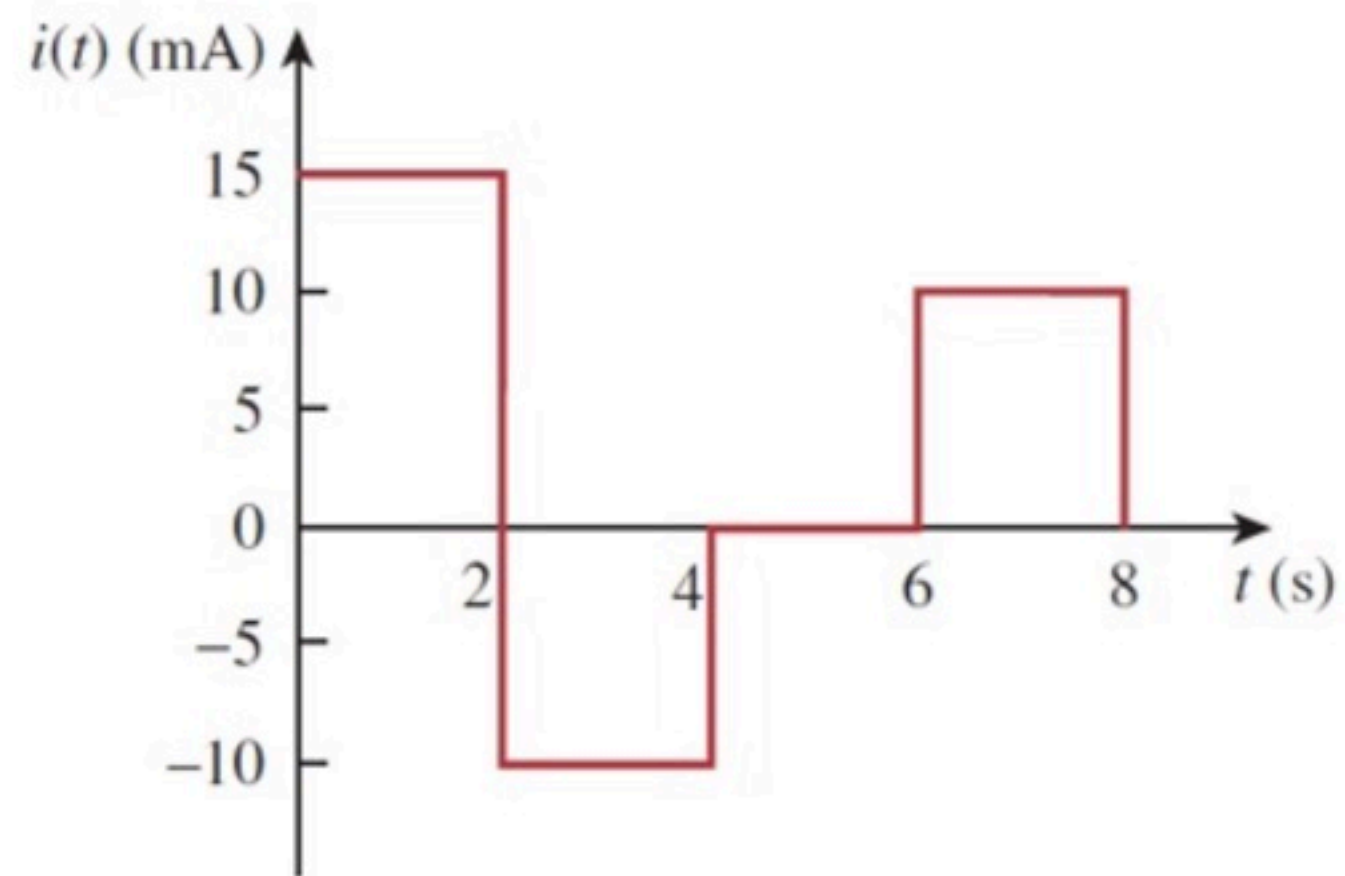What is the voltage v_2 across the capacitor at time $t = 8\ \text{s}$?



Given Variables:

...

Calculate the following:

v_1 (V) :

55



v_2 (V) :

80



Hint: Check the units.


PP Capacitors Inductors 003

Unlimited Attempts.

Below is the voltage across a 4 H inductor. The current through the inductor at time $t = 1$ s is -1 A.

What is the current i_1 through the inductor at time $t = 3$ s?

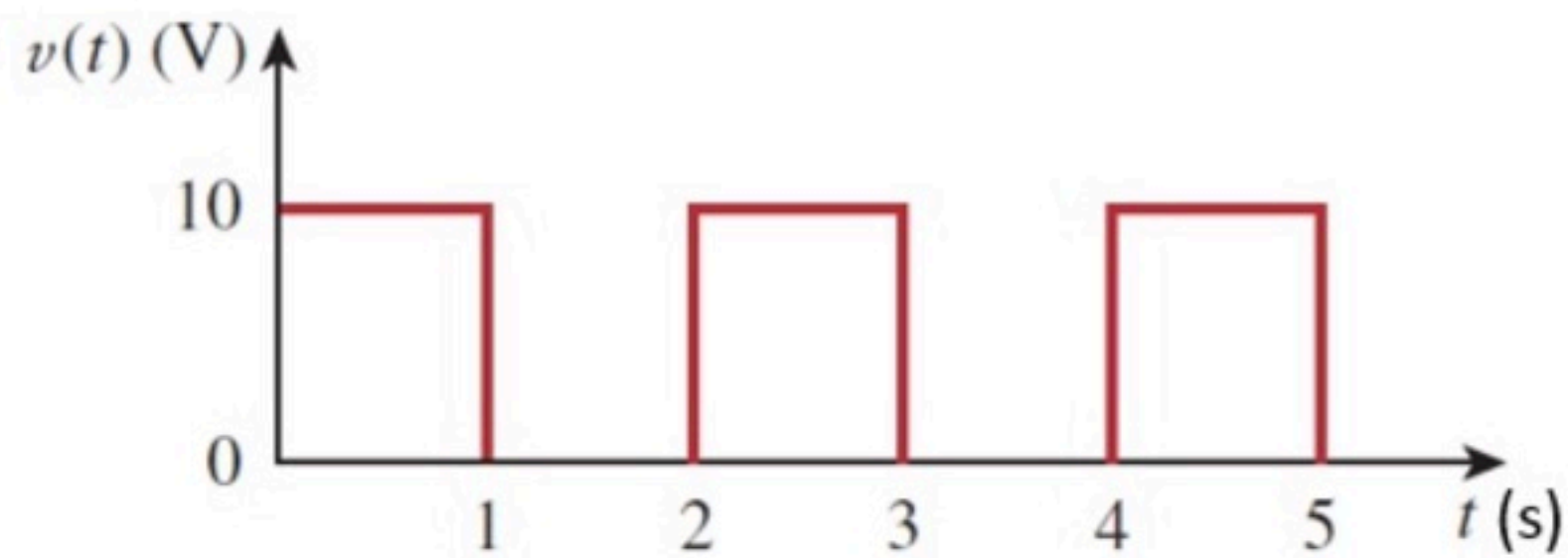What is the current i_2 through the inductor at time $t = 4.5$ s?



Given Variables:

...

Calculate the following:

i_1 (A) :

1.5



i_2 (A) :

2.75



Hint: Check initial condition.

PP Capacitors Inductors 004

Unlimited Attempts.

The current through a 400 nF capacitor is $0.05e^{-\frac{t}{2 \mu s}}$ A. The voltage across the capacitor at time $t = 0$ is 1 V.

What is the voltage v across the capacitor at time $t = \infty$?

Given Variables:

...

Calculate the following:

v (V) :

1.25



Hint: Check the units

PP Capacitors Inductors 005

Unlimited Attempts.

The current through a 20 mH inductor is $0.04te^{-\frac{t}{2\mu s}}$ A.

What is the voltage v_1 across the inductor at time $t = 0$?

Given Variables:

...

Calculate the following:

v_1 (mV) :

0.8





Hint: Check the units

PP Capacitors Inductors 006

Unlimited Attempts.

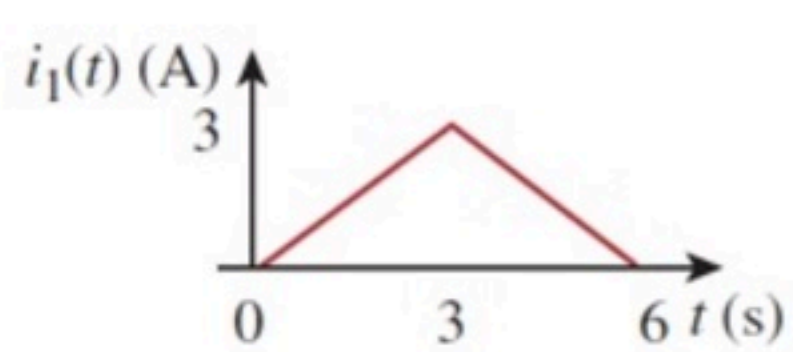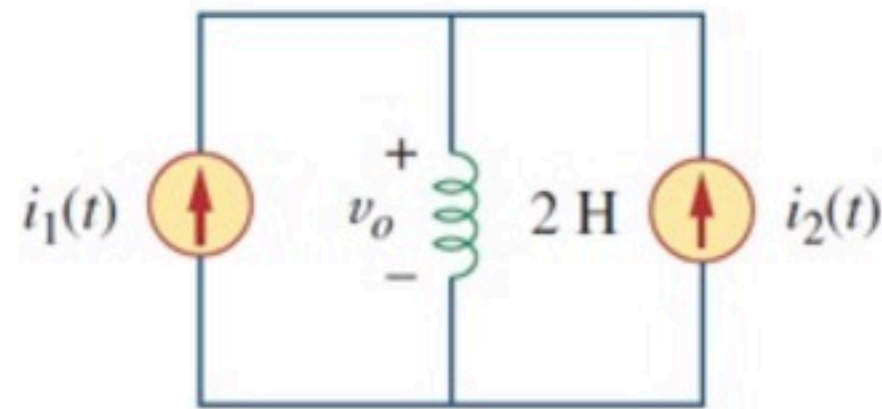What is the voltage v_o at time $t = 5$ s?



Given Variables:

...

Calculate the following:

v_o (V) :

-6




Hint: Use superposition

PP Capacitors Inductors 007

Unlimited Attempts.

Find $X = \frac{L_{eq}}{L}$.

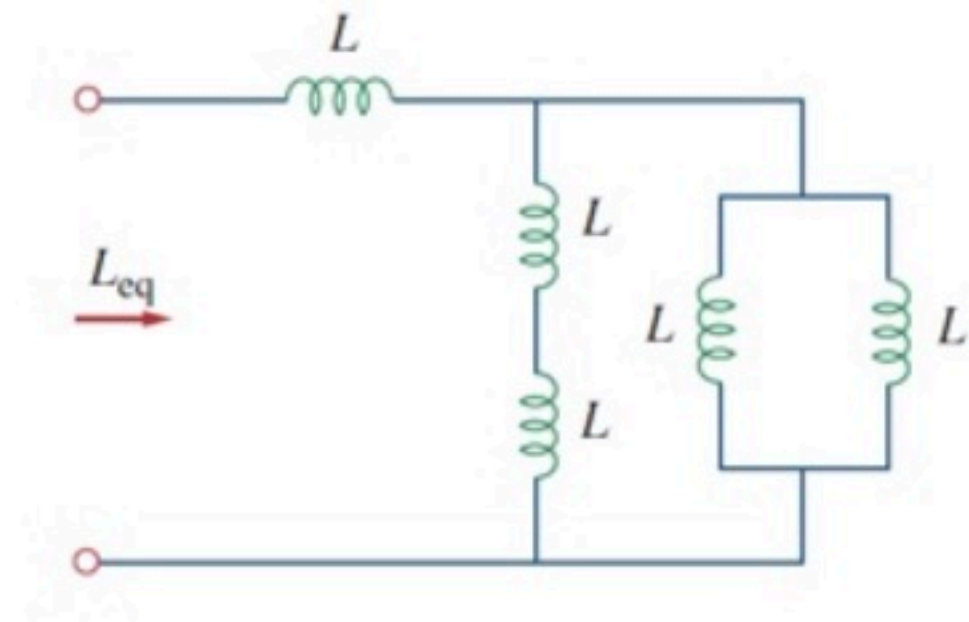

Given Variables:

$\therefore \dots$

Calculate the following:

X (H/H) :

1.4




Hint: Series and parallel connection of inductors

PP Capacitors Inductors 008

Unlimited Attempts.

Find $X = \frac{C_{eq}}{C}$.

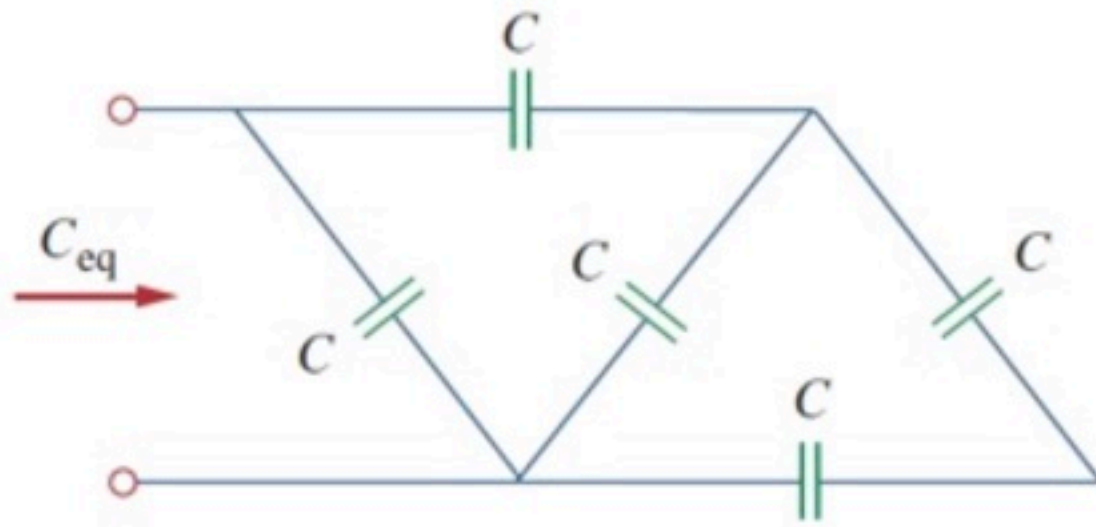

Given Variables:

...

Calculate the following:

X (F/F) :

1.6



Hint: Series/parallel equations are 'opposite' of those for resistors.