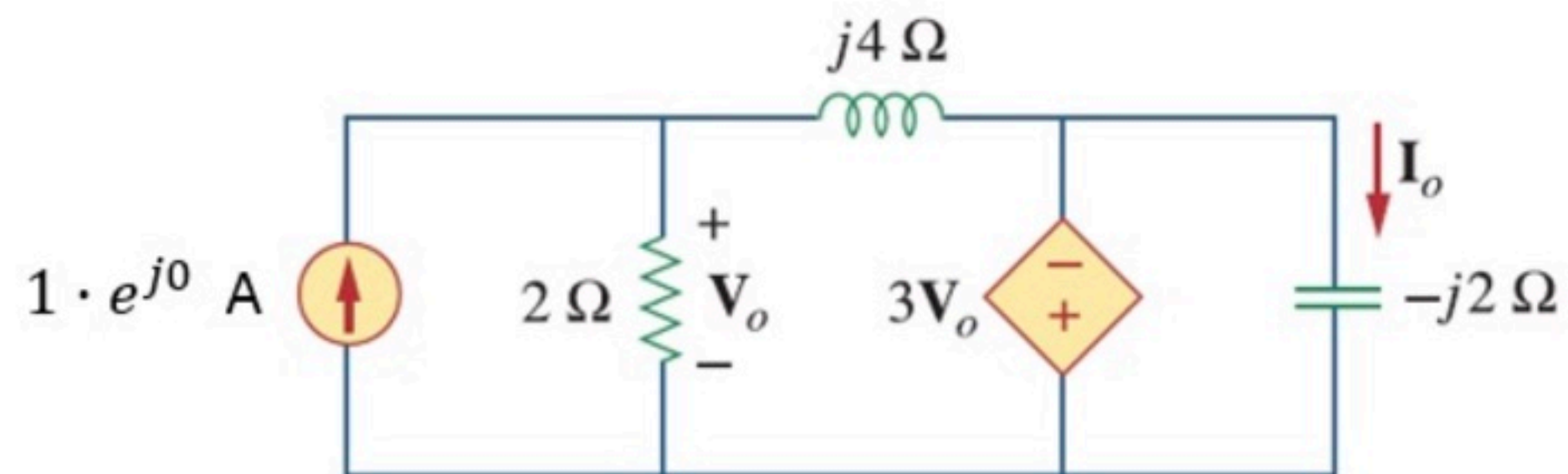


# PP Phasors 017

Unlimited Attempts.

Find the phasors

$$\mathbf{V}_o = a + jb \quad \text{and} \quad \mathbf{I}_o = c + jd$$



Given Variables:

...

Calculate the following:

a (V) :

0.4



b (V) :

0.8



c (A) :

1.2



d (A) :

-0.6



Hint: Use mesh analysis.