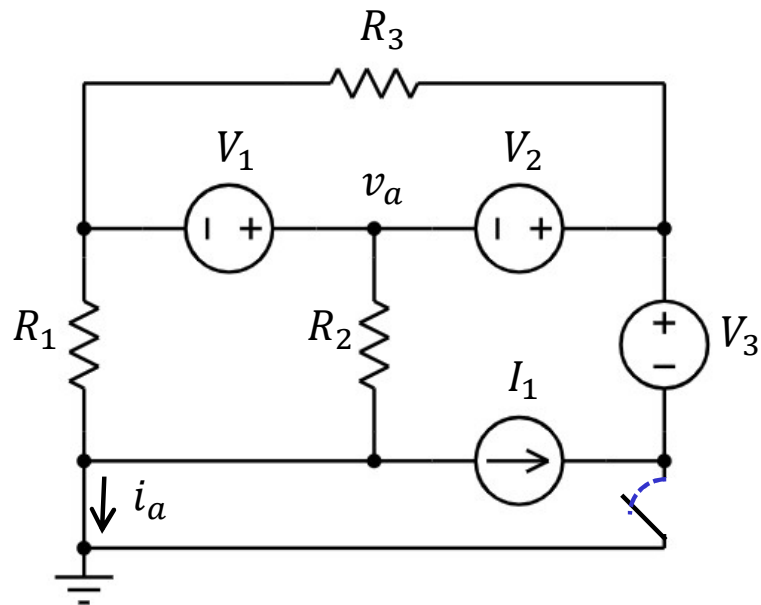



For $t < 1$ s, the switch is open. The switch closes at $t = 1$ s and remains closed.

- (a) Find $v_a(0 \text{ s})$
- (b) Find $i_a(0 \text{ s})$
- (c) Find $v_a(2 \text{ s})$
- (d) Find $i_a(2 \text{ s})$




R1:	1 Ω
R2:	1 Ω
R3:	2 Ω
V1:	1 V
V2:	2 V
V3:	0 V
I1:	2 A

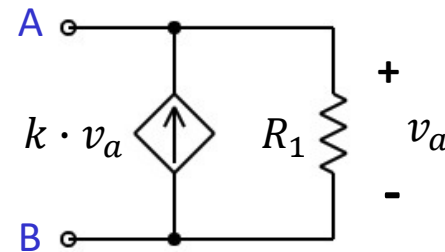- (a) For the circuit on the right, find the Thevenin equivalent model between A and B. Draw the model and don't forget to label A and B.




R1:	2 Ω
k:	1 A/V
X:	4 V
Y:	1 V

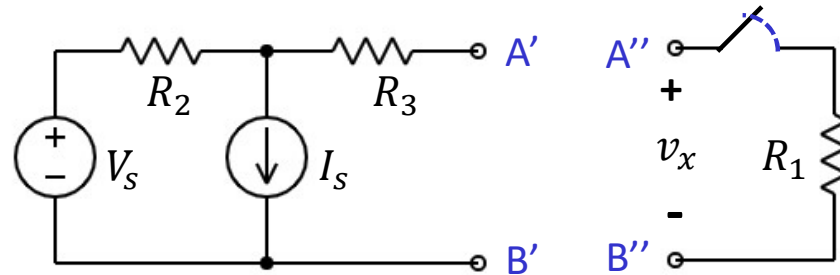- (b) Consider the two circuits on the right (you are not given the values of R_2 , R_3 , V_s or I_s). We connect the two circuits together, A' to A'' and B' to B'' and do two measurements. When the switch is open, we measure $v_x = X$. When the switch is closed, we measure $v_x = Y$.



On the right, the circuit between A' and B' is the same as the one above and the circuit between A and B is the same as the one in part (a).

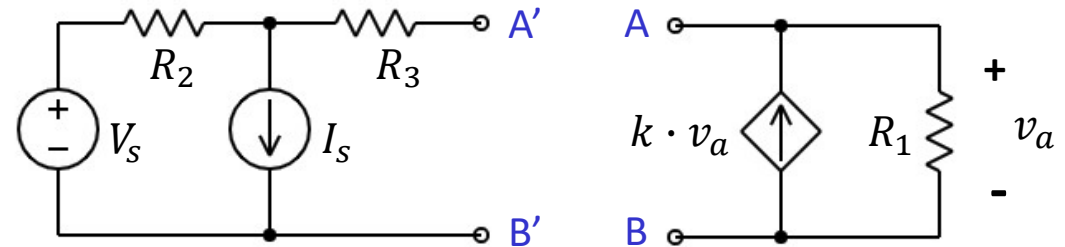If we connect them together, A' to A and B' to B, what is value of v_a ?




For $t < 0$ s, the switch is closed and you may assume the system has reached steady state. The switch opens at $t = 0$ s and remains open.

- (a) Find $i_a(0^-)$ (i.e., just before the switch opens)
- (b) Find $v_b(0^+)$ (i.e., right after the switch opens)
- (c) Find $i_a(4 \text{ s})$
- (d) Find $v_b(4 \text{ s})$


Note: For any of the parts, you can leave your answers as a function of e .

R1:	4 Ω
R2:	1 Ω
R3:	1 Ω
R4:	3 Ω
I _s :	12 A
k:	2 A/A
C:	4 F
L:	8 H

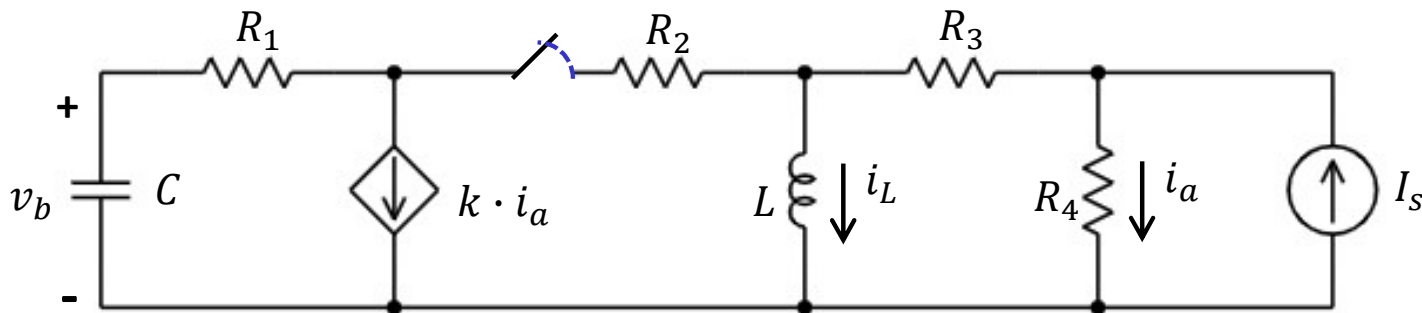



The AC circuit below is in steady state.

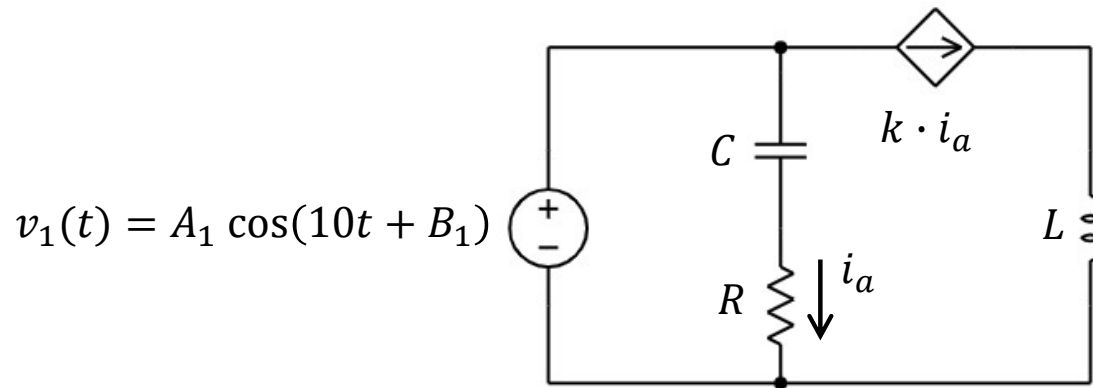- What is the maximum value of the waveform $i_a(t)$?
- Find the complex power \underline{S} supplied by the voltage source v_1 .
- Find the average power \underline{P} received by that same voltage source v_1 .



R:	2Ω
C:	100 mF
L:	100 mH
k:	3 A/A
A1:	10 V
B1:	-15 degrees
T:	4 s

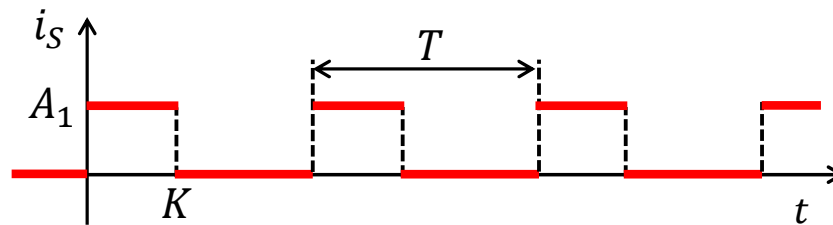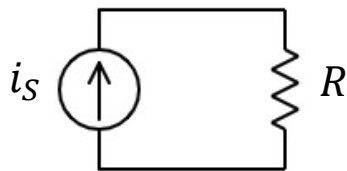- In the circuit below, the waveform $i_S(t)$ is periodic with period T . The resistor R is the same as in the circuit above. Find the value of K such that the average power received by the resistor in the circuit below is the same as by the resistor in the circuit above.



In the circuit, v_1 and v_2 are AC sources with $\omega = 100 \text{ rad/s}$. The phasor diagram shows the phasors of v_1 and v_2 . It is not drawn to scale. You may assume the system is in steady state.

V_3 is a DC source.

$ V_1 $:	2 V
$ V_2 $:	3 V
alpha:	30 degrees
V_3 :	3 V
C:	10 mF
L:	25 mH

(a) What is $v_2 \left(\frac{T}{4} \right)$ where T is the period of the waveform?

(b) What is the waveform $i_a(t)$?

(c) What is the maximum value of the waveform $v_a(t)$?

