

# AC power 008

Problem has been graded.

Both  $v_S$  and  $i_S$  are AC sources with  $\omega = 400$  rad/s. Someone did two measurements on the circuit and found:


$$v_1(t) = A_1 \cos(400t + B_1) \quad (\text{this is } v_L, \text{ not } v_S !)$$

$$i_S(t) = 2 \cos\left(400t + \frac{\pi}{6}\right)$$

(a) Find the average power  $P_1$  received by the resistor

(b) Find the average power  $P_2$  supplied by current source  $i_S$

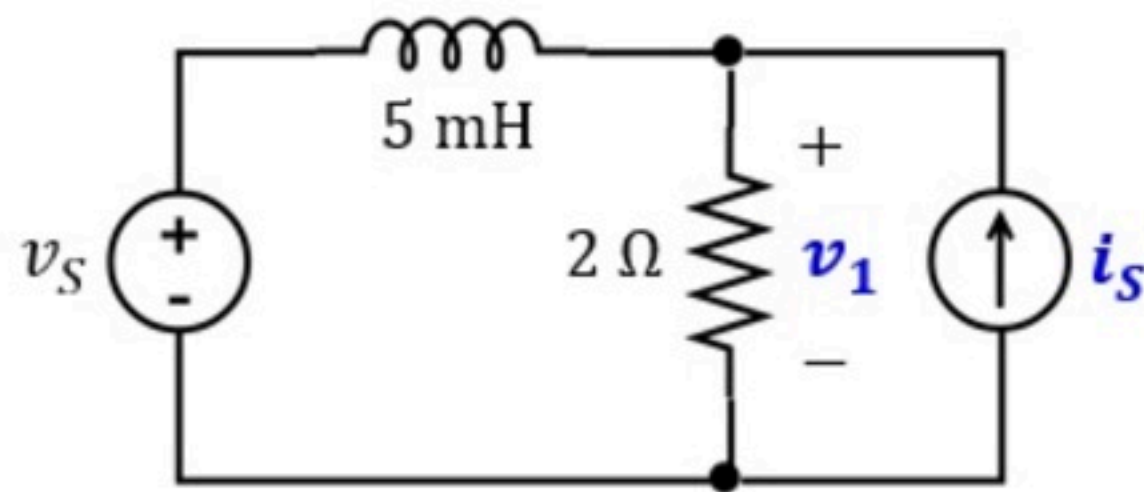(c) Find the average power  $P_3$  received by the inductor



Given Variables:

A1 : 8 V

B1 : 90 degrees

Calculate the following:

P1 (W) :

16

✓

P2 (W) :

4

✓

P3 (W) :

0

✓

Hint: Find S symbolically first. Find phasors and plug in. For c, what do you know about the element?