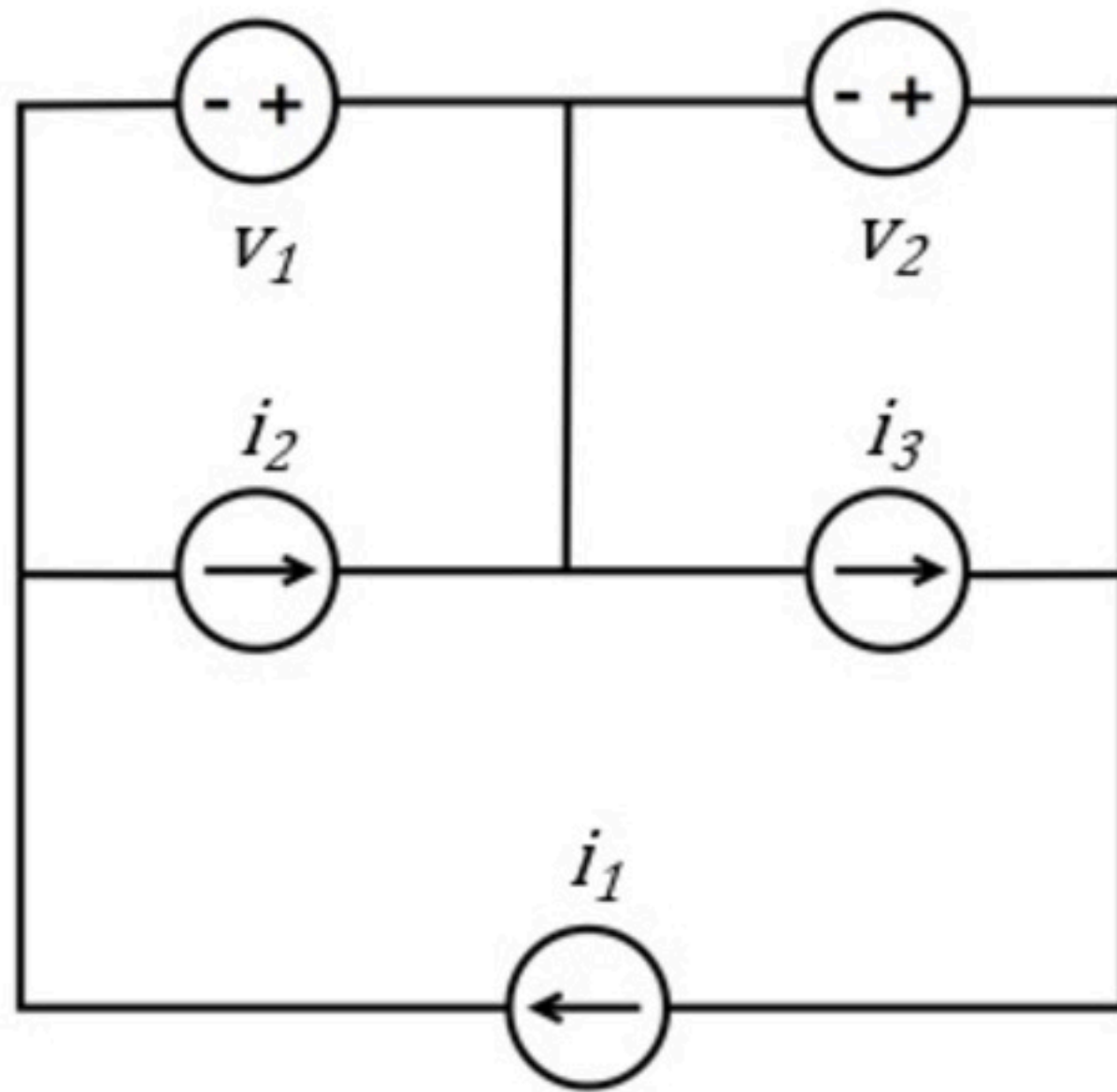


Basic analysis 002

Problem has been graded.

Determine the power P_1 supplied by voltage source v_1 and the power P_2 supplied by voltage source v_2 .



Given Variables:

i_1 : 4 A

i_2 : 2 A

i_3 : 3 A

v_1 : 3 V

v_2 : 4 V

Calculate the following:

P_1 (W) :

P_2 (W) :