

ECE 35, Winter 2019

Quiz 4

/ 12

Last name

First + middle  
name(s)

PID

**Instructions:**

- Read each problem completely and thoroughly before beginning
- All calculations need to be done on these sheets
- Write your answers in the answer boxes for each question. Make sure you list units!
- Answers without supporting calculations will receive zero credit

(1) The system is in steady state. The phasor diagram shows the voltages  $V_a$  and  $V_b$  (but you are not told which one is which). The current source is a sine wave with  $\omega = 1$  rad/s.

(a) Find  $v_i\left(\frac{3\pi}{4}\text{ s}\right)$ , i.e.,  $v_i$  at time  $t = \frac{3\pi}{4}$  seconds.  
(2 points)



$v_i\left(\frac{3\pi}{4}\text{ s}\right)$



(b) What is the value of  $A$ ?  
(2 points)

$A$

(c) What is the value of capacitor  $C_a$ ?  
(3 points)

$C_a$

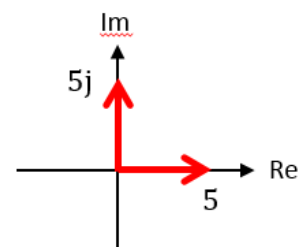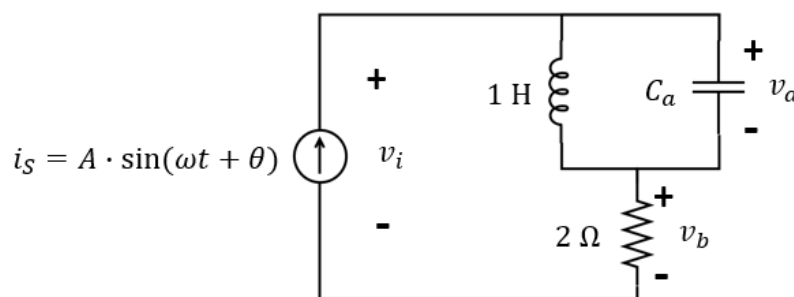

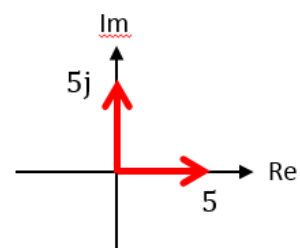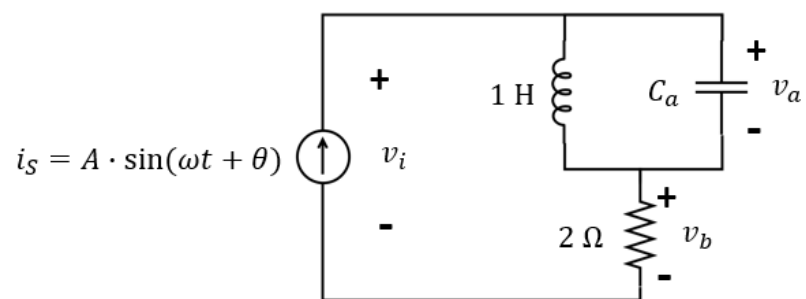

- (2) The system is in steady state. Find  $v_a\left(\frac{\pi}{10}\text{ s}\right)$ , i.e.,  $v_a$  at time  $t = \frac{\pi}{10}$  seconds. (5 points)

$$v_a\left(\frac{\pi}{10}\text{ s}\right)$$

