

ECE 35, Fall 2017
Quiz 3 - Section A

Last name

First + middle
name(s)

PID

Instructions:

- Read each problem completely and thoroughly before beginning
- All calculations need to be done on these sheets
- Write your answers in the answer boxes for each question. Make sure you list units!
- Answers without supporting calculations will receive zero credit

(1) Consider the system below (it is repeated on the next page). For $t < 0$, the switch is closed. At $t = 0$, the switch is opened and it remains open. At time $t = 0^-$, just before the switch was opened, the system was not in steady state, but it is given that $v_C(0^-) = 1V$ and $i_L(0^-) = 2A$.

(a) What is the energy in the capacitor at time $t = 0^+$, (right after the switch is opened)?


(b) Find the expression for the inductor voltage $v_L(t)$, for $t > 0$.


$v_L(t)$ in V =

(c) At time $t = 1000$, the switch is closed again. Find the capacitor voltage v_C and the inductor current i_L at time $t = \infty$.

v_C

i_L

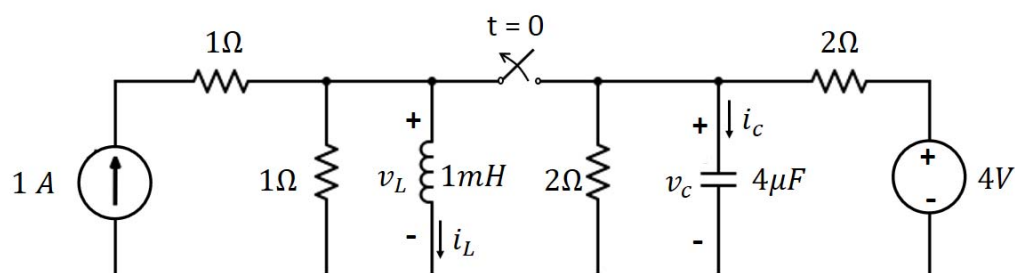

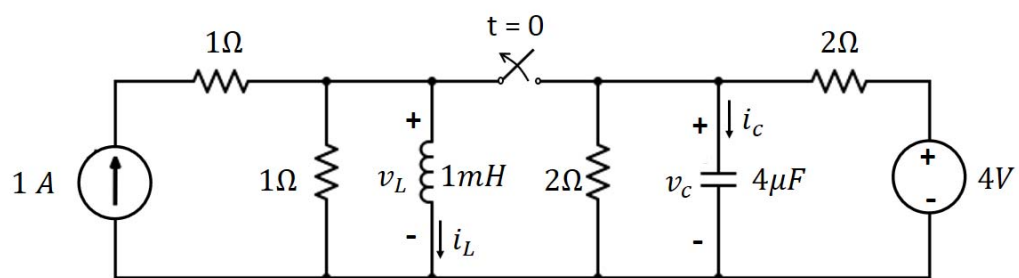

(2) Find $i_C(t)$. (Hint: you can use nodal analysis)

