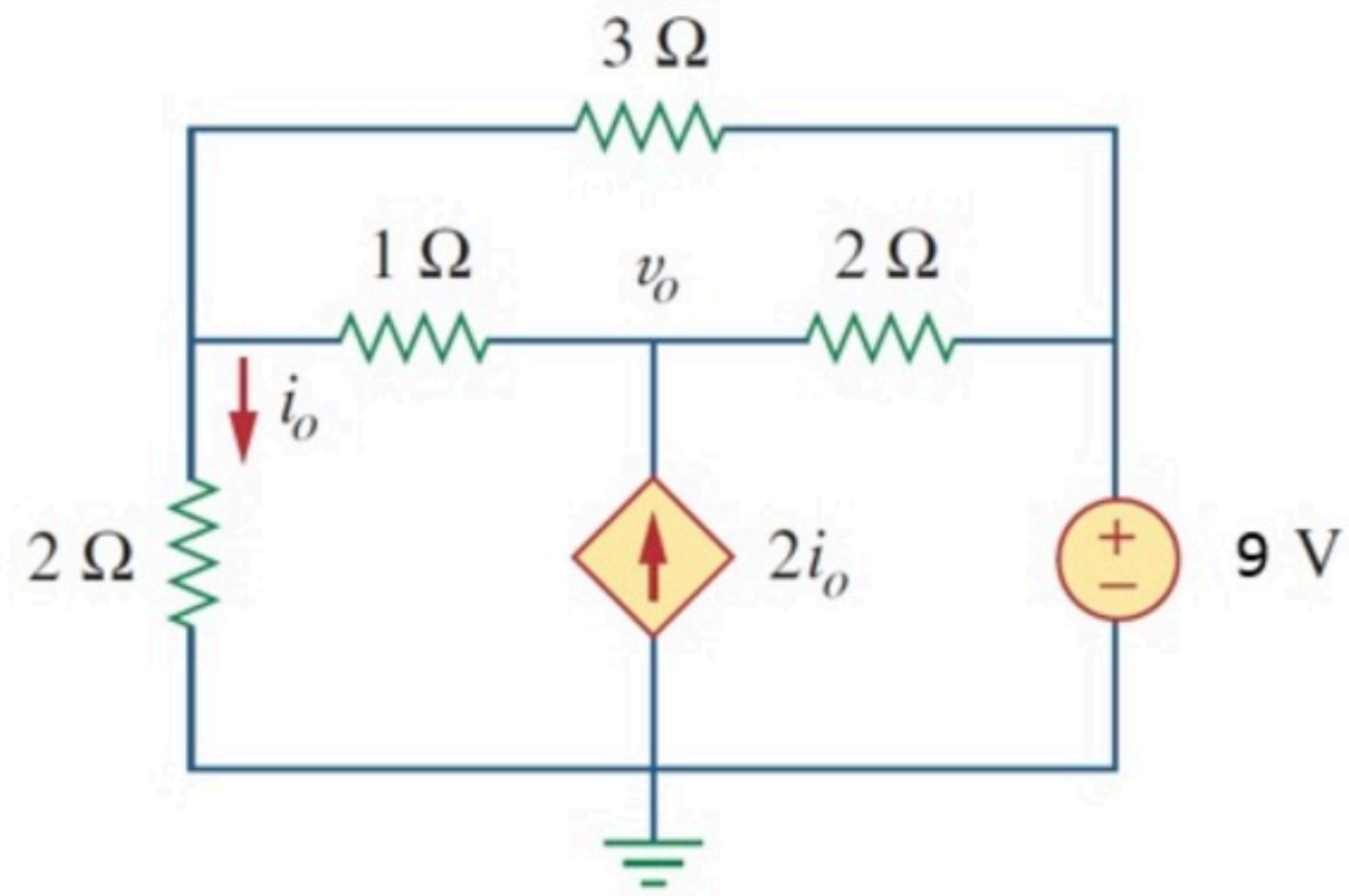


# PP Nodal Mesh 018

Unlimited Attempts.

Find the current  $i_o$  and the voltage  $v_o$ . Solve using mesh analysis.

For extra practice: Afterwards solve again using nodal analysis.



Given Variables:

...

Calculate the following:

$i_o$  (A) :

6



$v_o$  (V) :

19



Hint: Use a supermesh