Capacitors Inductors 004


Find the current i(t) in the circuit, when i(0) = 1 A and the voltage is as shown in the graph.




$$i(t) = a_3 t + a_4$$
 for 1 s < t < 4 s

$$i(t) = a_5 t + a_6$$
 for $4 s < t < 9 s$

$$i(t) = a_7 t + a_8$$
 for 9 s < t

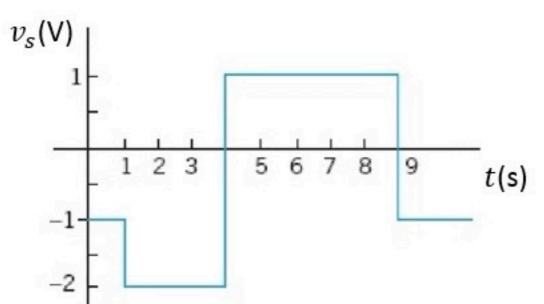

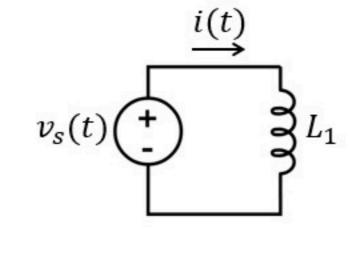

Given Variables:

L1:0.2 H

Calculate the following:

a1 (A/s):

a3 (A/s):

-10

a4 (A):

a5 (A/s):

a6 (A):

-54

a7 (A/s):

a8 (A):

36

Find the current i(t) in the circuit, when i(0) = 1 A and the voltage is as shown in the graph.

L1 = 0.1 H


$$(a) \quad i(t) = a_1 t + a_2$$


for
$$0 \le t < 1 \le$$

$$(b) \quad i(t) = a_3t + a_4$$

$$(i(t) = a_5t + a_6$$

$$0 \quad i(t) = a_7 t + a_8$$

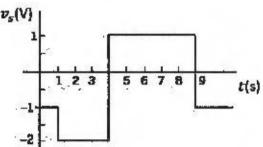

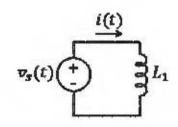

(a)
$$t_0 = 0 P$$
 : $\hat{L}(b) = 1 + \frac{1}{6.1} \int_{0}^{b} (-1) du = 1 - 10 b$

$$a_1 = 1 A$$

(1)
$$E_0 = 15$$
 $E(E) = -9 + \frac{1}{0.1} \int_{1}^{E} (-2) du = -9 - 20(E-1) = 11 - 20E$

where $E = 45$ $E(4) = 11 - 20.4 = -69A$
 $E(4) = 11 - 20.4 = -69A$
 $E(4) = 11 - 20.4 = -69A$

€
$$E_0 = 4n$$
. $\hat{c}(t) = -69 + \frac{1}{0.1} \int_{4}^{6} 1 du = -69 + 10(t-4) = -109 + 10t$
of $t = 9n$. $\hat{c}(t) = -109 + 10.9 = -13A$

$$\frac{d_5 = 10 \text{ M}_0}{06 = -109 \text{ A}}$$

(1)
$$E_0 = 30$$
. $i(t) = -19 + \frac{1}{0.1} \int_{0.1}^{t} \frac{(-1)du}{3} = -19 \cdot i0(t-5) = 71 - 10t$

$$a_8 = 71 A$$