


# Circuit theorems 017

No more attempts left.


The box contains a linear circuit. This same circuit is placed into the three configurations shown below.

The reading of the ammeter in configuration 1 is given as  $X$ .

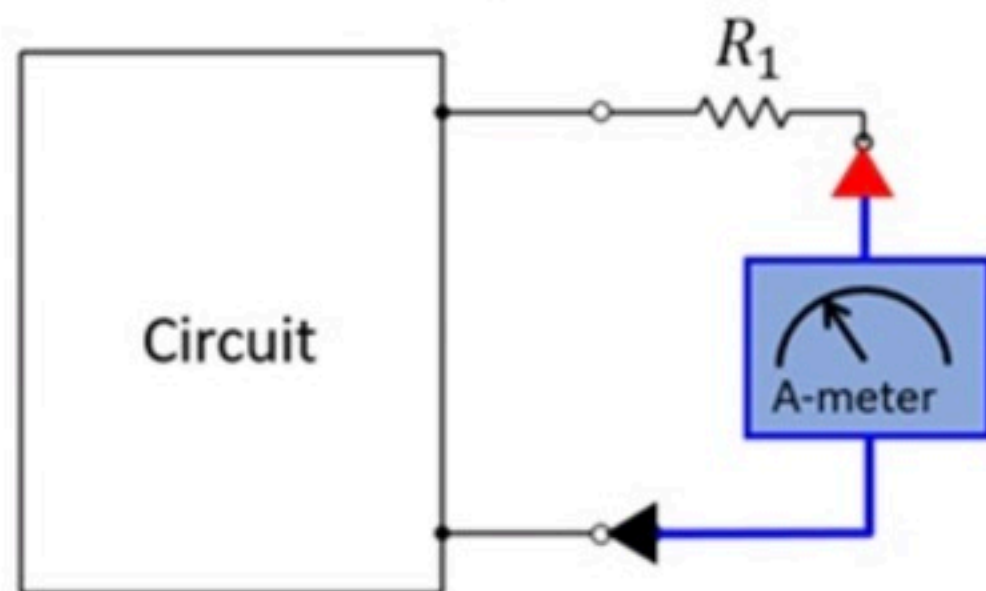
Find the current  $i_3$  in configuration 3.



Configuration 1

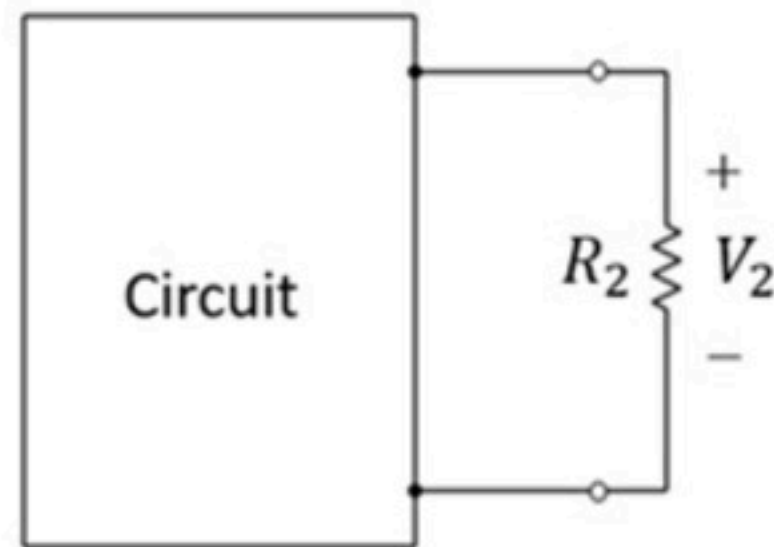

Configuration 2

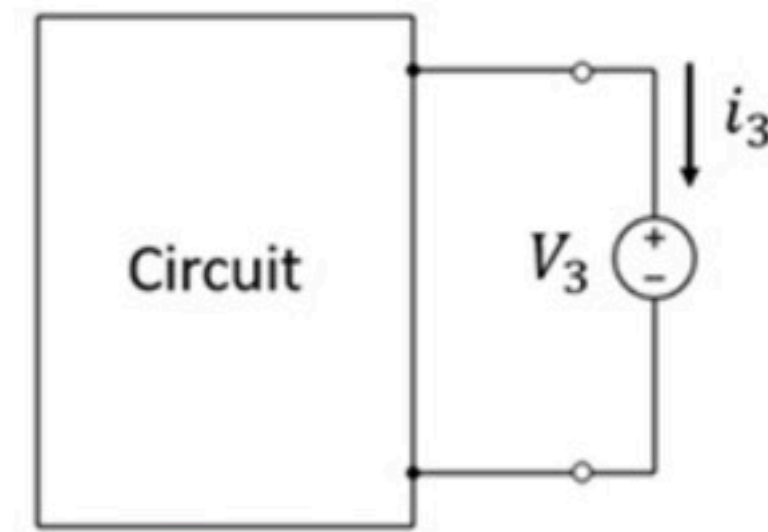

Configuration 3

Given Variables:

$X : 8 \text{ A}$

$R1 : 1 \text{ ohm}$

$V2 : 20 \text{ V}$

$R2 : 10 \text{ ohm}$

$V3 : 2 \text{ V}$

Calculate the following:

$i_3 \text{ (A)} :$

Hint: Replace the circuit in the box as its Thevenin equivalent model