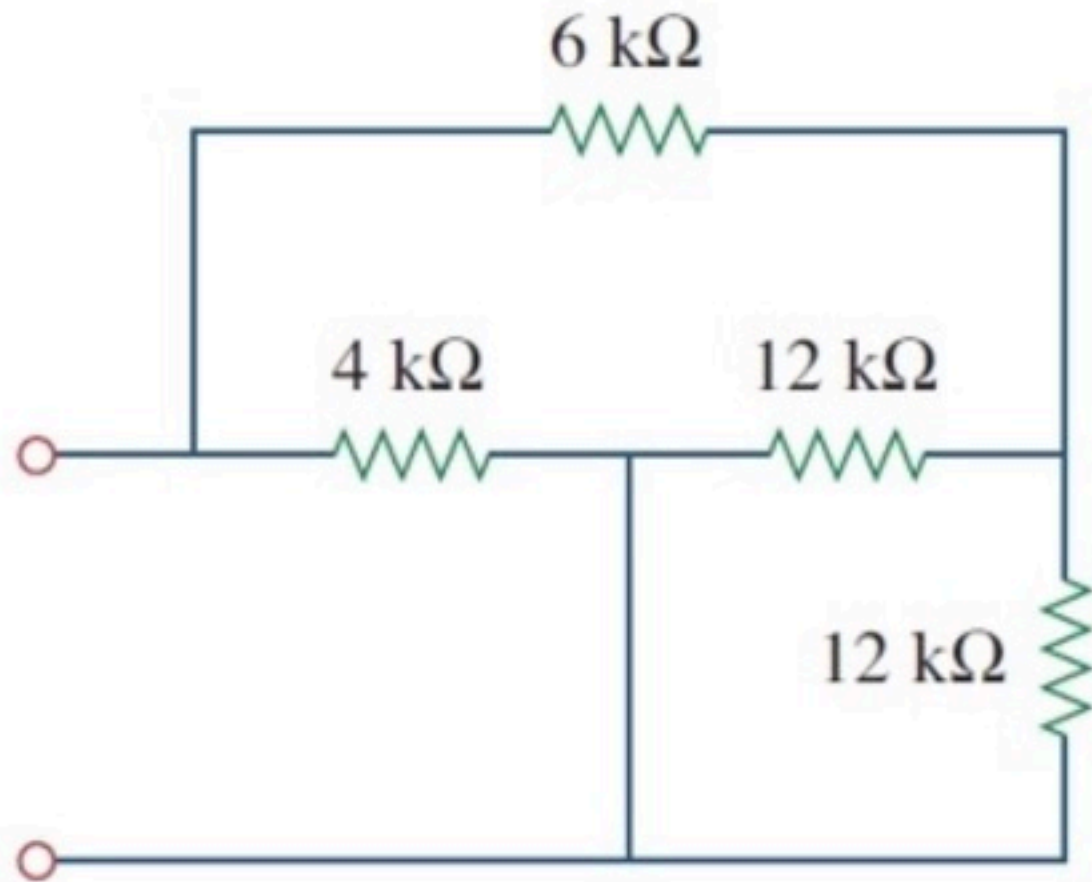


# PP - Basic analysis 010

Problem has been graded.

Find  $R_{eq}$  looking into the terminals.



Given Variables:

...

Calculate the following:

Req (ohm) :

3000



Hint: Check units