

AC power 008


Problem has been graded.

Both v_S and i_S are AC sources with $\omega = 400$ rad/s. Someone did two measurements on the circuit and found:

$$v_1(t) = A_1 \cos(400t + B_1) \quad (\text{this is } v_L, \text{ not } v_S !)$$

$$i_S(t) = 2 \cos\left(400t + \frac{\pi}{6}\right)$$

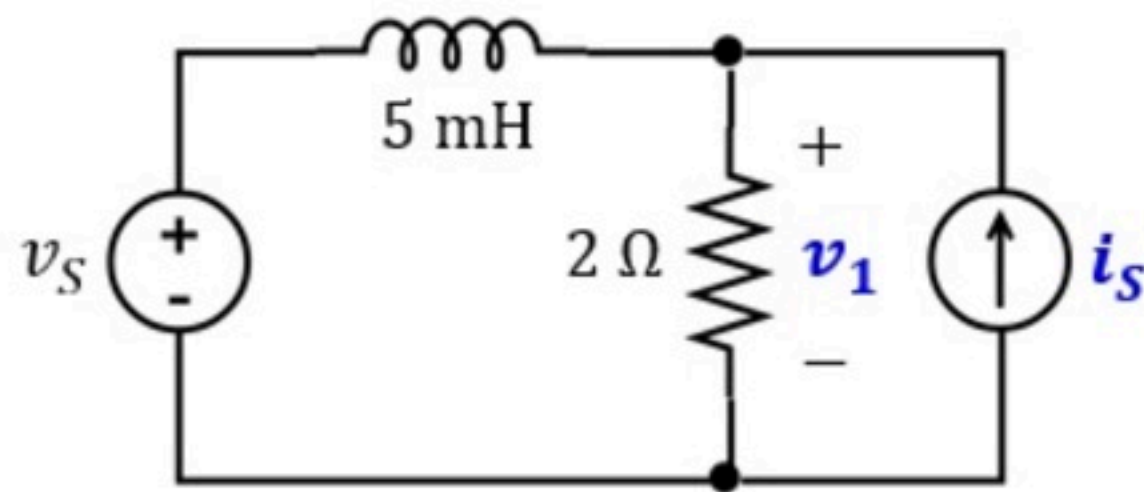- (a) Find the average power P_1 received by the resistor
- (b) Find the average power P_2 supplied by current source i_S
- (c) Find the average power P_3 received by the inductor



Given Variables:

A1 : 8 V

B1 : 90 degrees

Calculate the following:

P1 (W) :

16

✓

P2 (W) :

4


✓

P3 (W) :

0

✓

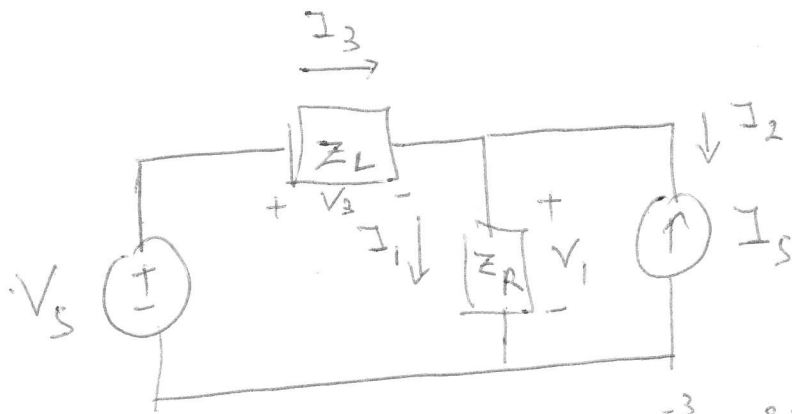Hint: Find S symbolically first. Find phasors and plug in. For c, what do you know about the element?



$$A_1: 10 \text{ V}$$

$$B_1: -90^\circ$$

$$Z_L = j\omega L = j \cdot 400 \cdot 5 \cdot 10^{-3} = 2j$$

$$Z_R = 2$$

$$\begin{aligned} \textcircled{a} \quad S_1 &= \frac{1}{2} V_1 \cdot I_1^* & I_1 &= \frac{V_1}{Z_R} \\ &= \frac{1}{2} V_1 \left(\frac{V_1}{Z_R} \right)^* = \frac{1}{2} \frac{V_1 V_1^*}{Z_R} = \frac{|V_1|^2}{2} \cdot \frac{1}{Z_R} = \frac{A_1^2}{2} \cdot \frac{1}{Z_R} = \frac{100}{2 \cdot 2} = 25 \end{aligned}$$

$$P_1 = \text{Re}[S_1] \quad \boxed{P_1 = 25 \text{ W}} \text{ received}$$

$$\begin{aligned} \textcircled{b} \quad S_2 &= \frac{1}{2} V_1 I_2^* \leadsto \text{PASSIVE SIGN CONVENTION (POWER RECEIVED)} \\ &= \frac{1}{2} V_1 (-I_S)^* \\ &= -\frac{1}{2} V_1 I_S^* \\ &= -\frac{1}{2} \cdot 10 e^{-j\frac{\pi}{2}} \cdot 2 e^{-j\frac{\pi}{6}} = -10 e^{-j\frac{4\pi}{6}} = -10 e^{-j\frac{2\pi}{3}} \end{aligned}$$

$$P_2 = \text{Re}[S_2] = -10 \cos\left(-\frac{2\pi}{3}\right) = -10 \left(-\frac{1}{2}\right) = +5 \leadsto \text{received}$$

$$\boxed{P_2 = -5 \text{ W}} \text{ supplied}$$

$$\textcircled{c} \quad \boxed{P_3 = 0 \text{ W}} \text{ inductor always has } P=0$$

$$\begin{aligned} \text{we can check: } S_3 &= \frac{1}{2} V_3 I_3^* & V_3 &= Z_L \cdot I_3 \\ &= \frac{1}{2} Z_L I_3 \cdot I_3^* = \frac{Z_L}{2} |I_3|^2 = \frac{|I_3|^2}{2} \cdot (2j) \end{aligned}$$

no real part $\Rightarrow P = \text{Re}[S] = 0$