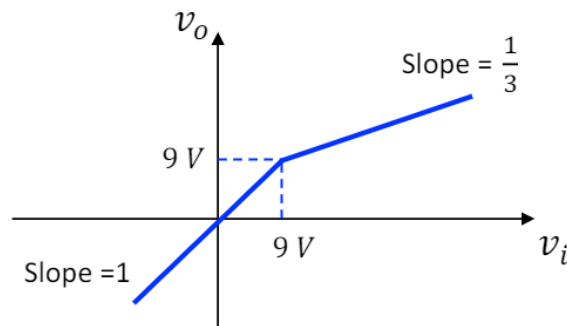


- a) Design a diode waveform shaping circuit that would have the below transfer characteristics.
- You can use PN junction diodes and Zener diodes with  $V_{D0} = 0.7\text{ V}$ ,  $V_Z = 4\text{ V}$ , DC voltage sources, and resistors in your design.
  - You must use a Zener diode in your design.**
  - In your circuit schematic, show  $v_i$  with the symbol of a voltage source. Clearly label the terminals that are used to measure the output.
- b) Write the possible cases of the operation of the diode(s) in your designed circuit, and for each case, include the calculation of finding  $v_o$  and the range of  $v_i$ .
- Show your work.**
- c) Sketch the output,  $v_o(t)$ , for  $0 \leq t \leq 2\text{ ms}$ , if the input is a 5V DC signal,  $v_i(t) = 5\text{ V}$ .



### Solution:

(a) Here,

$$v_o = \begin{cases} v_i; & v_i < 9 \\ \frac{v_i}{3} + 9 \times \frac{2}{3}; & v_i \geq 9 \end{cases}$$


- (b) D2 can never be ON as  $i_{D2}$  must be less than or equal to 0 depending on the state of D1. Therefore, there are two possible cases of operation.

#### D1 ON, D2 Zener

$$v_o = 4.3 + V_{D0} + V_Z + (v_i - (4.3 + V_{D0} + V_Z)) \frac{R2}{R1 + R2}$$

$$\Rightarrow v_o = v_i \frac{R2}{R1 + R2} + 9 \frac{R1}{R1 + R2} = \frac{v_i}{3} + 9 \times \frac{2}{3}$$

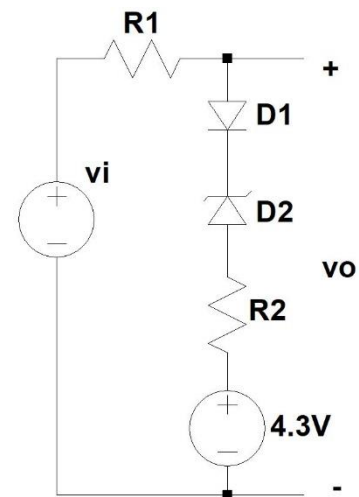From the equation,  $R1 = 2R2$ . Taking  $R1=2\text{k}\Omega$  and  $R2=1\text{k}\Omega$



To operate in this condition, we need to make sure that  $i_{D1} \geq 0$ . Then,

$$\begin{aligned} i_{D1} &\geq 0 \\ \Rightarrow \frac{v_i - 9}{1k + 2k} &\geq 0 \Rightarrow v_i \geq 9 \end{aligned}$$

### D1 OFF, D2 OFF

$$i_{D1} = i_{D2} = 0$$

Then,

$$v_o = v_i$$

To operate in this condition, we need to make sure that  $v_{D1} < V_{Do}$  and  $-V_Z < v_{D2} < V_{Do}$ . Thus,

$$\begin{aligned} v_o = v_i &= v_{D1} - v_{D2} + 4.3 \\ \Rightarrow v_i &< V_{Do} + V_Z + 4.3 \\ \Rightarrow v_i &< 9 \end{aligned}$$

(c)

