

Quiz 2

/ 12

Last name

First + middle
name(s)

PID

Instructions:

- Read each problem completely and thoroughly before beginning.
- All calculations need to be done on these sheets.
- Write your answers in the answer boxes for each question. Make sure you list units!
- Answers without supporting calculations will receive zero credit.

- (1) (6 points) Consider the circuit below. At time $t = 1$ s, the current source changes as shown in the figure, and will not change after that. Immediately before the current source changes, the system is not guaranteed to have reached steady-state.

However, you are told that immediately after the change, i.e., at time $t = 1^+$, the node voltage $v_a = 2$ V. In other words: $v_a(1^+ \text{ s}) = 2$ V.

- (a) Find $i_x(1^+ \text{ s})$. (i.e., the current just after the current source changes)

 $i_x(1^+ \text{ s})$



- (b) Find $v_a(1^- \text{ s})$. (i.e., the node voltage just before the current source changes)

 $v_a(1^- \text{ s})$



- (c) Find $i_x(\infty)$.

 $i_x(\infty)$



- (d) Find $i_x(6 \text{ s})$. (i.e., the current at time $t = 6$ s).
You can leave your answer as a function of e.

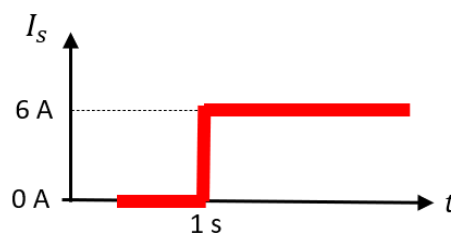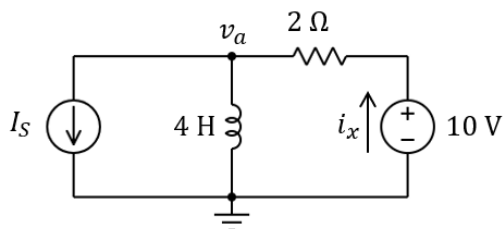 $i_x(6 \text{ s})$ 

Repeated
from the
previous
page ...

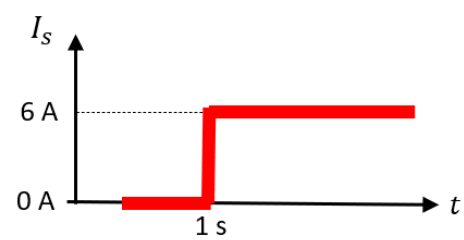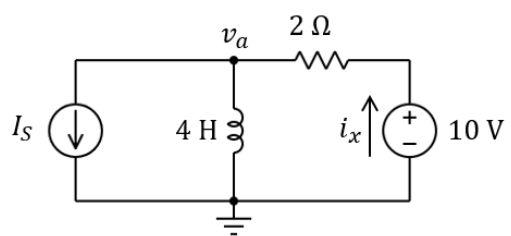

Repeated
from the
previous
page ...

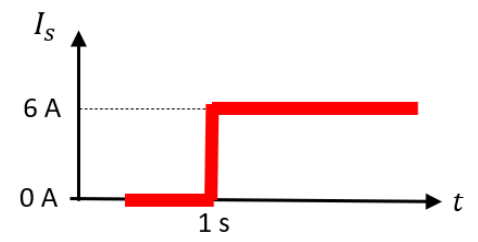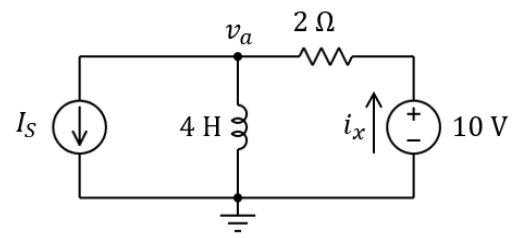

- (2) (6 points) Consider the circuit below in Figure 1. You are not told the values of I_1 and V_1 . However, you are told that if you attach the circuit from Figure 2 to the one from Figure 1 (with A' connected to A and B' connected to B), the value of $i_a = 3$ A.

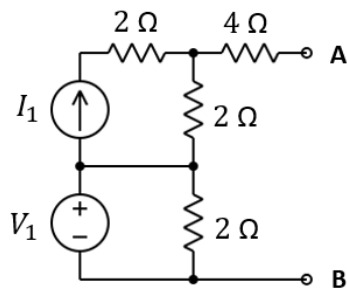


Figure 1

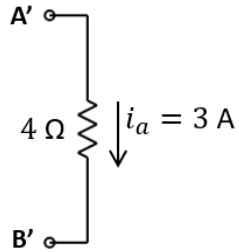


Figure 2

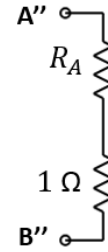


Figure 3

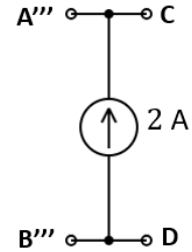


Figure 4


- (a) Draw the Thevenin model between A and B for the circuit in Figure 1 (make sure you label A and B in your drawing).



- (b) The circuit from Figure 3 is attached to the one from Figure 1 (with A'' connected to A and B'' connected to B). What should be the value of R_A to maximize the power received by R_A ?

R_A

 - (c) The circuit from Figure 4 is attached to the one from Figure 1 (with A''' connected to A and B''' connected to B). For this new combined circuit, draw the Norton model between C and D (make sure you label C and D in your drawing).



Repeated
from the
previous
page ...

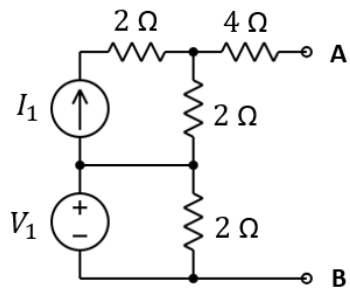


Figure 1

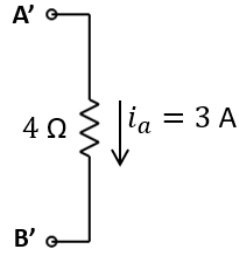


Figure 2

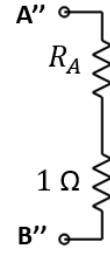


Figure 3

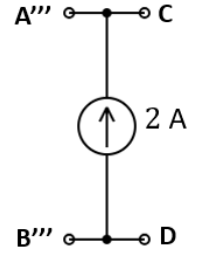


Figure 4

Repeated
from the
previous
page ...

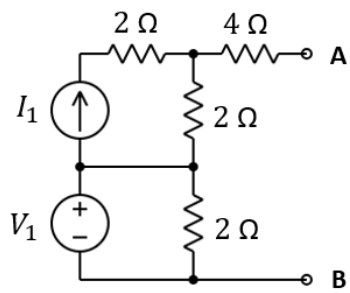


Figure 1

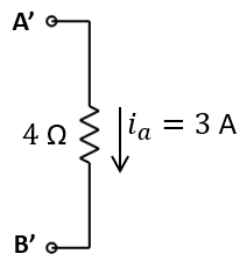


Figure 2

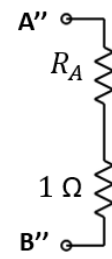


Figure 3

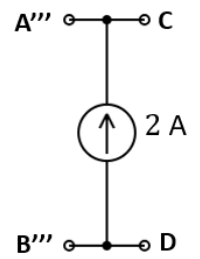


Figure 4

ECE35 Equation Sheet

Basics: $i \triangleq \frac{dq}{dt}$ $v_{ab} \triangleq \frac{dw}{dq}$ $R = \rho \frac{l}{A}$

Capacitors: $C = \epsilon \cdot \frac{A}{d}$ $Q = C \cdot v$ $w_C = \frac{1}{2} C v^2$

Inductors: $L = \mu \cdot \frac{N^2 A}{l}$ $B \sim i$ $w_L = \frac{1}{2} L i^2$

AC power: $p(t) = \frac{1}{2} V_m I_m \cdot \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cdot \cos(2\omega t + \theta_v + \theta_i)$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \quad Q = \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i) \quad X_{rms} = \sqrt{\frac{1}{T} \int_0^T x(t)^2 dt}$$

Trigonometry:

$\sin(-\alpha) = -\sin(\alpha)$	$\cos(-\alpha) = \cos(\alpha)$
$\sin(\pi - \alpha) = \sin(\alpha)$	$\cos(\pi - \alpha) = -\cos(\alpha)$
$\sin\left(\frac{\pi}{2} - \alpha\right) = \cos(\alpha)$	$\cos\left(\frac{\pi}{2} - \alpha\right) = \sin(\alpha)$
$\sin\left(\alpha - \frac{\pi}{2}\right) = -\cos(\alpha)$	$\cos\left(\alpha - \frac{\pi}{2}\right) = \sin(\alpha)$
$\sin(2\alpha) = 2 \sin(\alpha) \cos(\alpha)$	$\cos(2\alpha) = \cos^2(\alpha) - \sin^2(\alpha)$

$\sin(\alpha \pm \beta) = \sin(\alpha) \cos(\beta) \pm \cos(\alpha) \sin(\beta)$	$\alpha:$	0	$\frac{\pi}{6}$	$\frac{\pi}{4}$	$\frac{\pi}{3}$	$\frac{\pi}{2}$
$\cos(\alpha \pm \beta) = \cos(\alpha) \cos(\beta) \mp \sin(\alpha) \sin(\beta)$						
$\sin(\alpha) \sin(\beta) = 0.5 \cdot (\cos(\alpha - \beta) - \cos(\alpha + \beta))$	$\sin(\alpha):$	0	$\frac{1}{2}$	$\frac{\sqrt{2}}{2}$	$\frac{\sqrt{3}}{2}$	1
$\cos(\alpha) \cos(\beta) = 0.5 \cdot (\cos(\alpha - \beta) + \cos(\alpha + \beta))$	$\tan(\alpha):$	0	$\frac{\sqrt{3}}{3}$	1	$\sqrt{3}$	∞
$\sin(\alpha) \cos(\beta) = 0.5 \cdot (\sin(\alpha - \beta) + \sin(\alpha + \beta))$						