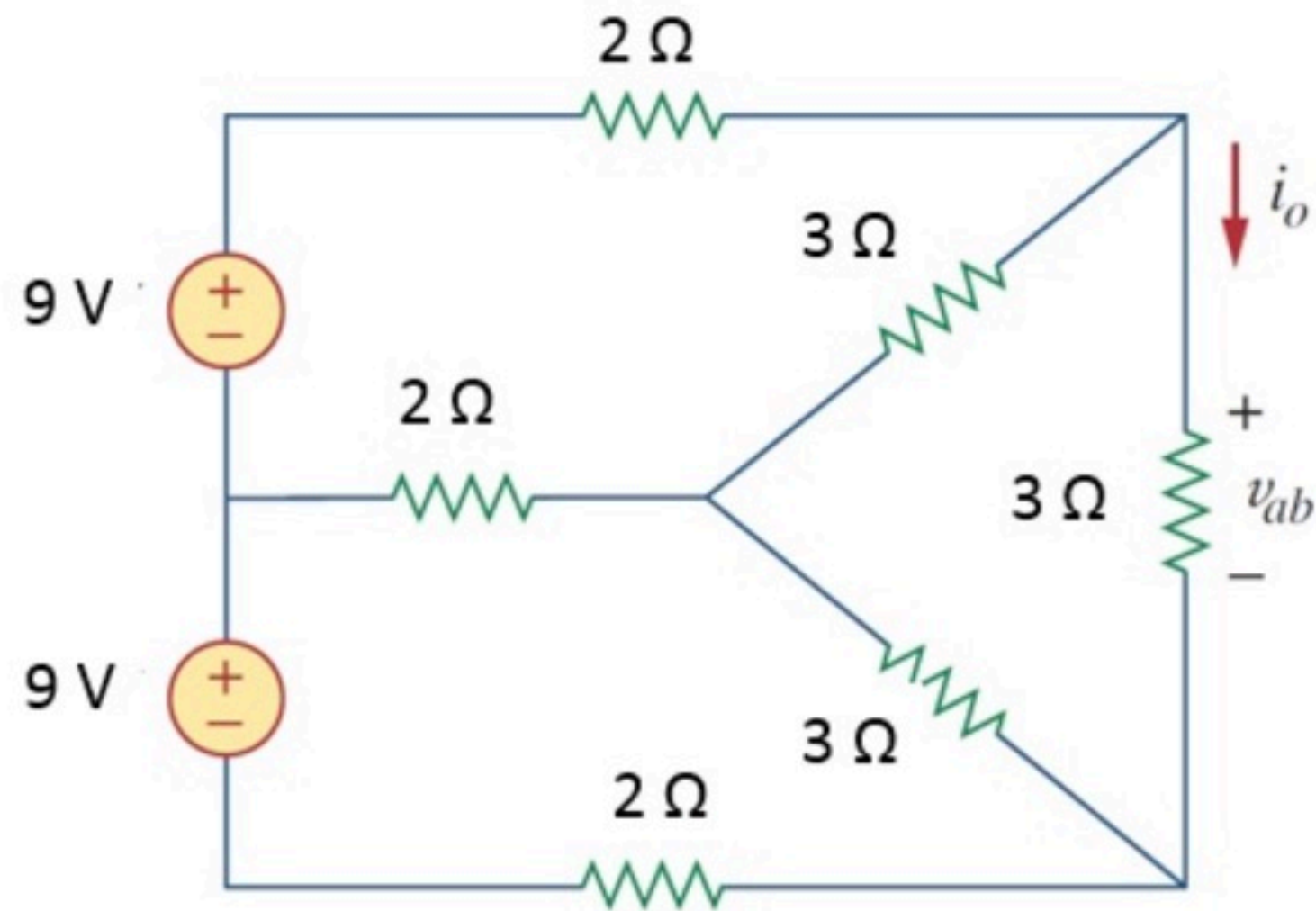


PP Nodal Mesh 016

Unlimited Attempts.

Find the current i_o and the voltage v_{ab} . Solve using mesh analysis.

For extra practice: Afterwards solve again using nodal analysis.



Given Variables:

. . .

Calculate the following:

i_o (A) :

2



v_{ab} (V) :

6



Hint: Afterward, check the symmetry