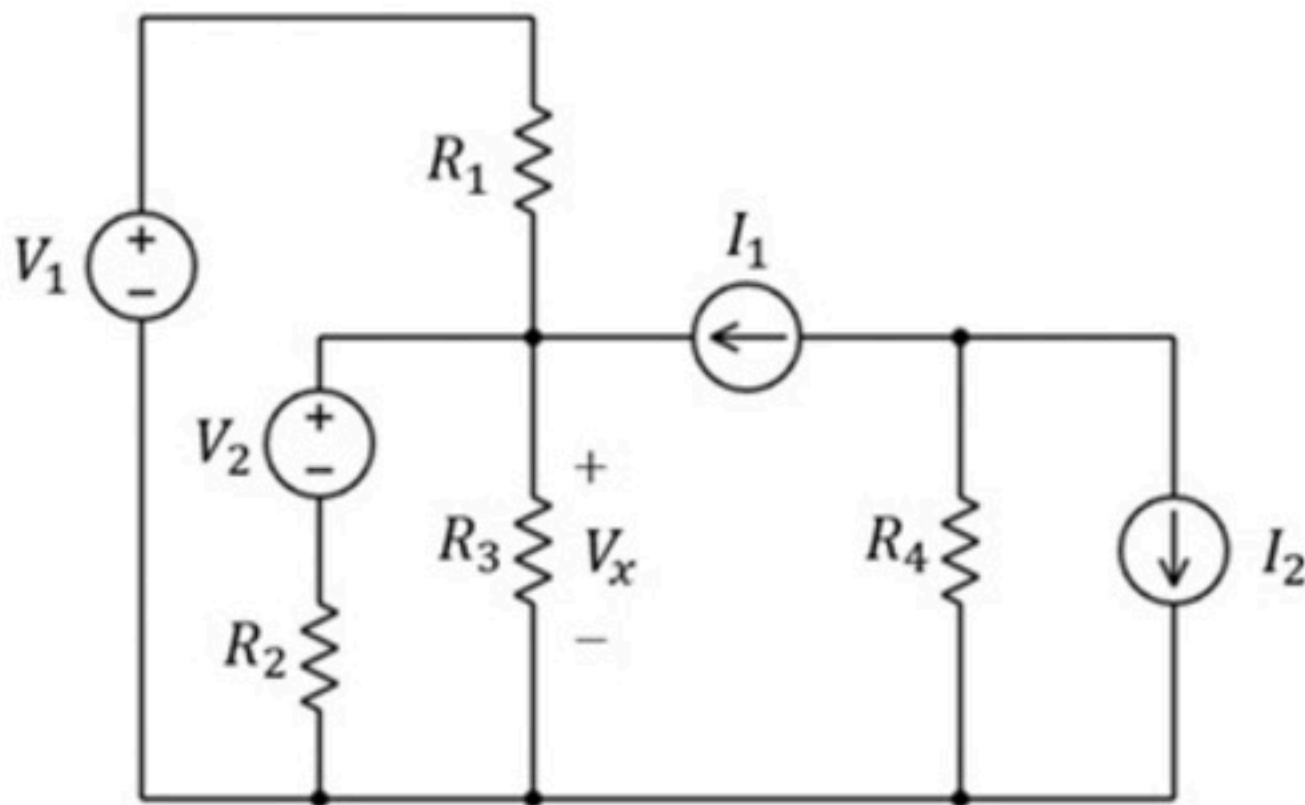


Circuit theorems 015

Problem has been graded.

Consider the circuit below. You are not given the values of V_1 , V_2 and I_2 . However, you are told the values of the other components and that of V_x .

- (a) What is the new value of V_x when all the source values (i.e., V_1 , V_2 , I_1 and I_2) are doubled? We will call this new value V_{x1} .
- (b) What is the new value of V_x when only I_1 is doubled and the other sources are what they were originally? We will call this new value V_{x2} .



Given Variables:

R_1 : 10 ohm

R_2 : 10 ohm

R_3 : 5 ohm

R_4 : 7 ohm

I_1 : 2 A

V_x : 16 V

Calculate the following:

V_{x1} (V) :

V_{x2} (V) :

Hint: Use linearity and superposition to express V_x as a linear combination of all sources