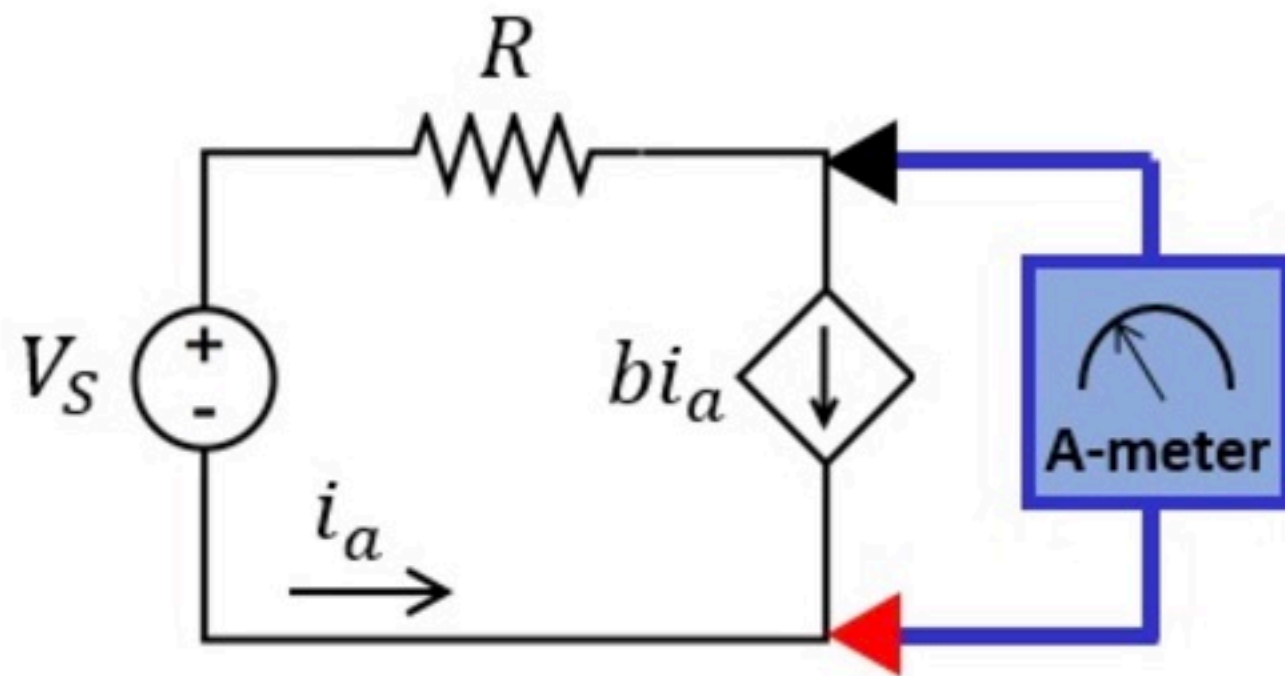


Basic analysis 014

No more attempts left.

What is the reading X from the ammeter?

What would be the reading Y if we replaced the ammeter by a volt-meter?



Given Variables:

V_S : 8 V

R : 4 ohm

b : 2 A/A

Calculate the following:

X (A) :

Y (V) :

Hint: Ammeters and volt meters behave as short and open circuits respectively. Trust the math.