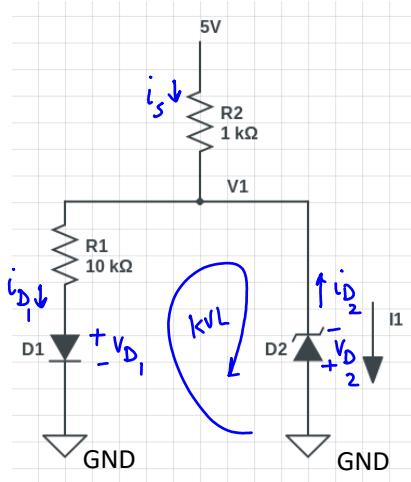


ECE 65 - HW#1 solutions

Problem 1.

In the following circuit find V1 and I1. ($V_Z = 3 \text{ V}$ and $V_{D0} = 0.7 \text{ V}$)



Assume D_1 is ON and D_2 is in Zener region:

$$V_{D_1} = V_{D_0} = 0.7 \text{ V} \quad \& \quad V_{D_2} = -V_Z = -3 \text{ V} \quad \& \quad i_{D_2} \leq 0 \quad \& \quad i_{D_1} \geq 0$$

$$\text{KVL: } -V_{D_1} + 10\text{k}\Omega \times (-i_{D_1}) - V_{D_2} = 0 \rightarrow -0.7 \text{ V} - 10\text{k}\Omega \times i_{D_1} + 3 \text{ V} = 0$$

$$\rightarrow i_{D_1} = \frac{2.3 \text{ V}}{10\text{k}\Omega} = 0.23 \text{ mA} \geq 0 \quad \checkmark$$

$$V_1 = -V_{D_2} = +V_Z = 3 \text{ V}$$

$$\text{Ohm's law: } i_s = \frac{5\text{V} - V_1}{1\text{k}\Omega} = \frac{5\text{V} - 3\text{V}}{1\text{k}\Omega} = 2 \text{ mA}$$

$$\text{KCL: } i_s = i_{D_1} - i_{D_2} \rightarrow i_{D_2} = i_{D_1} - i_s = 0.23 \text{ mA} - 2 \text{ mA} = -1.77 \text{ mA} \leq 0 \quad \checkmark$$

$i_{D_1} \geq 0$ & $i_{D_2} \leq 0$ → assumption was correct.



$$\boxed{I_1 = -i_{D_2} = 1.77 \text{ mA}}$$

$$\boxed{V_1 = 3 \text{ V}}$$

Problem 2.

Design a diode waveform shaping circuit that would have the below transfer function.

$$V_{D_0} = 0.7 \text{ V}$$

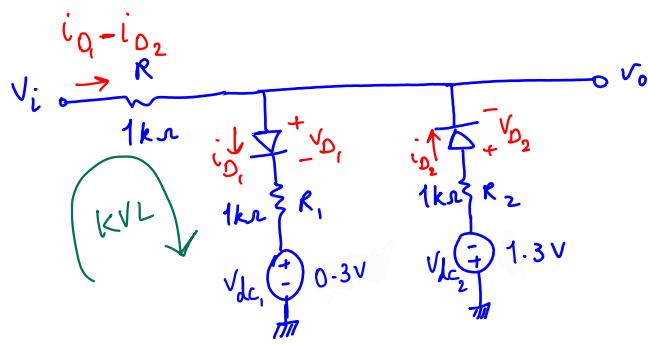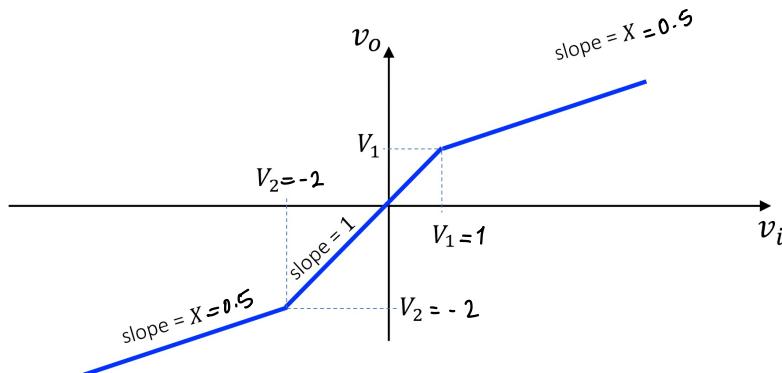

From the graph:

$$\left\{ \begin{array}{l} \text{For } v_i \geq 1 \text{ V}, \quad V_o = \frac{1}{2} v_i + \frac{1}{2} \\ \text{For } v_i \leq -2 \text{ V}, \quad V_o = \frac{1}{2} v_i - 1 \\ \text{For } -2 \leq v_i \leq 1, \quad V_o = v_i \end{array} \right.$$

Case 1: D_1 ON and D_2 OFF

$$\boxed{i_{D_1} \geq 0}, \quad V_{D_1} = V_{D_0}, \quad i_{D_2} = 0, \quad V_{D_2} < V_{D_0} \quad \text{Assumed } V_{D_0} = 0.7 \text{ V}$$

$$kV L: \quad v_i = R (i_{D_1} - i_{D_2}) + V_{D_1} + R_1 i_{D_1} + V_{dc_1}$$

$$v_i = 1k\Omega \times i_{D_1} + 0.7V + 1k\Omega \times i_{D_1} + V_{dc_1}$$

$$\rightarrow i_{D_1} = \frac{v_i - 0.7V - V_{dc_1}}{2k\Omega} \geq 0 \quad \rightarrow v_i \geq 0.7V + V_{dc_1}$$


$$V_o = V_{D_1} + R_1 i_{D_1} + V_{dc_1} = V_{D_0} + 1k\Omega \times \left(\frac{v_i - 0.7V - V_{dc_1}}{2k\Omega} \right) + V_{dc_1}$$

$$V_o = \frac{1}{2} v_i + 0.35V + \frac{1}{2} V_{dc_1}$$


Problem 2.

Design a diode waveform shaping circuit that would have the below transfer function.

$$V_{D_0} = 0.7 \text{ V}$$

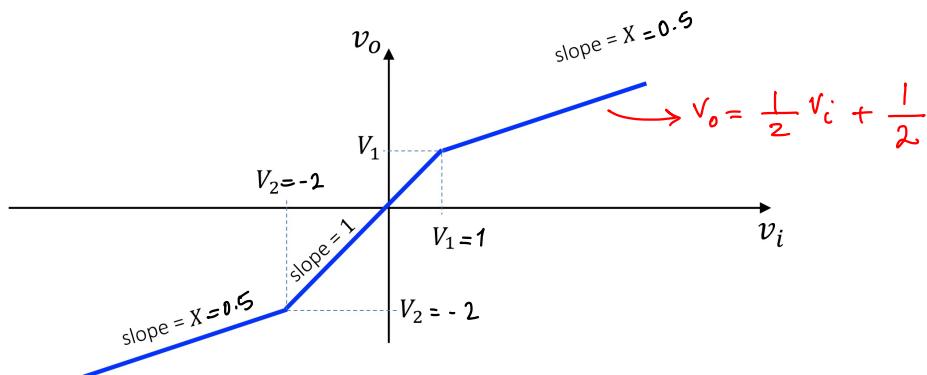

From the graph:

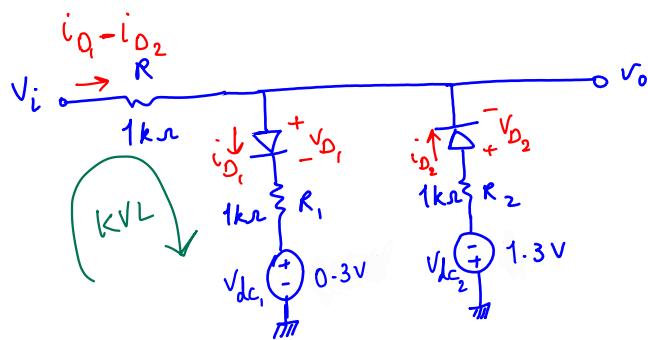

$$\left\{ \begin{array}{l} \text{For } v_i > 1 \text{ V}, \quad v_o = \frac{1}{2} v_i + \frac{1}{2} \\ \text{For } v_i \leq -2 \text{ V}, \quad v_o = \frac{1}{2} v_i - 1 \\ \text{For } -2 \leq v_i \leq 1, \quad v_o = v_i \end{array} \right.$$

Case 1: D_1 on and D_2 off

$$\text{For } v_i \geq 0.7 \text{ V} + V_{dc_1}, \quad v_o = \frac{1}{2} v_i + 0.35 \text{ V} + \frac{1}{2} V_{dc_1}$$

From the graph:



$$\text{For } v_i \geq 1 \text{ V}, \quad v_o = \frac{1}{2} v_i + \frac{1}{2}$$

If we choose $V_{dc_1} = 0.3 \text{ V} \rightarrow$ the response of the circuit will match the transfer function

Problem 2.

Design a diode waveform shaping circuit that would have the below transfer function.

$$V_{D_0} = 0.7 \text{ V}$$

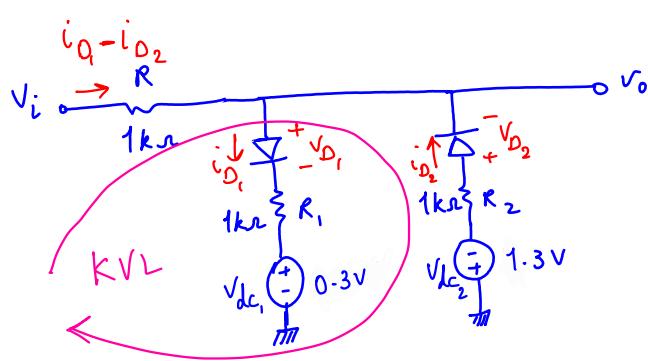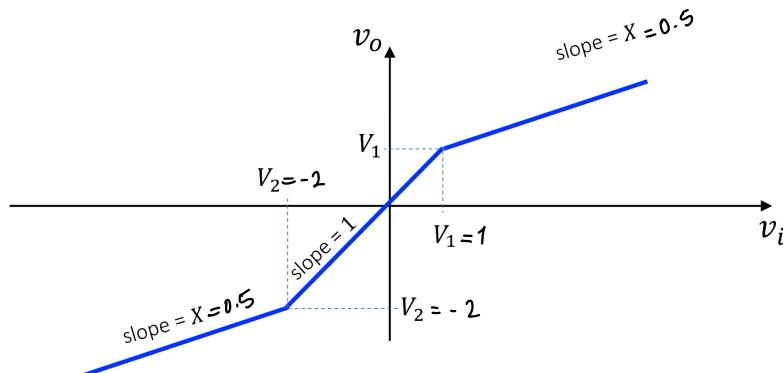

From the graph:

$$\left\{ \begin{array}{l} \text{For } v_i \geq 1V, \quad V_o = \frac{1}{2}v_i + \frac{1}{2} \\ \text{For } v_i \leq -2V, \quad V_o = \frac{1}{2}v_i - 1 \\ \text{For } -2 \leq v_i \leq 1, \quad V_o = v_i \end{array} \right.$$

Case 2: D_1 off and D_2 on

$$i_{D_2} \geq 0, \quad V_{D_2} = V_{D_0}, \quad i_{D_1} = 0, \quad V_{D_1} < V_{D_0} \quad \text{Assumed } V_{D_0} = 0.7 \text{ V}$$

$$KVL: \quad V_i = R (i_{D_1} - i_{D_2}) - V_{D_2} - R_2 i_{D_2} - V_{dc_2}$$

$$V_i = -1k\Omega \times i_{D_2} - 0.7V - 1k\Omega \times i_{D_2} - V_{dc_2}$$

$$\rightarrow i_{D_2} = \frac{-V_i - 0.7V - V_{dc_2}}{2k\Omega} \geq 0 \quad \rightarrow V_i \leq -0.7V - V_{dc_2}$$



$$V_o = -V_{D_2} - R_2 i_{D_2} - V_{dc_2} = -V_{D_0} - 1k\Omega \times \left(\frac{-V_i - 0.7V - V_{dc_2}}{2k\Omega} \right) - V_{dc_2}$$

$$V_o = \frac{1}{2}V_i - 0.35V - \frac{1}{2}V_{dc_2}$$

Problem 2.

Design a diode waveform shaping circuit that would have the below transfer function.

$$V_{D_0} = 0.7 \text{ V}$$

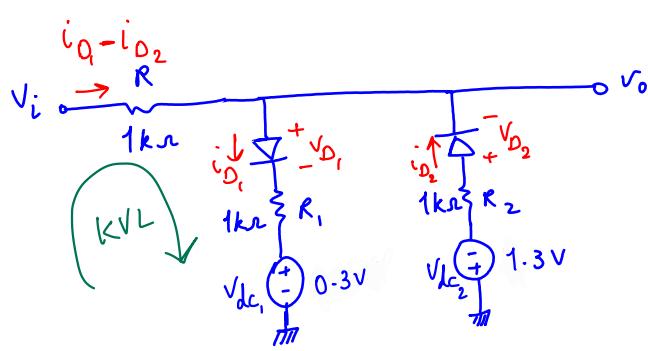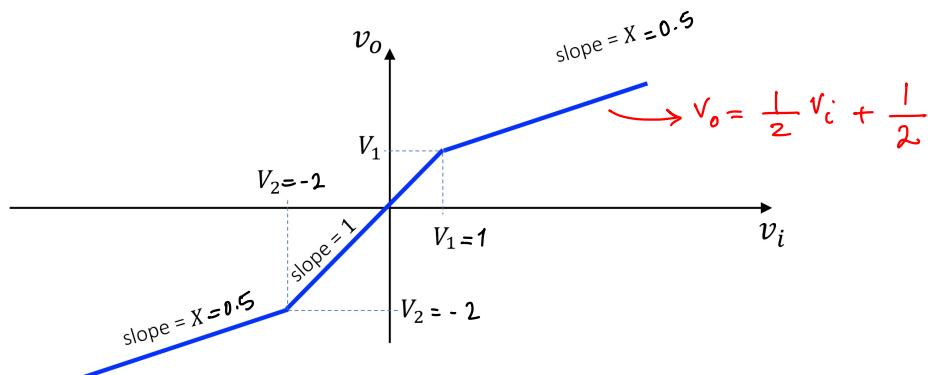

From the graph:

$$\left\{ \begin{array}{l} \text{For } v_i > 1 \text{ V}, V_o = \frac{1}{2}v_i + \frac{1}{2} \\ \text{For } v_i \leq -2 \text{ V}, V_o = \frac{1}{2}v_i - 1 \\ \text{For } -2 \leq v_i \leq 1, V_o = v_i \end{array} \right.$$

$$\left\{ \begin{array}{l} \text{For } v_i > 1 \text{ V}, V_o = \frac{1}{2}v_i + \frac{1}{2} \\ \text{For } v_i \leq -2 \text{ V}, V_o = \frac{1}{2}v_i - 1 \\ \text{For } -2 \leq v_i \leq 1, V_o = v_i \end{array} \right.$$

$$\left\{ \begin{array}{l} \text{For } v_i > 1 \text{ V}, V_o = \frac{1}{2}v_i + \frac{1}{2} \\ \text{For } v_i \leq -2 \text{ V}, V_o = \frac{1}{2}v_i - 1 \\ \text{For } -2 \leq v_i \leq 1, V_o = v_i \end{array} \right.$$

Case 2: D_1 off and D_2 on

$$\text{For } v_i \leq -0.7 \text{ V} - V_{dc2}, V_o = \frac{1}{2}v_i - 0.35 \text{ V} - \frac{1}{2}V_{dc2}$$

From the graph:



$$\text{For } v_i \leq -2 \text{ V}, V_o = \frac{1}{2}v_i - 1$$

If we choose $V_{dc2} = 1.3 \text{ V} \rightarrow$ the response of the circuit will match the transfer function

Problem 2.

Design a diode waveform shaping circuit that would have the below transfer function.

$$V_{D_0} = 0.7 \text{ V}$$

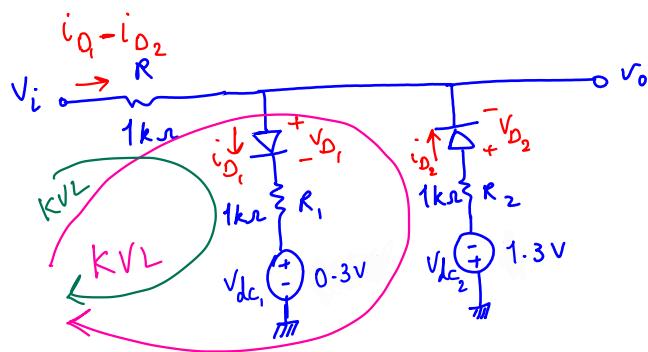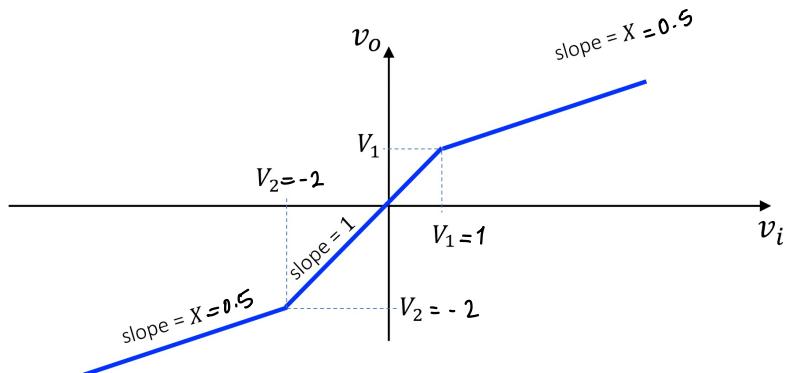

From the graph:

$$\left\{ \begin{array}{l} \text{For } v_i \geq 1 \text{ V}, \quad V_o = \frac{1}{2} v_i + \frac{1}{2} \\ \text{For } v_i \leq -2 \text{ V}, \quad V_o = \frac{1}{2} v_i - 1 \\ \text{For } -2 \leq v_i \leq 1, \quad V_o = v_i \end{array} \right.$$

Case 3 : D_1 off and D_2 off

$$i_{D_2} = 0, \quad V_{D_2} < V_{D_0}, \quad i_{D_1} = 0, \quad V_{D_1} < V_{D_0} \quad \text{Assumed } V_{D_0} = 0.7 \text{ V}$$

$$\text{KVL: } v_i = R(i_{D_1} - i_{D_2}) - V_{D_2} - R_2 i_{D_2} - V_{dc_2}$$

$$v_i = -V_{D_2} - 1.3 \text{ V} \rightarrow V_{D_2} = -v_i - 1.3 \text{ V}, \quad V_{D_2} < 0.7 \rightarrow \left\{ \begin{array}{l} v_i > -2 \text{ V} \\ v_i < 1 \text{ V} \end{array} \right.$$

$$\text{KVL: } v_i = R(i_{D_1} - i_{D_2}) + V_{D_1} + R_1 i_{D_1} + V_{dc_1}$$

$$v_i = V_{D_1} + 0.3 \text{ V} \rightarrow V_{D_1} = v_i - 0.3 \text{ V}, \quad V_{D_1} < 0.7 \text{ V} \rightarrow \left\{ \begin{array}{l} v_i < 1 \text{ V} \\ -2 \text{ V} < v_i < 1 \text{ V} \end{array} \right.$$

$$V_o = -R(i_{D_1} - i_{D_2}) + v_i \rightarrow V_o = v_i$$



Problem 3.

The circuits (a) and (b) shown below are connected as follows:


The two input terminals are tied together, and the two output terminals are tied together.

- Find, sketch and label the transfer function. (Assume $V_{D0} = 0.7 \text{ V}$).
- Draw the output voltage waveform if $v_i = 5 \sin(\omega t)$. No need for labeling the time axis.


Show your work.

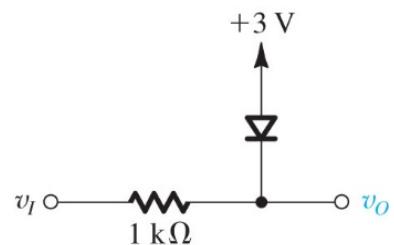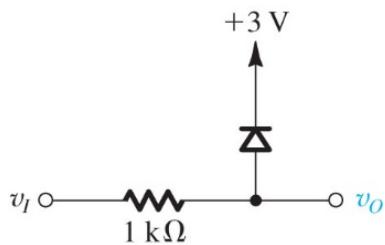

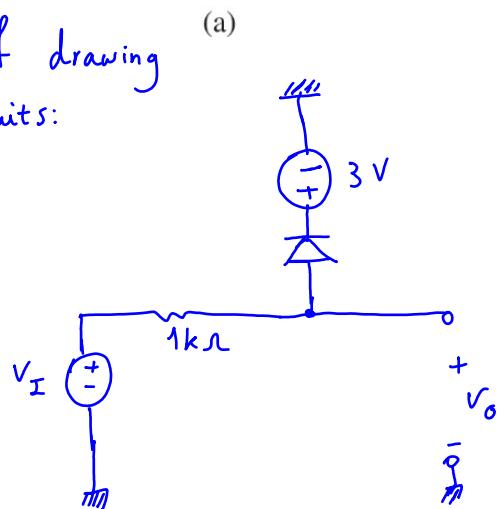
*other ways of drawing
the same circuits:*




(a)

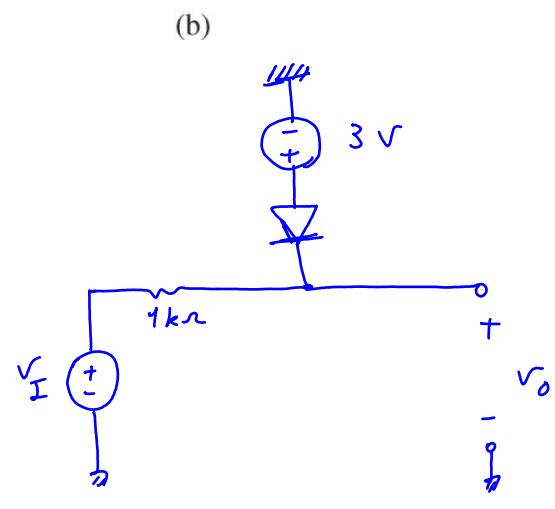

(b)


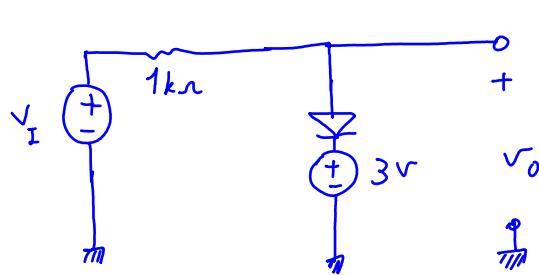


(a)

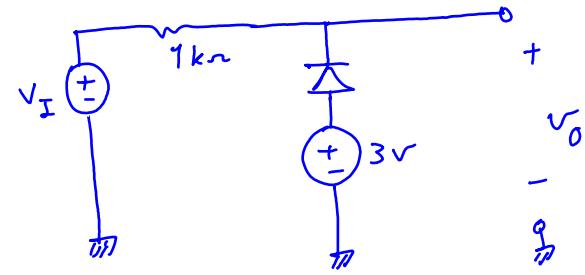

(b)

part a)

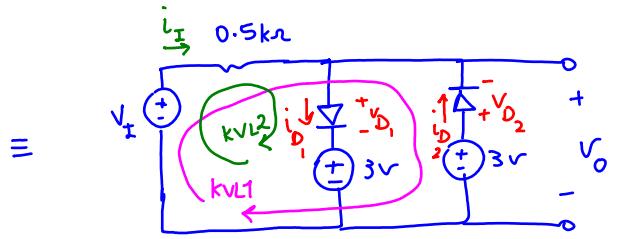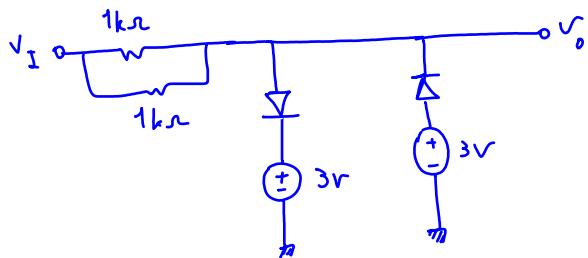

Case 1: D_1 is OFF and D_2 is ON

$$i_{D_1} = 0 \quad \& \quad V_{D_1} < 0.7V, \quad i_{D_2} \geq 0 \quad \& \quad V_{D_2} = 0.7V$$

$$\text{KCL: } i_I = i_{D_1} - i_{D_2} \rightarrow \text{for this case: } i_I = -i_{D_2}$$

$$\text{KVL1: } -V_I + 0.5k\Omega \times (-i_{D_2}) - V_{D_2} + 3V = 0 \rightarrow i_{D_2} = \frac{-V_I - 0.7V + 3V}{0.5k\Omega} = \frac{-V_I + 2.3V}{0.5k\Omega}$$

$$i_{D_2} \geq 0 \rightarrow V_I \leq 2.3V$$

$$V_O = -V_{D_2} + 3V = -0.7V + 3V \rightarrow V_O = 2.3V$$

Case 2: D_1 is ON and D_2 is OFF

$$i_{D_1} \geq 0 \quad \& \quad V_{D_1} = 0.7V, \quad i_{D_2} = 0 \quad \& \quad V_{D_2} < 0.7V$$

$$\text{KVL2: } -V_I + 0.5k\Omega \times i_{D_1} + V_{D_1} + 3V = 0 \rightarrow i_{D_1} = \frac{V_I - 0.7V - 3V}{0.5k\Omega}$$

$$i_{D_1} \geq 0 \rightarrow V_I \geq 3.7V$$

$$V_O = +V_{D_1} + 3V = 0.7V + 3V \rightarrow V_O = 3.7V$$

Case 3: D_1 and D_2 are both OFF:


$$i_{D_1} = i_{D_2} = 0, \quad v_{D_1} < 0.7V \quad \& \quad v_{D_2} < 0.7V$$

$$\text{KVL1: } -v_I + 0.5 \text{ k}\Omega \times 0 - v_{D_2} + 3V = 0 \rightarrow v_{D_2} = -v_I + 3V < 0.7V \rightarrow v_I > 2.3V$$


$$\text{KVL2: } -v_I + 0.5 \text{ k}\Omega \times 0 + v_{D_1} + 3V = 0 \rightarrow v_{D_1} = v_I - 3V < 0.7V \rightarrow v_I < 3.7V$$

$$\Rightarrow 2.3V < v_I < 3.7V$$
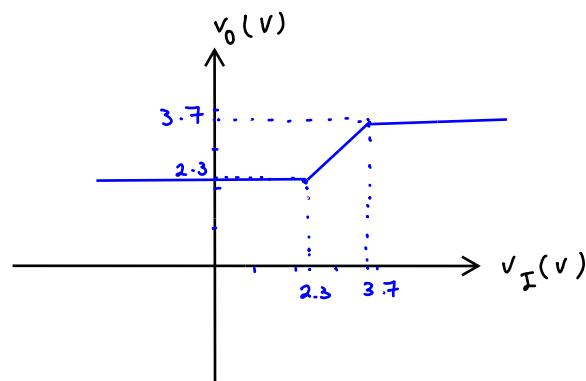
$$v_o = 0.5 \text{ k}\Omega \times 0 + v_I \Rightarrow v_o = v_I$$





b) $v_c(t) = 5 \sin \omega t$

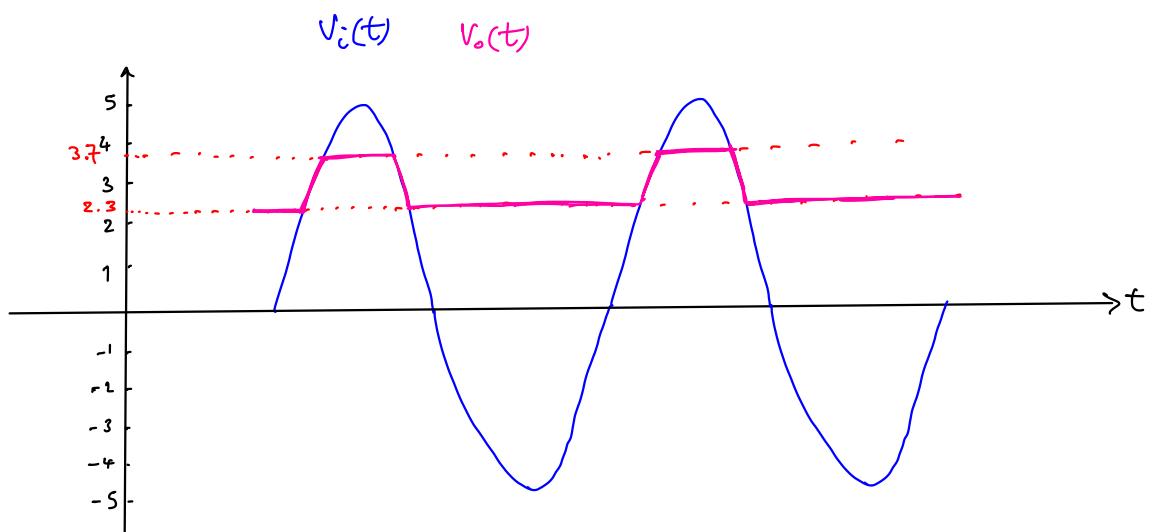

Problem 4.

Plot the transfer function of the following full-wave rectifier. Find v_o for different ranges of v_i and plot a graph that shows the relationship between v_o and v_i .

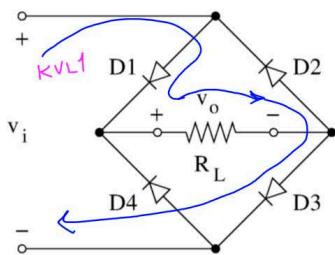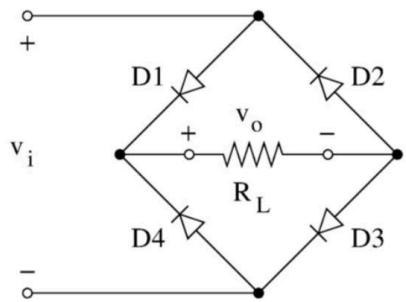

Case 1: D₁ and D₃ ON, D₂ and D₄ off

$$i_{D_1} \geq 0 \quad \& \quad v_{D_1} = V_{D_0} \quad \& \quad i_{D_3} \geq 0 \quad \& \quad v_{D_3} = V_{D_0}$$

$$i_{D_2} = 0 \quad \& \quad v_{D_2} < V_{D_0} \quad \& \quad i_{D_4} = 0 \quad \& \quad v_{D_4} < V_{D_0}$$

$$\text{KVL1: } -v_i + v_{D_1} + R i_{D_1} + v_{D_3} = 0$$

$$\rightarrow -v_i + V_{D_0} + R i_{D_1} + V_{D_0} = 0 \rightarrow i_{D_1} = \frac{v_i - 2V_{D_0}}{R} \geq 0$$


$$\rightarrow v_i \geq 2V_{D_0}$$

$$V_o = R \times i_{D_1} = R \times \frac{v_i - 2V_{D_0}}{R} \Rightarrow V_o = v_i - 2V_{D_0}$$

For $v_i \geq 2V_{D_0}$

$$V_o = v_i - 2V_{D_0}$$

case 2: D_2 and D_4 ON, D_1 and D_3 OFF

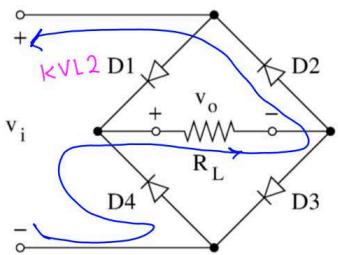

$$i_{D_1} = 0 \& i_{D_3} = 0 \& V_{D_1} < V_{D_0} \text{ and } V_{D_3} < V_{D_0}$$

$$V_{D_2} = V_{D_0} \& V_{D_4} = V_{D_0} \& i_{D_2} \geq 0 \& i_{D_4} \geq 0$$

$$\text{KVL 2: } V_{D_4} + R \times i_{D_4} + V_{D_2} + V_i = 0$$


$$\rightarrow V_i + 2V_{D_0} + R i_{D_4} = 0 \rightarrow i_{D_4} = \frac{-V_i - 2V_{D_0}}{R} \geq 0$$

$$V_o = R \times i_{D_4} = R \times \frac{-V_i - 2V_{D_0}}{R} \Rightarrow V_o = -V_i - 2V_{D_0}$$

$$\rightarrow V_i \leq -2V_{D_0}$$

For $V_i \leq -2V_{D_0}$

$$V_o = -V_i - 2V_{D_0}$$

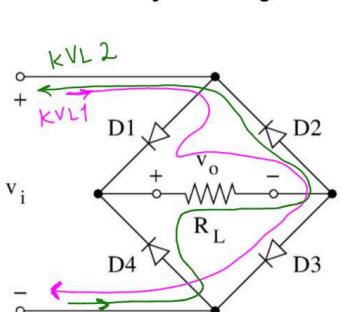

case 3: all diodes OFF

$$i_{D_1} = i_{D_2} = i_{D_3} = i_{D_4} = 0, V_{D_1} < V_{D_0} \& V_2 < V_{D_0} \&$$

$$V_{D_3} < V_{D_0} \& V_{D_4} < V_{D_0}$$

$$\text{KVL1: } -V_i + V_{D_1} + R i_{D_1} + V_{D_3} = 0 \rightarrow V_i = V_{D_3} + V_{D_4}$$

$$V_{D_3} < V_{D_0}$$

$$V_{D_1} < V_{D_0}$$

$$\frac{V_{D_3} + V_{D_1}}{2} < V_{D_0} \rightarrow$$

$$V_i < 2V_{D_0}$$


$$\text{KVL2: } V_{D_4} + i_{D_4} \times R + V_{D_2} + V_i = 0 \rightarrow -V_i = V_{D_2} + V_{D_4}$$

$$V_o = R i_{D_1} = 0 \rightarrow V_o = 0$$

$$\begin{aligned} V_{D_2} &< V_{D_0} \\ V_{D_4} &< V_{D_0} \\ \frac{V_{D_2} + V_{D_4}}{2} &< V_{D_0} \end{aligned}$$


$$\rightarrow -V_i < 2V_{D_0} \rightarrow V_i > -2V_{D_0}$$

For $-2V_{D_0} < V_i < 2V_{D_0}$
 $V_o = 0$

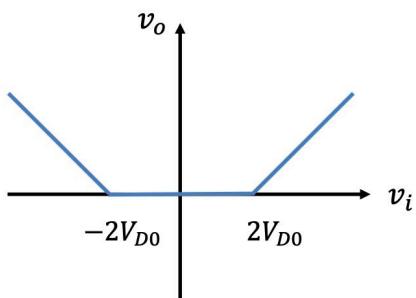

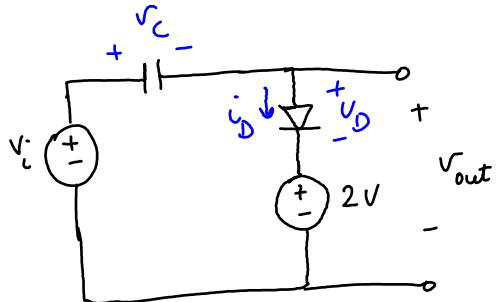Problem 5.

In the circuit below, $v_i(t) = 10 \sin(\omega t)$ where $\omega = 1000 \text{ rad/s}$, Assume $V_{D0} = 0.7 \text{ V}$ and $v_o(0) = 0 \text{ V}$. Calculate and plot $v_o(t)$ for $0 \leq t \leq 5 \text{ ms}$.



$$v_o(0) = v_i(0) - v_C(0) \rightarrow v_C(0) = 0$$

when $0 < v_i < 2.7 \text{ V}$, the diode will be off. $i_D = 0$, $v_C = 0$, $v_o = v_i$

- when $2.7 \text{ V} \leq v_i \leq 10 \text{ V}$
diode is ON. $v_D = V_{D0} = 0.7 \text{ V}$ $\rightarrow v_o = v_D + 2 \text{ V} = 2.7 \text{ V}$
- after v_i passed its first positive peak, the diode will turn off.
the voltage across the capacitor will stay at a constant value.

$$V_C = v_{i_{\text{peak}}} - 2 - 0.7 = 10 - 2.7 = 7.3 \text{ V}$$

Since the diode is off, $v_D \neq V_{D0}$ and v_o can be calculated


using

$$v_o = -v_C + v_i = v_i - 7.3 \text{ V}$$

$$v_i(t) = 10 \sin(1000t)$$


$$\omega = 1000 \text{ rad/s}$$

$$T = \frac{2\pi}{\omega} = 2 \times 3.14 \text{ ms}$$

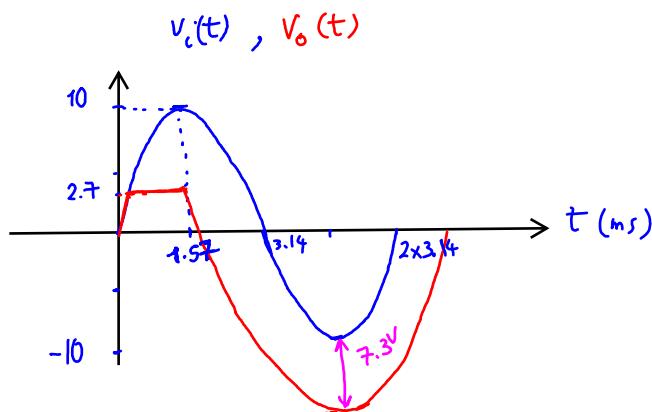

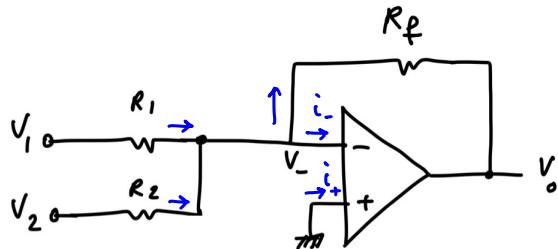Problem 6.

Design the following op-amp circuit to achieve the weighted sum of v_1 (input 1), and v_2 (input 2) at the output. It is required that $v_o = -(v_1 + 5v_2)$. Assume an ideal op-amp.



$$\left\{ \begin{array}{l} \text{ideal op-amp : } i_+ = i_- = 0 \\ \text{negative feedback: } V_+ = V_- \end{array} \right.$$

KCL at the inverting input terminal:

$$\frac{V_1 - V_-}{R_1} + \frac{V_2 - V_-}{R_2} = \frac{V_- - V_o}{R_f} + i_-$$

$$V_- = V_+ = 0$$

$$\rightarrow \frac{V_1 - 0}{R_1} + \frac{V_2 - 0}{R_2} = \frac{0 - V_o}{R_f} \Rightarrow V_o = \left(\frac{-R_f}{R_1} \right) V_1 + \left(\frac{-R_f}{R_2} \right) V_2$$

$$V_o = -V_1 - 5V_2 \Rightarrow \frac{R_f}{R_1} = 1 \quad \text{and} \quad \frac{R_f}{R_2} = 5$$


We can choose $R_f = 5 \text{ k}\Omega$ $R_1 = 5 \text{ k}\Omega$ $R_2 = 1 \text{ k}\Omega$

Problem 7.

Using the structure of a non-inverting amplifier, design an op-amp circuit to achieve

$$v_o = 6v_1 + 4v_2$$

Assume an ideal op-amp.

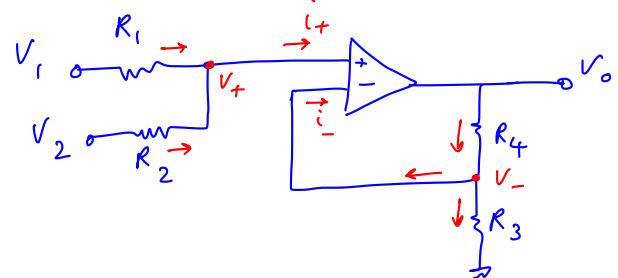

$$\left\{ \begin{array}{l} \text{ideal op-amp : } i_+ = i_- = 0 \\ \text{negative feedback: } V_+ = V_- \end{array} \right.$$

$$\text{negative feedback: } V_+ = V_-$$

$$\text{KCL at the inverting input terminal: } \frac{V_o - V_-}{R_4} - \frac{V_-}{R_3} = 0$$

$$\frac{V_o}{R_4} = \left(\frac{1}{R_4} + \frac{1}{R_3} \right) V_- \implies V_o = R_4 \left(\frac{R_3 + R_4}{R_3 R_4} \right) V_- \implies V_o = \left(\frac{R_3 + R_4}{R_3} \right) V_-$$

$$\text{or } V_- = \left(\frac{R_3}{R_3 + R_4} \right) V_o$$

$$\text{KCL at the non-inverting input terminal: } \frac{V_1 - V_+}{R_1} + \frac{V_2 - V_+}{R_2} = 0$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} = \left(\frac{1}{R_1} + \frac{1}{R_2} \right) V_+ = \left(\frac{R_1 + R_2}{R_1 R_2} \right) V_+ \implies V_+ = \left(\frac{R_2}{R_1 + R_2} \right) V_1 + \left(\frac{R_1}{R_1 + R_2} \right) V_2$$

$$\text{negative feedback: } V_+ = V_-$$


$$\left\{ \begin{array}{l} V_- = \left(\frac{R_3}{R_3 + R_4} \right) V_o \\ V_+ = \left(\frac{R_2}{R_1 + R_2} \right) V_1 + \left(\frac{R_1}{R_1 + R_2} \right) V_2 \end{array} \right.$$

Problem 7.

Using the structure of a non-inverting amplifier, design an op-amp circuit to achieve

$$v_o = 6v_1 + 4v_2$$

Assume an ideal op-amp.

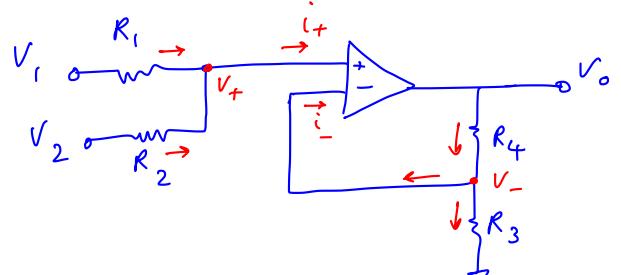

$$\begin{cases} V_- = \left(\frac{R_3}{R_3 + R_4} \right) V_o \\ V_+ = \left(\frac{R_2}{R_1 + R_2} \right) V_1 + \left(\frac{R_1}{R_1 + R_2} \right) V_2 \end{cases}$$

$$\text{negative feedback: } V_+ = V_-$$

$$\Rightarrow \left(\frac{R_3}{R_3 + R_4} \right) V_o = \left(\frac{R_2}{R_1 + R_2} \right) V_1 + \left(\frac{R_1}{R_1 + R_2} \right) V_2$$

$$\Rightarrow V_o = \left(\frac{R_3 + R_4}{R_3} \right) \left(\frac{R_2}{R_1 + R_2} \right) V_1 + \left(\frac{R_3 + R_4}{R_3} \right) \left(\frac{R_1}{R_1 + R_2} \right) V_2$$