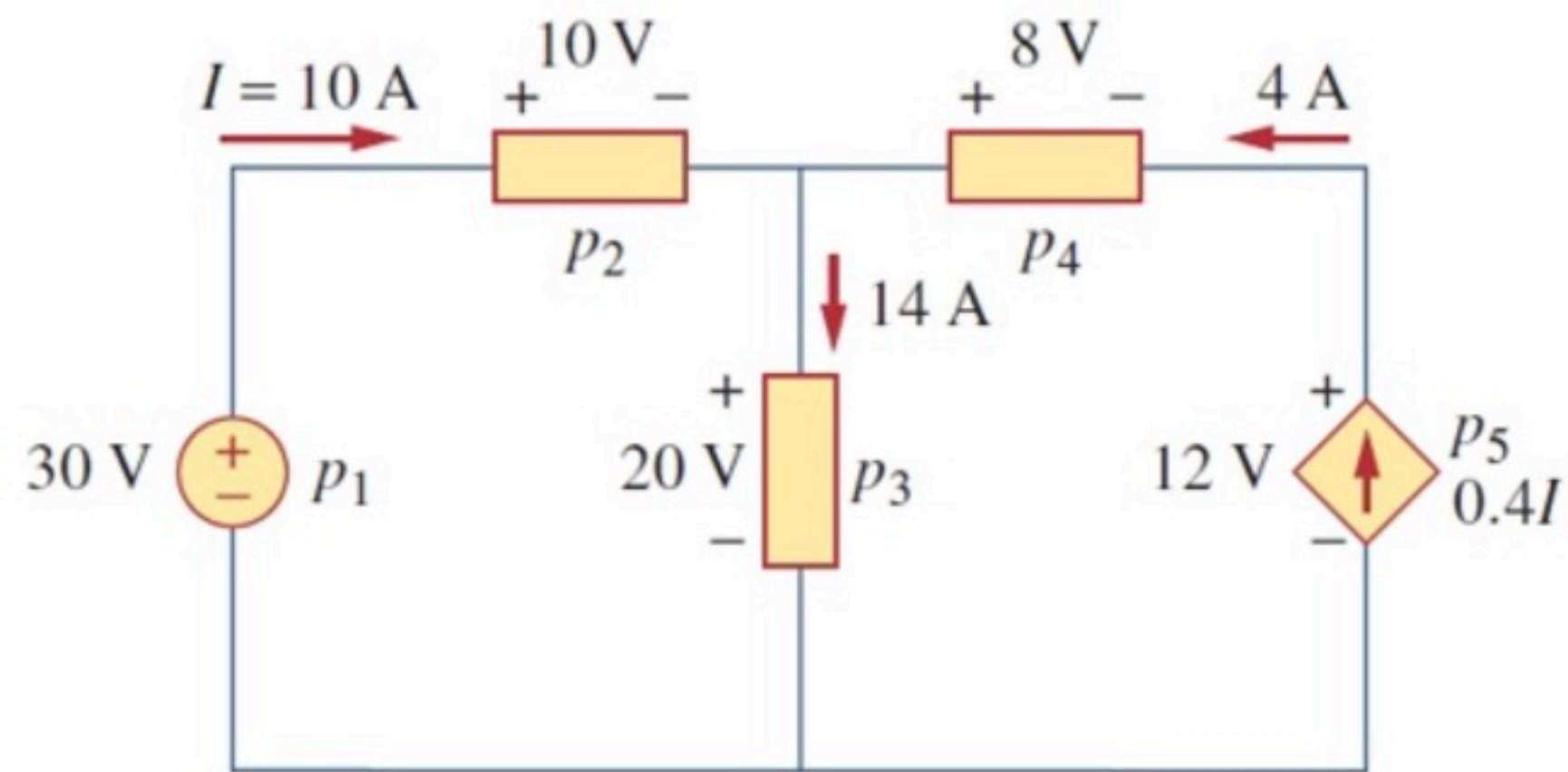


# PP - Basic concepts 010

Problem has been graded.

Find the power supplied by each of the elements.



Given Variables:

...

Calculate the following:

$p_1$  (W) :

300

✓

$p_2$  (W) :

-100

✓

$p_3$  (W) :

-280

✓

$p_4$  (W) :

32

✓

$p_5$  (W) :

48

✓

Hint: Check with conservation of power.