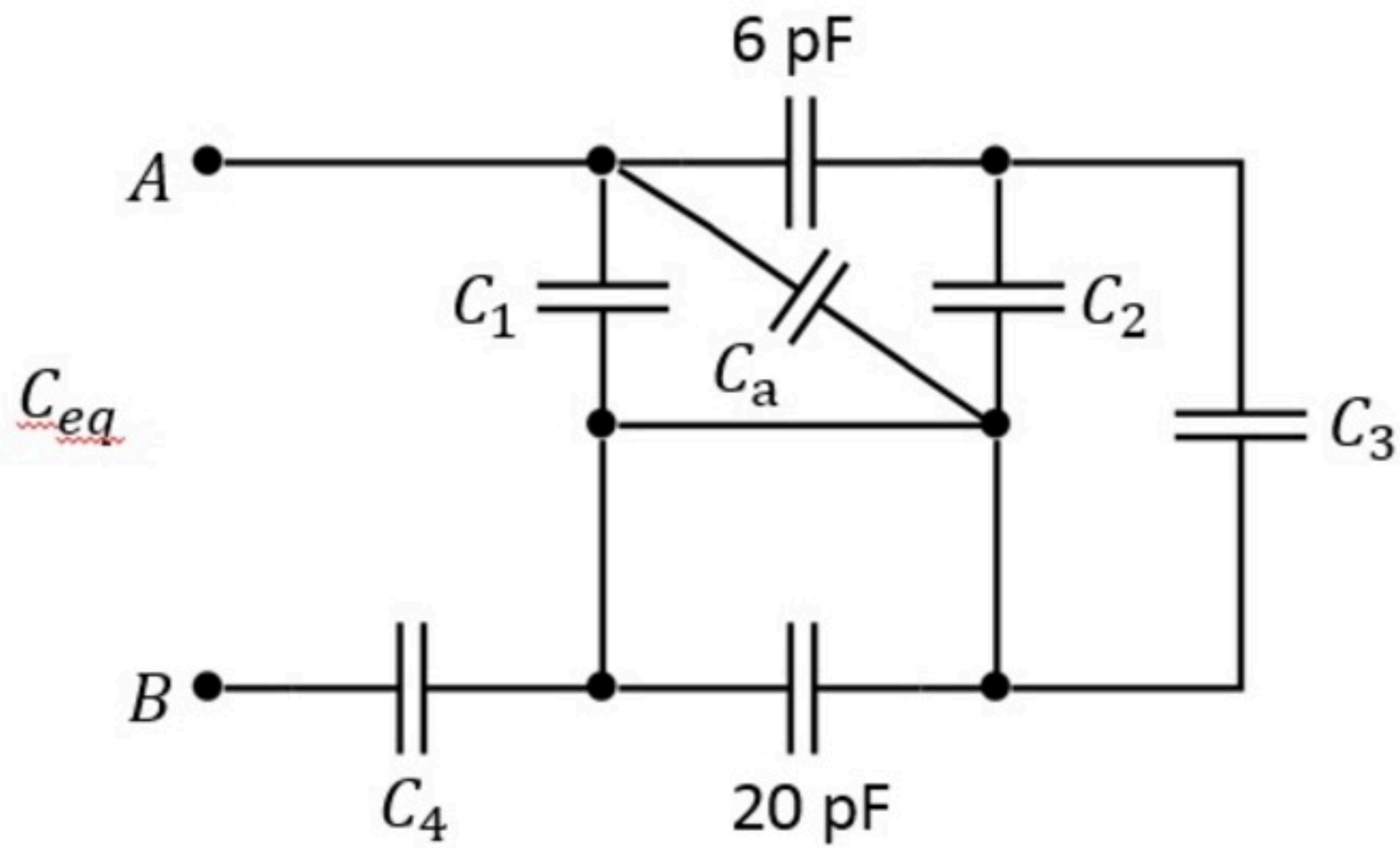


Capacitors Inductors 002

Problem has been graded.

Given C_{eq} between points A and B , what is C_a ?



Given Variables:

C_1 : 2 pF

C_2 : 2 pF

C_3 : 4 pF

C_4 : 6 pF

C_{eq} : 3 pF

Calculate the following:

C_a (pF) :