

ECE 35, Fall 2019  
Quiz 3 – Section B

Sequence  
number

Grade

 / 10

Last name

First + middle  
name(s)

**PID**

**Instructions:**

- Read each problem completely and thoroughly before beginning.
- All calculations need to be done on these sheets.
- Write your answers in the answer boxes for each question. Make sure you list units!
- Answers without supporting calculations will receive zero credit.


(1) (5 points) For  $t < 2$  s, the switch is open, and you may assume the system has reached steady state. The switch closes at time  $t = 2$  s.


(a) Find  $i_a(2^- \text{ s})$ .

$i_a(2^- \text{ s})$

(b) Find  $i_a(t)$  for  $t > 2$  s.  
Write the equation.

$i_a(t)$

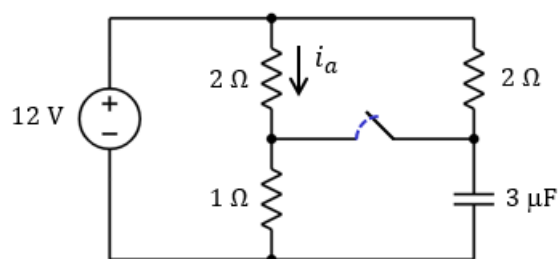

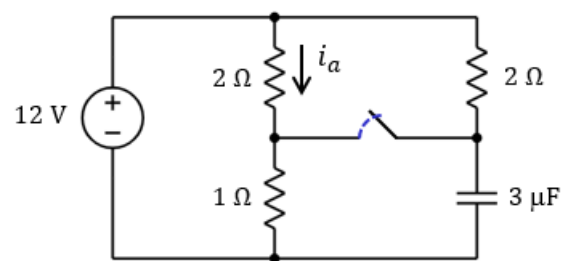



(2) (2 points) The capacitor is fully discharged at  $t = 0$  s. For  $t < 3$  s, the switch is in position 1. The switch moves from position 1 to position 2 at time  $t = 3$  s. You are given the curve of the voltage source  $v_S$ .

(a) Find  $v_c$  at time  $t = 4$  s.

$v_c(4)$

(b) Find  $i_c$  at time  $t = 2$  s.

$i_c(2)$

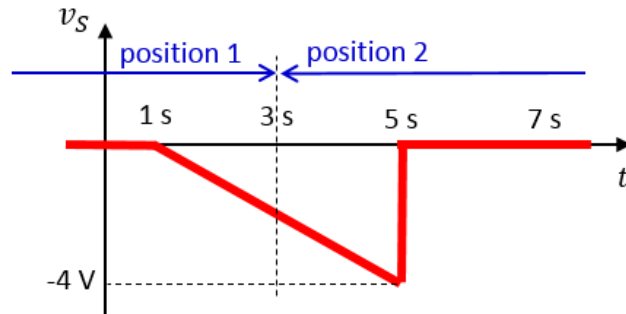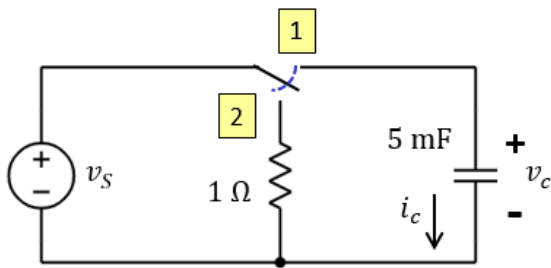

- (3) (3 points) For  $t < 0$  s, the switch is closed, and you may assume the system has reached steady state. The switch opens at time  $t = 0$  s. You are given the curve of the current  $i_L$  through the inductor for  $t > 0$  s.

(a) On the curve, we see that  $i_L = 1.5$  A at time  $t_1$ .

What is the voltage  $v_a$  at that same time  $t_1$ ?



$v_a(t_1)$

(b) What is the time constant  $\tau$  of  $i_L(t)$  for  $t > 0$  s?

$\tau$

(c) What is the time constant  $\tau$  of the node voltage  $V_1(t)$  for  $t > 0$  s?

$\tau$

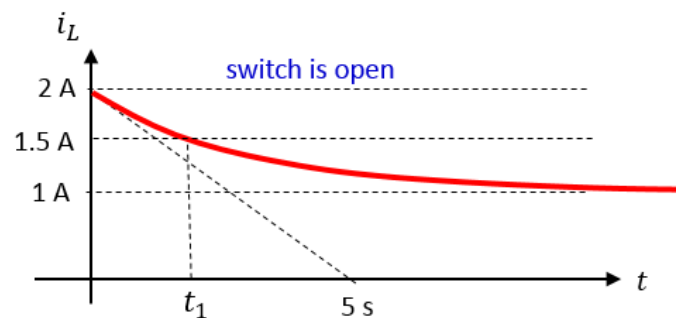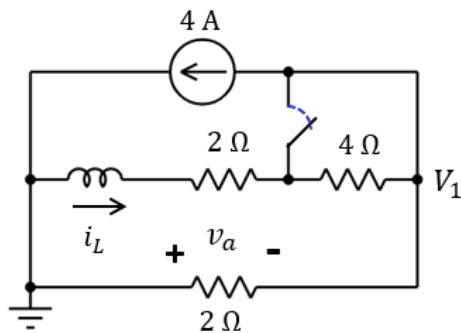

## ECE35 Equation Sheet

**Basics:**  $i \triangleq \frac{dq}{dt}$        $v_{ab} \triangleq \frac{dw}{dq}$        $R = \rho \frac{l}{A}$

**Capacitors:**  $C = \epsilon \cdot \frac{A}{d}$        $Q = C \cdot v$        $w_C = \frac{1}{2} C v^2$

**Inductors:**  $L = \mu \cdot \frac{N^2 A}{l}$        $B \sim i$        $w_L = \frac{1}{2} L i^2$

**AC power:**  $p(t) = \frac{1}{2} V_m I_m \cdot \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cdot \cos(2\omega t + \theta_v + \theta_i)$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \quad Q = \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i) \quad X_{rms} = \sqrt{\frac{1}{T} \int_0^T x(t)^2 dt}$$

**Trigonometry:**

$\sin(-\alpha) = -\sin(\alpha)$	$\cos(-\alpha) = \cos(\alpha)$
$\sin(\pi - \alpha) = \sin(\alpha)$	$\cos(\pi - \alpha) = -\cos(\alpha)$
$\sin\left(\frac{\pi}{2} - \alpha\right) = \cos(\alpha)$	$\cos\left(\frac{\pi}{2} - \alpha\right) = \sin(\alpha)$
$\sin\left(\alpha - \frac{\pi}{2}\right) = -\cos(\alpha)$	$\cos\left(\alpha - \frac{\pi}{2}\right) = \sin(\alpha)$
$\sin(2\alpha) = 2 \sin(\alpha) \cos(\alpha)$	$\cos(2\alpha) = \cos^2(\alpha) - \sin^2(\alpha)$

$$\sin(\alpha \pm \beta) = \sin(\alpha) \cos(\beta) \pm \cos(\alpha) \sin(\beta)$$

$$\cos(\alpha \pm \beta) = \cos(\alpha) \cos(\beta) \mp \sin(\alpha) \sin(\beta)$$

$$\sin(\alpha) \sin(\beta) = 0.5 \cdot (\cos(\alpha - \beta) - \cos(\alpha + \beta))$$

$$\cos(\alpha) \cos(\beta) = 0.5 \cdot (\cos(\alpha - \beta) + \cos(\alpha + \beta))$$

$$\sin(\alpha) \cos(\beta) = 0.5 \cdot (\sin(\alpha - \beta) + \sin(\alpha + \beta))$$

$\alpha:$	0	$\frac{\pi}{6}$	$\frac{\pi}{4}$	$\frac{\pi}{3}$	$\frac{\pi}{2}$
$\sin(\alpha):$	0	$\frac{1}{2}$	$\frac{\sqrt{2}}{2}$	$\frac{\sqrt{3}}{2}$	1
$\tan(\alpha):$	0	$\frac{\sqrt{3}}{3}$	1	$\sqrt{3}$	$\infty$