

Find the energy received by this element between time  $t = 0$  and  $t = T_1$ .

For this element


$$v(t) = 2\pi \cdot \cos(A_1 \cdot \pi \cdot t) \quad \text{V}$$

$$i(t) = A_2 \cdot \sin(A_1 \cdot \pi \cdot t)$$


$$A_1 = 1 \text{ Hz}$$

$$A_2 = 5 \text{ A}$$

$$T_1 = 1.5 \text{ s}$$

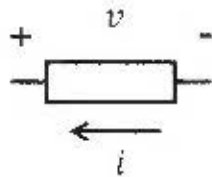

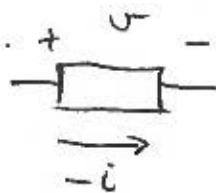(Note: Hz is the unit used for frequency. It is equal to  $s^{-1}$ )



for passive sign convention  $\leadsto$  gives power received

$$p(t) = v(t) \cdot (-i(t)) = -2\pi \cos(\pi t) \cdot 5 \sin(\pi t)$$

$$= -10\pi \sin(\pi t) \cos(\pi t) = -5\pi \sin(2\pi t)$$

$$E = \int_0^{1.5} p(t) dt = -5\pi \int_0^{1.5} \sin(2\pi t) dt = -\frac{5\pi}{2\pi} \int_0^{1.5} \sin(2\pi t) d(2\pi t)$$

$$= -\frac{5}{2} (-\cos(2\pi t)) \Big|_0^{1.5}$$

$$= -2.5 (-\cos(3\pi) + 1)$$

$$= -2.5 (-(-1) + 1)$$

$$= -5$$

$$\boxed{E = -5 \text{ J}} \quad \text{received}$$