

ECE 35, Fall 2024

Quiz 1

/ 12

Your sequence number

Last name


First + middle
name(s)

PID

Instructions:


- Read each problem completely and thoroughly before beginning
- All calculations need to be done on these sheets
- Write your answers in the answer boxes for each question. Make sure you list units!
- Answers without supporting calculations will receive zero credit

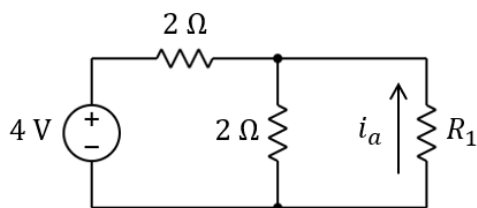- (1) (1 point) How can you connect an ammeter to measure i_a , which is the current through resistor R_1 ? **Redraw** the circuit so that it shows how to connect the ammeter. Do not forget to indicate the red and black terminals.



(2) (2 points) What is the current i_a ?

i_a

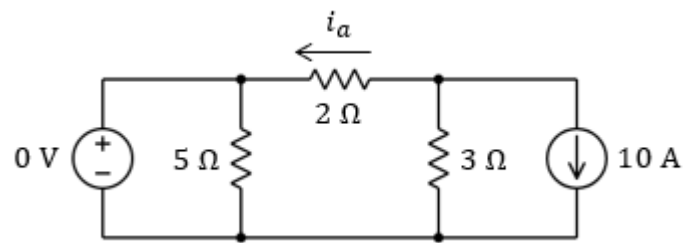

(3) (4 points) In the problem below, the voltmeter is ideal.

(a) What is the reading X of the voltmeter?


X

(b) What is the power P_1 supplied by the independent source?

P_1

(c) What is the power P_2 supplied by the dependent source?

P_2

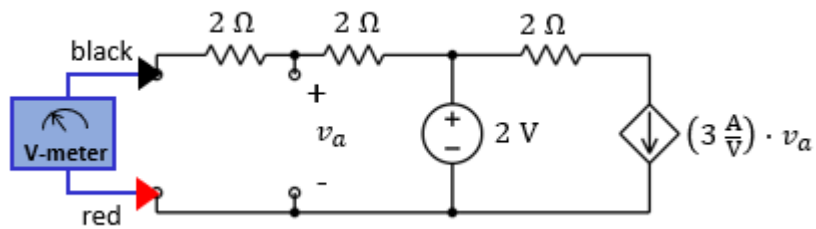

- (4) (5 points) For this problem, you can use any analysis method you like. To maximize your opportunity for partial credit, lay out your equations first before solving.
Hint: Think carefully about your analysis method.

(a) What is the current i_a in the circuit on the left?



i_a



(b) What is the node voltage v_x in the circuit on the right?
This is the same circuit as the one on the left, just with the ground added.

v_x

(c) What is the mesh current i_x in the circuit on the right?

i_x

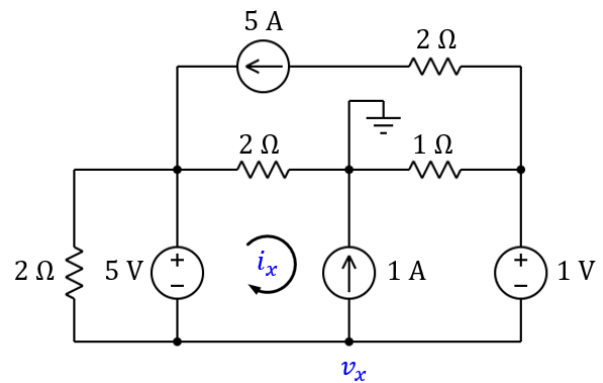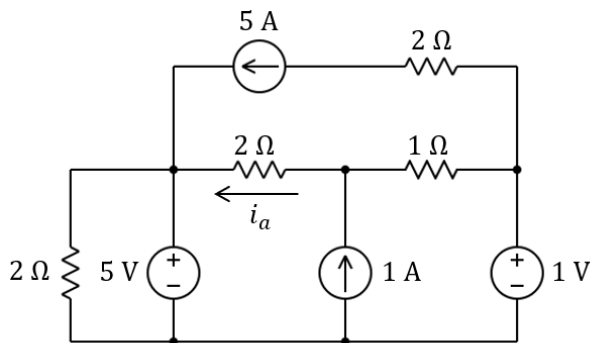

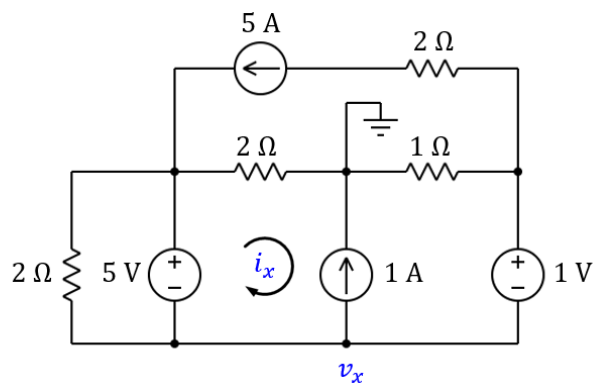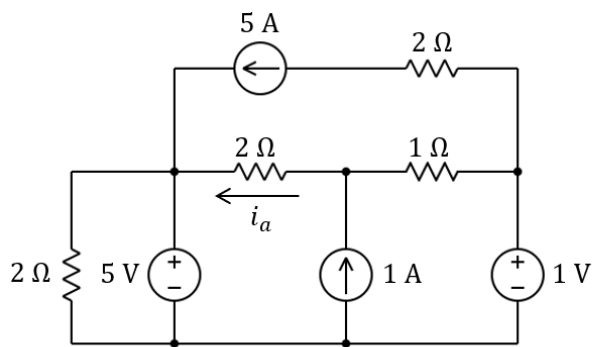

ECE35 Equation Sheet

Basics: $i \triangleq \frac{dq}{dt}$ $v_{ab} \triangleq \frac{dw}{dq}$ $R = \rho \frac{l}{A}$

Capacitors: $C = \epsilon \cdot \frac{A}{d}$ $Q = C \cdot v$ $w_C = \frac{1}{2} C v^2$

Inductors: $L = \mu \cdot \frac{N^2 A}{l}$ $B \sim i$ $w_L = \frac{1}{2} L i^2$

AC power: $p(t) = \frac{1}{2} V_m I_m \cdot \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cdot \cos(2\omega t + \theta_v + \theta_i)$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \quad Q = \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i) \quad X_{rms} = \sqrt{\frac{1}{T} \int_0^T x(t)^2 dt}$$

Trigonometry:

$\sin(-\alpha) = -\sin(\alpha)$	$\cos(-\alpha) = \cos(\alpha)$
$\sin(\pi - \alpha) = \sin(\alpha)$	$\cos(\pi - \alpha) = -\cos(\alpha)$
$\sin\left(\frac{\pi}{2} - \alpha\right) = \cos(\alpha)$	$\cos\left(\frac{\pi}{2} - \alpha\right) = \sin(\alpha)$
$\sin\left(\alpha - \frac{\pi}{2}\right) = -\cos(\alpha)$	$\cos\left(\alpha - \frac{\pi}{2}\right) = \sin(\alpha)$
$\sin(2\alpha) = 2 \sin(\alpha) \cos(\alpha)$	$\cos(2\alpha) = \cos^2(\alpha) - \sin^2(\alpha)$

$\sin(\alpha \pm \beta) = \sin(\alpha) \cos(\beta) \pm \cos(\alpha) \sin(\beta)$	$\alpha:$	0	$\frac{\pi}{6}$	$\frac{\pi}{4}$	$\frac{\pi}{3}$	$\frac{\pi}{2}$
$\cos(\alpha \pm \beta) = \cos(\alpha) \cos(\beta) \mp \sin(\alpha) \sin(\beta)$						
$\sin(\alpha) \sin(\beta) = 0.5 \cdot (\cos(\alpha - \beta) - \cos(\alpha + \beta))$	$\sin(\alpha):$	0	$\frac{1}{2}$	$\frac{\sqrt{2}}{2}$	$\frac{\sqrt{3}}{2}$	1
$\cos(\alpha) \cos(\beta) = 0.5 \cdot (\cos(\alpha - \beta) + \cos(\alpha + \beta))$	$\tan(\alpha):$	0	$\frac{\sqrt{3}}{3}$	1	$\sqrt{3}$	∞
$\sin(\alpha) \cos(\beta) = 0.5 \cdot (\sin(\alpha - \beta) + \sin(\alpha + \beta))$						