


First order circuits 009

Problem has been graded.

For $t < 0$, the switch has been in position A for a long time. At time $t = 0$, it moves from A to B .

Find the time t_1 it takes to reduce the capacitor voltage to 37% of its initial voltage ($\frac{1}{e} \approx .37$).

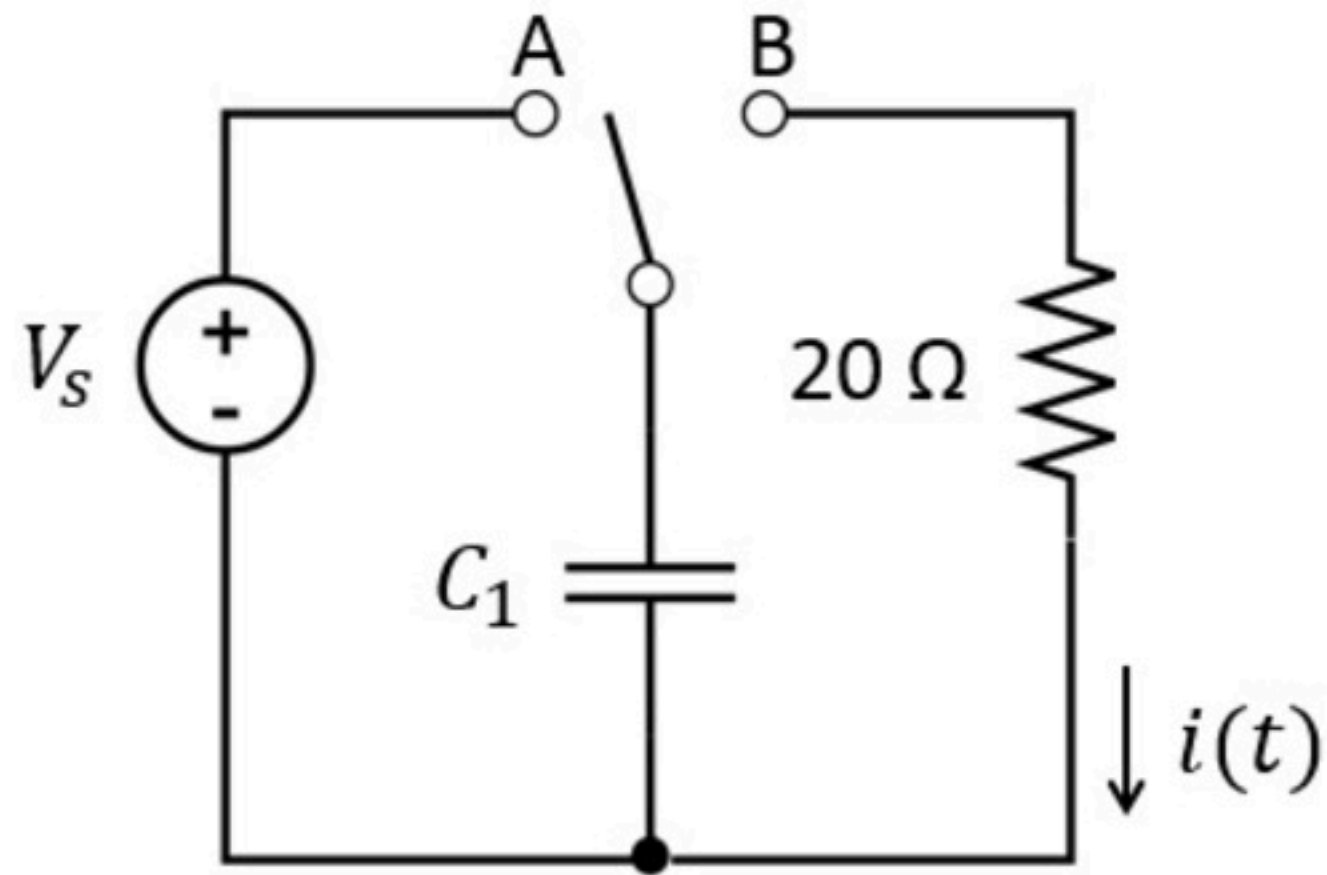What is the total energy E received by the resistor from the moment the switch is flipped until the capacitor is completely discharged?



Given Variables:

$V_s : 12\text{ V}$

$C_1 : 2\text{ }\mu\text{F}$

Calculate the following:

$t_1\text{ (ms)} :$

0.04

✓

$E\text{ (mJ)} :$

0.144

✓

Hint: To calculate E , consider where the energy is coming from. Verify by integrating the $P(t)$.