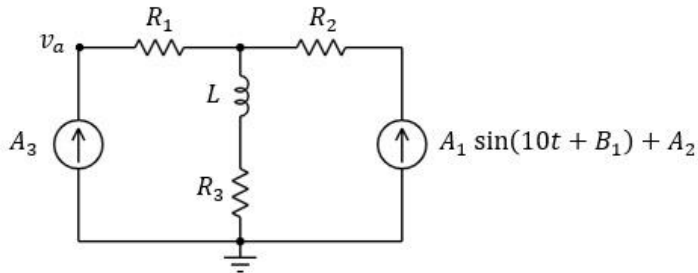


Q1

Find steady state node voltage $v_a(t)$.





R1: 3 Ω
 R2: 2 Ω
 R3: 2 Ω
 L: 200 mH
 A1: 2 A
 B1: -20 degrees
 A2: 2 A
 A3: 1 A

Q2

The AC circuit below has $\omega = 10$ rad/s and is in steady state. The phasor diagram shows the phasors of v_S and i_S . You are given the angle α , $|I_S|$ and $|V_S|$. The diagram is not necessarily drawn to scale (but V_S is along the imaginary axis).

The element in the center (rectangular box) is either an inductor or a capacitor but you are not told which.

- At what time t_0 does the waveform of v_R reach its maximum value? (if there are multiple such times, giving one of them is sufficient).
- We select the mystery element such that $|I_a|$ is minimized (not $|I_b|$). What is the mystery element (capacitor or inductor) and what is its value?

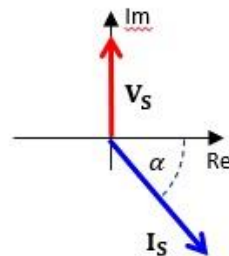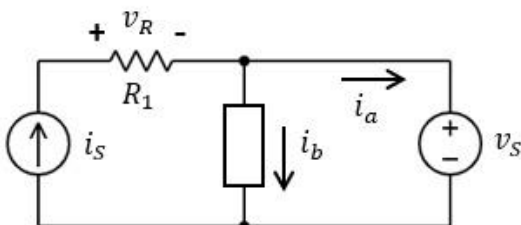

$|I_S|$: 2 A
 alpha: -30 degrees

$|V_S|$: 3 V
 R1: 3 Ω