

# **ECE 65: Components & Circuits Lab**

## **Lecture 3**

### **Operational Amplifier limitations**


Reference notes: sections 7.5

Sedra & Smith (7<sup>th</sup> Ed): sections 2-2.3

Saharnaz Baghdadchi

# Course map

## 7. Operational amplifiers

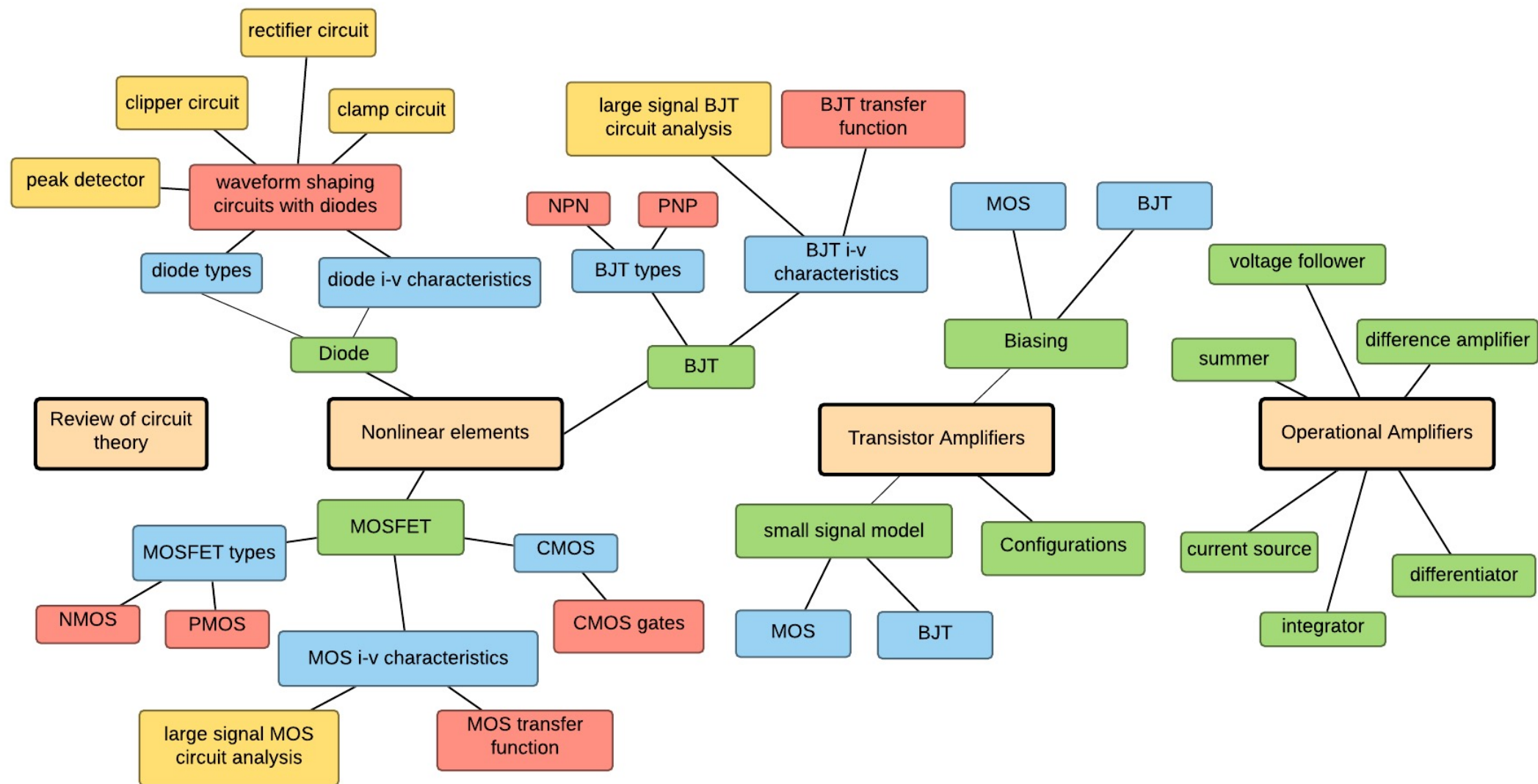

# Voltage-supply limit or Saturation

As we saw before, the maximum output voltage of op-amps is limited by the positive and negative voltage sources ( $V_{S+}$  and  $V_{S-}$ ) used to power up the op-amp chip.

$$V_{S-} < V_o < V_{S+}$$

$$V_{sat-} \leq V_o \leq V_{sat+}$$


$$V_{sat+} = 14V$$

$$V_{sat-} = -14V$$

Assume an ideal op-amp  $\Rightarrow i_+ = i_- = 0$

Because of negative feedback:  $v_+ = v_-$
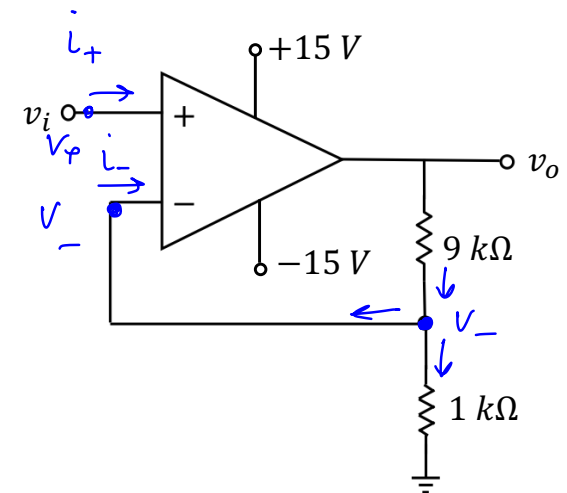
$$\text{here, } V_+ = V_i, \quad \frac{V_-}{1k\Omega} = \frac{V_o - V_-}{9k\Omega} \Rightarrow V_o = 10 V_- \Rightarrow \boxed{V_o = 10 V_i}$$



# Voltage-supply limit or Saturation

As we saw before, the maximum output voltage of op-amps is limited by the positive and negative voltage sources ( $V_{S+}$  and  $V_{S-}$ ) used to power up the op-amp chip.


$$V_{S-} < V_o < V_{S+}$$

$$V_{sat-} \leq V_o \leq V_{sat+}$$

$$V_{sat+} = 14V$$



$$V_{sat-} = -14V$$
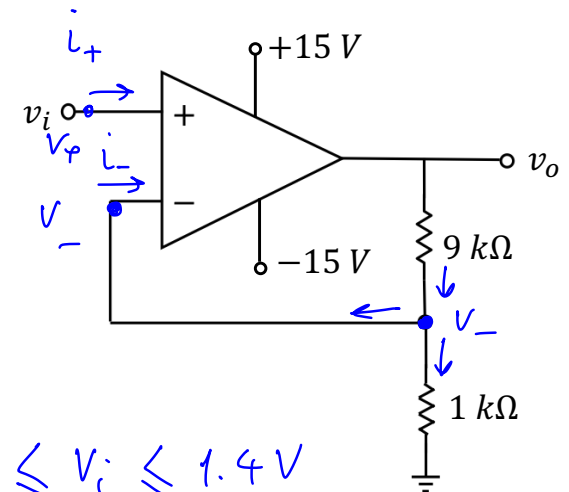
$$V_o = 10 V_i \Rightarrow -\frac{14V}{10} \leq V_i \leq \frac{14}{10} V \Rightarrow -1.4V \leq V_i \leq 1.4V$$



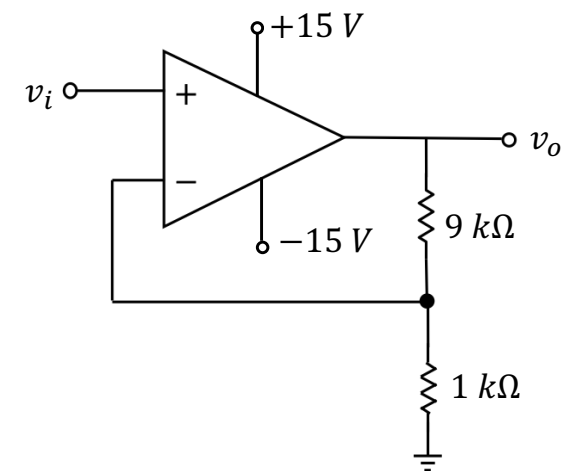
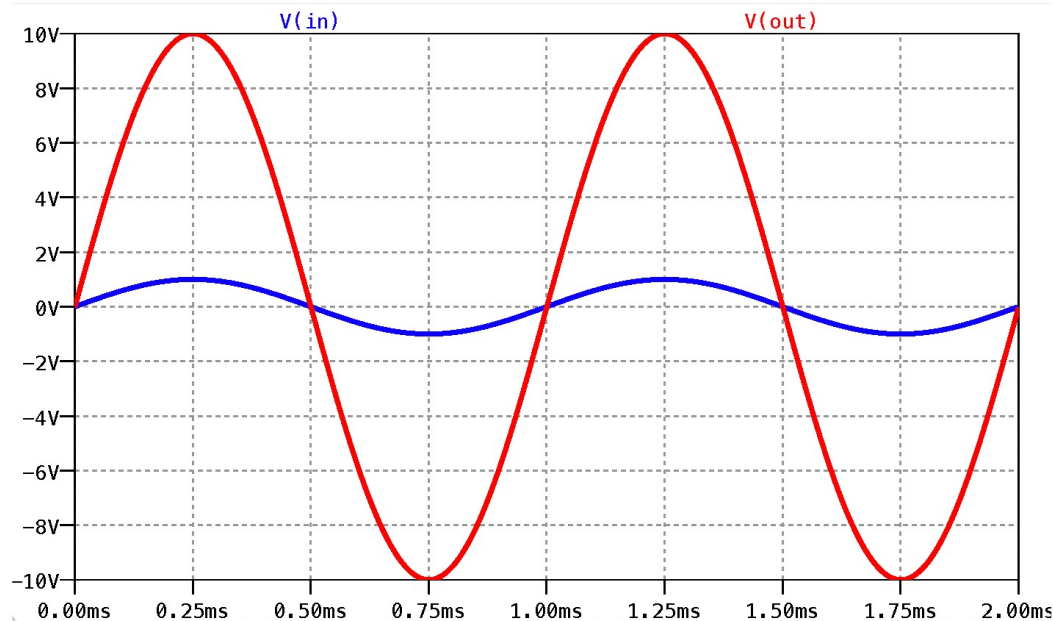
# Voltage-supply limit or Saturation

As we saw before, the maximum output voltage of op-amps is limited by the positive and negative voltage sources ( $V_{S+}$  and  $V_{S-}$ ) used to power up the op-amp chip.


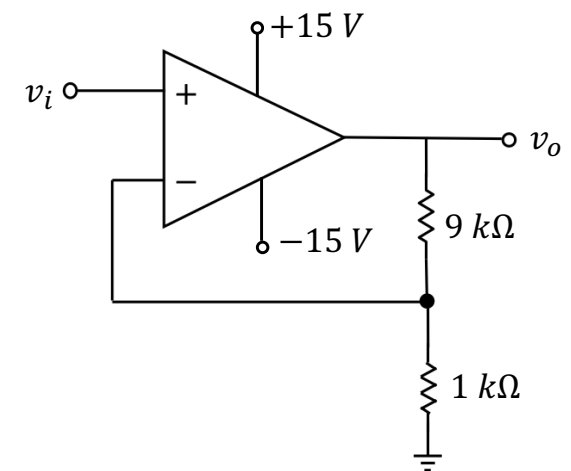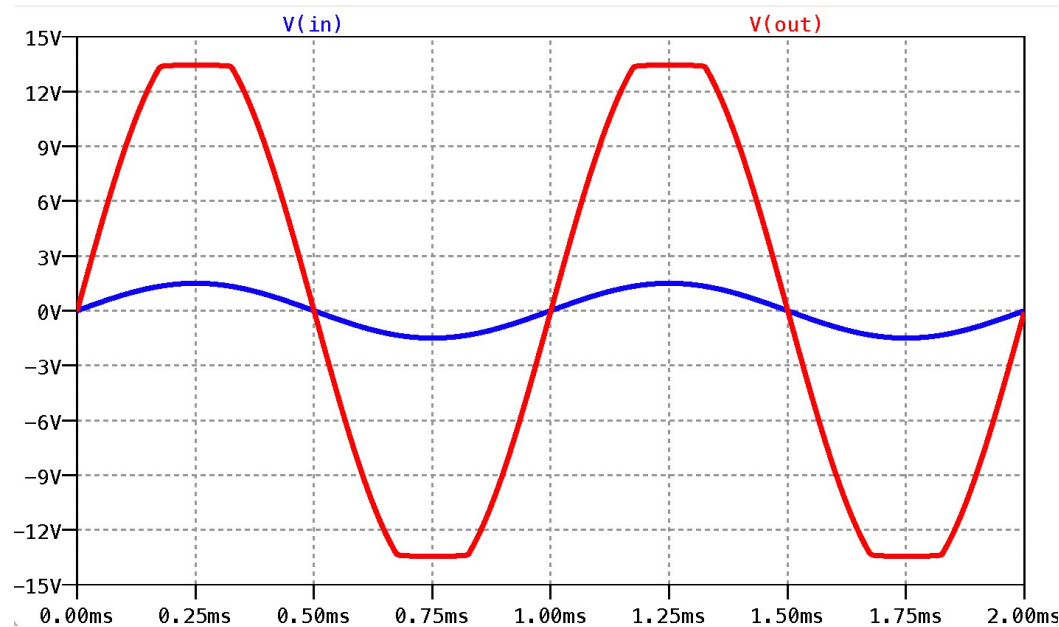
# Voltage-supply limit or Saturation


As we saw before, the maximum output voltage of op-amps is limited by the positive and negative voltage sources ( $V_{S+}$  and  $V_{S-}$ ) used to power up the op-amp chip.


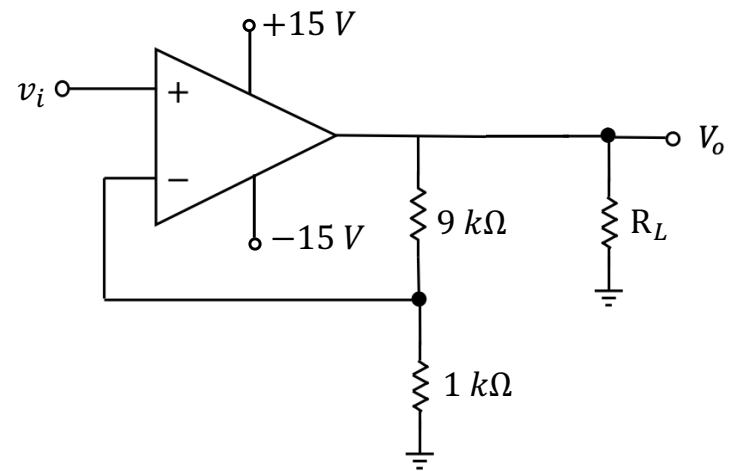
# Maximum Output Current



The output current of an op-amp is limited to a specified maximum value.

For example, in the 741 op-amp, the maximum output current is  $\pm 20\text{mA}$ .


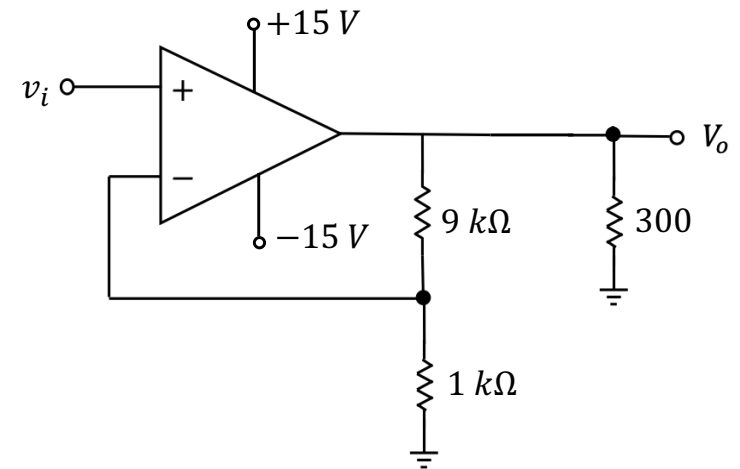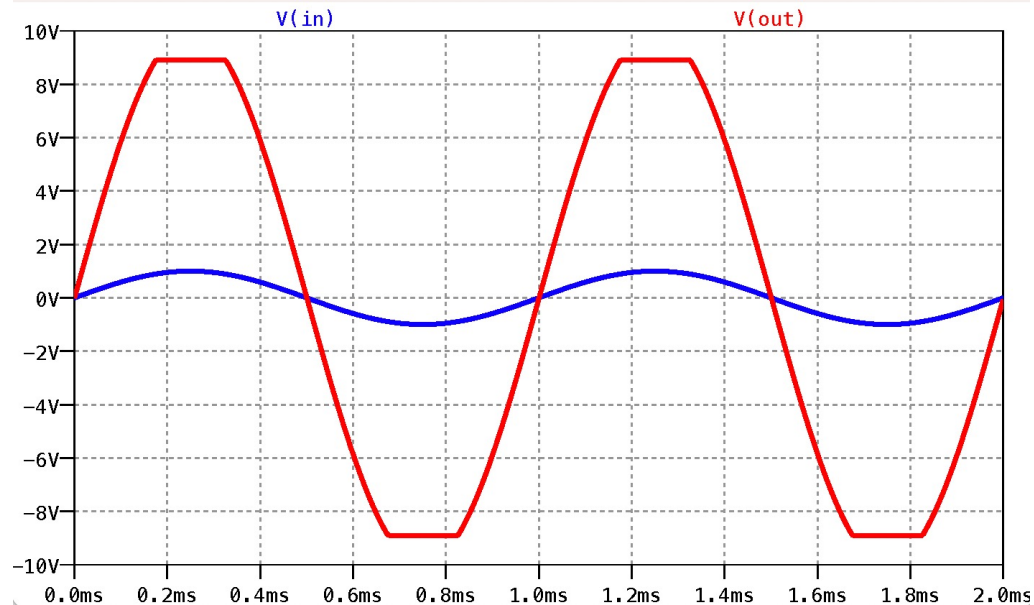
# Maximum Output Current

If the circuit requires a current larger than the maximum output current, in either direction, the output voltage will saturate at a level corresponding to the maximum allowed output current.





# Maximum Output Current - Example


The following op-amp circuit is fed with a low-frequency sinusoidal signal with peak amplitude of  $1\text{ V}$ . The maximum output current is  $\pm 20\text{ mA}$ . If  $R_L = 1\text{ k}\Omega$ , specify and sketch the output voltage.

assume an ideal op-amp:  $i_+ = i_- = 0 \Rightarrow i_1 = i_2$

KCL:  $i_o = i_1 + i_L$

$$i_o = \frac{V_o}{9\text{ k}\Omega + 1\text{ k}\Omega} + \frac{V_o}{R_L}$$
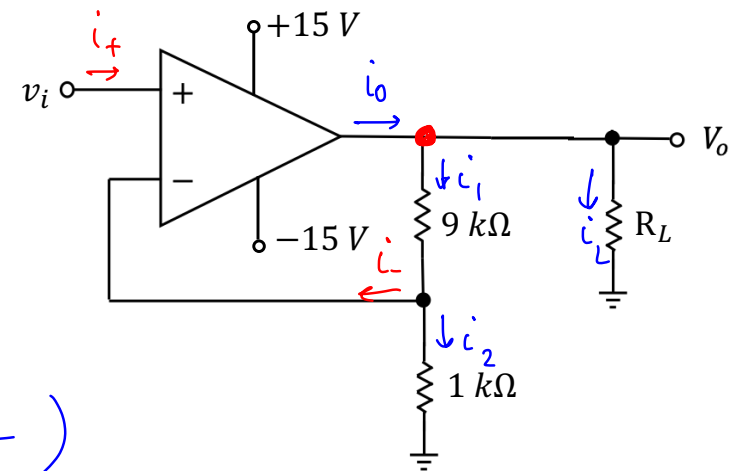
$$i_o = \frac{V_o}{10\text{ k}\Omega} + \frac{V_o}{1\text{ k}\Omega} = V_o \left( \frac{1}{10\text{ k}\Omega} + \frac{1}{1\text{ k}\Omega} \right)$$
$$= V_o \times 1.1$$



# Maximum Output Current - Example

The following op-amp circuit is fed with a low-frequency sinusoidal signal with peak amplitude of  $1\text{ V}$ . The maximum output current is  $\pm 20\text{ mA}$ . If  $R_L = 1\text{ k}\Omega$ , specify and sketch the output voltage.

assume an ideal op-amp:  $i_+ = i_- = 0 \Rightarrow i_1 = i_2$



$$i_o = V_o \times 1.1$$

Assume linear amplification:

$$\frac{V_o}{V_i} = 10 \text{ V/V} \Rightarrow \text{if } V_{i_{\max}} = 1\text{ V} \Rightarrow V_{o_{\max}} = 10\text{ V}$$

$$\Rightarrow i_{o_{\max}} = 10 \times 1.1 = 11\text{ mA} < +20\text{ mA}$$

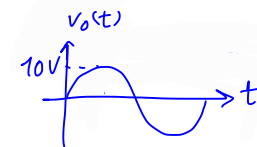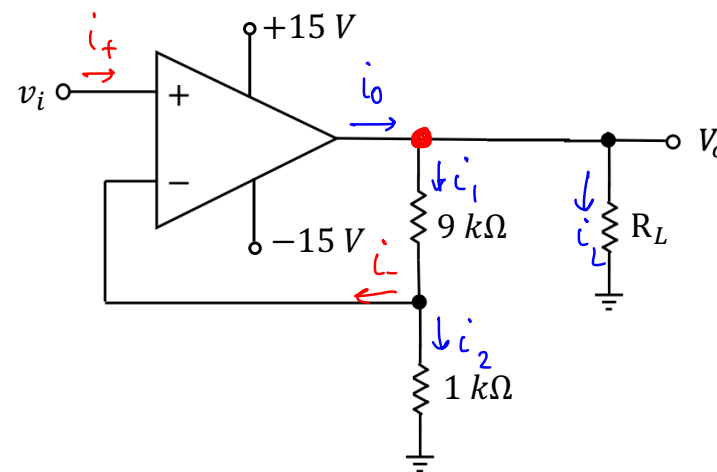$\Rightarrow$  We are not limited by the maximum output current  $\Rightarrow V_{o_{\max}} = 10\text{ V}$




## Lecture 3 reading quiz

The following op-amp circuit is fed with a low-frequency sinusoidal signal with the peak amplitude of  $V_P$ . The output saturation voltage is  $\pm 13\text{ V}$ , and the maximum output current is  $\pm 20\text{ mA}$ . If  $R_L = 0.5\text{ k}\Omega$ , find the maximum value of  $V_P$  for which an undistorted sinusoidal signal is obtained at the output?

Let's first find the voltage gain of the amplifier:

Assume an ideal op-amp:  $i_+ = i_- = 0$   
Negative feedback:  $V_+ = V_-$
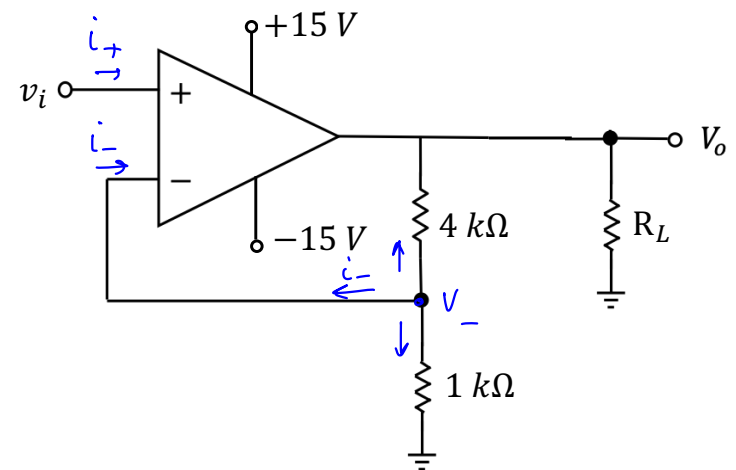
$$V_+ = V_i \rightarrow V_- = V_+ = V_i$$



## Lecture 3 reading quiz


The following op-amp circuit is fed with a low-frequency sinusoidal signal with the peak amplitude of  $V_P$ . The output saturation voltage is  $\pm 13\text{ V}$ , and the maximum output current is  $\pm 20\text{ mA}$ . If  $R_L = 0.5\text{ k}\Omega$ , find the maximum value of  $V_P$  for which an undistorted sinusoidal signal is obtained at the output?

Let's first find the voltage gain of the amplifier:

Assume an ideal op-amp:  $i_+ = i_- = 0$   
Negative feedback:  $V_+ = V_-$

$$V_+ = V_i \rightarrow V_- = V_+ = V_i$$
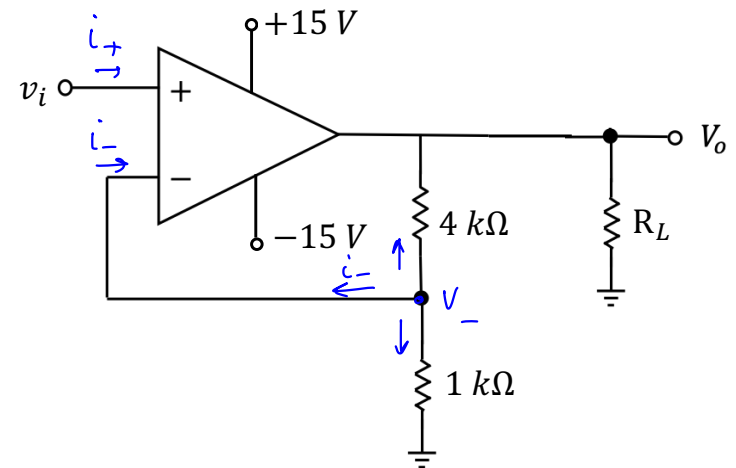
$$\text{KCL: } \frac{V_-}{1\text{ k}\Omega} = \frac{V_o - V_-}{4\text{ k}\Omega} \Rightarrow V_o = 5V_- = 5V_i \Rightarrow \boxed{V_o = 5V_i}$$




This relationship is valid if there is no distortion.
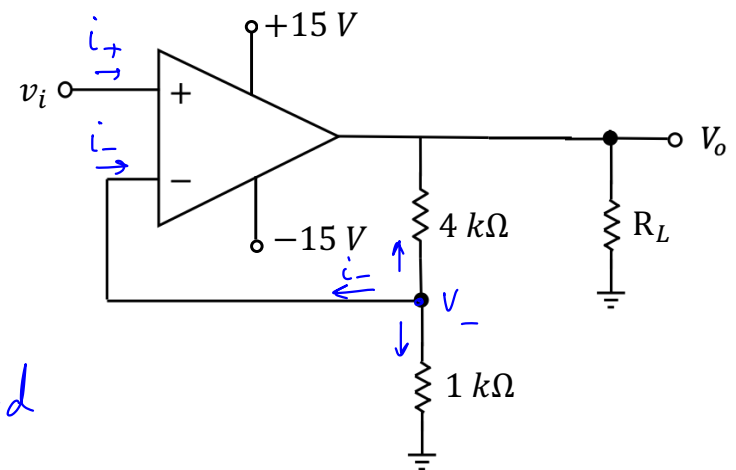
## Lecture 3 reading quiz

The following op-amp circuit is fed with a low-frequency sinusoidal signal with the peak amplitude of  $V_P$ . The output saturation voltage is  $\pm 13\text{ V}$ , and the maximum output current is  $\pm 20\text{ mA}$ . If  $R_L = 0.5\text{ k}\Omega$ , find the maximum value of  $V_P$  for which an undistorted sinusoidal signal is obtained at the output?

let's assume that the output voltage can reach the max possible  $\pm 13\text{ V}$ . We need to check if the op-amp can supply the required output current to maintain  $\pm 13\text{ V}$  across  $R_L$ .



## Lecture 3 reading quiz

The following op-amp circuit is fed with a low-frequency sinusoidal signal with the peak amplitude of  $V_P$ . The output saturation voltage is  $\pm 13\text{ V}$ , and the maximum output current is  $\pm 20\text{ mA}$ . If  $R_L = 0.5\text{ k}\Omega$ , find the maximum value of  $V_P$  for which an undistorted sinusoidal signal is obtained at the output?


KCL at the output node:

$$i_o = \frac{V_o}{R_L} + \frac{V_o}{4\text{ k}\Omega + 1\text{ k}\Omega}$$

The required  $i_o$  to reach  $V_{o\text{ max}} = \pm 13\text{ V}$  is:

$$|i_o| = \frac{13\text{ V}}{0.5\text{ k}\Omega} + \frac{13\text{ V}}{5\text{ k}\Omega} = 28.6\text{ mA} > 20\text{ mA}$$

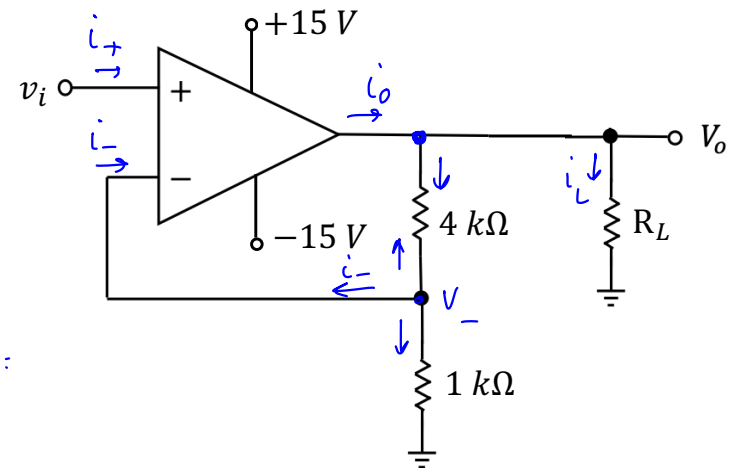$\Rightarrow$  the output voltage cannot reach to  $\pm 13\text{ V}$ .




## Lecture 3 reading quiz

The following op-amp circuit is fed with a low-frequency sinusoidal signal with the peak amplitude of  $V_P$ . The output saturation voltage is  $\pm 13\text{ V}$ , and the maximum output current is  $\pm 20\text{ mA}$ . If  $R_L = 0.5\text{ k}\Omega$ , find the maximum value of  $V_P$  for which an undistorted sinusoidal signal is obtained at the output?

We can find the maximum output voltage using the same KCL and  $i_{o\max}$ .

KCL at the output node:

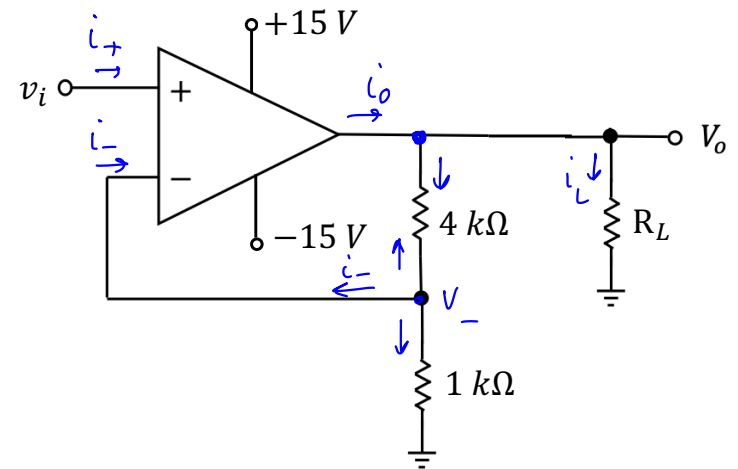

$$i_{o\max} = \frac{V_{o\max}}{R_L} + \frac{V_{o\max}}{4\text{ k}\Omega + 1\text{ k}\Omega} \quad \rightarrow \quad 20\text{ mA} = V_{o\max} \left( \frac{1}{0.5\text{ k}\Omega} + \frac{1}{5\text{ k}\Omega} \right)$$
$$\rightarrow V_{o\max} = 9.09\text{ V}$$


## Lecture 3 reading quiz

The following op-amp circuit is fed with a low-frequency sinusoidal signal with the peak amplitude of  $V_P$ . The output saturation voltage is  $\pm 13\text{ V}$ , and the maximum output current is  $\pm 20\text{ mA}$ . If  $R_L = 0.5\text{ k}\Omega$ , find the maximum value of  $V_P$  for which an undistorted sinusoidal signal is obtained at the output?

$$V_{o\max} = 9.09\text{ V}$$

To get an undistorted signal:
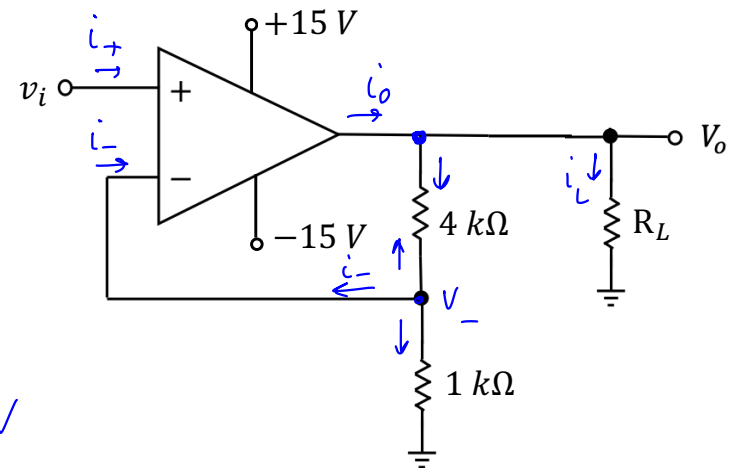
$$V_o = 5 V_i \Rightarrow V_{i\max} = V_P = \frac{9.09}{5} = 1.82\text{ V}$$






# Discussion question 1.

What is  $v_o/v_i$  in this op-amp circuit? Assume an ideal op-amp.

ideal op-amp :  $i_+ = i_- = 0$   
negative feedback:  $v_+ = v_-$

KCL at the inverting terminal:

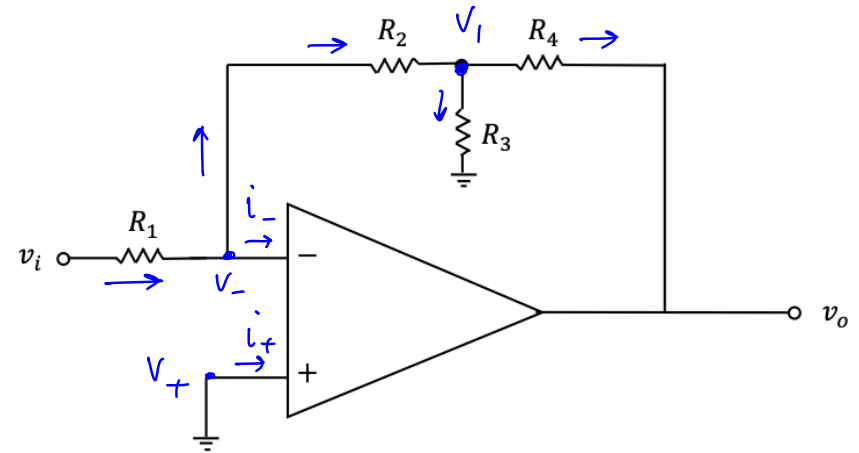
$$\begin{cases} \frac{v_i - v_-}{R_1} = \frac{v_- - v_1}{R_2} \\ v_- = v_+ = 0 \end{cases} \Rightarrow \frac{v_i}{R_1} = \frac{-v_1}{R_2} \Rightarrow v_1 = \frac{-R_2}{R_1} v_i$$


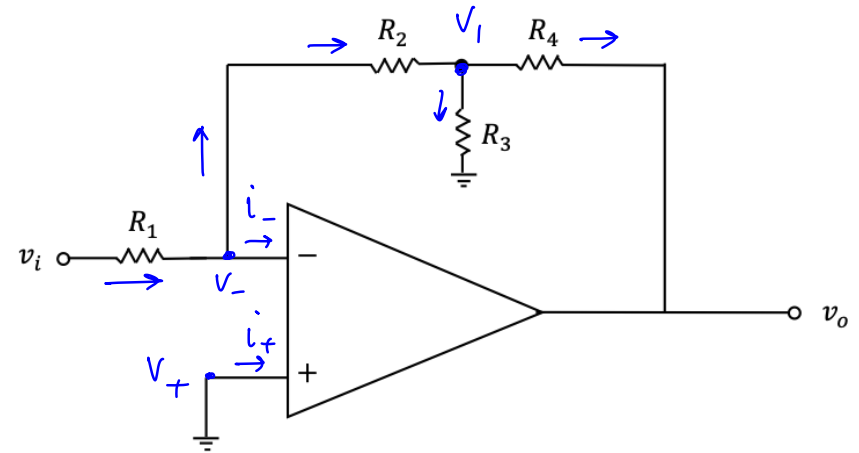
# Discussion question 1.

What is  $v_o/v_i$  in this op-amp circuit? Assume an ideal op-amp.

ideal op-amp :  $i_+ = i_- = 0$   
negative feedback:  $v_+ = v_-$



KCL at node  $V_1$  :

$$\frac{0 - V_1}{R_2} = \frac{V_1}{R_3} + \frac{V_1 - v_o}{R_4} \Rightarrow \frac{v_o}{R_4} = \left( \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) V_1$$


$$v_o = \left( 1 + \frac{R_4}{R_2} + \frac{R_4}{R_3} \right) V_1$$

# Discussion question 1.

What is  $v_o/v_i$  in this op-amp circuit? Assume an ideal op-amp.

$$\begin{cases} V_o = \left( 1 + \frac{R_4}{R_2} + \frac{R_4}{R_3} \right) V_1 \\ V_1 = \frac{-R_2}{R_1} V_i \end{cases}$$
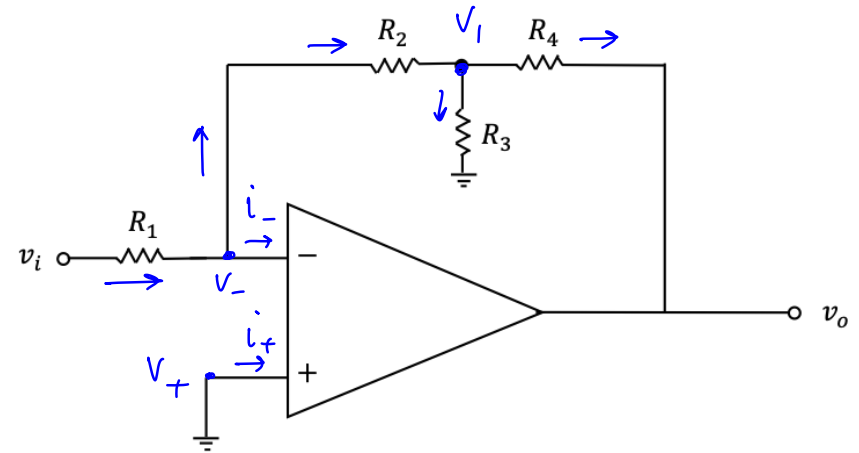
$$\Rightarrow V_o = \frac{-R_2}{R_1} \left( 1 + \frac{R_4}{R_2} + \frac{R_4}{R_3} \right) V_i$$




## Discussion question 2.

The following circuit uses a  $10\text{ k}\Omega$  potentiometer to obtain an adjustable gain amplifier.

- Derive an expression for the gain as a function of the potentiometer setting  $x$ .
- What is the range of the gain obtained?
- Show how to add a fixed resistor so that the gain range can be 1 to 11 V/V. What is the value of that resistor?

Assume an ideal op-amp.

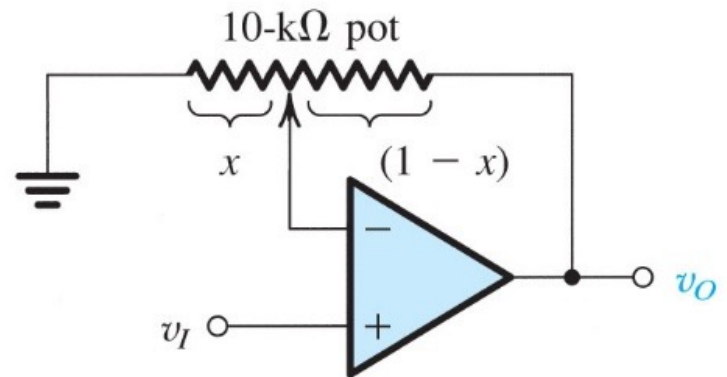

## Discussion question 2.

The following circuit uses a  $10\text{ k}\Omega$  potentiometer to obtain an adjustable gain amplifier.


- Derive an expression for the gain as a function of the potentiometer setting  $x$ .
- What is the range of the gain obtained?
- Show how to add a fixed resistor so that the gain range can be 1 to 11 V/V. What is the value of that resistor?

Assume an ideal op-amp.

$$R_1 = x \times 10\text{ k}\Omega$$

$$R_2 = (1-x) \times 10\text{ k}\Omega$$

$$R_1 + R_2 = 10\text{ k}\Omega$$

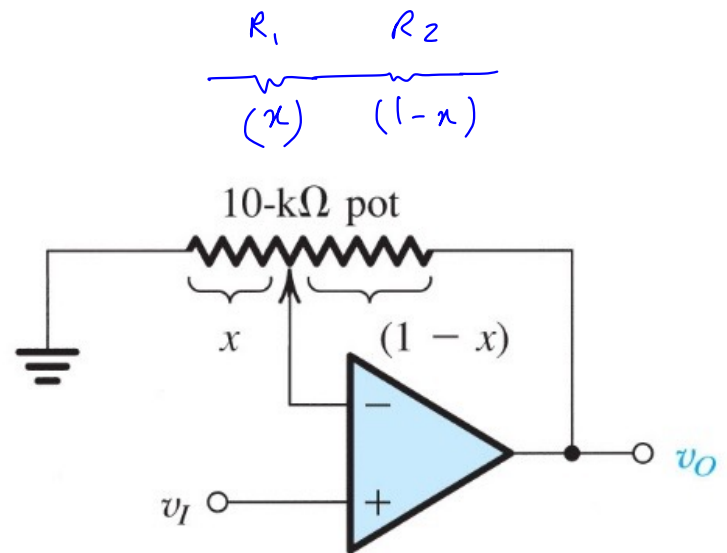

## Discussion question 2.

- a) Derive an expression for the gain as a function of the potentiometer setting  $x$ .

Assume an ideal op-amp.

$$\left\{ \begin{array}{l} \text{ideal op-amp : } i_+ = i_- = 0 \\ \text{negative feedback: } v_+ = v_- \end{array} \right.$$


$$v_+ = v_I \rightarrow v_- = v_+ = v_I$$

KCL at the inverting terminal:

$$\frac{v_-}{R_1} = \frac{v_o - v_-}{R_2} \rightarrow \frac{v_I}{R_1} = \frac{v_o - v_I}{R_2}$$

$$\Rightarrow v_o = \left(1 + \frac{R_2}{R_1}\right) v_I$$

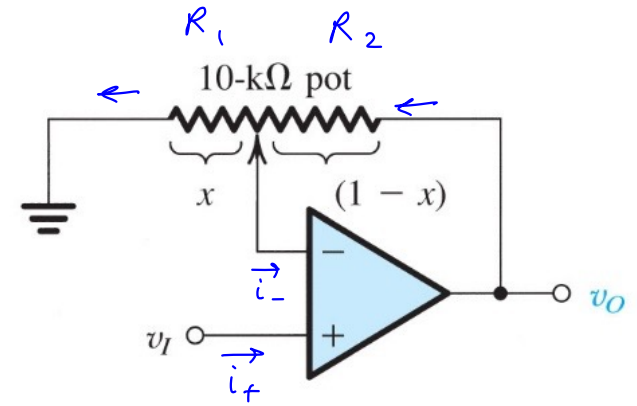
$$R_1 = 10x \quad \text{and} \quad R_2 = 10(1-x) \Rightarrow v_o = \left(1 + \frac{1-x}{x}\right) v_I = \frac{v_I}{x}$$



## Discussion question 2.

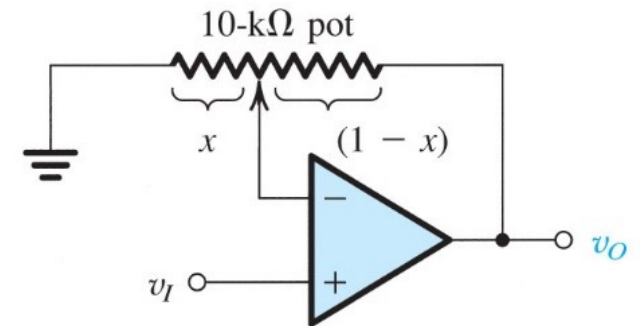- a) What is the range of the gain obtained?  
Assume an ideal op-amp.

$$\text{Voltage gain} = \frac{V_o}{V_i} = \frac{1}{x}$$



$$0 \leq x \leq 1 \rightarrow 1 \leq \text{Voltage gain} < \infty$$

not achievable

$V_{out}$  will not exceed  $V_{sat}$




## Discussion question 2.

- a) What is the range of the gain obtained?  
Assume an ideal op-amp.

$$V_o = A (V_+ - V_-) = A V_+ = A V_{in}$$

output will quickly go to  $V_{sat}^+$  when

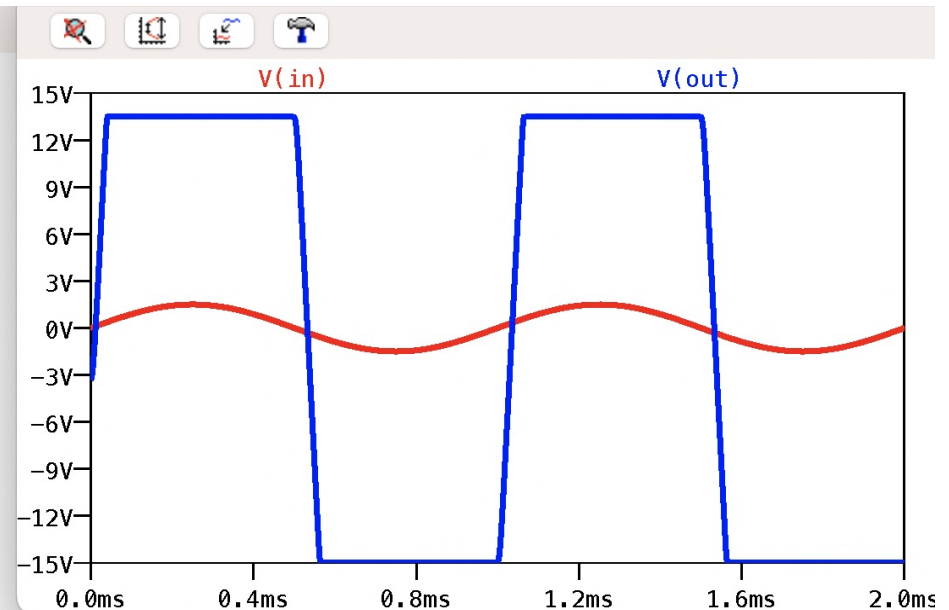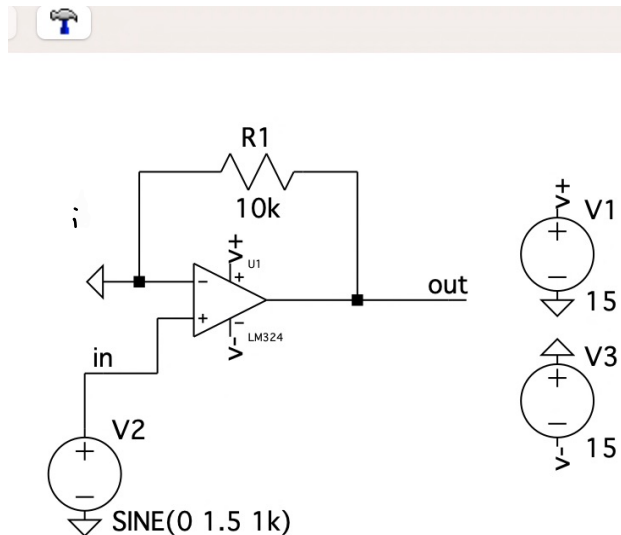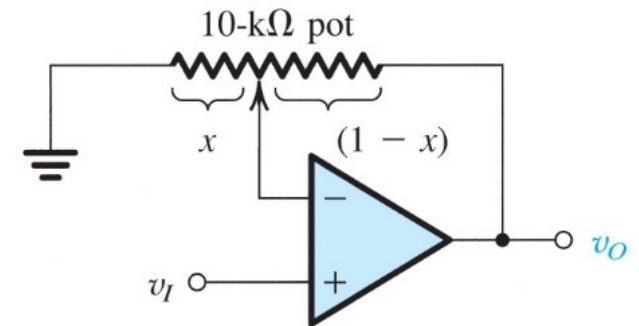$V_i$  is positive and will quickly go to  $V_{sat}^-$  when  $V_i$  is negative.






## Discussion question 2.

- a) Show how to add a fixed resistor so that the gain range can be 1 to 11 V/V. What is the value of that resistor?

Assume an ideal op-amp.

$$\left\{ \begin{array}{l} \text{ideal op-amp : } i_+ = i_- = 0 \\ \text{negative feedback: } v_+ = v_- \end{array} \right.$$
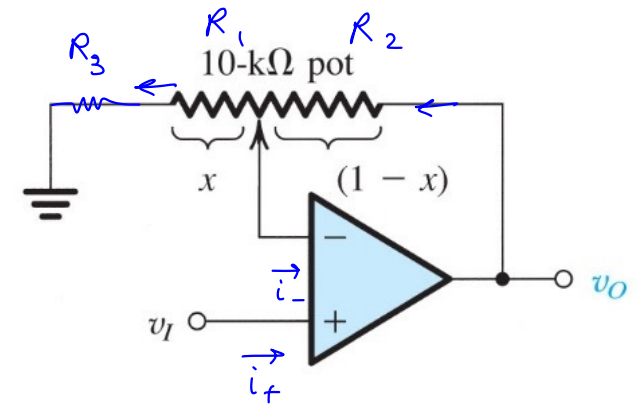
$$v_+ = v_I \rightarrow v_- = v_+ = v_I$$



$$\text{KCL at the inverting terminal: } \frac{v_-}{R_1 + R_3} = \frac{v_O - v_-}{R_2}$$

$$\Rightarrow v_O = \left( 1 + \frac{R_2}{R_1 + R_3} \right) v_I$$

## Discussion question 2.


- a) Show how to add a fixed resistor so that the gain range can be 1 to 11 V/V. What is the value of that resistor?

Assume an ideal op-amp.

$$V_o = \left( 1 + \frac{R_2}{R_1 + R_3} \right) V_I$$

$$R_1 = 10x \quad \text{and} \quad R_2 = 10(1-x)$$
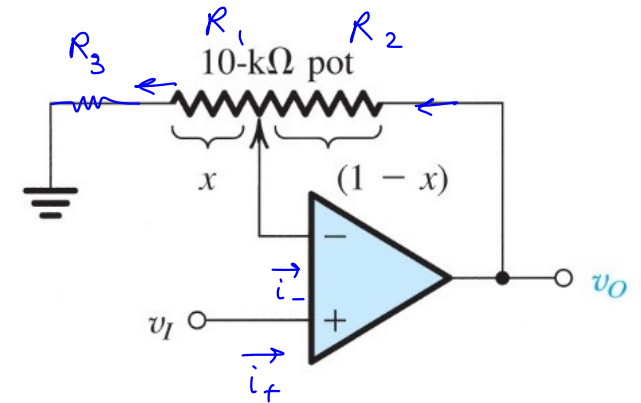
$$V_o = \left( 1 + \frac{10(1-x)}{10x + R_3} \right) V_I = \left( 1 + \frac{1-x}{x + \frac{R_3}{10}} \right) V_I$$



## Discussion question 2.

- a) Show how to add a fixed resistor so that the gain range can be 1 to 11 V/V. What is the value of that resistor?

Assume an ideal op-amp.

$$V_o = \left( 1 + \frac{R_2}{R_1 + R_3} \right) V_I$$

$$R_1 = 10x \quad \text{and} \quad R_2 = 10(1-x)$$

$$V_o = \left( 1 + \frac{10(1-x)}{10x + R_3} \right) V_I = \left( 1 + \frac{1-x}{x + \frac{R_3}{10}} \right) V_I$$

$$0 \leq x \leq 1, \quad \text{to have } \frac{V_o}{V_I} = 11 \text{ V/V} \rightarrow x=0 \quad \text{and} \quad 1 + \frac{1}{\frac{R_3}{10}} = 11$$

$$\Rightarrow R_3 = 1 \text{ k}\Omega$$

