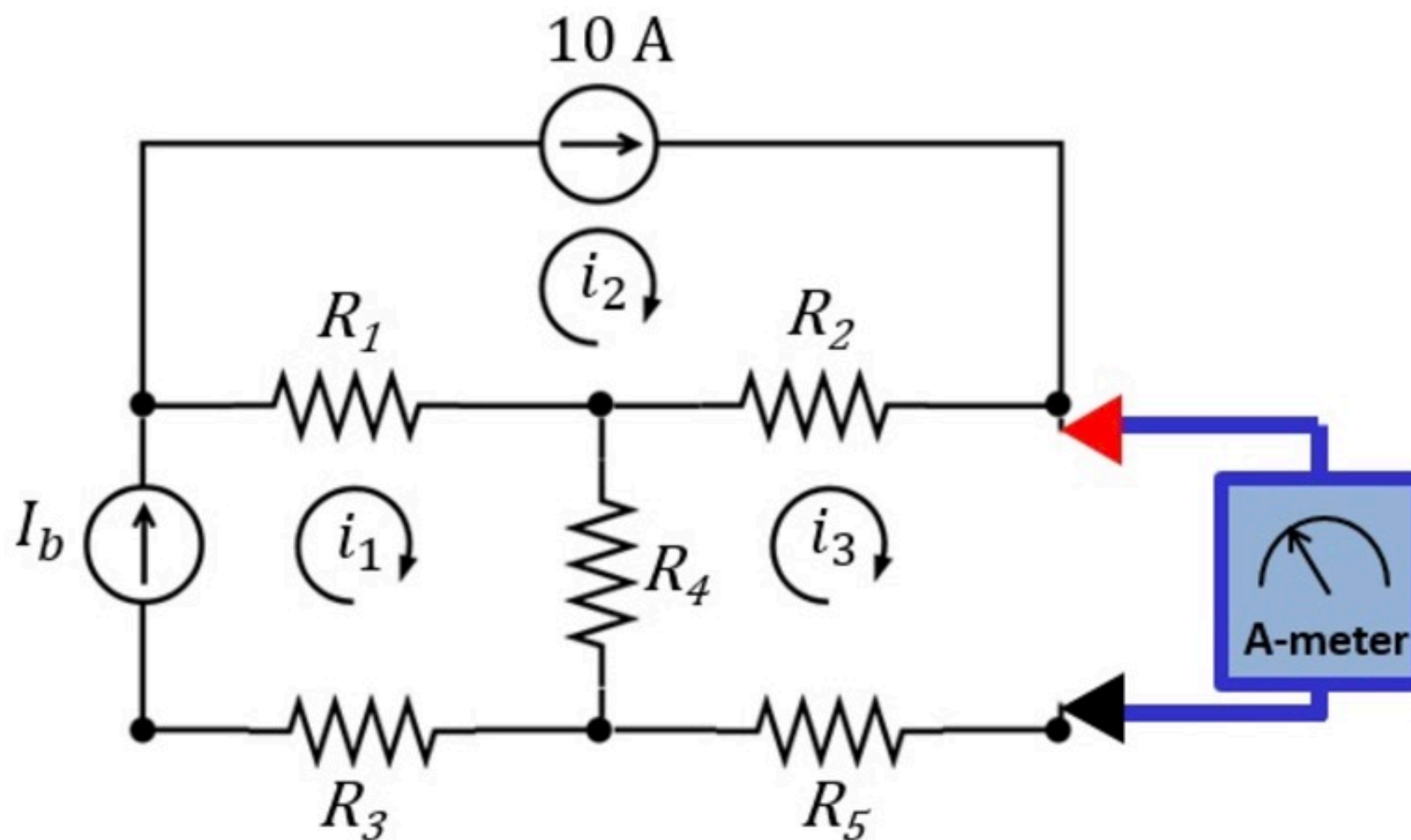


Nodal Mesh 007

Problem has been graded.

Given the ammeter reading X ,
find the value of resistance R_4 .



Given Variables:

R_1 : 2 ohm

R_2 : 3 ohm

R_3 : 2 ohm

R_5 : 5 ohm

X : 3 A

I_b : 1 A

Calculate the following:

R_4 (ohm) :

Hint: Find the voltage over R_4 using KVL in any loop