

Name

PID

**UNIVERSITY OF CALIFORNIA, SAN DIEGO**

Electrical and Computer Engineering Department

ECE 65 – Spring 2023

*Components and Circuits lab*

Midterm Exam#1 *solutions*

Closed books, one one-sided cheat sheet, and calculators are allowed

Electronic devices are not allowed.

Please put all answers in the provided sheets.

Be sure to write your name and PID.

Please do not begin until told.


**Show your work.**

Good luck.

**Problem 1.** (10 points)

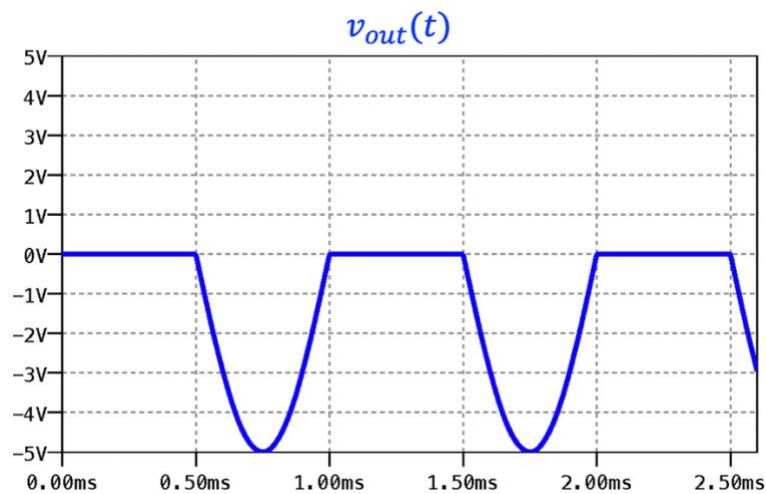
- a) Design a diode circuit that would generate the output waveform shown in the below graph when the input signal  $v_i(t) = 5 \sin(2\pi \times 1000 t)$  V is applied to the circuit.

You can use regular PN junction diodes ( $V_{D0} = 0.7$  V), Zener diodes (any desired  $V_Z$ ), resistor(s), and other circuit elements in your design. Make sure to label  $v_i$  and  $v_{out}$  on your circuit diagram.



- a) Parametrically solve your designed circuit. That means find the relationship between  $v_i$  and  $v_{out}$ .

**Show your work.**

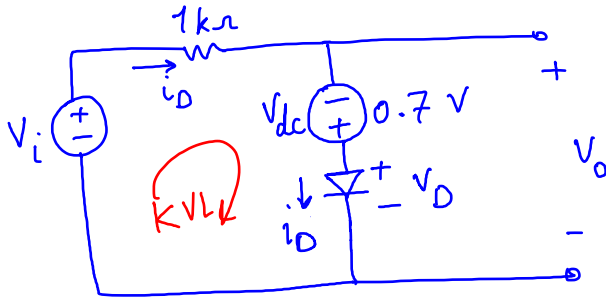

Case 1: Diode ON

$$i_D \geq 0 \text{ and } V_D = V_{D_0}$$

$$\text{KVL: } V_i = i_D \times 1k\Omega - 0.7V + V_D$$

$$V_i = i_D \times 1k\Omega - 0.7 + 0.7$$

$$i_D = \frac{V_i}{1k\Omega} \geq 0 \Rightarrow V_i \geq 0$$

$$V_o = -0.7 + V_{D_0} = 0$$

Case 2: Diode OFF

$$i_D = 0 \text{ and } V_D < V_{D_0}$$

$$\text{KVL: } V_i = i_D \times 1k\Omega - 0.7V + V_D$$

$$V_i = 0 - 0.7 + V_D$$


$$V_D = V_i + 0.7 < 0.7$$

$$\Rightarrow V_i < 0$$

$$V_o = V_i - i_D \times 1k\Omega = V_i$$

$$V_o = V_i$$

Another correct circuit:

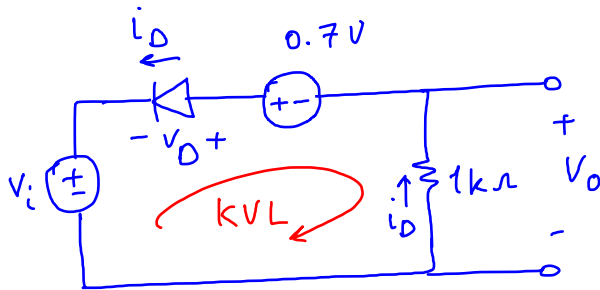

Case 1: Diode ON

$$i_D \geq 0 \text{ and } V_D = V_{D0}$$

$$\text{KVL: } V_i = -V_D + 0.7V - i_D \times 1k\Omega$$

$$V_i = -0.7 + 0.7 - i_D \times 1k\Omega$$

$$i_D = \frac{-V_i}{1k\Omega} \geq 0 \Rightarrow V_i \leq 0$$

$$V_o = V_i + V_D - 0.7V = V_i + 0.7 - 0.7$$

$$V_o = V_i$$

Case 2: Diode OFF

$$i_D = 0 \text{ and } V_D < V_{D0}$$

$$\text{KVL: } V_i = -V_D + 0.7V - i_D \times 1k\Omega$$

$$V_i = -V_D + 0.7 - 0$$

$$V_D = -V_i + 0.7 < 0.7$$

$$\Rightarrow V_i > 0$$


$$V_o = -i_D \times 1k\Omega = 0$$

$$V_o = 0$$

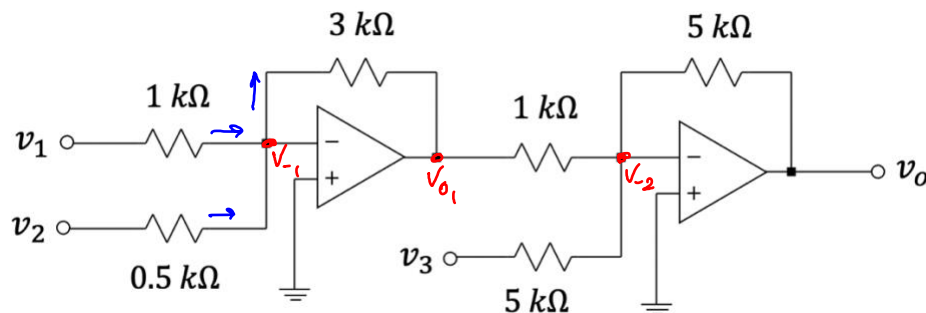**Problem 2.** (6 points)

Assuming ideal op-amps with  $V_{sat} = \pm 15V$  in the below circuit,

- find (derive) an expression relating  $v_o$  to  $v_1$ ,  $v_2$ , and  $v_3$ .
- Sketch the output waveform if  $v_1 = 0.5 V$ ,  $v_2 = 0.5 V$ , and  $v_3 = 1 \sin(2 \times 1000t) V$ .  
You do not need to label the time axis.



**Show your work.**

ideal op-amp  $\rightarrow i_+ = i_- = 0$  : for both op-amps  
negative feedback  $\rightarrow V_+ = V_-$

KCL :

$$\frac{V_1 - V_{-1}}{1k\Omega} + \frac{V_2 - V_{-2}}{0.5k\Omega} = \frac{V_- - V_{o1}}{3k\Omega}$$

$$V_{+1}=0 \rightarrow V_{-1}=0 \rightarrow \frac{V_1}{1k\Omega} + \frac{V_2}{0.5k\Omega} = \frac{-V_{o1}}{3k\Omega}$$

$$\rightarrow V_{o1} = -3V_1 - 6V_2$$

Name

PID

KCL:

$$\frac{V_{o1} - V_{-2}}{1k\Omega} + \frac{V_3 - V_{-2}}{5k\Omega} = \frac{V_{-2} - V_o}{5k\Omega}$$

$$V_{+2} = 0 \rightarrow V_{-2} = 0$$

$$\frac{V_{o1}}{1k\Omega} + \frac{V_3}{5k\Omega} = \frac{-V_o}{5k\Omega} \rightarrow V_o = -5 V_{o1} - V_3$$

$$V_{o1} = -3 V_1 - 6 V_2$$

$$V_1 = 0.5 V \text{ and } V_2 = 0.5 V \rightarrow V_{o1} = -1.5 V - 3V = -4.5 V < V_{sat-}$$

$$\rightarrow V_{o1} = -4.5 V$$

$$V_o = -5 V_{o1} - V_3$$

$$V_{o1} = -4.5 V \text{ and } V_3 = 1 \sin(\omega t) \rightarrow V_o = 22.5 - 1 \sin(\omega t) > V_{sat+}$$

The output voltage will saturate and  $V_o$  will not exceed  $V_{sat+}$

$$\Rightarrow V_o = V_{sat+} = 15 V$$

