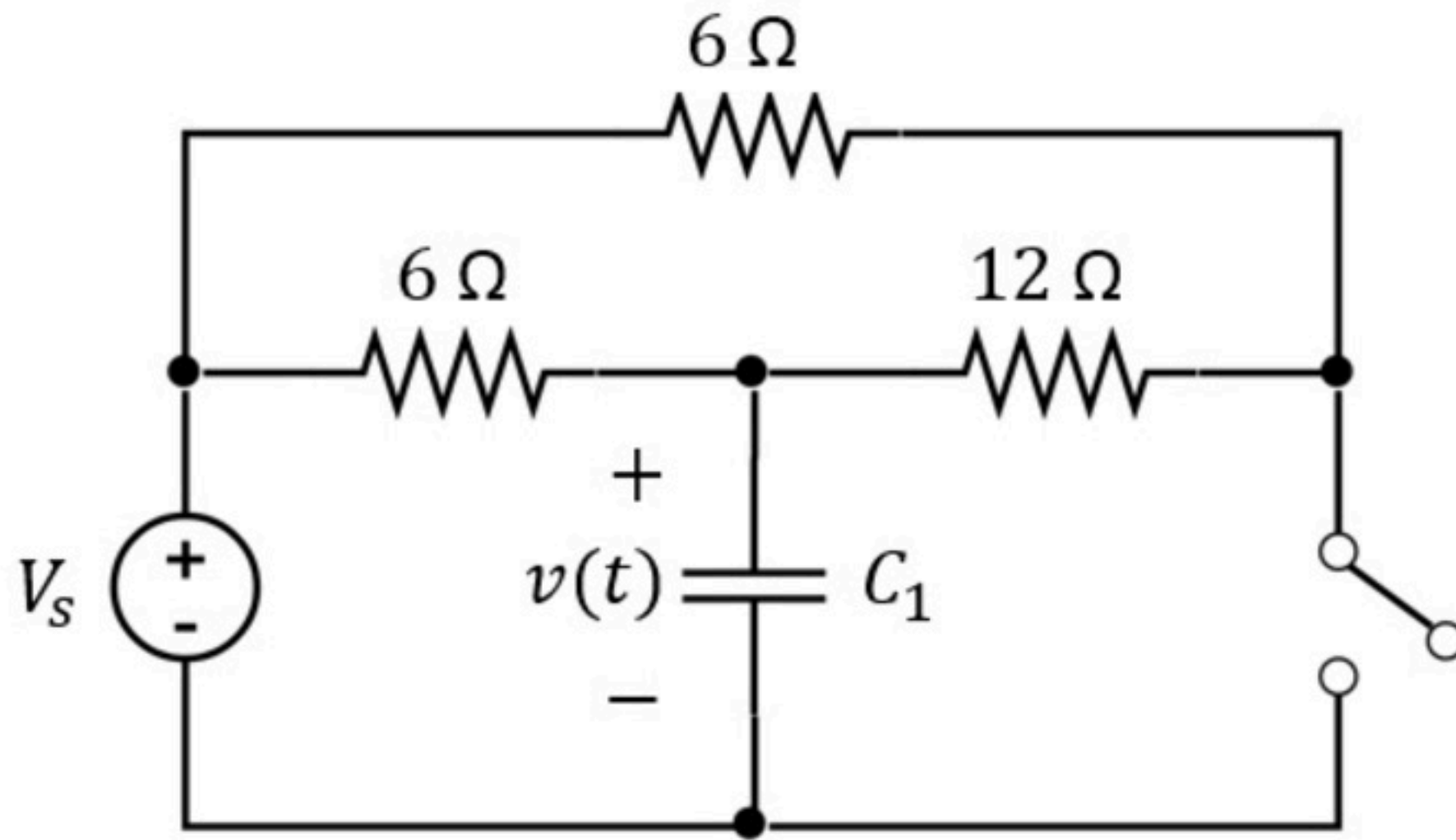


First order circuits 002

Unlimited Attempts.

- a) Find the time constant τ_1 and the steady state capacitor voltage $v_1 = v(\infty)$ when the switch is open.
- b) Find the time constant τ_2 and the steady state capacitor voltage $v_2 = v(\infty)$ when the switch is closed.



Given Variables:

V_s : 30 V

C_1 : 8 nF

Calculate the following:

τ_1 (ns) :

36



v_1 (V) :

30



τ_2 (ns) :

32



v_2 (V) :

20






Hint: The circuit is different in the two cases

- a) Find the time constant τ_1 and the steady state capacitor voltage $v_1 = v(\infty)$ when the switch is open.
- b) Find the time constant τ_2 and the steady state capacitor voltage $v_2 = v(\infty)$ when the switch is closed.


$V_s : 60 \text{ V}$

$C_1 : 6 \text{ nF}$

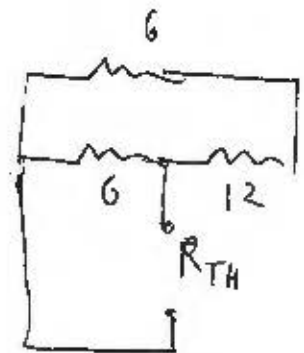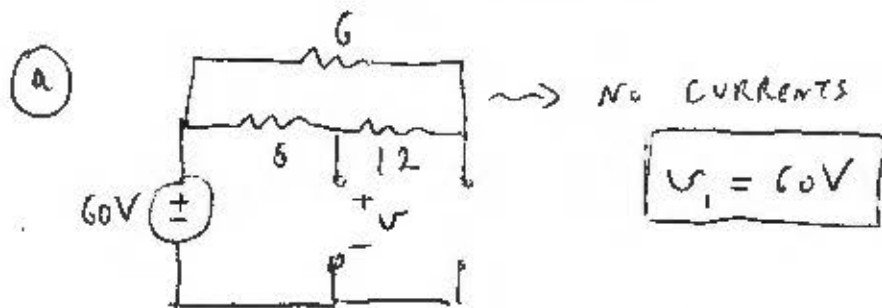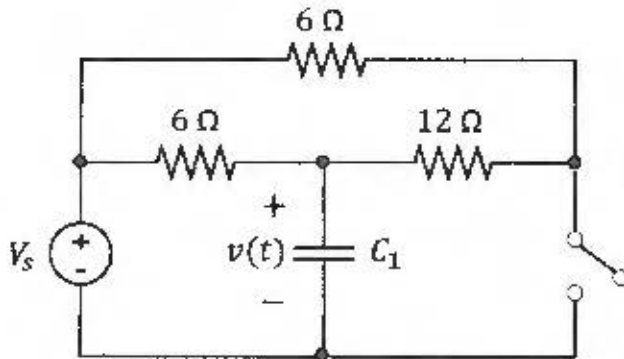



$$\tau_1 = R_{TH} \cdot C_1 \Rightarrow \tau_1 = 27 \text{ ns}$$
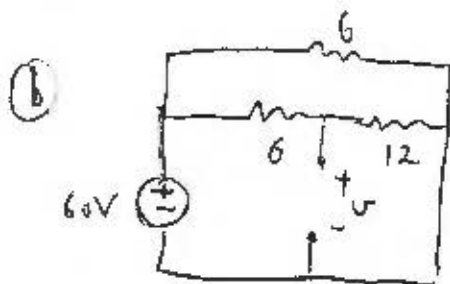
$$R_{TH} = 6 // 12 = \frac{9}{2} \Omega$$



$$v = 60 \cdot \frac{12}{6+12} = 40$$

$$v_2 = 40 \text{ V}$$

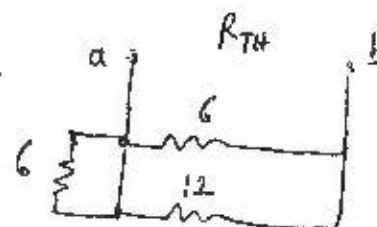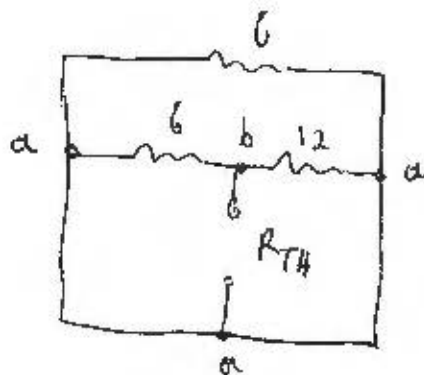

$$R_{TH} = 6 // 12 = 4 \Omega$$

$$\tau_2 = R_{TH} \cdot C_1 \Rightarrow \tau_2 = 24 \text{ ns}$$