

ECE 65: Components & Circuits Lab

Lecture 2

Operational Amplifier (op-amp)


Reference notes: sections 7.1, 7.2

Sedra & Smith (7th Ed): sections 2-2.3

Saharnaz Baghdadchi


Course map

7. Operational amplifiers

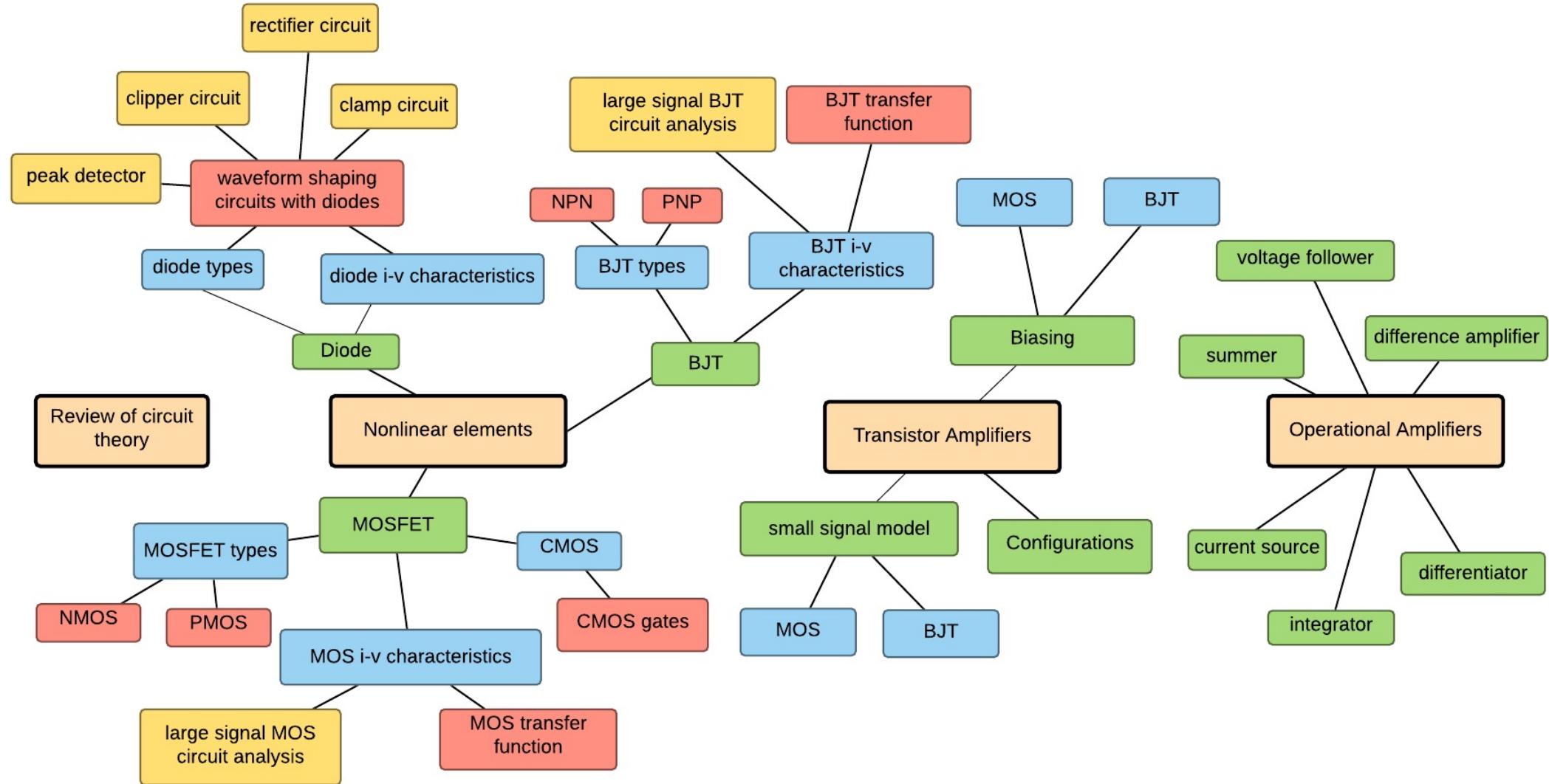

Operational Amplifiers

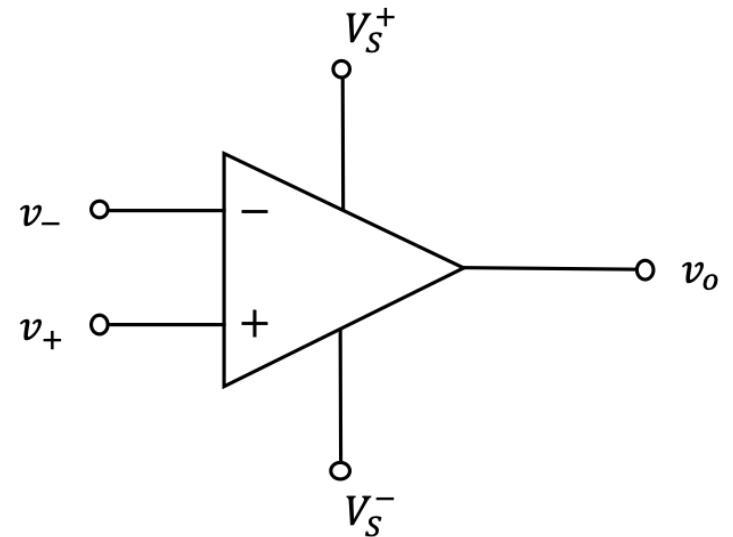
Operational amplifiers (op-amps) are general purpose voltage amplifiers.



Operational Amplifiers

Operational amplifiers (op-amps) are general purpose voltage amplifiers.

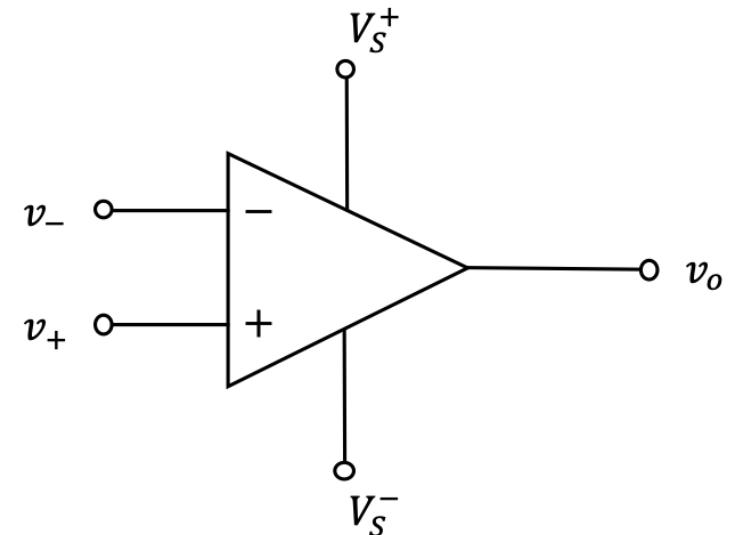They are constructed such that they amplify the voltage difference between the two input signals.



$$v_o = A(v_+ - v_-) = Av_d$$



open-loop voltage gain

Operational Amplifiers

Operational amplifiers (op-amps) are general purpose voltage amplifiers.

They are constructed such that they amplify the voltage difference between the two input signals.

$$v_o = A(v_+ - v_-) = Av_d$$

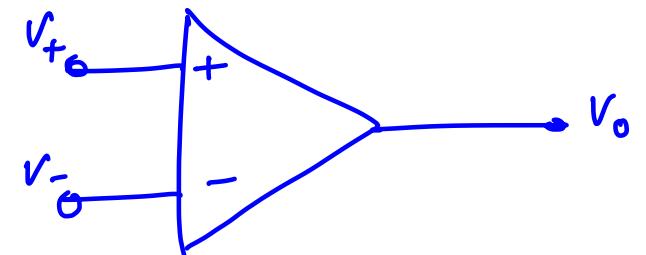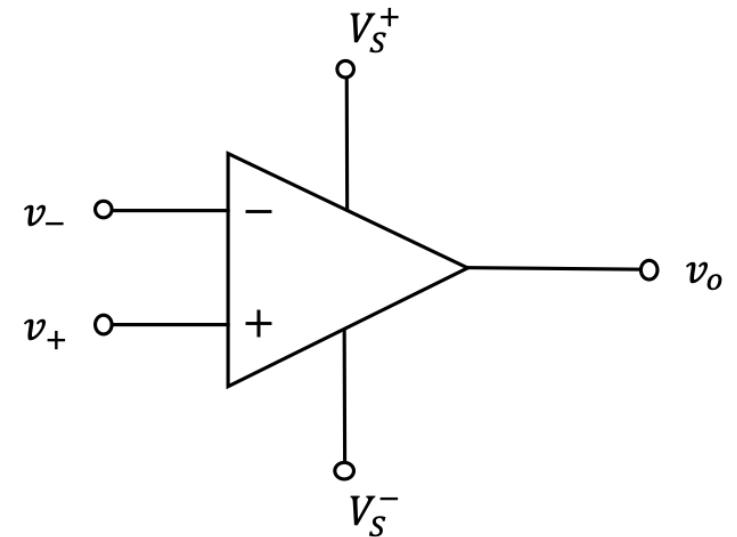


The $-$ and $+$ terminals are called the inverting and non-inverting terminals, respectively.

Operational Amplifiers

Operational amplifiers (op-amps) are general purpose voltage amplifiers.

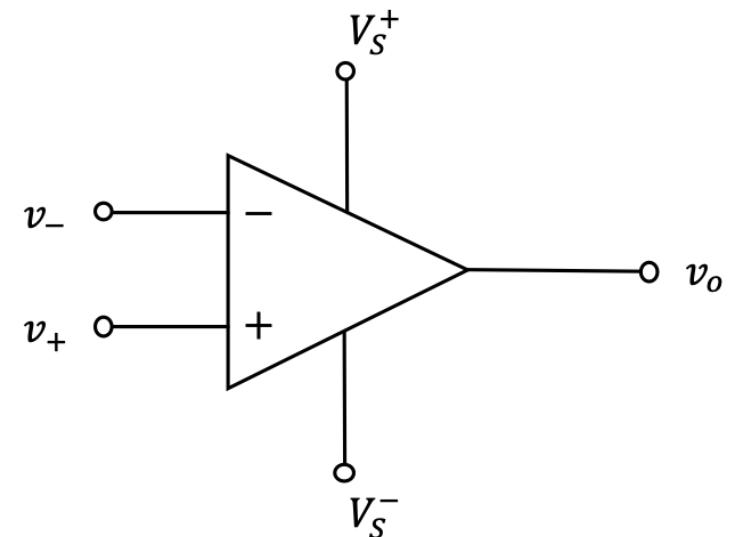
They are constructed such that they amplify the voltage difference between the two input signals.



$$v_o = A(v_+ - v_-) = Av_d$$

They have a very large gain. Typically, $A \sim 10^5$ to 10^7 .


LM 741 op-amp

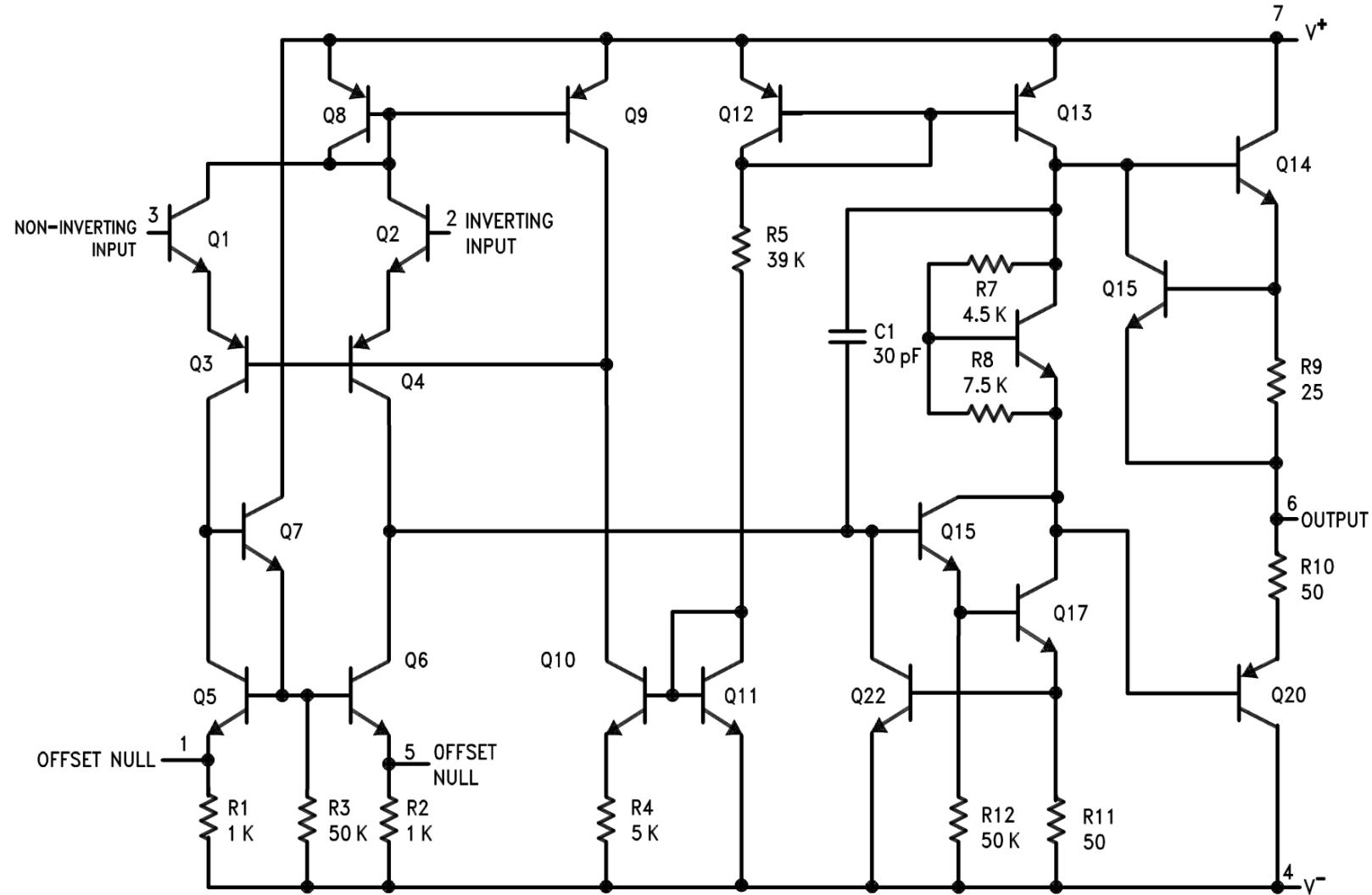


LM 741 op-amp (ti.com)

OpAmp models

Linear model

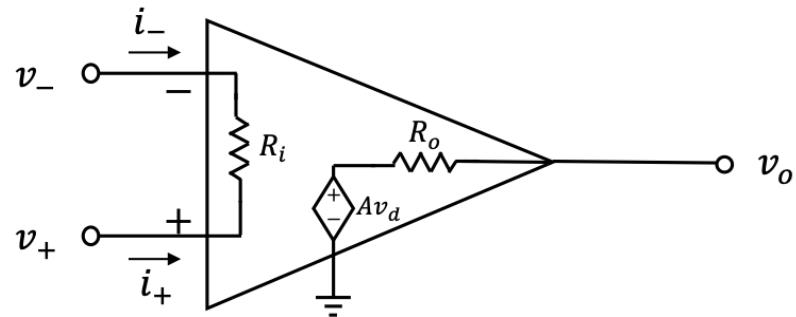


Ideal model

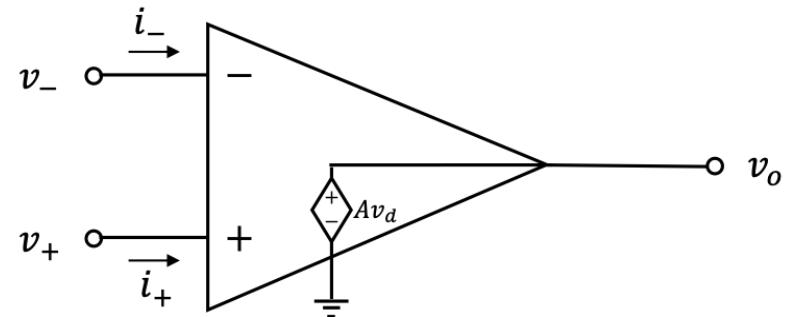


In op-amps, the input resistance, R_i , is very large, and the output resistance, R_o , is very small.

OpAmp models

Linear model

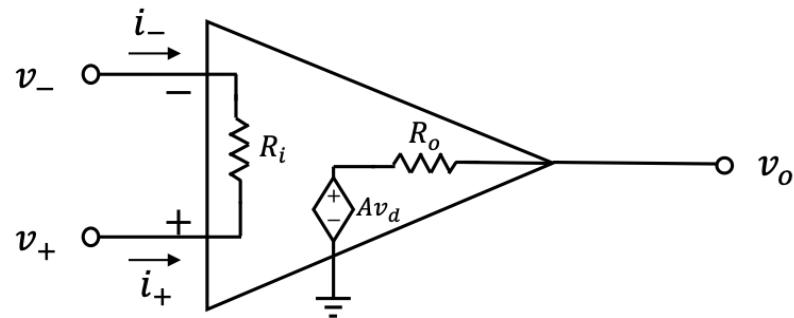

Ideal model

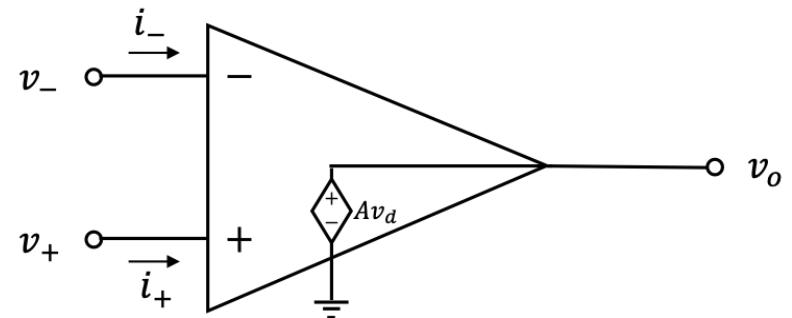


Because the input impedance of the op-amps is very large, the input current to the op-amp is very small.


$$i_- \approx i_+ \approx 0$$

OpAmp models

Linear model

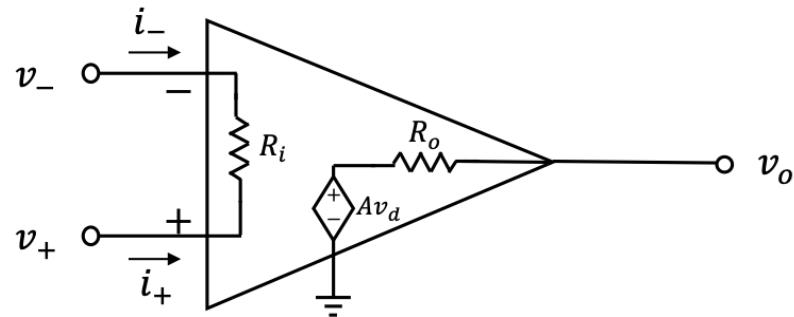

Ideal model

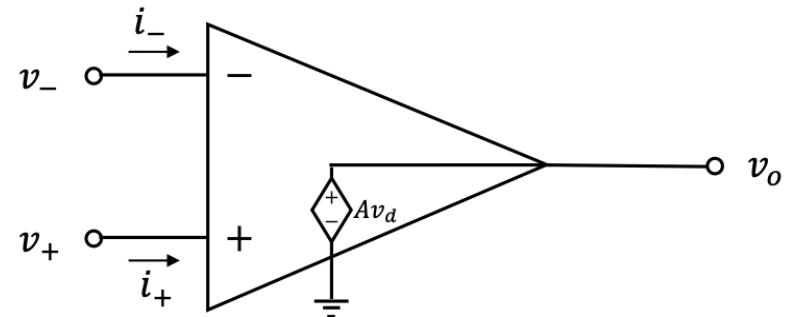


In the **ideal op-amp model**, $R_i = \infty$, $R_o = 0$, $i_- = i_+ = 0$

Output voltage and power supplies

The output voltage of an op-amp is limited by the power supplies used to power up the op-amp chip.



$$V_{S^-} < V_o < V_{S^+}$$

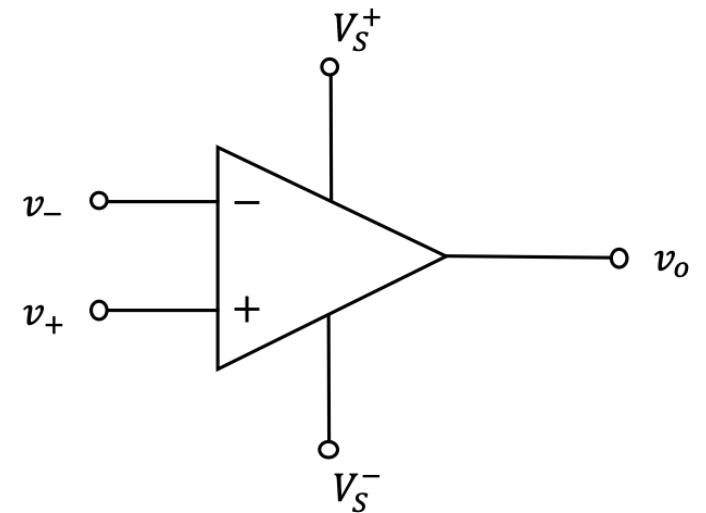

Open-loop operation of op-amps (no feedback)

$$A = 10^5$$
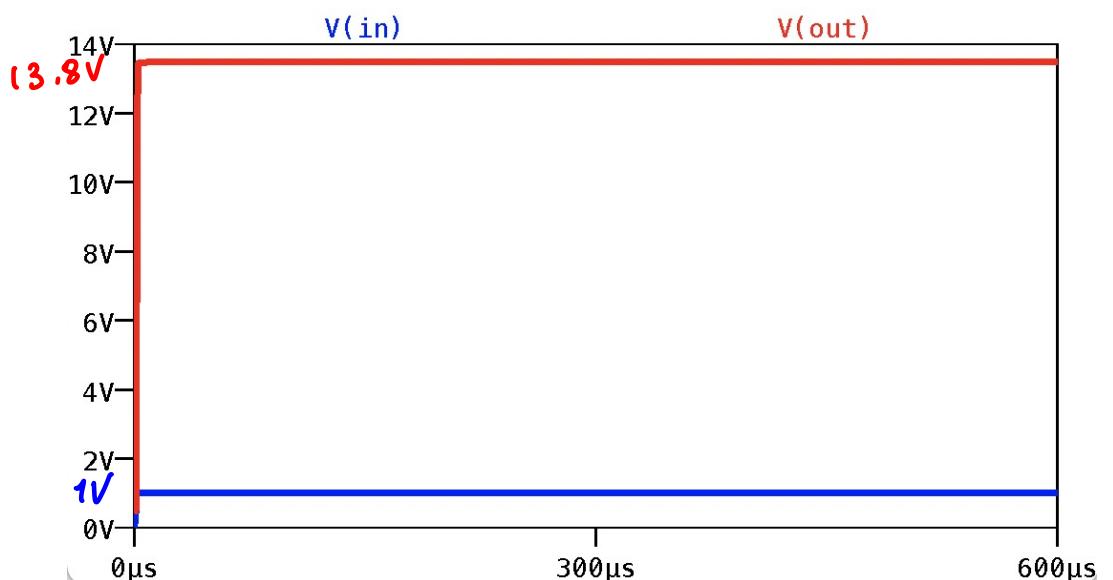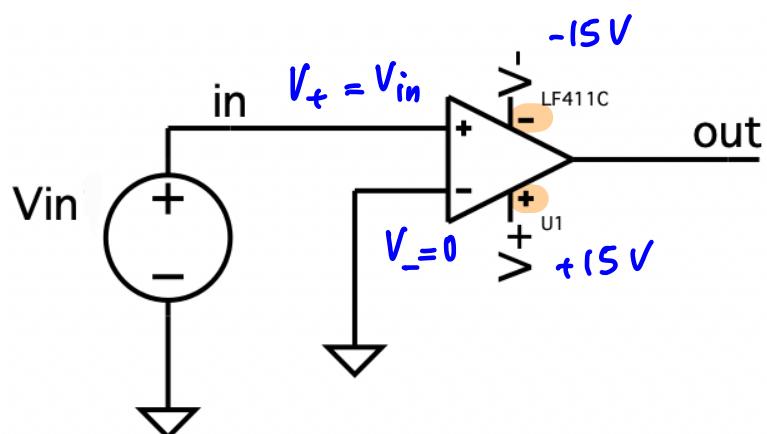
$$V_o = A (V_+ - V_-) = 10^5 (V_{in} - 0) = 10^5 \times V_{in}$$



$$V_{omax} = 13.8V, \text{ hence .}$$



$$V_o = 10^5 V_{in} \rightarrow V_{inmax} = \frac{V_{omax}}{10^5} = \frac{13.8V}{10^5} = 13.8 \times 10^{-5} = 138 \times 10^{-6} V = 138 \mu V$$

In open-loop configuration, op-amp cannot amplify input voltages greater than a few micro volts. It cannot be used as a voltage amplifier.

Feedback:

the concept, negative and positive feedback

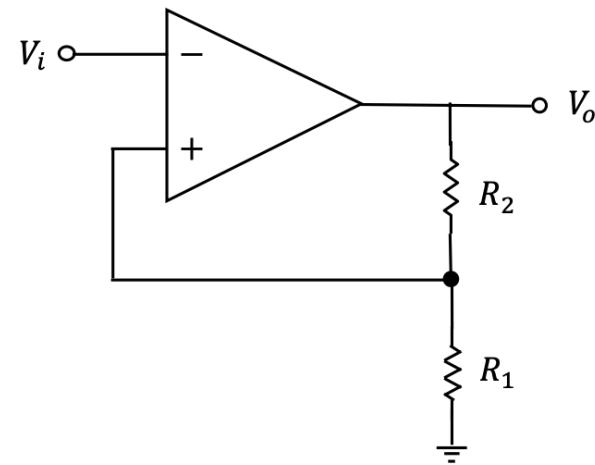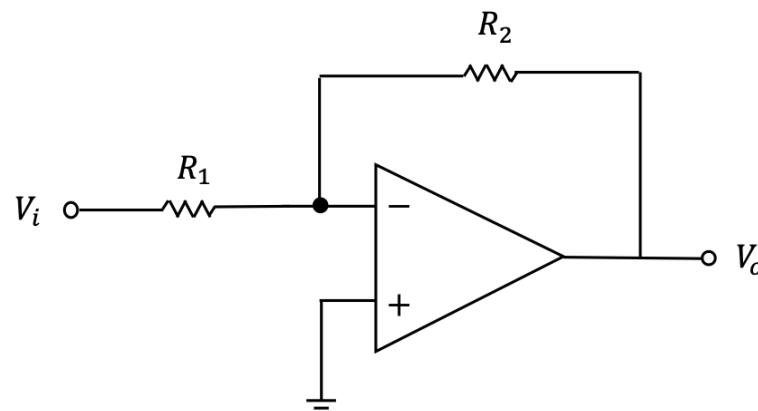- In circuits with feedback, a portion of the output signal is fed back to the circuit input.



- There are two types of feedback: Negative and Positive

Feedback:

the concept, negative and positive feedback

Negative feedback: In circuits with negative feedback, as the output increases, the input will decrease, and vice versa, such that the output signal would reach the desired stable level.


desired output : speed of 50 mph

if output ↗ 55 mph

input ↓ \Rightarrow output ↓ \rightarrow output : 50 mph

if output ↓ 45 mph

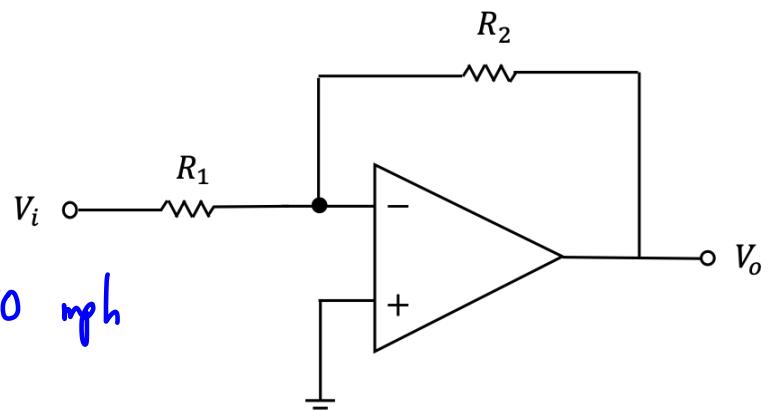input ↑ \Rightarrow output ↑ \rightarrow output : 50 mph



Feedback:


the concept, negative and positive feedback

Negative feedback: In circuits with negative feedback, as the output increases, the input will decrease, and vice versa, such that the output signal would reach the desired stable level.

$$V_o = A V_d$$

$$V_d = V_+ - V_-$$
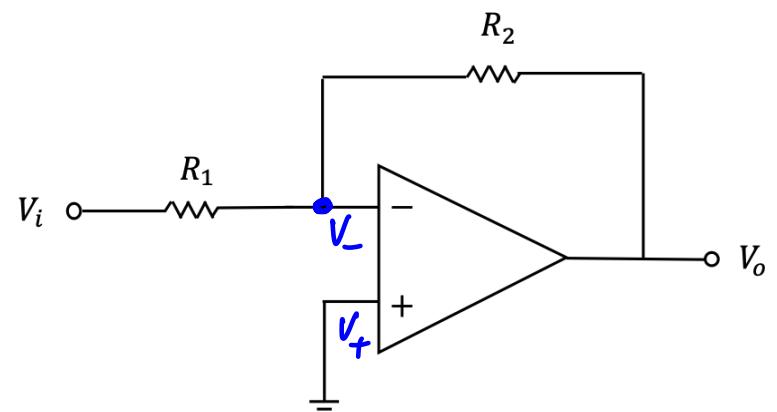
$$V_- = \frac{R_2}{R_1 + R_2} V_i + \frac{R_1}{R_1 + R_2} V_o$$




Feedback:

the concept, negative and positive feedback

Positive feedback: In circuits with positive feedback, when the output increases, the input will also increase, and vice versa. The output of circuits with positive feedback is always at its limits.

$$V_+ = \frac{R_1}{R_1 + R_2} V_o$$


$$V_o = A (V_+ - V_-) = A (V_+ - V_i)$$

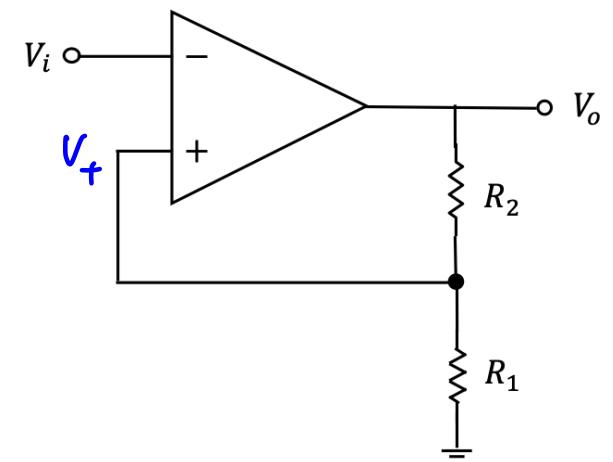

Solving op-amp circuits – example 1

Comprehensive solution

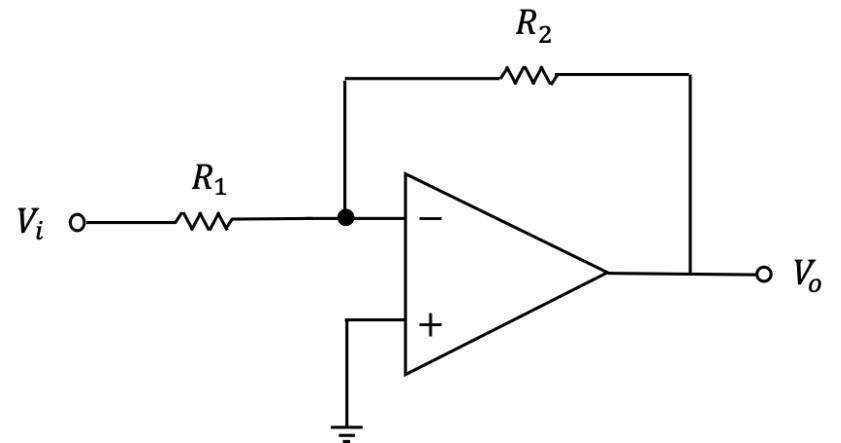Find $\frac{v_o}{v_i}$ in the following op-amp circuit assuming an ideal op-amp.



Solving op-amp circuits – example 1


Comprehensive solution

Find $\frac{v_o}{v_i}$ in the following op-amp circuit assuming an ideal op-amp.

assume an ideal op-amp: $i_+ = i_- = 0$

$$V_+ = 0$$
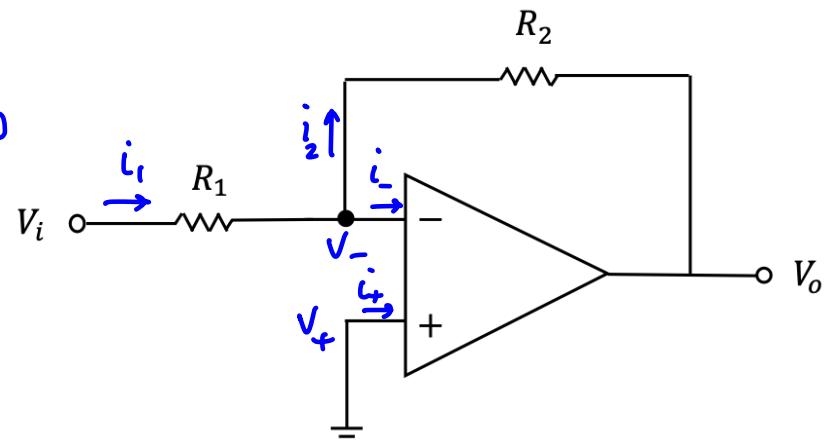
$$V_o = A(V_+ - V_-) \rightarrow V_o = -AV_-$$



KCL at the inverting input node:

$$i_1 = i_2 + i_- \quad , \quad i_- = 0 \quad \rightarrow \quad i_1 = i_2$$

$$i_1 = \frac{V_i - V_-}{R_1} \quad , \quad i_2 = \frac{V_- - V_o}{R_2}$$

Solving op-amp circuits – example 1

Comprehensive solution


$$i_1 = \frac{V_i - V_-}{R_1} , \quad i_2 = \frac{V_- - V_o}{R_2}$$

$$i_1 = i_2 \rightarrow \frac{V_i - V_-}{R_1} = \frac{V_- - V_o}{R_2}$$

$$\left(\frac{-1}{R_1} - \frac{1}{R_2} \right) V_- = -\frac{1}{R_1} V_i - \frac{1}{R_2} V_o$$

$$-\left(\frac{R_1 + R_2}{R_1 R_2} \right) V_- = -\frac{1}{R_1} V_i - \frac{1}{R_2} V_o$$

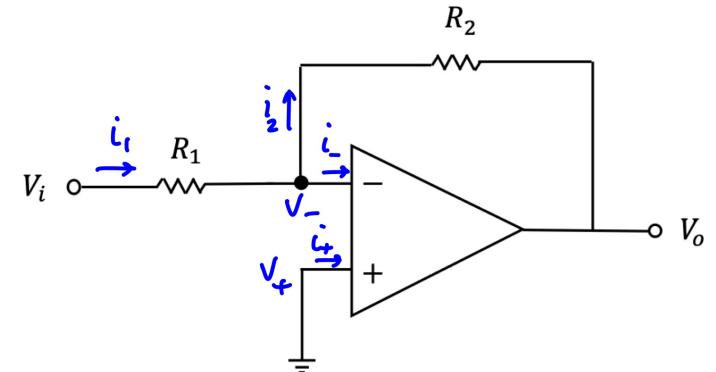
$$\left(\frac{R_1 + R_2}{R_1 R_2} \right) V_- = \frac{1}{R_1} V_i + \frac{1}{R_2} V_o$$



Solving op-amp circuits – example 1

Comprehensive solution
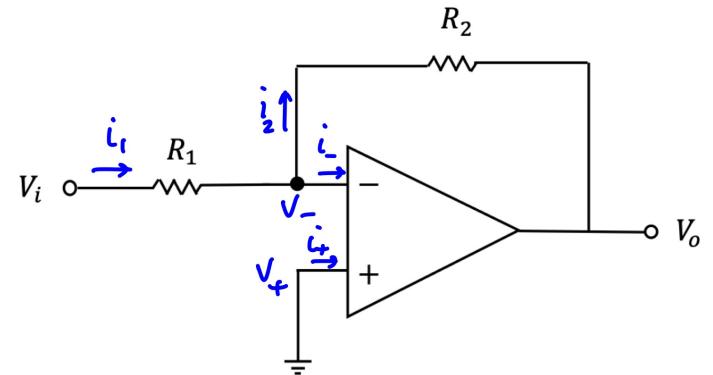
$$\left(\frac{R_1 + R_2}{R_1 R_2} \right) V_- = \frac{1}{R_1} V_i + \frac{1}{R_2} V_o$$



$$V_- = \frac{R_1 R_2}{R_1 + R_2} \left(\frac{1}{R_1} V_i + \frac{1}{R_2} V_o \right)$$


$$V_- = \left(\frac{R_2}{R_1 + R_2} \right) V_i + \left(\frac{R_1}{R_1 + R_2} \right) V_o$$

Solving op-amp circuits – example 1

Comprehensive solution

$$V_- = \left(\frac{R_2}{R_1 + R_2} \right) V_i + \left(\frac{R_1}{R_1 + R_2} \right) V_o$$

$$V_o = -AV_-$$

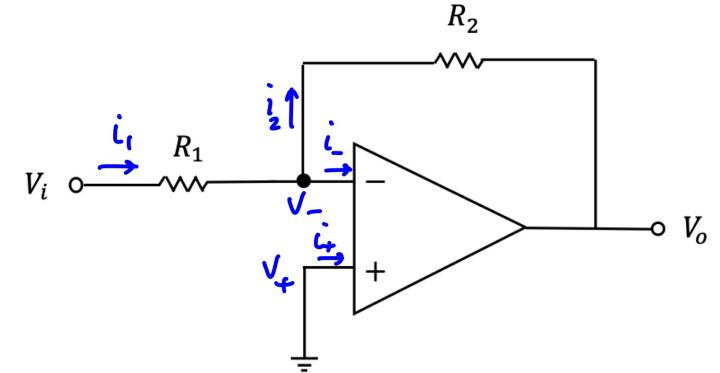

$$V_o = -A \left[\left(\frac{R_2}{R_1 + R_2} \right) V_i + \left(\frac{R_1}{R_1 + R_2} \right) V_o \right]$$

$$V_o + \left(\frac{A R_1}{R_1 + R_2} \right) V_o = -\left(A \frac{R_2}{R_1 + R_2} \right) V_i$$

$$\left[1 + \left(\frac{A R_1}{R_1 + R_2} \right) \right] V_o = -\left(A \frac{R_2}{R_1 + R_2} \right) V_i$$

Solving op-amp circuits – example 1


Comprehensive solution

$$\left[1 + \left(A \frac{R_1}{R_1 + R_2} \right) \right] V_o = - \left(A \frac{R_2}{R_1 + R_2} \right) V_i$$

define $B = \frac{R_1}{R_1 + R_2}$

$$\rightarrow \frac{R_2}{R_1 + R_2} = \frac{R_2}{R_1} \times \frac{R_1}{R_1 + R_2} = \frac{R_2}{R_1} \times B$$
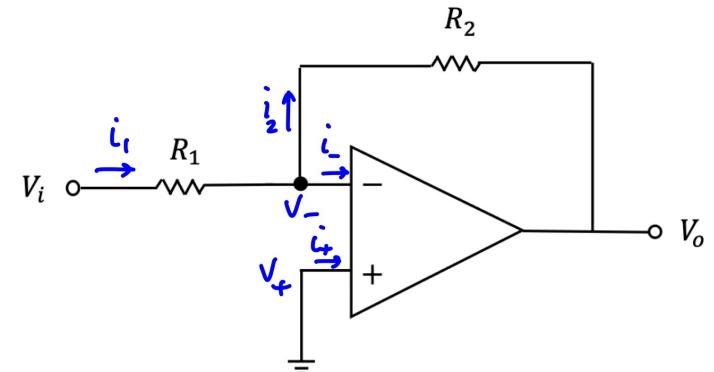
$$(1 + AB) V_o = - \frac{R_2}{R_1} AB V_i$$



Solving op-amp circuits – example 1


Comprehensive solution

$$B = \frac{R_1}{R_1 + R_2}$$

$$\frac{1}{AB} \times (1 + AB) V_o = \frac{1}{AB} \times -\frac{R_2}{R_1} AB V_i$$

$$\left(\frac{1}{AB} + 1 \right) V_o = -\frac{R_2}{R_1} V_i$$
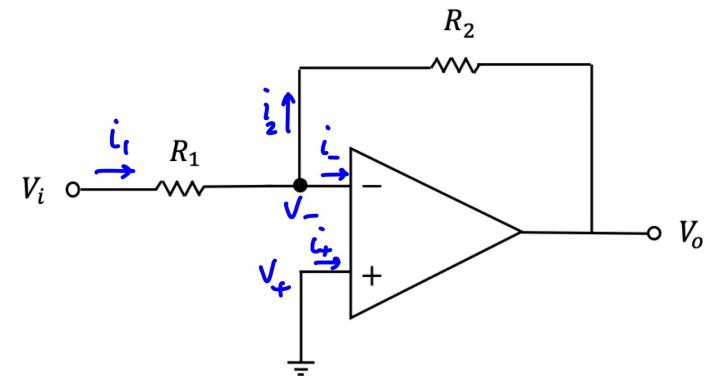
$$\frac{V_o}{V_i} = -\frac{R_2}{R_1} \cdot \frac{1}{1 + \frac{1}{AB}}$$




Solving op-amp circuits – example 1

Comprehensive solution

$$\frac{V_o}{V_i} = -\frac{R_2}{R_1} \cdot \frac{1}{1 + \frac{1}{AB}}$$

$$B = \frac{R_1}{R_1 + R_2}$$

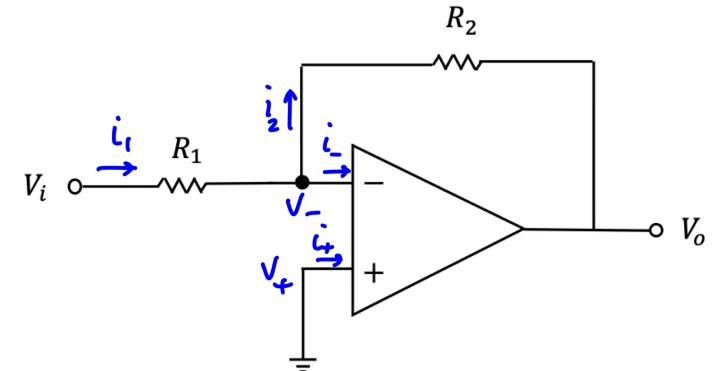

Example numbers : $R_1 = 1 \text{ k}\Omega$, $R_2 = 9 \text{ k}\Omega$, $A = 10^5$

$$B = \frac{1 \text{ k}\Omega}{1 \text{ k}\Omega + 9 \text{ k}\Omega} = 0.1$$


$$\frac{V_o}{V_i} = -\frac{9 \text{ k}\Omega}{1 \text{ k}\Omega} \times \frac{1}{1 + \frac{1}{10^5 \times 0.1}} = -9 \times \frac{1}{1 + 10^{-4}} \underset{\approx 1}{\underbrace{\approx}} -9 \frac{V}{V}$$

virtual short principle in op-amp circuits with negative feedback

$v_o \approx \text{a finite value}$

$$v_o = A v_d \rightarrow v_d = \frac{v_o}{A} \approx 0$$

$$\Rightarrow v_+ \approx v_-$$

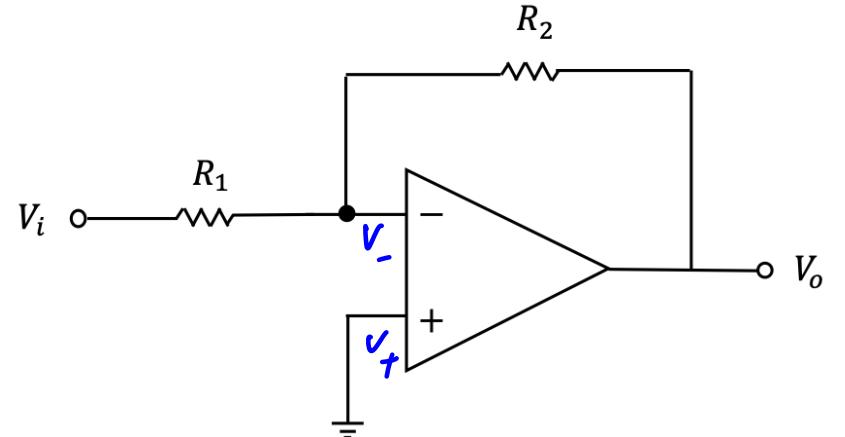


In op-amps with negative feedback and large open-loop gain, the op-amp adjusts its output voltage such that $v_d \approx 0$.

Solving op-amp circuits – example 1

Approximate solution

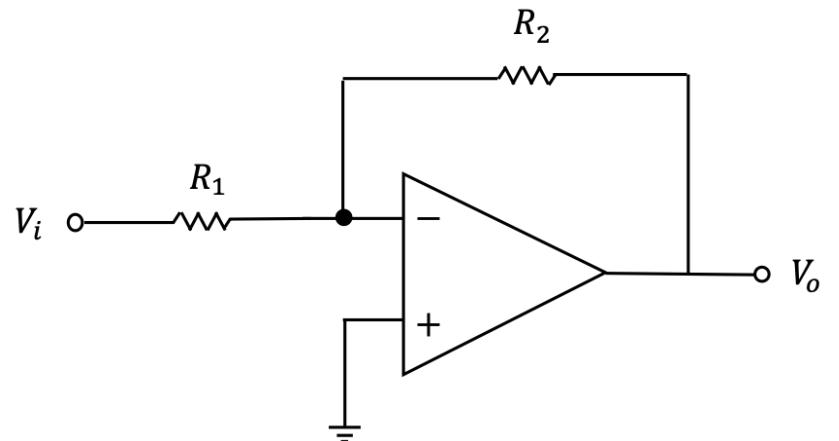Find $\frac{v_o}{v_i}$ in the following op-amp circuit assuming an ideal op-amp.



Solving op-amp circuits – example 1

Approximate solution

Find $\frac{v_o}{v_i}$ in the following op-amp circuit assuming an ideal op-amp.


$\left\{ \begin{array}{l} \text{ideal op-amp: } i_+ = i_- = 0 \\ \text{There is negative feedback: } v_+ \approx v_- \end{array} \right.$

$$v_+ = 0 \rightarrow v_- = 0$$

KCL at the inverting terminal: $i_1 = i_2 + i_- = i_2$

$$i_1 = i_2 \Rightarrow \frac{v_i - v_-}{R_1} = \frac{v_- - v_o}{R_2} ;$$

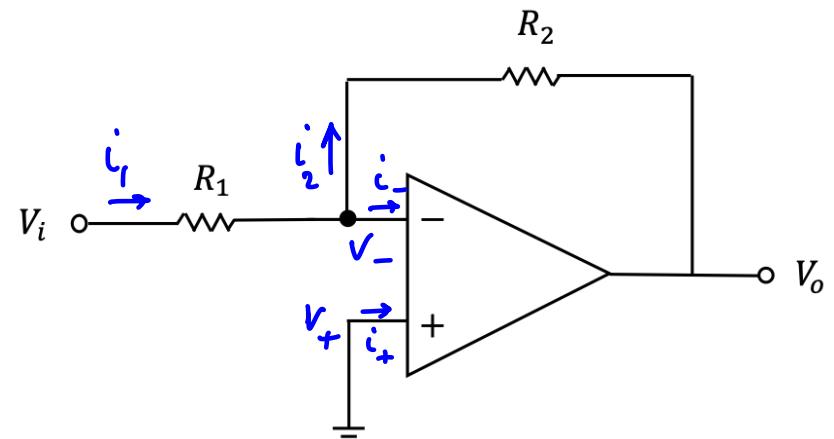
$$v_- = 0 \rightarrow \frac{v_i - 0}{R_1} = \frac{0 - v_o}{R_2} \Rightarrow \frac{v_o}{v_i} = \frac{-R_2}{R_1}$$



Lecture 2 reading quiz.

In the following amplifier circuit, the input signal is $v_i(t) = 1.5 \sin(2\pi \times 10^3 t)$ V

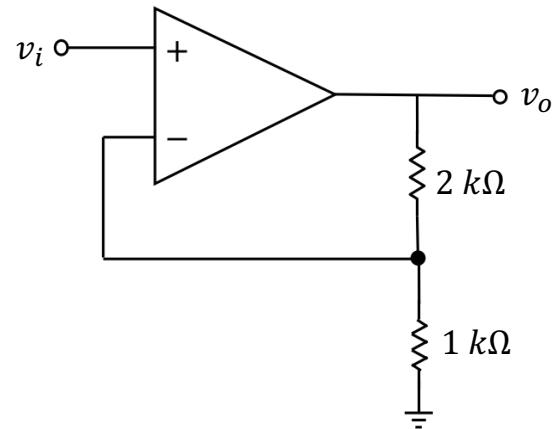
Which one of the options could be the output signal, $v_o(t)$?



Discussion question 1. (weighted summer)

Design the following op-amp circuit to achieve the weighted sum of input 1 and input 2 at the output. It is required that $v_o = -(v_1 + 5v_2)$.

Assume an ideal op-amp.

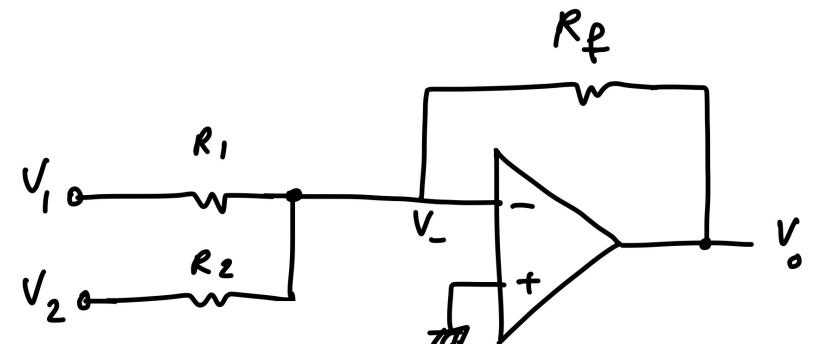


Discussion question 2. (non-inverting summer)

Using the structure of a non-inverting amplifier, design an op-amp circuit to achieve $v_o = 6v_1 + 4v_2$.

Assume an ideal op-amp.

Discussion question 3.

What is v_o/v_i in this op-amp circuit? Assume an ideal op-amp.

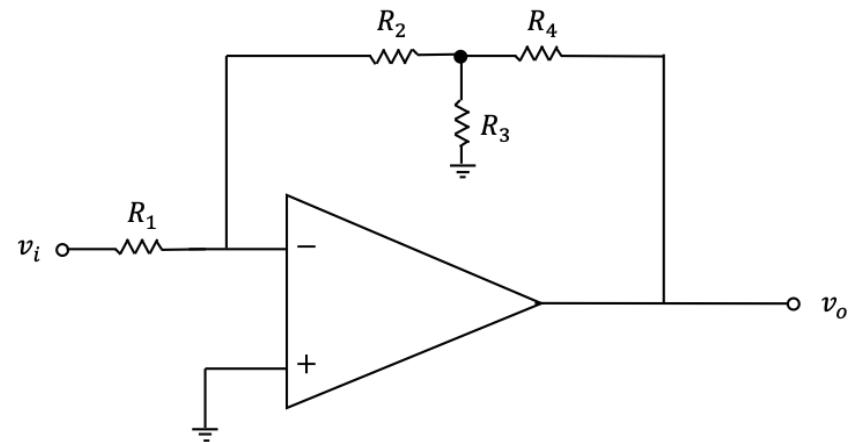

ECE 65: Components & Circuits Lab

Lecture 3

Operational Amplifier limitations


Reference notes: sections 7.5

Sedra & Smith (7th Ed): sections 2-2.3

Saharnaz Baghdadchi

Course map

7. Operational amplifiers

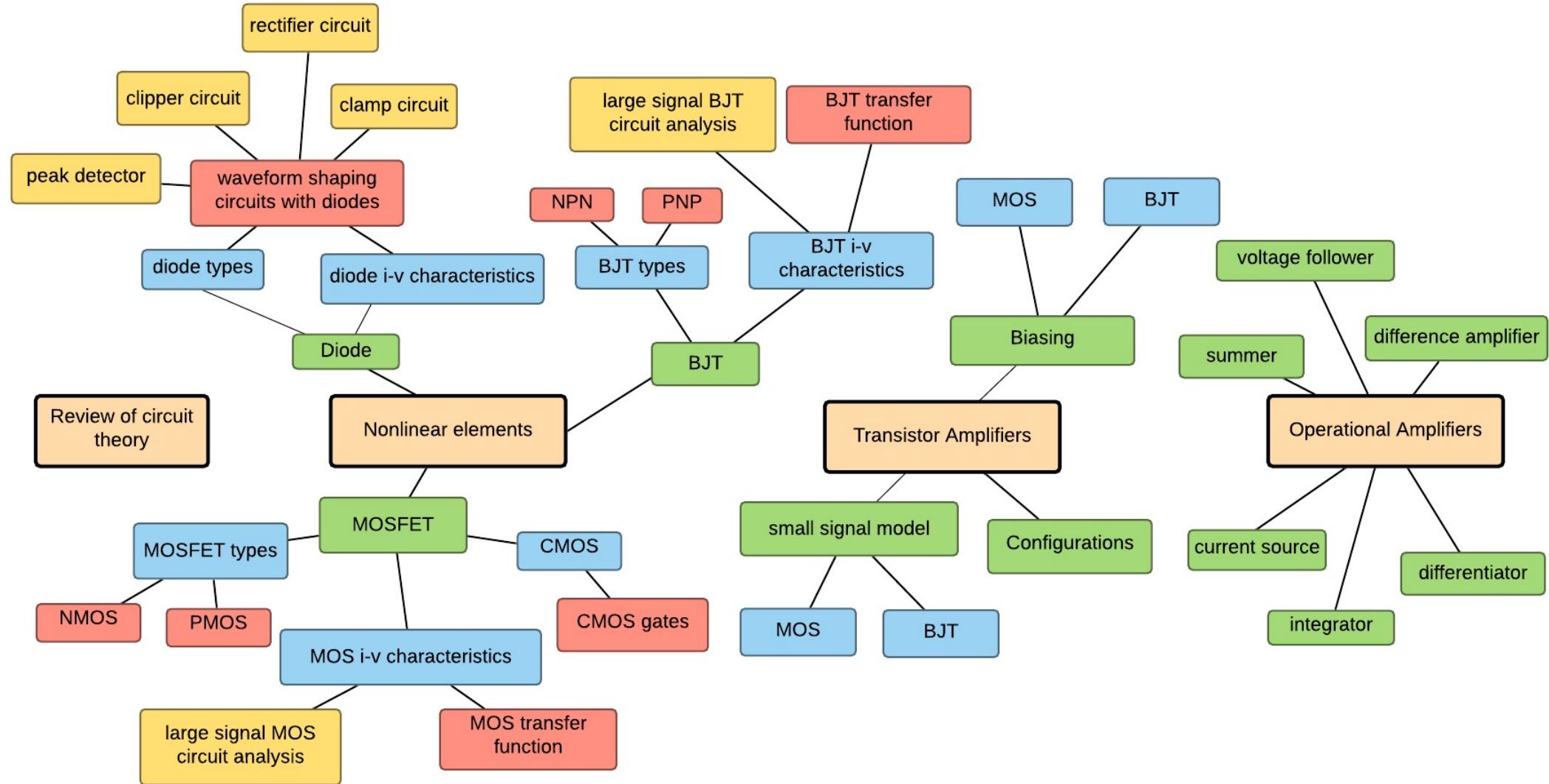

Voltage-supply limit or Saturation

As we saw before, the maximum output voltage of op-amps is limited by the positive and negative voltage sources (V_{S^+} and V_{S^-}) used to power up the op-amp chip.

$$V_{S^-} < V_o < V_{S^+}$$

$$V_{sat^-} \leq V_o \leq V_{sat^+}$$


$$V_{sat^+} = 14\text{ V}$$

$$V_{sat^-} = -14\text{ V}$$

Assume an ideal op-amp $\Rightarrow i_+ = i_- = 0$

Because of negative feedback : $v_+ = v_-$
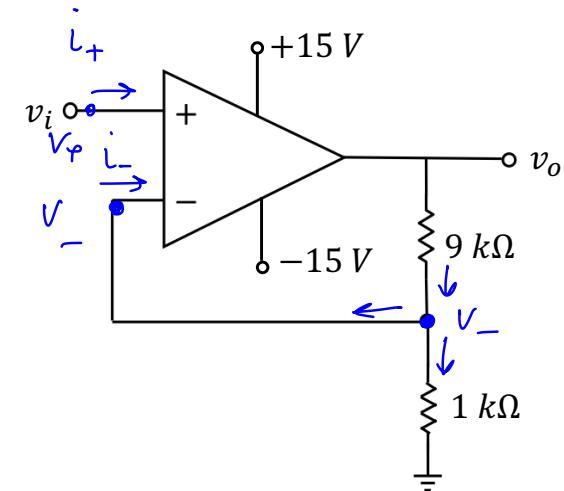
$$\text{here, } v_+ = v_i \quad , \quad \frac{v_-}{1\text{ k}\Omega} = \frac{V_o - V_-}{9\text{ k}\Omega} \quad \Rightarrow \quad V_o = 10 \cdot V_- \quad \Rightarrow \quad \boxed{V_o = 10 \cdot v_i}$$



Voltage-supply limit or Saturation

As we saw before, the maximum output voltage of op-amps is limited by the positive and negative voltage sources (V_{S+} and V_{S-}) used to power up the op-amp chip.


$$V_{S-} < V_o < V_{S+}$$

$$V_{Sat-} \leq V_o \leq V_{Sat+}$$

$$V_{Sat+} = 14\text{ V}$$



$$V_{Sat-} = -14\text{ V}$$
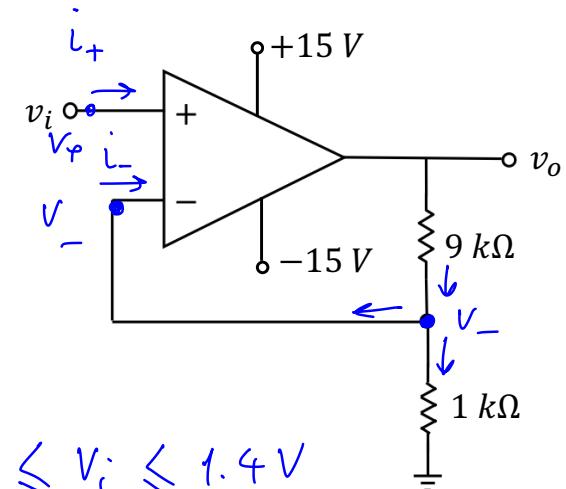
$$V_o = 10 \text{ V} \quad \Rightarrow \quad \frac{-14\text{ V}}{10} \leq V_i \leq \frac{14}{10} \text{ V} \quad \Rightarrow \quad -1.4\text{ V} \leq V_i \leq 1.4\text{ V}$$





Voltage-supply limit or Saturation

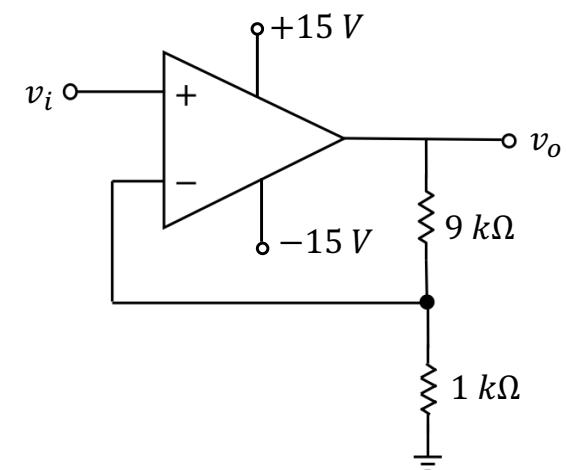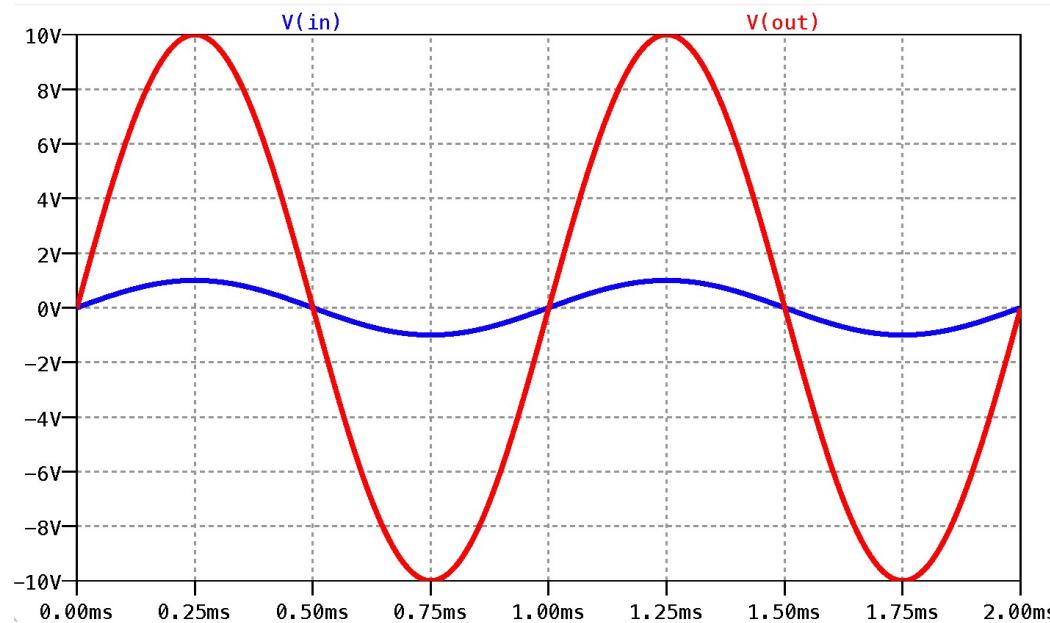As we saw before, the maximum output voltage of op-amps is limited by the positive and negative voltage sources (V_{S+} and V_{S-}) used to power up the op-amp chip.



Voltage-supply limit or Saturation

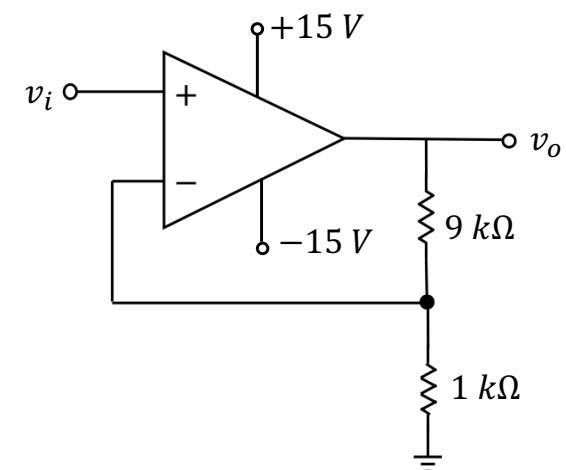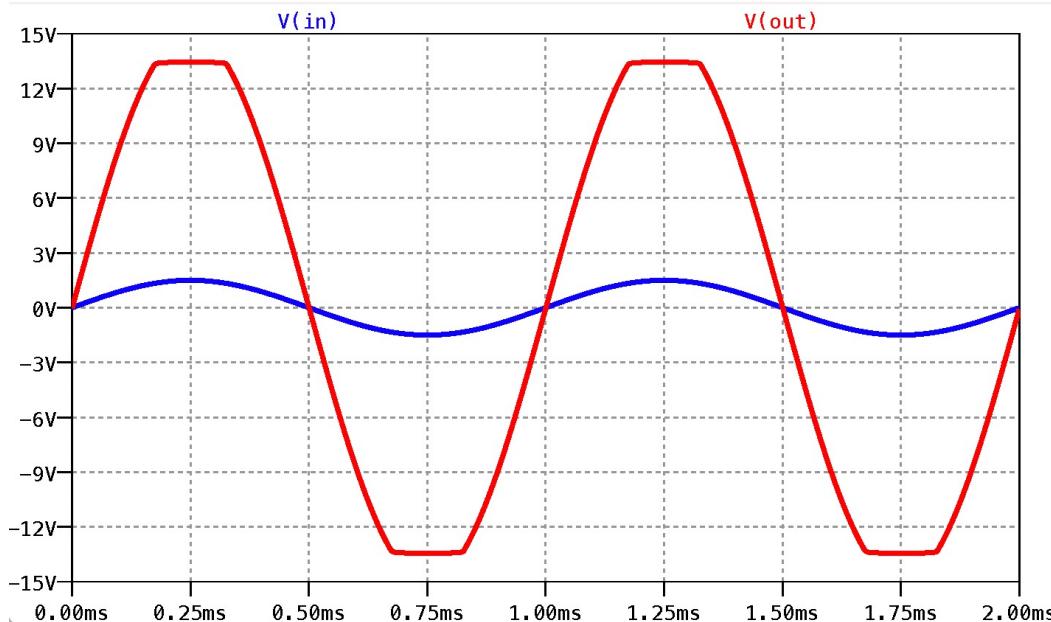
As we saw before, the maximum output voltage of op-amps is limited by the positive and negative voltage sources (V_{S+} and V_{S-}) used to power up the op-amp chip.



Maximum Output Current



The output current of an op-amp is limited to a specified maximum value.

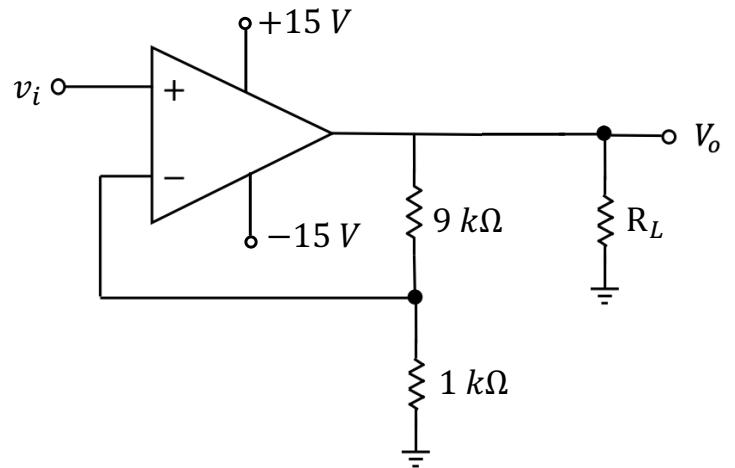For example, in the 741 op-amp, the maximum output current is $\pm 20\text{mA}$.



Maximum Output Current

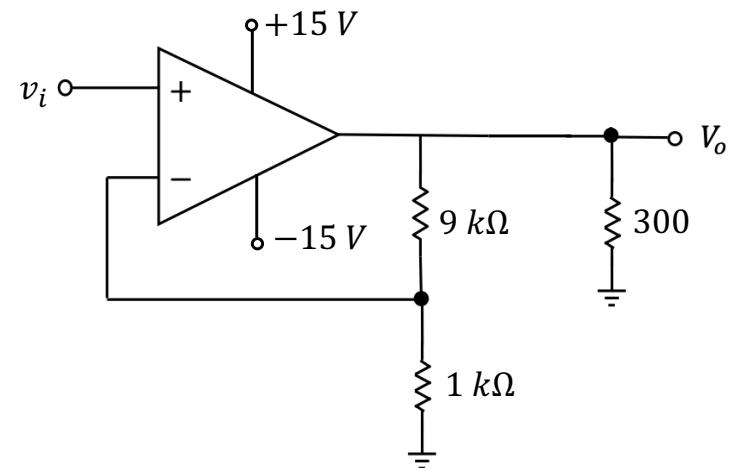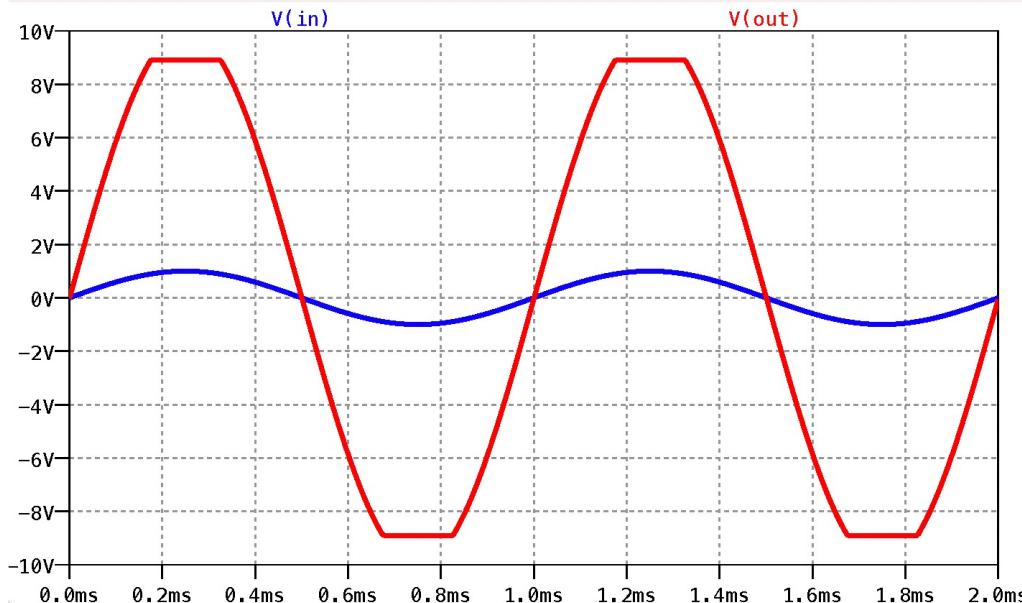If the circuit requires a current larger than the maximum output current, in either direction, the output voltage will saturate at a level corresponding to the maximum allowed output current.



Maximum Output Current - Example

The following op-amp circuit is fed with a low-frequency sinusoidal signal with peak amplitude of 1 V. The maximum output current is $\pm 20mA$. If $R_L = 1 k\Omega$, specify and sketch the output voltage.


$$\text{assume an ideal op-amp: } i_+ = i_- = 0 \Rightarrow i_1 = i_2$$

$$\text{kCL: } i_o = i_1 + i_L$$

$$i_o = \frac{V_o}{9k\Omega + 1k\Omega} + \frac{V_o}{R_L}$$

$$i_o = \frac{V_o}{10k\Omega} + \frac{V_o}{1k\Omega} = V_o \left(\frac{1}{10k\Omega} + \frac{1}{1k\Omega} \right)$$

$$= V_o \times 1.1$$

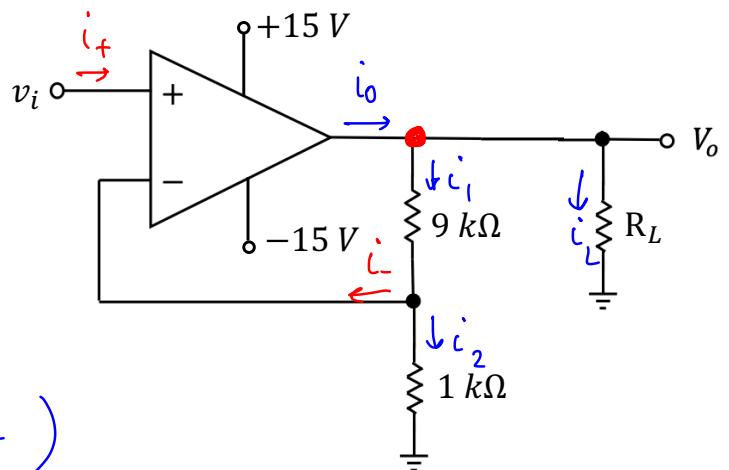

Maximum Output Current - Example

The following op-amp circuit is fed with a low-frequency sinusoidal signal with peak amplitude of 1 V. The maximum output current is $\pm 20mA$. If $R_L = 1 k\Omega$, specify and sketch the output voltage.

$$\text{assume an ideal op-amp: } i_+ = i_- = 0 \Rightarrow i_1 = i_2$$



$$i_o = V_o \times 1.1$$

Assume linear amplification:

$$\frac{V_o}{V_i} = 10 \text{ V/V} \Rightarrow \text{if } V_{i_{\max}} = 1V \Rightarrow V_{o_{\max}} = 10 \text{ V}$$


$$\Rightarrow i_{o_{\max}} = 10 \times 1.1 = 11 \text{ mA} < +20 \text{ mA}$$

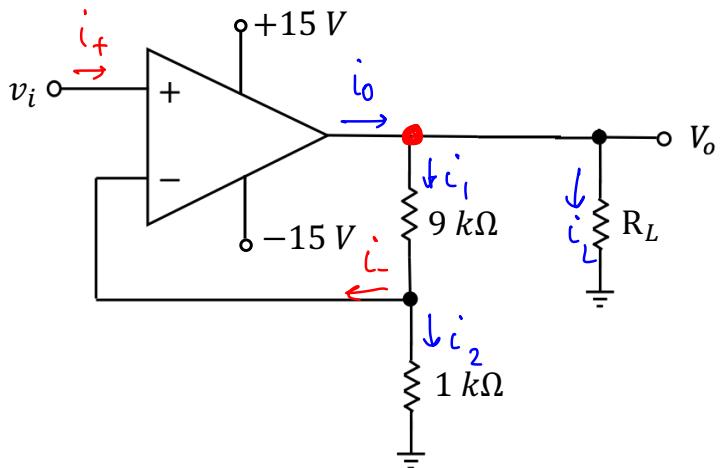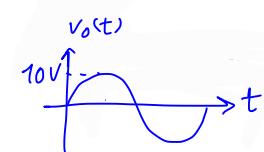\Rightarrow We are not limited by the maximum output current $\Rightarrow V_{o_{\max}} = 10 \text{ V}$




Lecture 3 reading quiz.

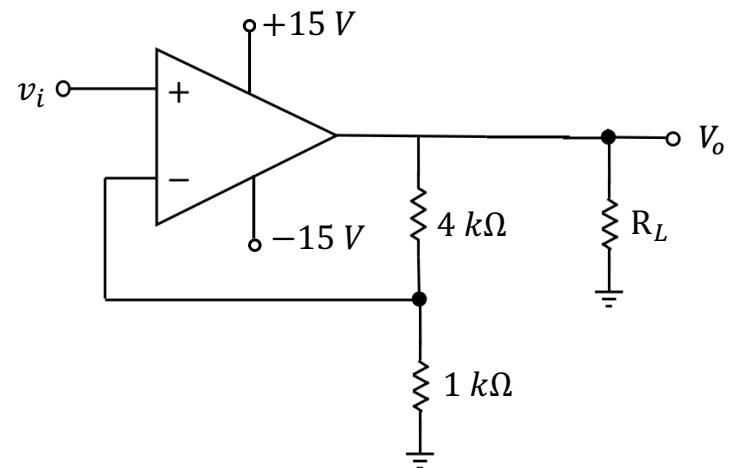The following op-amp circuit is fed with a low-frequency sinusoidal signal with the peak amplitude of V_P . The output saturation voltage is $\pm 13 V$, and the maximum output current is $\pm 20 \text{ mA}$. If $R_L = 0.5 \text{ k}\Omega$, find the maximum value of V_P for which an undistorted sinusoidal signal is obtained at the output?



Discussion question 1.

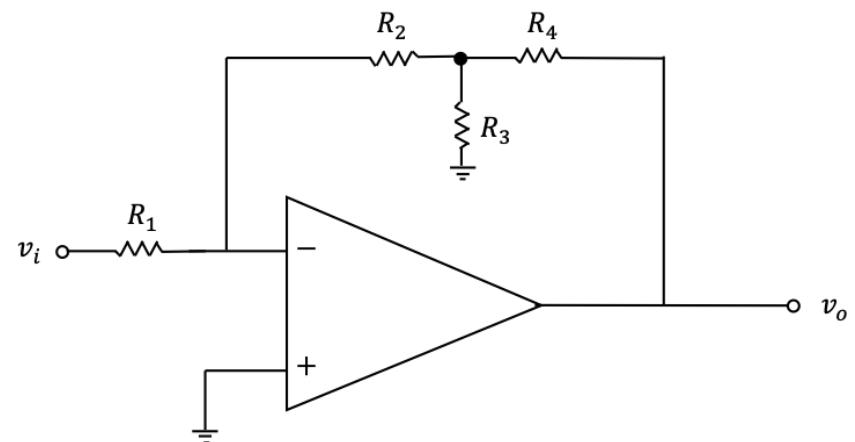What is v_o/v_i in this op-amp circuit? Assume an ideal op-amp.




Discussion question 2.

The following circuit uses a $10\text{ k}\Omega$ potentiometer to obtain an adjustable gain amplifier.

- Derive an expression for the gain as a function of the potentiometer setting x .
- What is the range of the gain obtained?
- Show how to add a fixed resistor so that the gain range can be 1 to 11 V/V. What is the value of that resistor?


Assume an ideal op-amp.

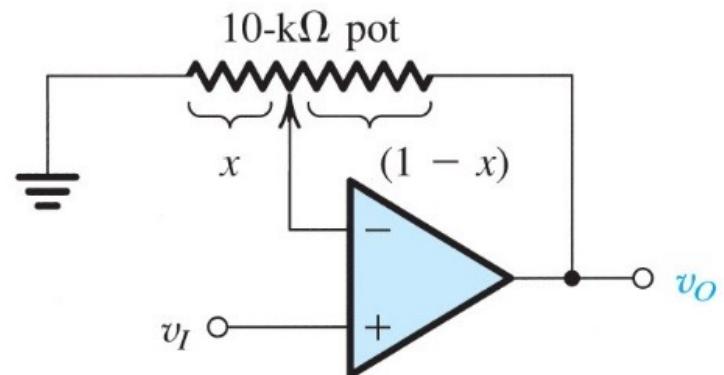

Discussion question 2.

- a) Derive an expression for the gain as a function of the potentiometer setting x .


Assume an ideal op-amp.

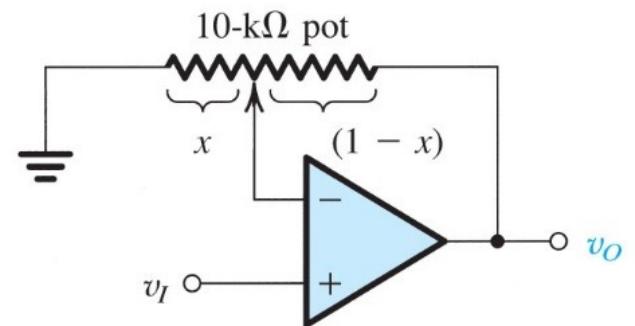

Discussion question 2.

a) What is the range of the gain obtained?


Assume an ideal op-amp.

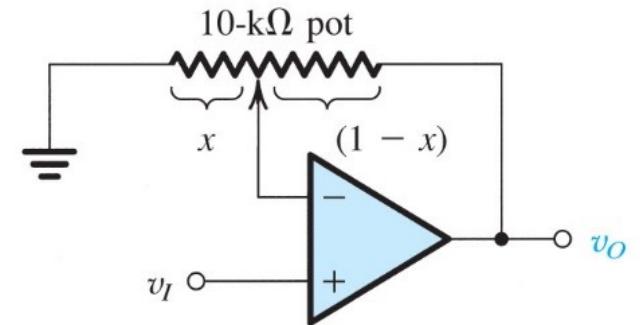

Discussion question 2.

- a) Show how to add a fixed resistor so that the gain range can be 1 to 11 V/V. What is the value of that resistor?

Assume an ideal op-amp.

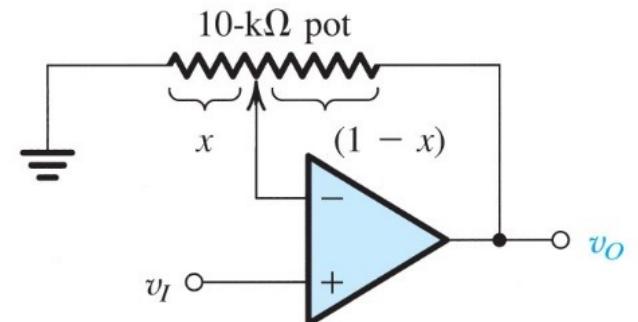

ECE 65: Components & Circuits Lab

Lecture 4

Diode introduction and review of circuit theory


Reference notes: sections 2.1-2.8

Sedra & Smith (7th Ed): sections 4.3-4.4


Saharnaz Baghdadchi

Course map

2. Diodes

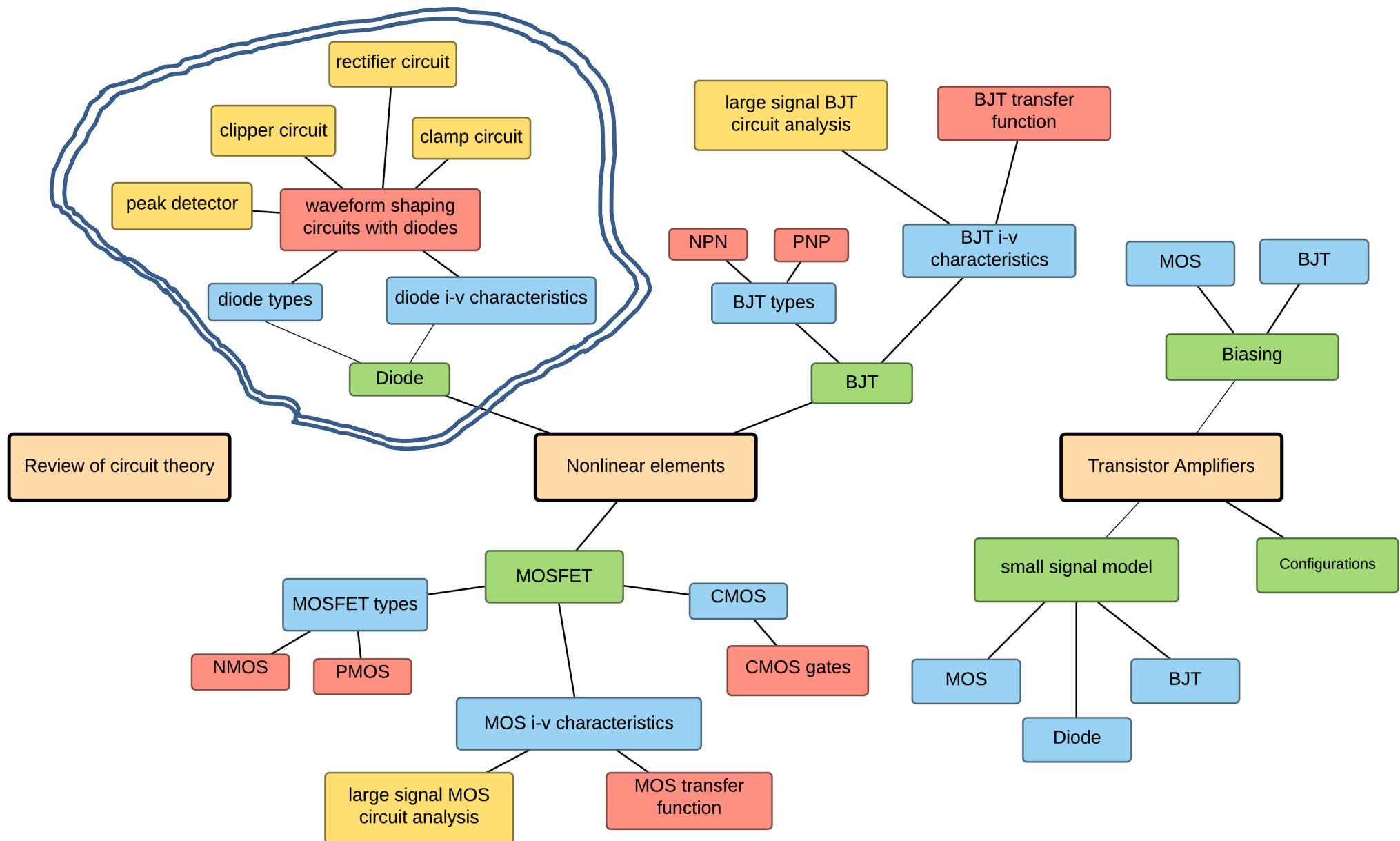

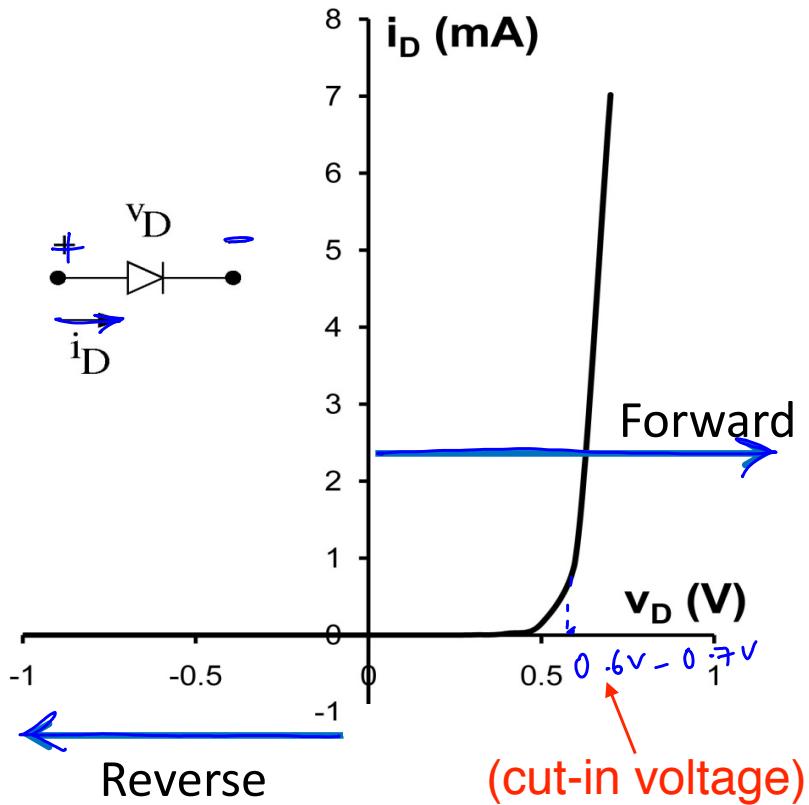The iv characteristics of a silicon junction diode




When the diode conducts,
 $i_D \gg I_S$ and:

$$i_D = I_S e^{v_D/V_T}$$


I_S : Saturation Current
(10^{-9} to 10^{-18} A)

V_T : Thermal voltage = 26mV at room temp.

Diode piecewise-linear model:

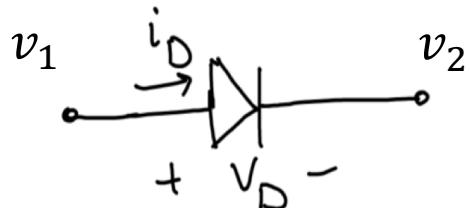

$$v_D = v_1 - v_2$$

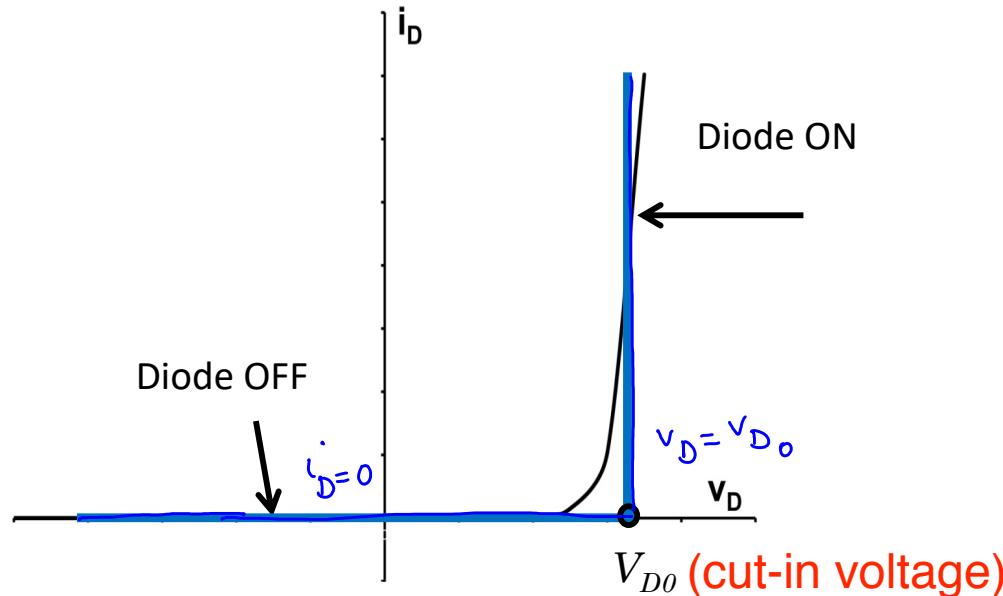


Assume Si Diode with $V_{D0} = 0.7V$

- { ① When $v_1 - v_2 < 0$ → diode is reverse-biased $\Rightarrow i_D = 0$
- ② When $0 < v_1 - v_2 < 0.7$ → diode is forward-biased, but it's not ON, yet $\Rightarrow i_D = 0$

- { ③ When $v_1 - v_2 = 0.7$ → diode is forward biased and it's ON $\Rightarrow i_D > 0$ & $v_D = V_{D0} = 0.7$


Diode piecewise-linear model:

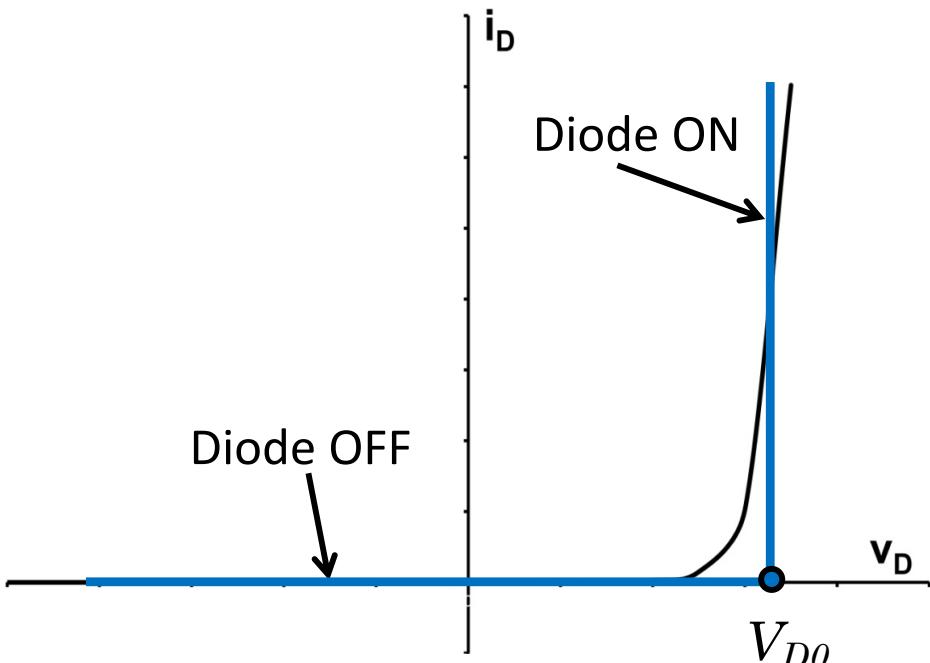


Constant Voltage drop Model:

Circuit Models:

ON:

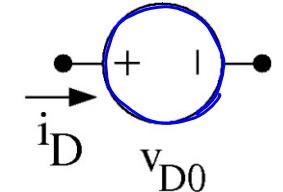

OFF:

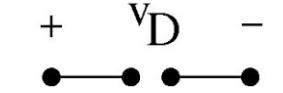


{ Diode ON: $v_D = V_{D0}$ and $i_D \geq 0$

Diode OFF: $i_D = 0$ and $v_D < V_{D0}$


(cut-in voltage) $V_{D0} = 0.6 - 0.7 \text{ V}$ for Si

Diode circuit models:

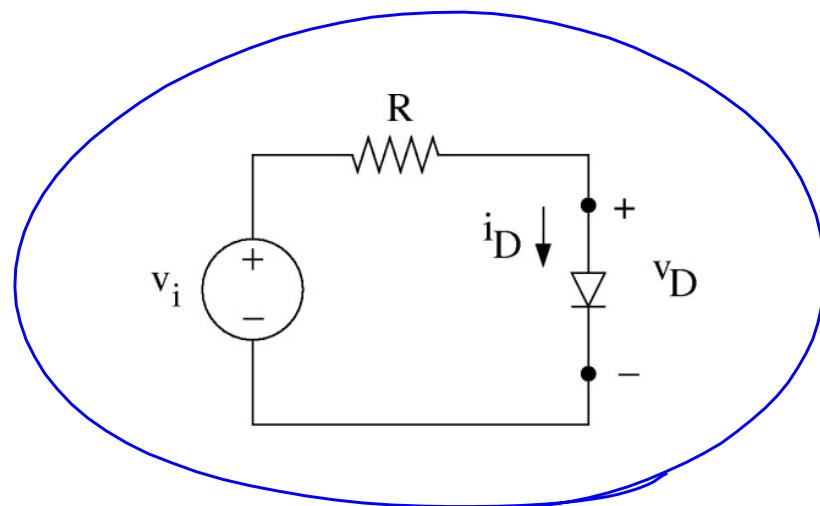


When Diode is OFF:

$$i_D = 0 \text{ and } v_D < V_{D0}$$

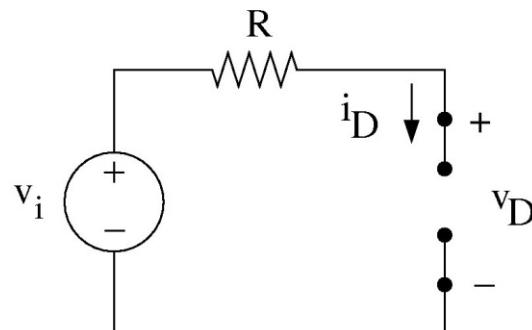

When Diode is ON:

$$i_D \geq 0 \text{ and } v_D = V_{D0}$$

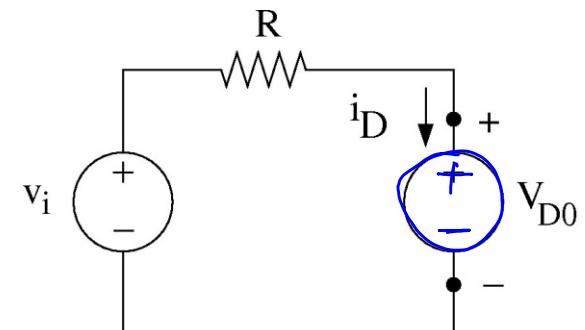


Example 1:

Find i_D and v_D for $R = 1k$, $V_i = 5 V$, and Si Diode ($V_{D0} = 0.7 V$).

Solution with diode circuit models:


Assume diode is off

$$i_D = 0, v_D < V_{D0}$$

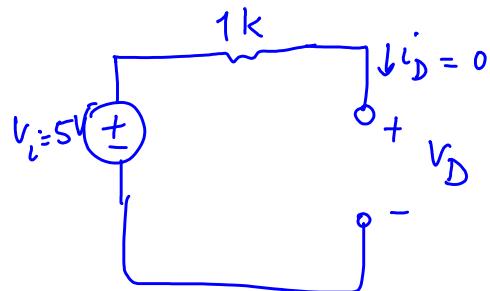

$$v_i = 1k \times i_D + v_D$$


$$v_i = v_D = 5V > 0.7$$

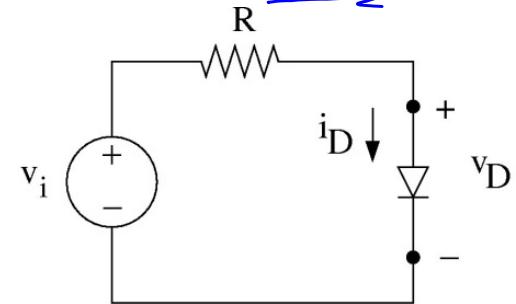

Assumption was wrong.

Assume diode is ON

$$i_D \geq 0, v_D = V_{D0}$$

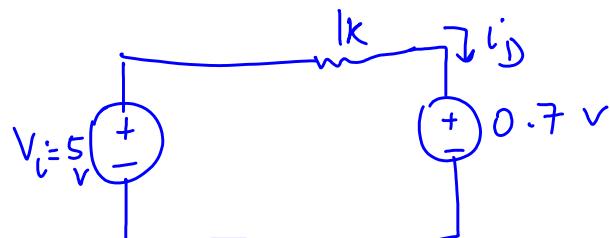

$$v_i = 1k \times i_D + 0.7V$$

$$\rightarrow i_D = \frac{5 - 0.7}{1k} = 4.3 \text{ mA} > 0$$

The diode is ON.

Example 2 :


For what range of V_i the diode will be ON and for what range it will be OFF?

Find i_D and v_D for each range.

$$\text{When diode is ON : } i_D \geq 0, V_D = V_{D_0}$$

$$V_i = R i_D + V_D = R i_D + 0.7$$
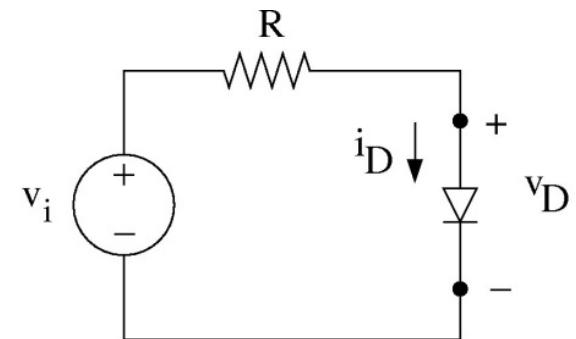
$$i_D = \frac{V_i - 0.7}{R} \geq 0 \rightarrow V_i \geq 0.7 \text{ V}$$



For $V_i \geq 0.7 \text{ V}$, diode is ON, $V_D = V_{D_0}$, $i_D \geq 0$

$$\text{when the diode is off : } i_D = 0, V_D < V_{D_0}$$


$$V_i = R i_D + V_D \rightarrow V_i = V_D, V_D < V_{D_0} \rightarrow V_i < V_{D_0}$$

For $V_i < V_{D_0}$, diode is off, $i_D = 0, V_D < V_{D_0}$

Lecture 4 reading quiz


In this diode circuit, what is the value of V_R for $V_i = 5 \text{ V}$ and $V_i = -5 \text{ V}$?

Assume $V_{D0} = 0.7 \text{ V}$

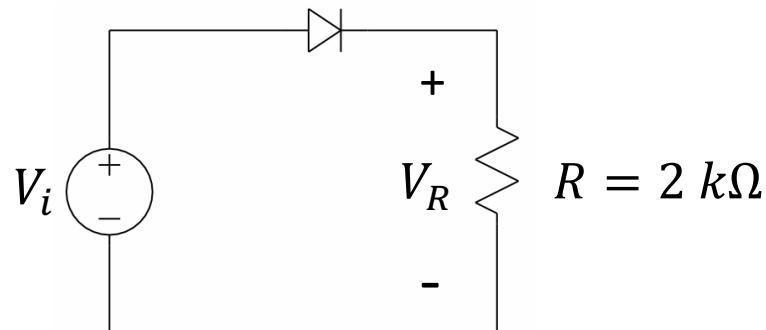

Clicker question 1.

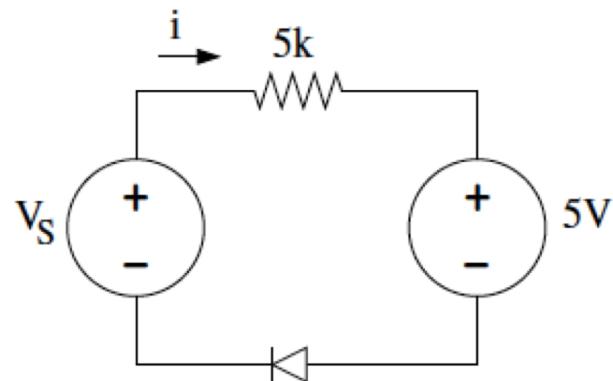
For what range of v_s , will the diode in the following circuit be ON?
(Si diodes with $V_{D0} = 0.7 V$)



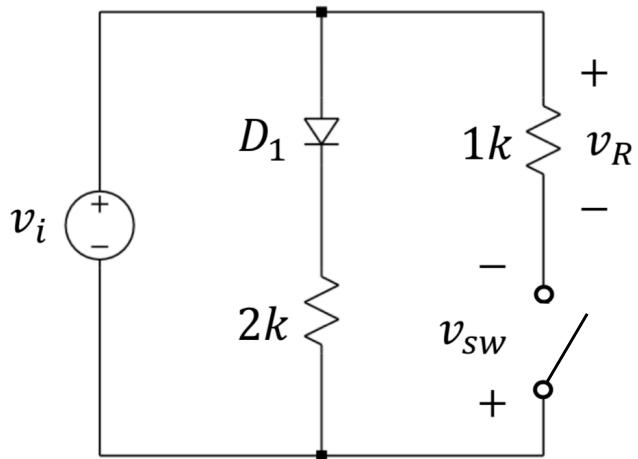- A. $v_s \geq 5 V$
- B. $v_s \geq 5.7 V$
- C. $v_s \geq 4.3 V$

Clicker question 2.

In the below circuit, find v_{SW} and v_R when $v_i = 5 V$.




- A. $v_{SW} = 0 V$ and $v_R = 0 V$
- B. $v_{SW} = 5 V$ and $v_R = 0 V$
- C. $v_{SW} = -5 V$ and $v_R = 5 V$
- D. $v_{SW} = -5 V$ and $v_R = 0 V$

Clicker question 3.

Find v_R and i in the below circuit for $v_s = 3V$.

(Assume Si diodes with $V_{D0} = 0.7 V$)

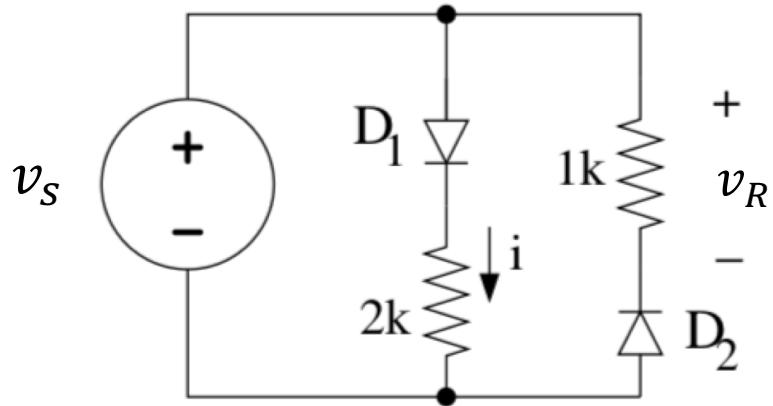

- A. $v_R = 2.3 V, i = 1.15 mA$
- B. $v_R = 0 V, i = 1.15 mA$
- C. $v_R = 0.6 V, i = 0.3 mA$

- A. $v_R = -2.3 V, i = 1.15 mA$

ECE 65: Components & Circuits Lab

Lecture 5

Zener Diode


Reference notes: sections 2.1-2.8

Sedra & Smith (7th Ed): sections 4.3-4.4

Saharnaz Baghdadchi


Course map

2. Diodes

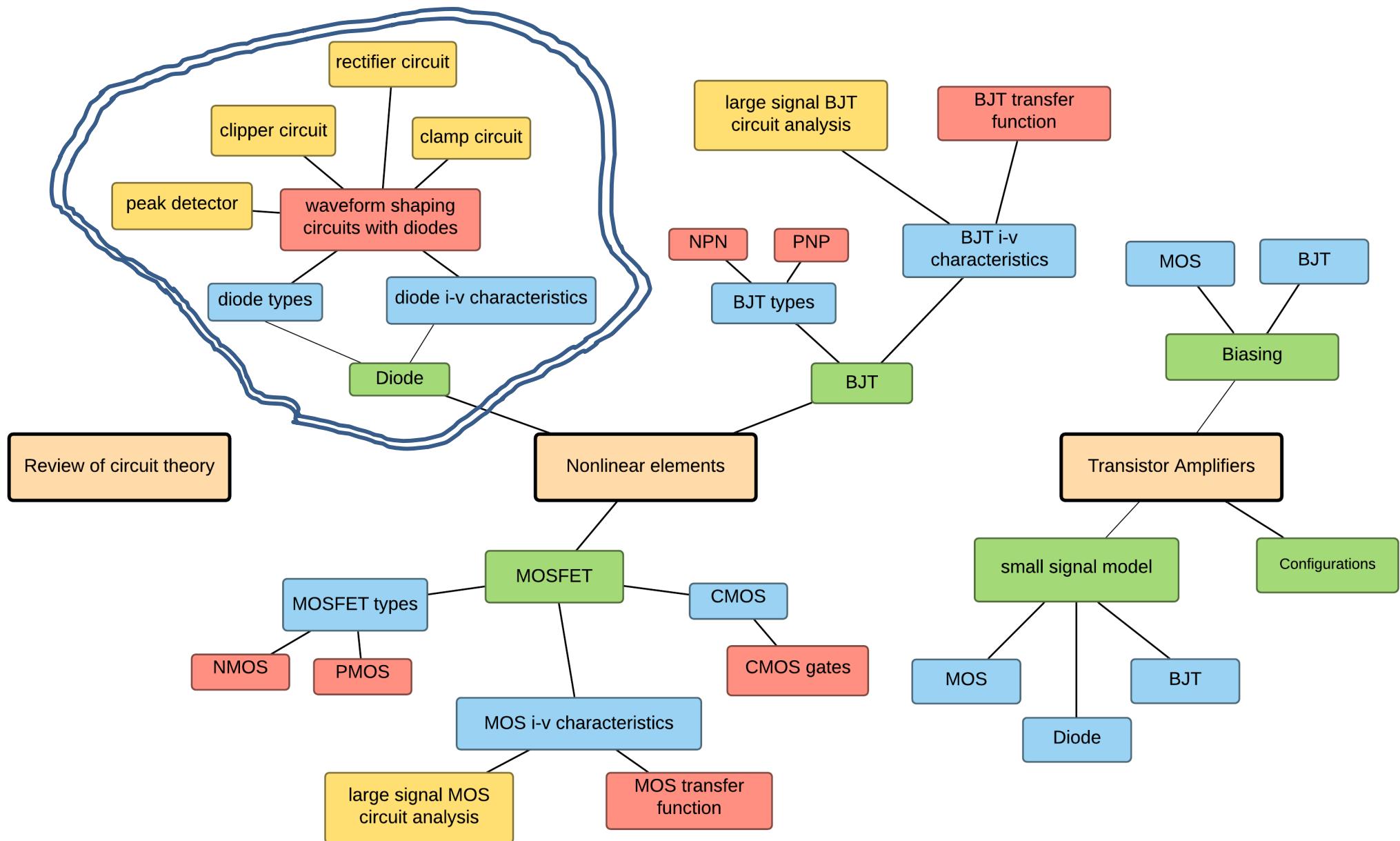


Other types of diodes

Light-emitting diode (LED)

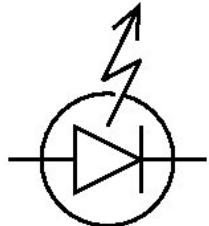

$$V_{D0} = 1.7 - 1.9 \text{ V}$$


Zener Diode

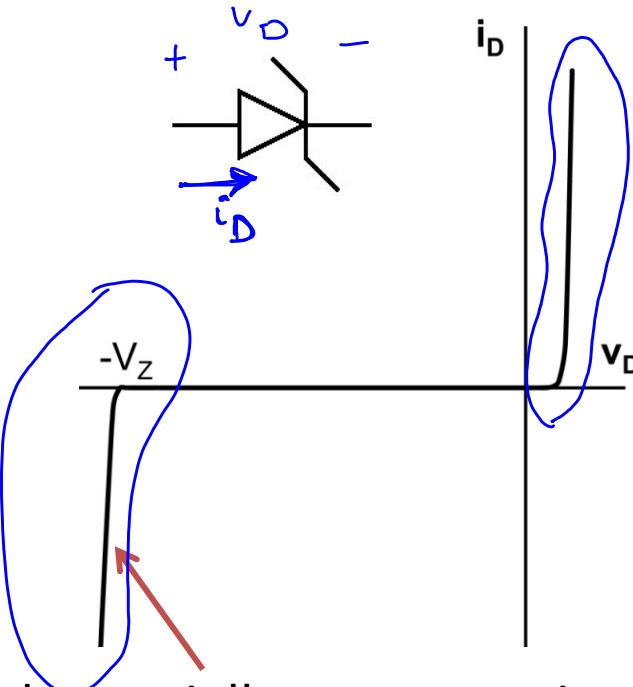

Made specially to operate in the reverse breakdown region.

Useful as a “reference” voltage in many circuits.

Zener Diode piecewise-linear model


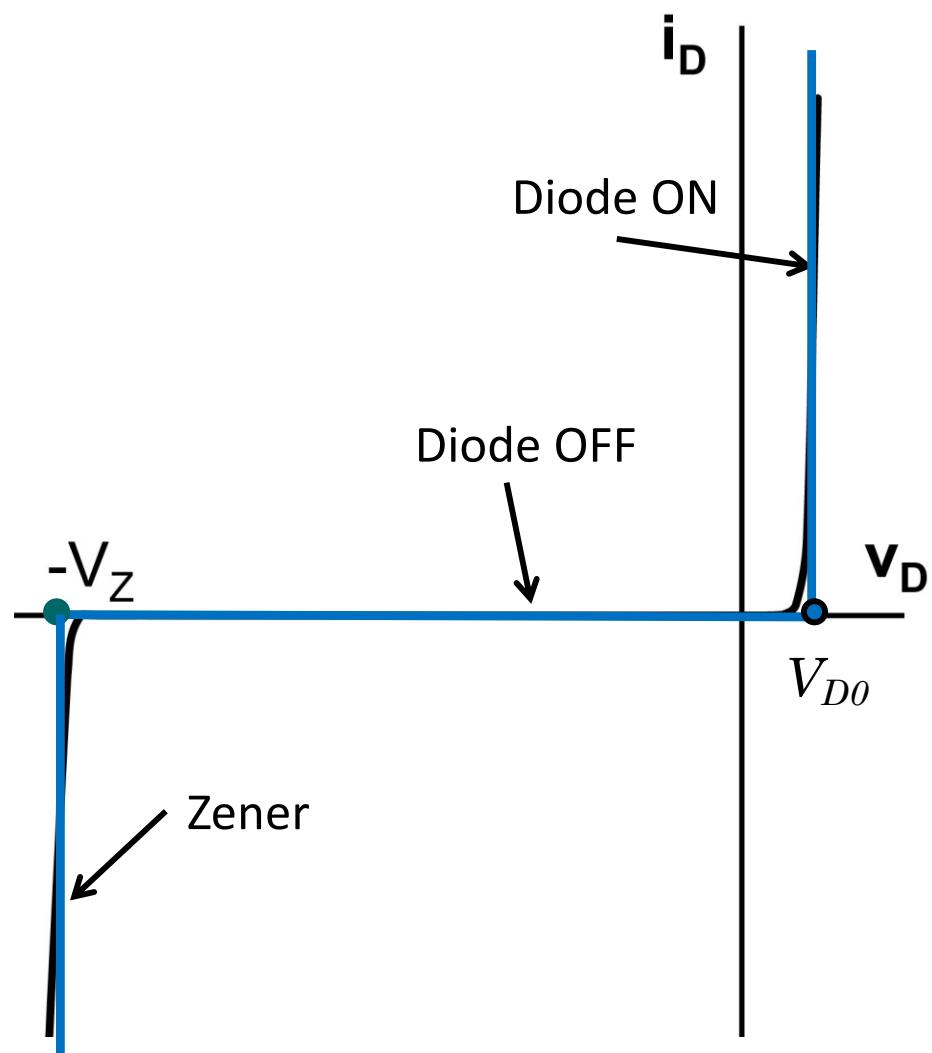


Diode ON: $v_D = V_{D0}$ and $i_D \geq 0$

Diode OFF: $i_D = 0$ and $-V_Z < v_D < V_{D0}$


Zener: $v_D = -V_Z$ and $i_D \leq 0$

Circuit Models:

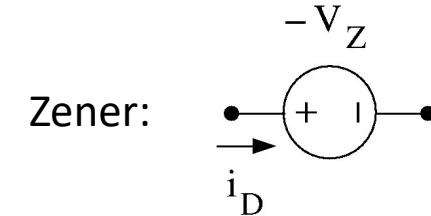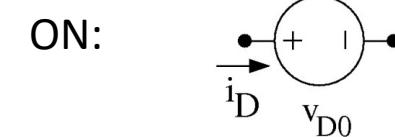

Zener Diode piecewise-linear model

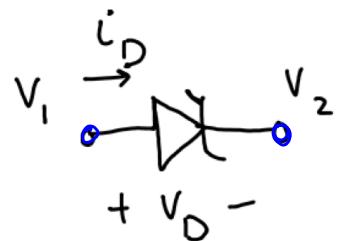Assume Zener diode with $V_D = 0.7 \text{ V}$ and $V_Z = 5 \text{ V}$.



(A) When $0 < V_1 - V_2 < 0.7$, diode is forward-biased.

but it's not ON, yet. $\Rightarrow i_D = 0$

(B) When $-5 < V_1 - V_2 < 0$, diode is reverse-biased, but it's not in the Zener region, so it's off. $\Rightarrow i_D = 0$

(C) When $V_1 - V_2 = 0.7$, diode is forward-biased and it's ON $\Rightarrow i_D > 0$ and $V_D = V_{D_0} = 0.7 \text{ V}$.

(D) When $V_1 - V_2 = -5 \text{ V}$, diode is in Zener region, it conducts, $\Rightarrow i_D \leq 0$ and $V_D = -V_2 = -5 \text{ V}$

Example:

In the following circuit, find i_L and v_L for $v_s = 10 V$. For what range of v_s and R_L the Zener diode will be in the Zener region and the circuit can operate as a voltage regulator? ($V_Z = 3 V, V_{D0} = 0.7 V$)


KCL:

$$\{ i_s + i_D - i_L = 0 \}$$

KVL:

$$\{ v_s = R_s i_s - v_D \}$$
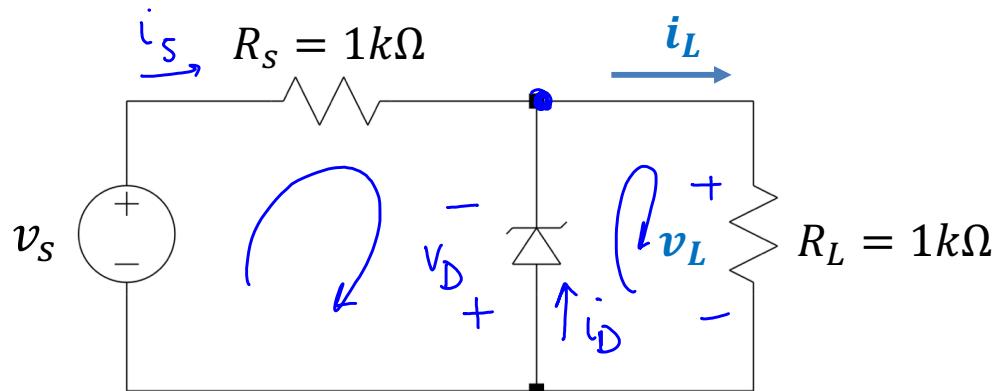
$$\{ v_D + v_L = 0 \rightarrow v_L = -v_D \}$$



Assume the diode is in the Zener region:

$$\{ v_D = -V_Z \}, \{ i_D \leq 0 \}$$

$$v_L = V_Z = 3 V$$

$$i_L = \frac{v_L}{R_L} = \frac{3 V}{1 k} = 3 mA$$

$$i_L = 3 mA$$

$$i_s = \frac{v_s + v_D}{R_s} = \frac{10 V - 3 V}{1 k}$$

$$i_s = 7 mA$$

$$\begin{aligned} i_D &= i_L - i_s = 3 mA - 7 mA \\ &= -4 mA < 0 \end{aligned}$$

when the diode is in the Zener region, $i_D \leq 0$.

$$i_D = i_L - i_S \leq 0 \rightarrow i_S \geq i_L$$

$$V_L = V_Z, \quad i_L = \frac{V_L}{R_L} = \frac{V_Z}{R_L}$$

$$i_S = \frac{V_S - V_Z}{R_S}$$


$$\frac{V_S - V_Z}{R_S} \geq \frac{V_Z}{R_L}$$

$$\frac{V_S}{R_S} \geq V_Z \left(\frac{1}{R_L} + \frac{1}{R_S} \right) \rightarrow V_S \geq \underline{\underline{V_Z \left(1 + \frac{R_S}{R_L} \right)}}$$

$$\frac{V_S/V_Z - 1}{R_S} \geq \frac{1}{R_L} \rightarrow R_L \geq \frac{R_S}{V_S/V_Z - 1}$$

Lecture 5 reading quiz

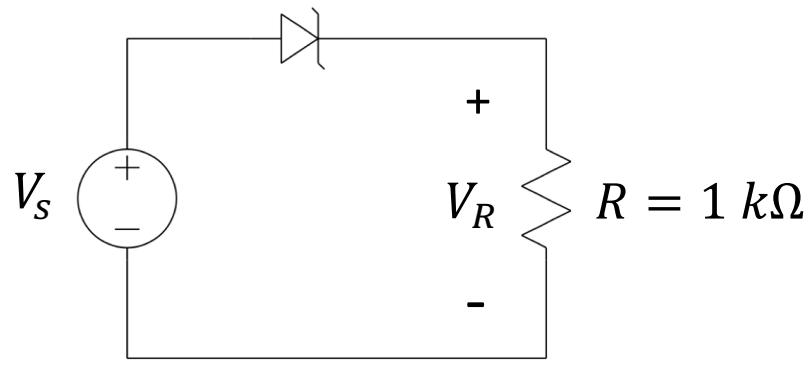
In the following circuit, find V_R for $V_s = +5 V$ and $V_s = -5 V$. Assume $V_Z = 3 V$ and $V_{Do} = 0.7 V$.



Discussion question 1.

In the below circuit find the range of v_i for which D_1 is ON and D_2 is in the Zener region. Calculate v_{out} .

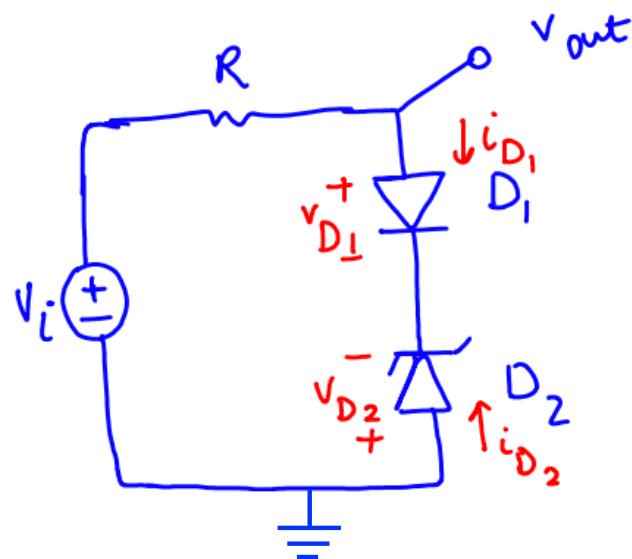
Are there any other possible states at which D_1 and D_2 can operate?
Assume $V_{D0} = 0.7 \text{ V}$ and $V_Z = 5 \text{ V}$.



Extra activity: find v_{out} for all ranges of v_i (solve the circuit parametrically).

Clicker question 1:

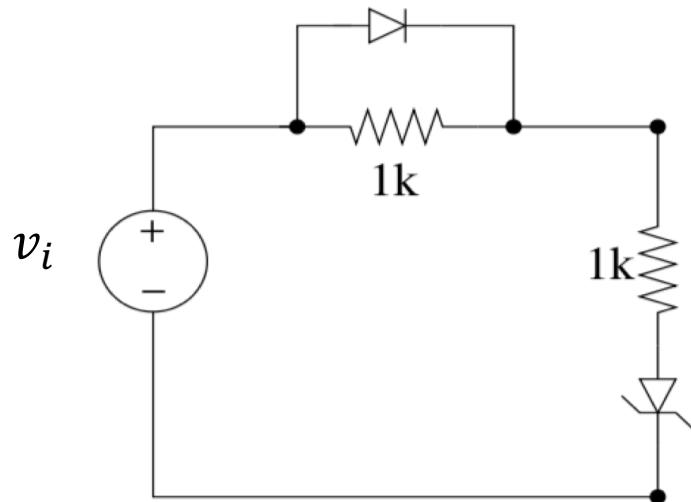What is the range of v_i for which both diodes are ON? Assume $V_Z = 4\text{ V}$ and $V_{Do} = 0.7\text{ V}$.



- A. $v_i \geq 2.1\text{ V}$
- B. $v_i \geq 1.4\text{ V}$
- C. $v_i \geq 0.7\text{ V}$
- D. Both diodes cannot be ON simultaneously.

ECE 65: Components & Circuits Lab

Lecture 6

Diode waveform shaping circuits

Rectifier circuits


Reference notes: sections 2.9

Sedra & Smith (7th Ed): sections 4.4-4.6

Saharnaz Baghdadchi

Course map



2. Diodes

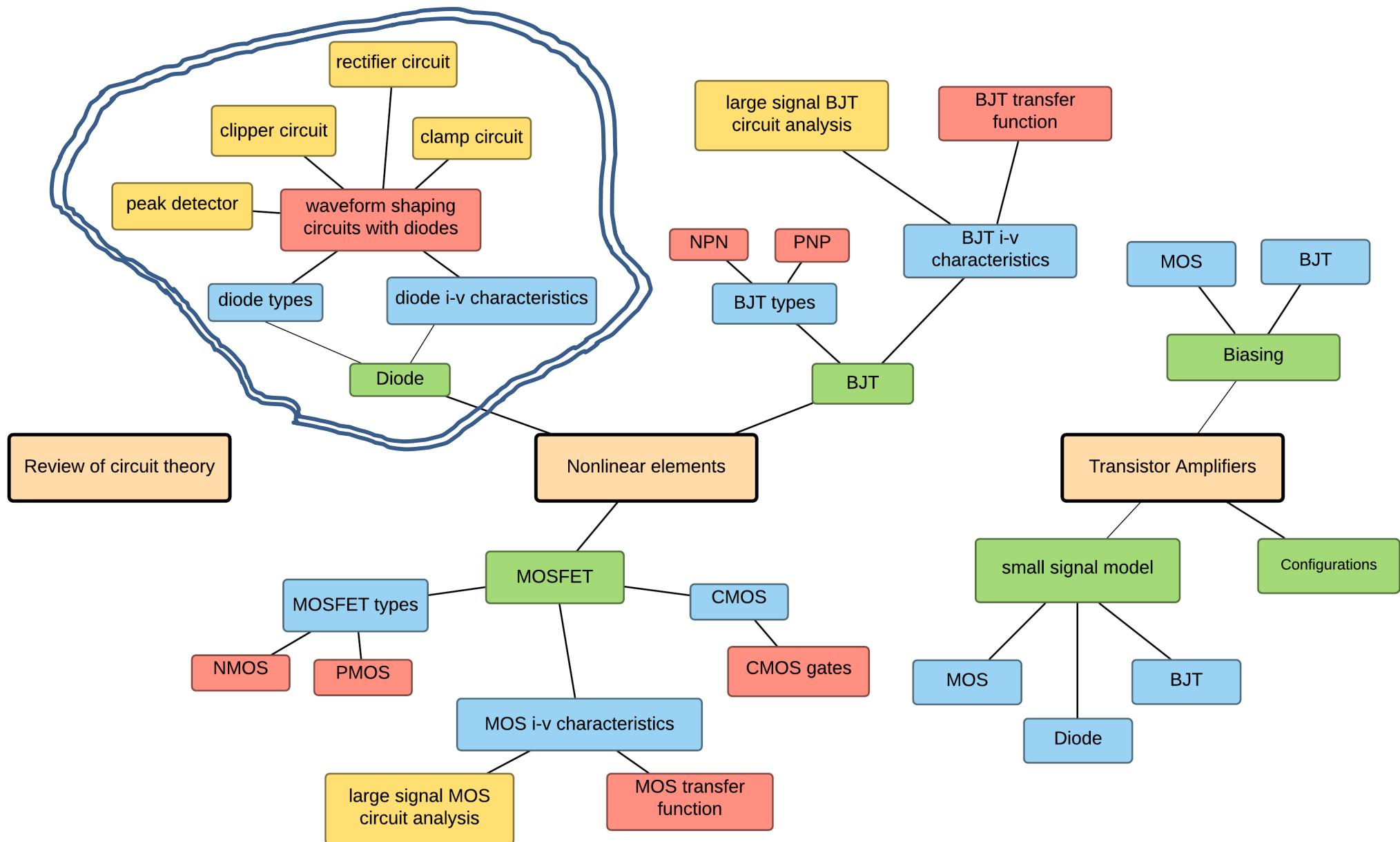

Diodes Waveform shaping Circuits

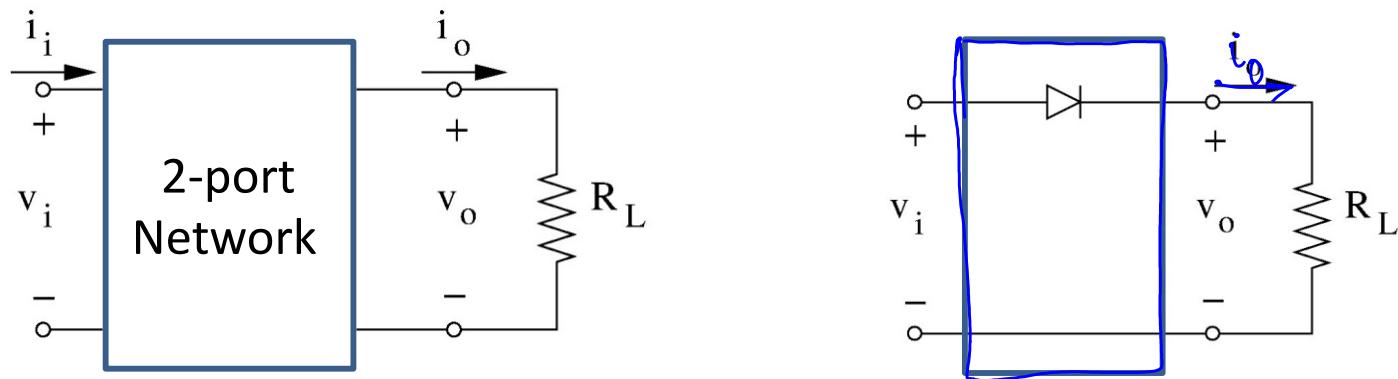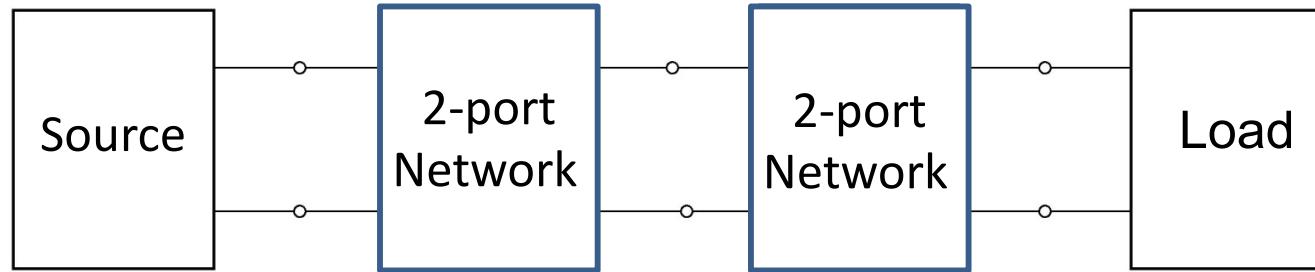- 1. Rectifier Circuit**
- 2. Clipper Circuit**
- 3. Peak Detector**
- 4. Clamp Circuit**

Diode waveform shaping circuits as two-port networks



We would like to find the transfer function, v_o vs v_i


"Open-loop" Transfer function is v_o vs v_i when $R_L \rightarrow \infty$ or $i_o = 0$.

Rectifier Circuit

$$\text{KVL: } v_i = v_D + v_o \rightarrow v_o = v_i - v_D$$

$$\text{Ohm's law: } i_D = v_o / R_L$$

$$i_D = i_o$$

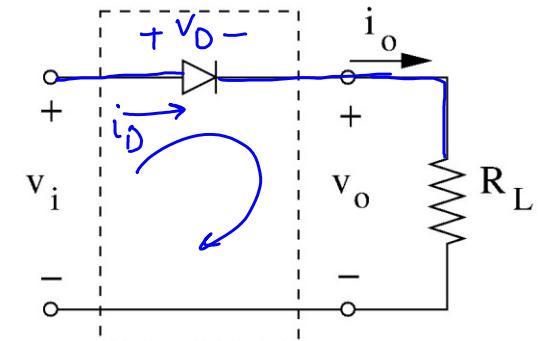

Diode OFF: $i_D = 0$ & $v_D < V_{D0}$

$$v_o = R_L i_D = 0$$

$$v_i = v_D + v_o \Rightarrow v_i = v_D < V_{D0} \rightarrow v_i < V_{D0}$$

Diode ON: $v_D = V_{D0}$ & $\underline{i_D \geq 0}$

$$v_o = v_i - V_{D0}$$



$$i_D = \frac{v_i - V_D}{R} = \frac{v_i - V_{D0}}{R} \geq 0 \rightarrow v_i \geq V_{D0}$$

Rectifier Circuit





Transfer Function is non-linear:

For $v_i \geq V_{D0}$, $v_o = v_i - V_{D0}$ (Diode is ON)

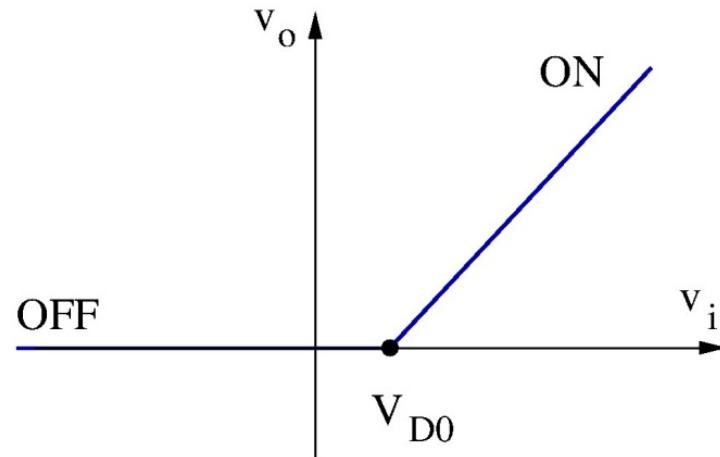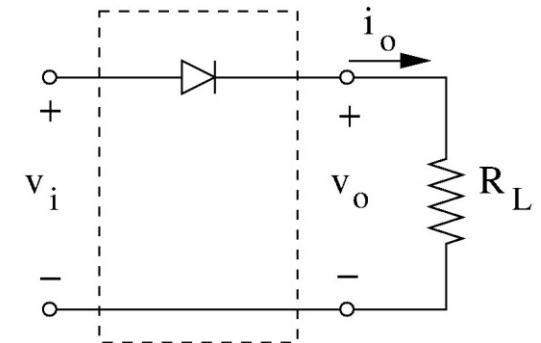For $v_i < V_{D0}$, $v_o = 0$ (Diode is OFF)



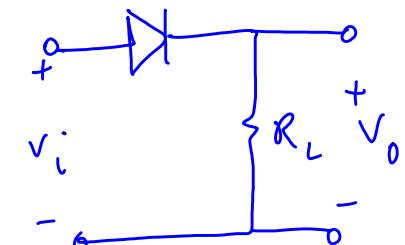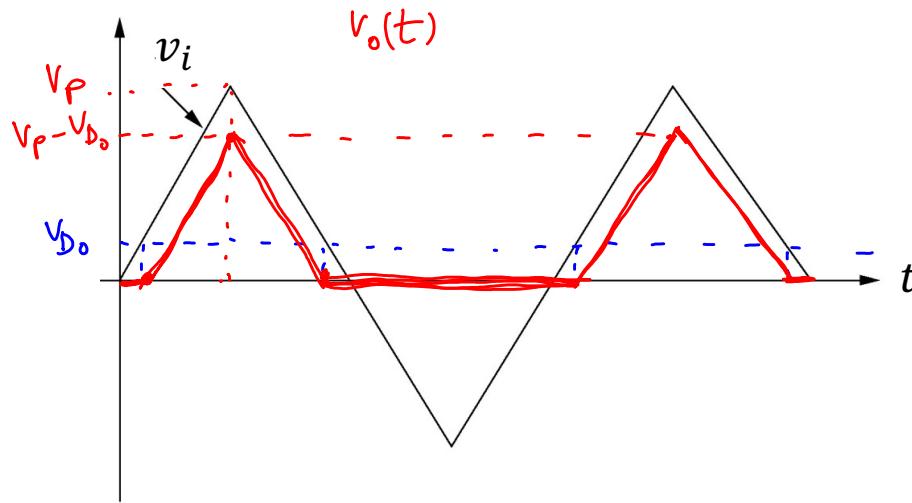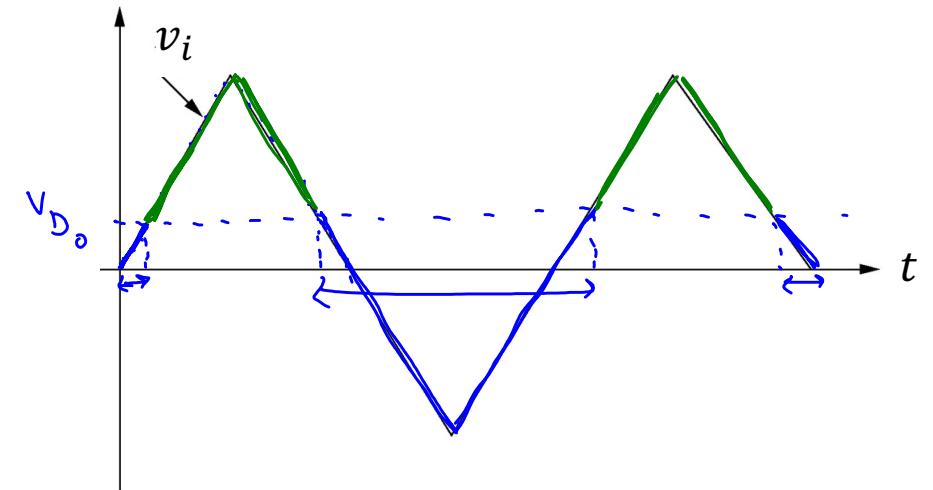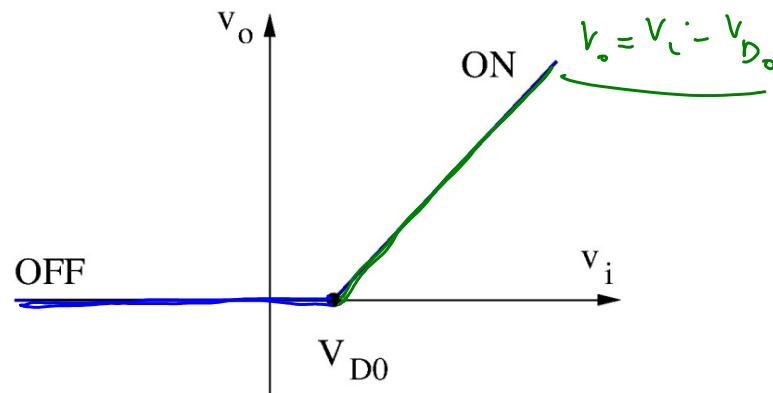Rectifier Circuit: example input - output waveforms



Rectifier Circuit for the negative part of v_i

Transfer Function is non-linear:

$$\text{For } v_i \leq -V_{D0}, \quad \underline{v_o = v_i + V_{D0}} \quad (\text{Diode is ON})$$

$$\text{For } v_i > -V_{D0}, \quad v_o = 0 \quad (\text{Diode is OFF})$$

$$\text{Diode ON: } i_D \geq 0, \quad V_D = V_{D0}$$



kVL:

$$v_i = -V_D - R_L i_D$$

$$\rightarrow i_D = \frac{-V_D - v_i}{R_L}$$



$$i_D = \frac{-V_{D0} - v_i}{R_L} \geq 0$$

$$\rightarrow v_i \leq -V_{D0}$$

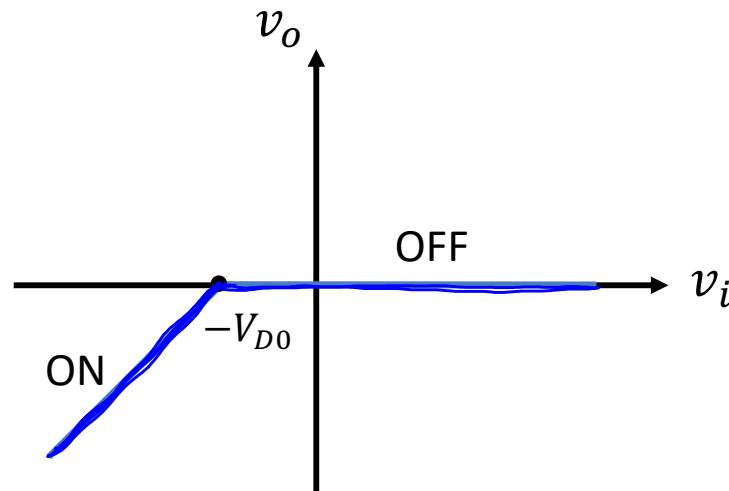
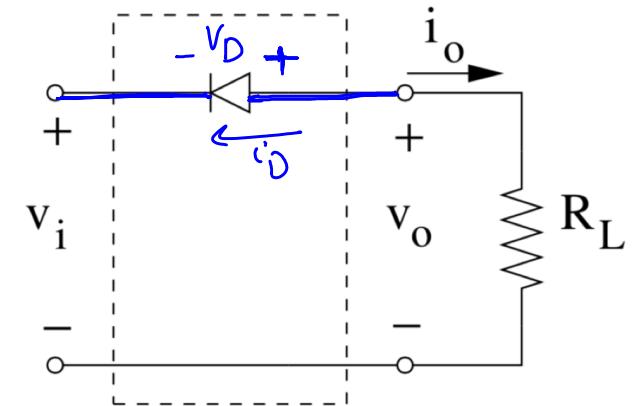


Application of Rectifier Circuit: AC to DC convertor for power supply




Half-wave rectifier

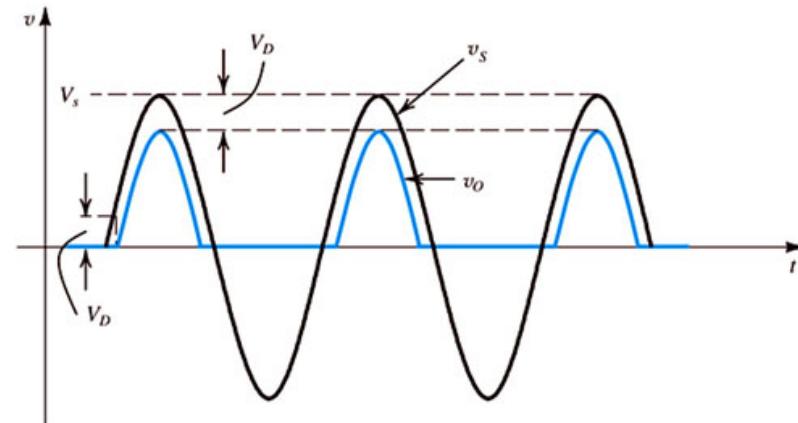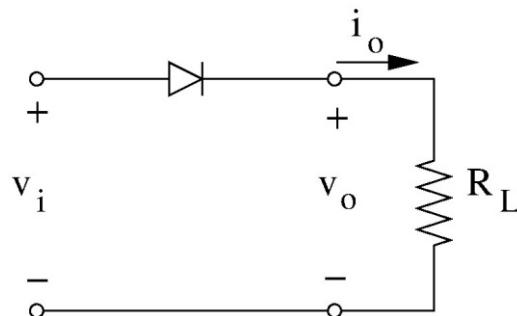

Full-wave rectifier

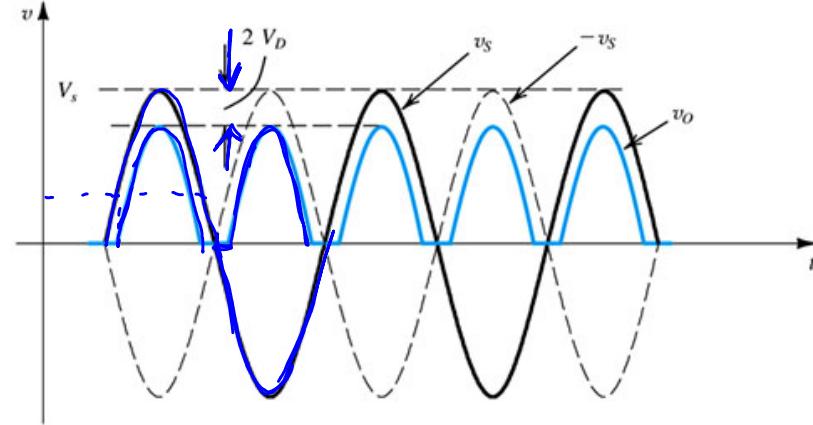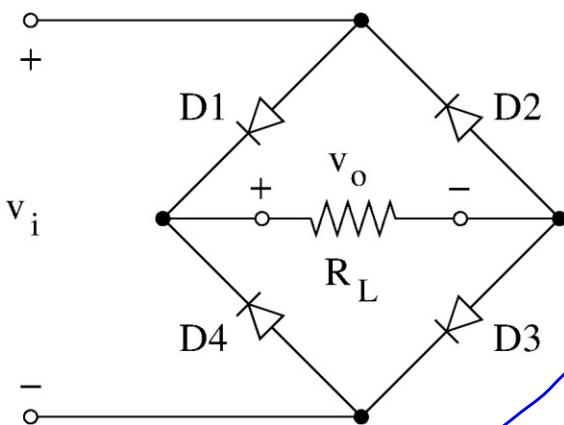

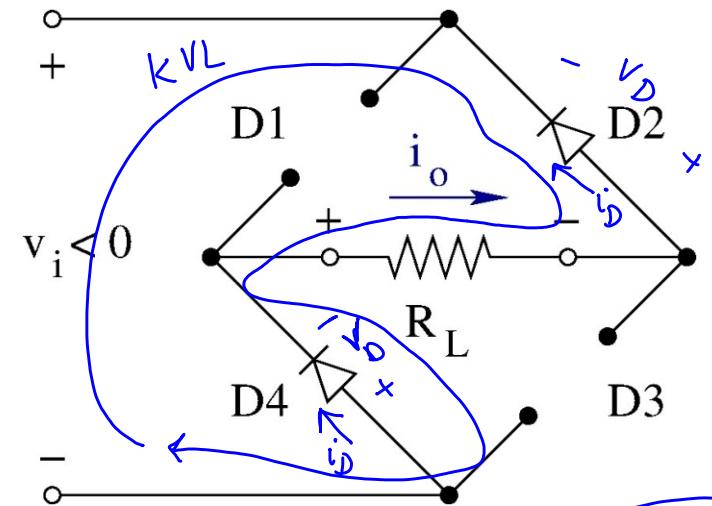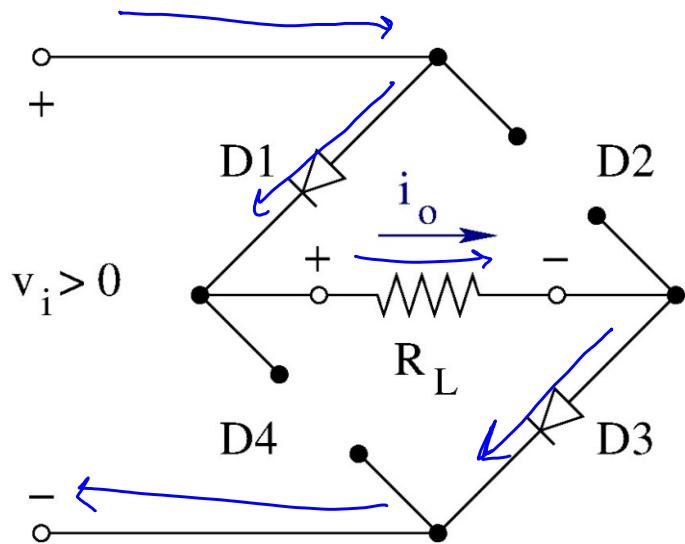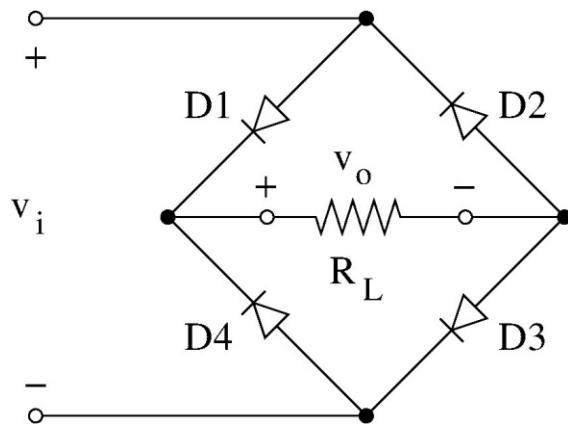Each pair of diodes conduct only for half of the cycle






$$-v_i - v_{D_0} - v_o - v_{D_0} = 0 \rightarrow v_o = -v_i - 2v_{D_0}$$


$$v_i \leq -2v_{D_0}$$

Lecture 6 reading quiz

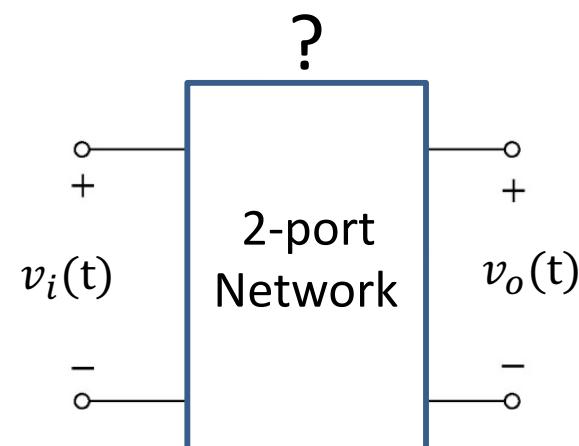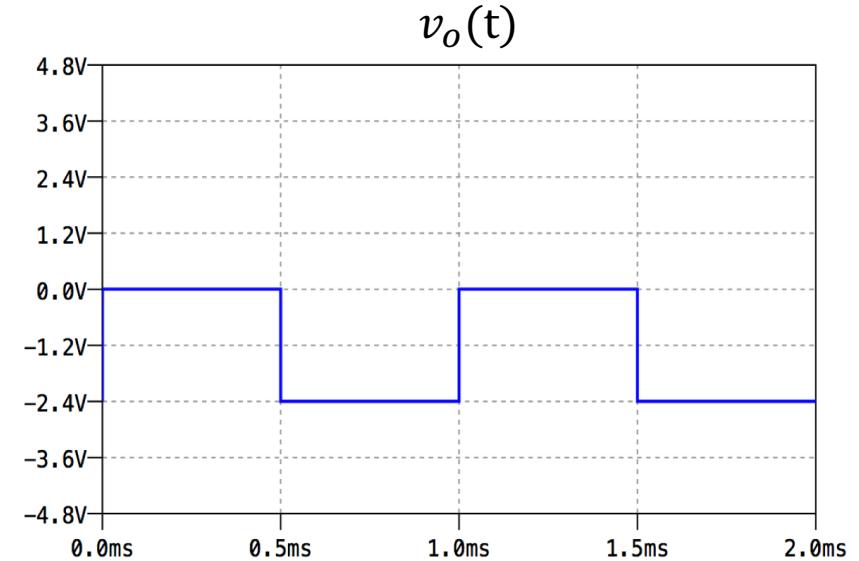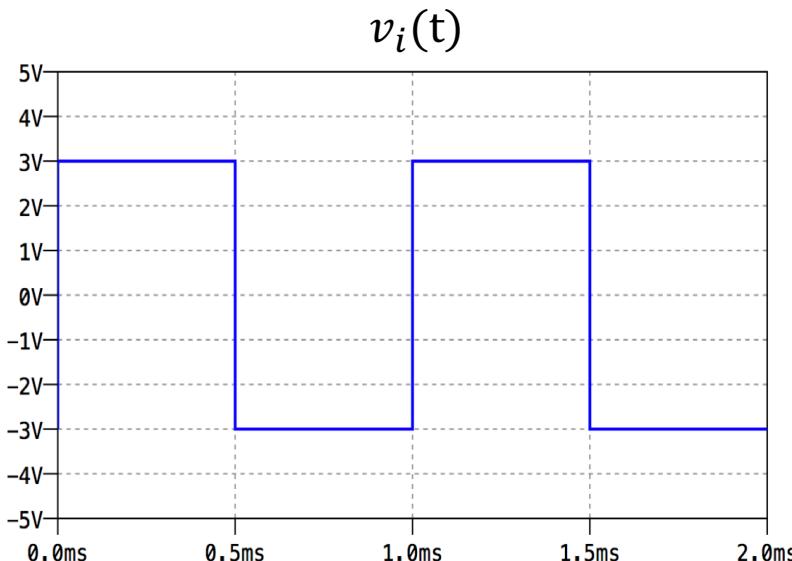Which one of the circuits in the provided options could produce the shown output waveform for the given input signal?




Block Diagram of a DC Power Supply

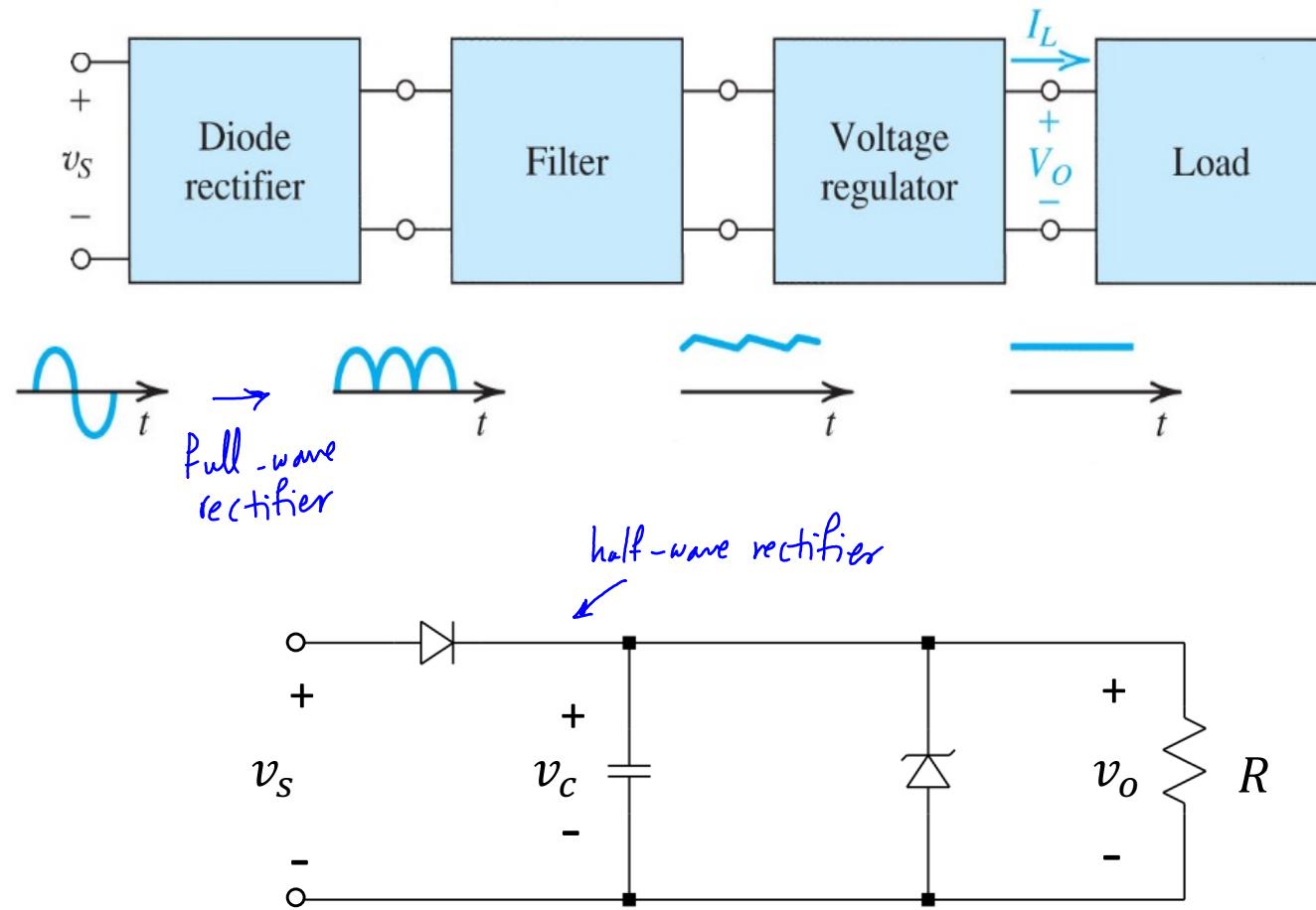

Discussion question 1.

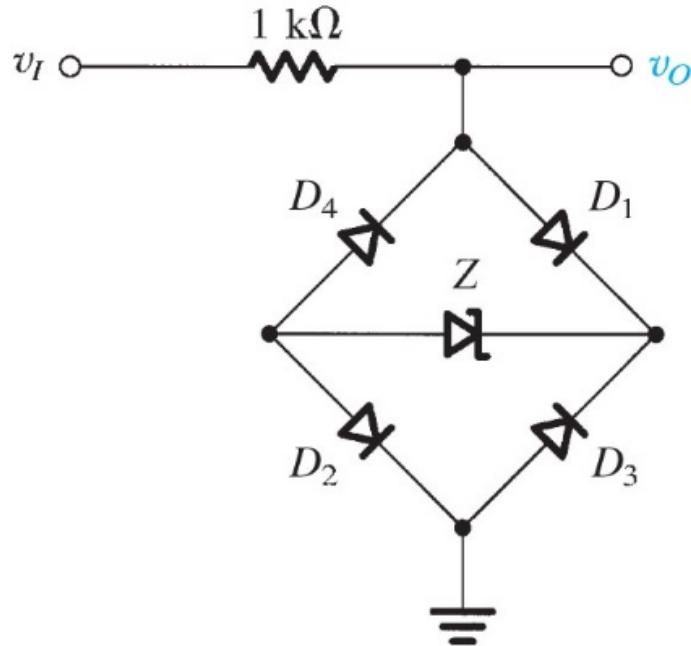Plot the transfer function of the following circuit. Find v_o for different ranges of v_i and plot a graph that shows the relationship between v_i and v_o . Assume $V_{D0} = 0.7 V$, $V_Z = 4 V$.




Extra activity:

Draw the output voltage waveform if $v_i = 2 \sin(\omega t)$.

Hints:

Discussion question 1.

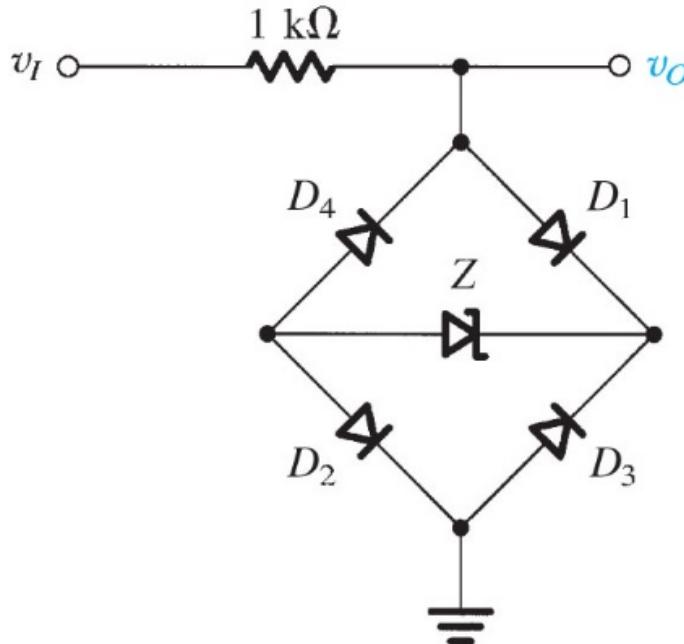Plot the transfer function of the following circuit. Find v_o for different ranges of v_i and plot a graph that shows the relationship between v_i and v_o . Assume $V_{D0} = 0.7 V$, $V_Z = 4 V$.



- Label all the diode currents and voltages.
- Think about how current can flow in the circuit. Trace the direction of the current flow, starting from the positive terminal of the v_i and ending at the negative terminal of v_i and the other way around.
- Which diodes will conduct when v_i is positive enough, and which diodes will conduct when v_i is negative enough?
- Use your answer to the above question to create the list of diode cases for this problem.
- For each case, using KVL (and KCL, if needed) and the diode current or voltage inequality, find the range of v_i .
- For each case, using KVL (and KCL, if needed), find v_o as a function of v_i . Note that v_o might be constant and independent of v_i for some ranges of v_i . It will translate to a line with a slope of zero in the graph of v_o vs. v_i (the transfer characteristic graph)


Extra activity:

Draw the output voltage waveform if $v_i = 2 \sin(\omega t)$.

Hints:

Discussion question 1.

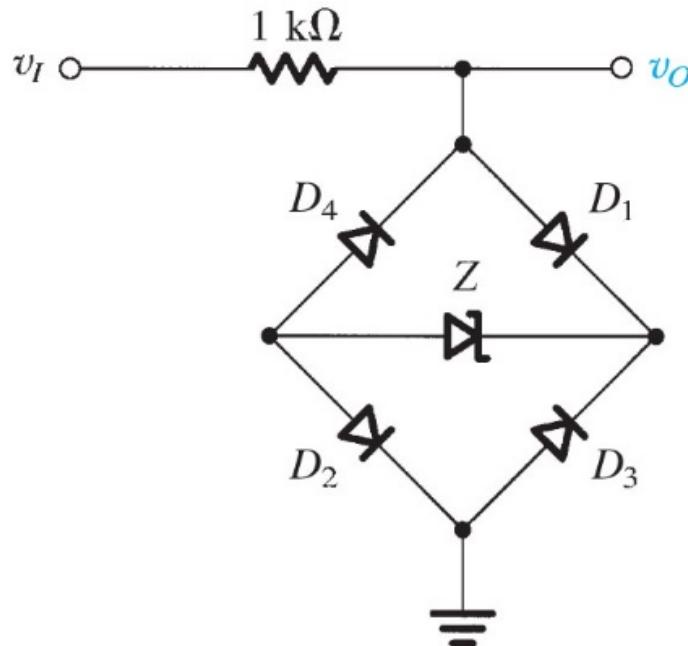Plot the transfer function of the following circuit. Find v_o for different ranges of v_i and plot a graph that shows the relationship between v_i and v_o . Assume $V_{D0} = 0.7 V$, $V_Z = 4 V$.



Extra activity:


- What are the maximum and minimum amplitudes of the given v_i ?
- Looking at the transfer characteristic graph, what are the corresponding amplitudes for v_o ?

Extra activity:

Draw the output voltage waveform if $v_i = 2 \sin(\omega t)$.

Discussion question 2.

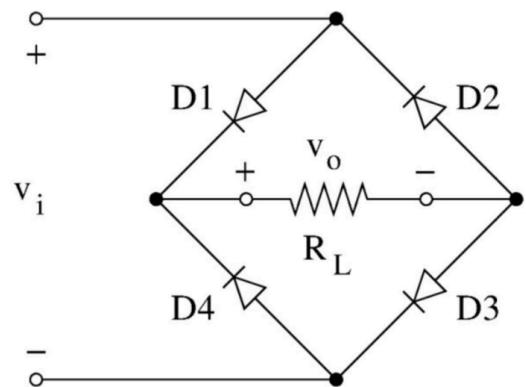Plot the transfer function of the following full-wave rectifier. Find v_o for different ranges of v_i and plot a graph that shows the relationship between v_i and v_o .



Extra activity: Draw the output voltage waveform if $v_i = 2 \sin(\omega t)$.

ECE 65: Components & Circuits Lab

Lecture 7

Diode waveform shaping circuits

Clipper circuits


Reference notes: sections 2.9

Sedra & Smith (7th Ed): sections 4.4-4.6

Saharnaz Baghdadchi



Course map

2. Diodes


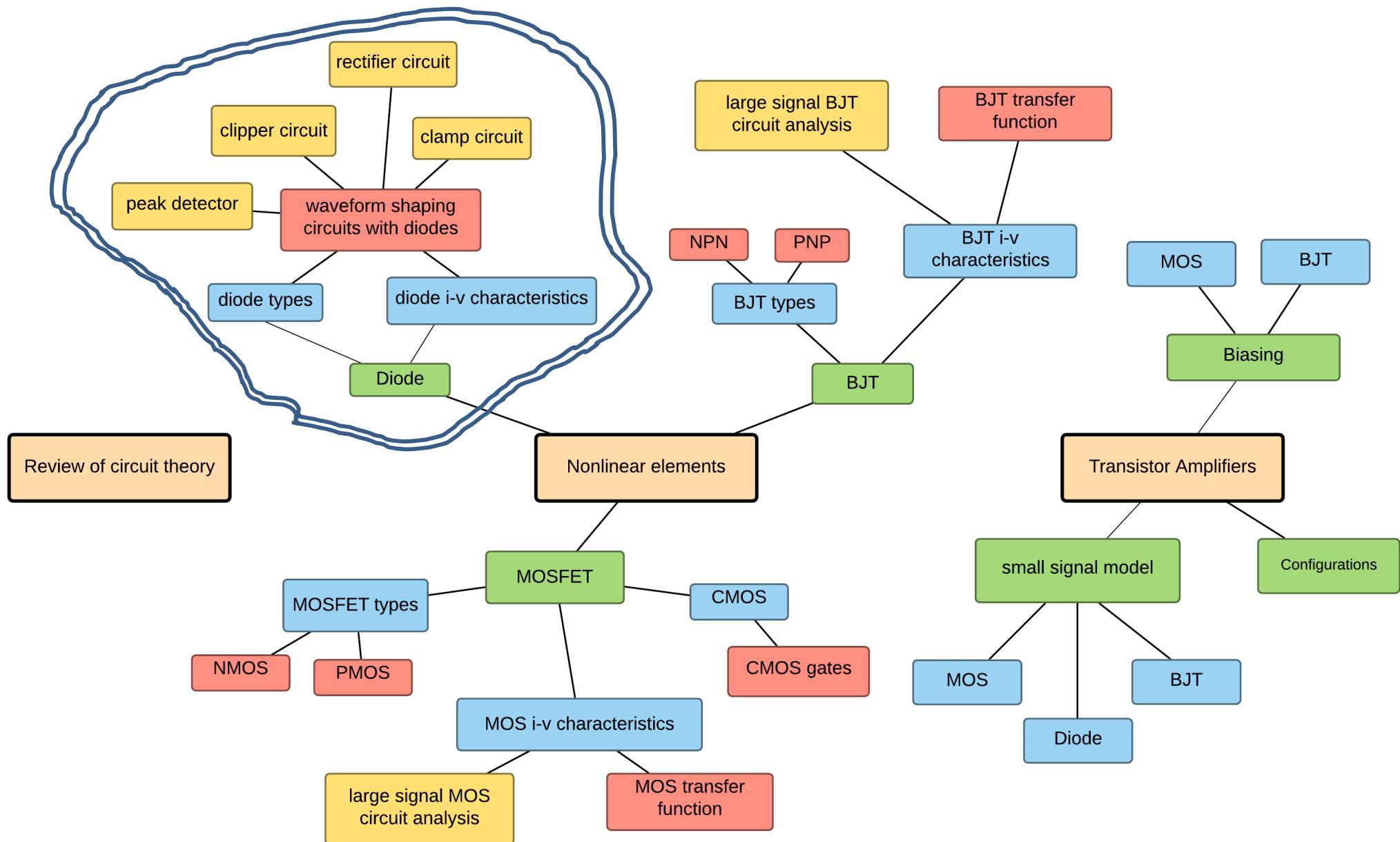


Rectifier & clipper circuits

**Half-wave
Rectifier**

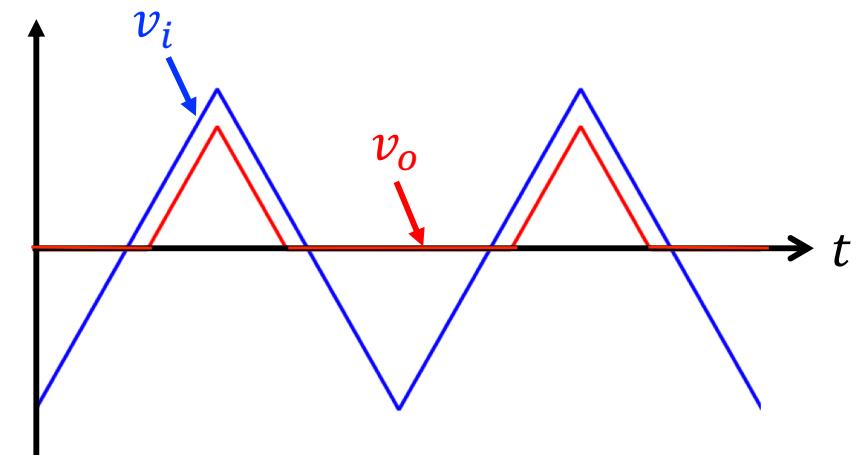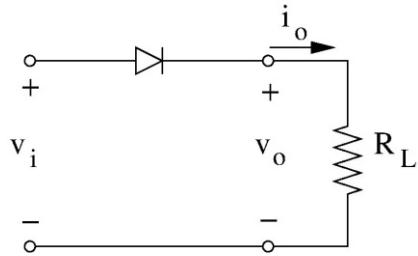


Clipper

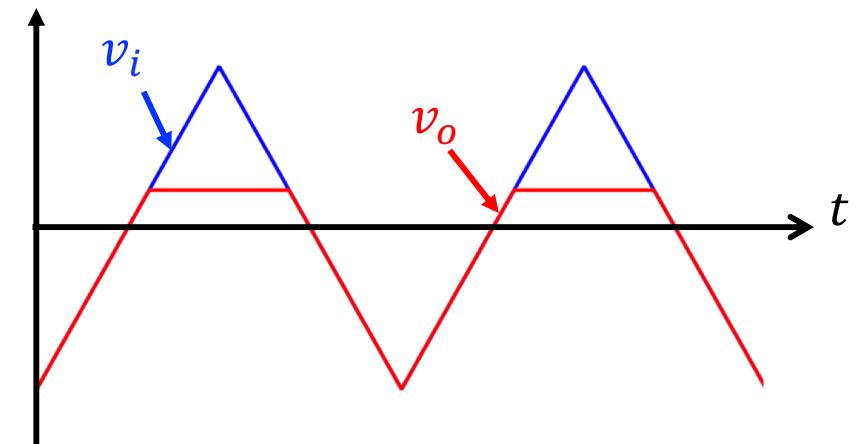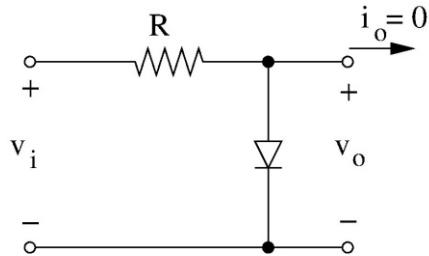

Clipper or Limiter Circuit

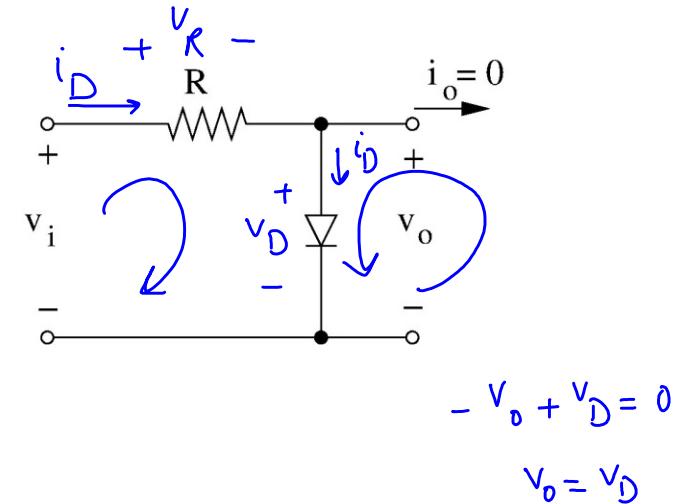KVL: $v_i = v_R + v_D$ ✓
 KVL: $v_o = v_D$ ✓
 Ohm's law: $i_D = v_R/R$



Diode OFF: $i_D = 0$ & $v_D < V_{D0}$

$$v_i = v_R + v_D = v_R + v_o = R \times i_D + v_o \rightarrow v_i = v_o$$

$$v_i = v_R + v_D \rightarrow v_i = v_D < V_{D0} \rightarrow v_i < V_{D0}$$

Diode ON: $v_D = V_{D0}$ & $i_D \geq 0$

$$v_o = v_D = V_{D0}, \quad v_o = V_{D0}$$



$$i_D = \frac{v_i - V_{D0}}{R} \geq 0 \rightarrow v_i \geq V_{D0}$$

Clipper Circuit




open loop transfer function

Transfer Function is non-linear:





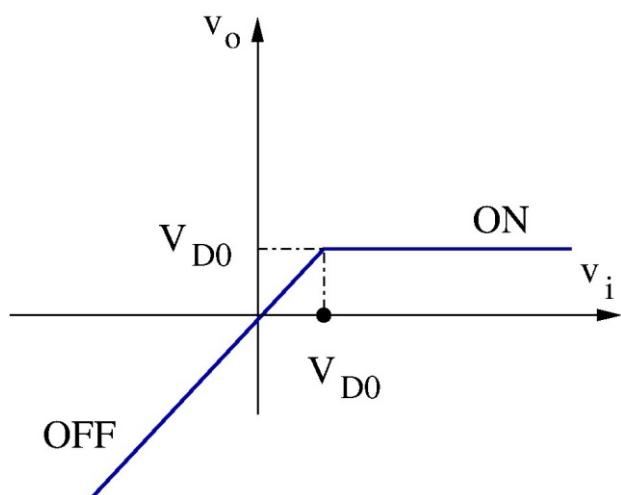
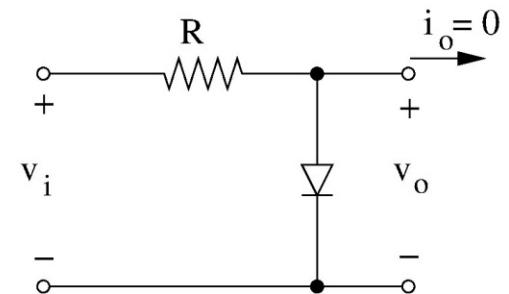
- { For $v_i \geq V_{D0}$, $v_o = V_{D0}$ (Diode is ON)
- For $v_i < V_{D0}$, $v_o = v_i$ (Diode is OFF)



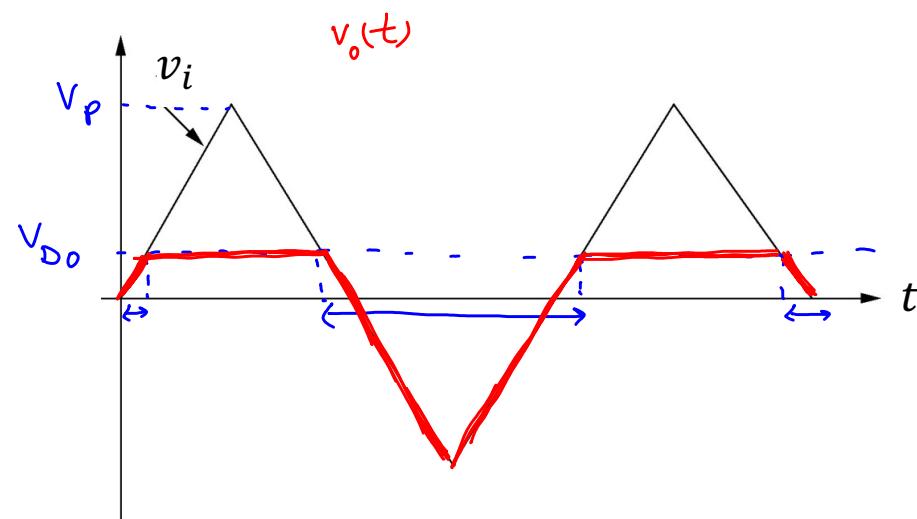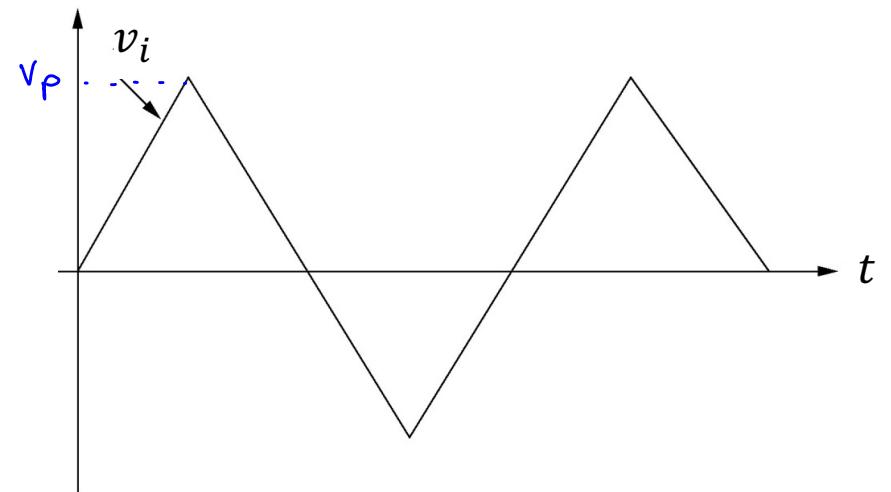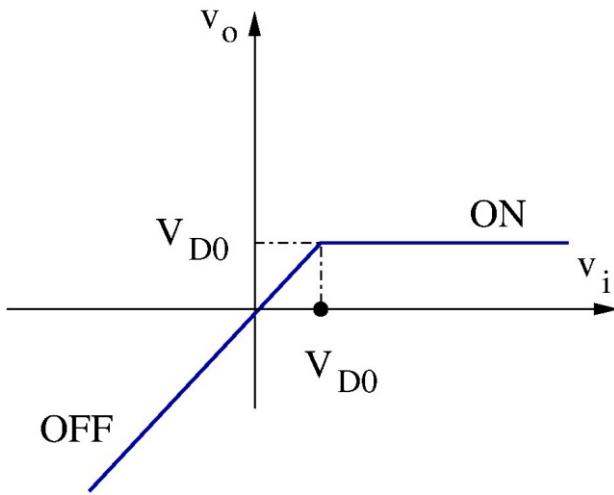Clipper Circuit: example input-output waveforms




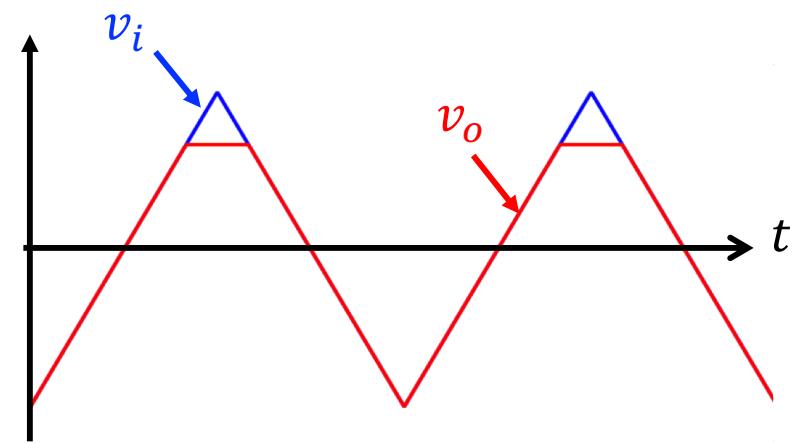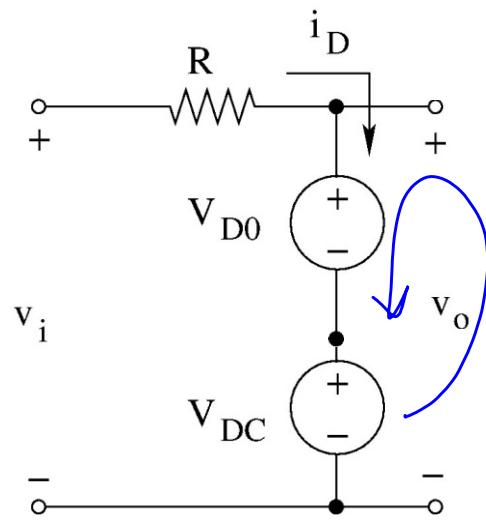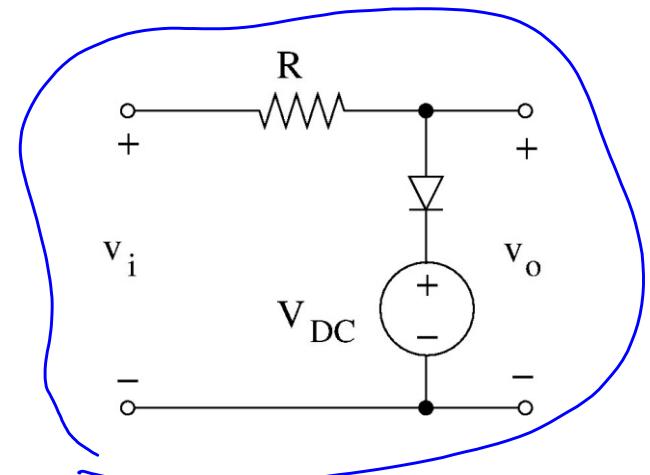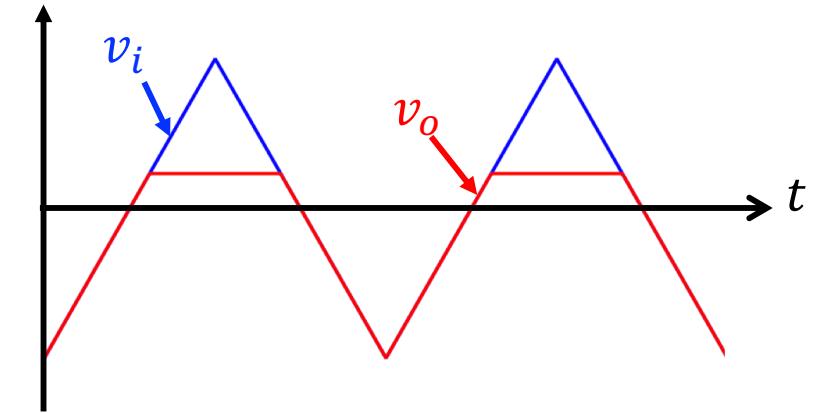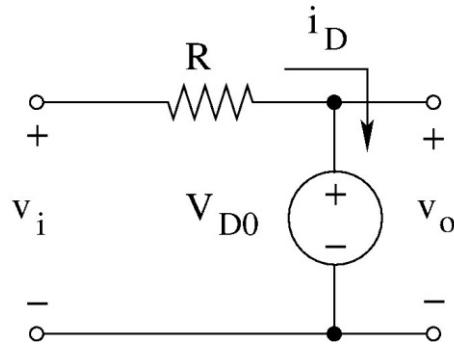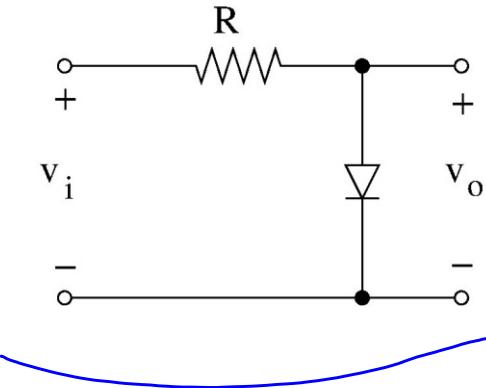Adjusting the limiting voltage in the clipper circuit




$$v_o = V_{D0} + V_{DC}$$

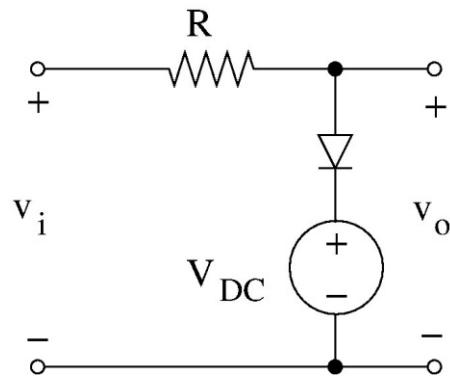
Using Zener diodes to adjust the limiting voltage in the clipper circuit




v_o limited to $\leq V_{D0} + V_Z$

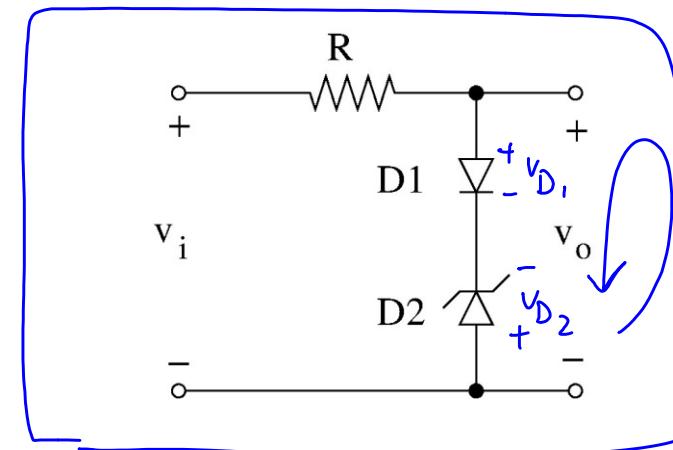
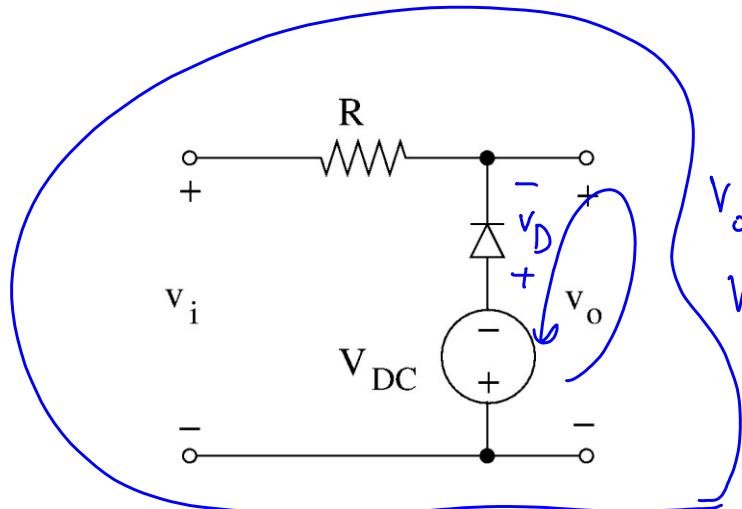
$$\begin{aligned} D_1 &\text{ is ON} \\ D_2 &\text{ is Zener} \\ V_{D1} &= V_{D_0} \\ v_{O_2} &= -V_Z \\ V_o &= V_{D_1} - V_{D_2} \\ V_o &= V_{D_0} + V_Z \end{aligned}$$




v_o limited $\geq -V_{D0} - V_Z$

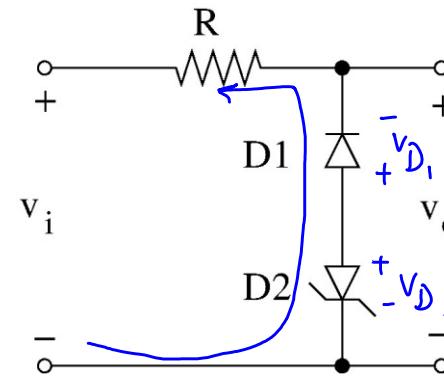


$$\begin{aligned} V_{D1} &= V_{D_0} \\ V_{D2} &= -V_Z \\ v_o &= -V_{D_0} - V_Z \\ v_o &= -V_{D_1} + V_{D_2} \end{aligned}$$

Clipping both the top & bottom portions of the signal simultaneously

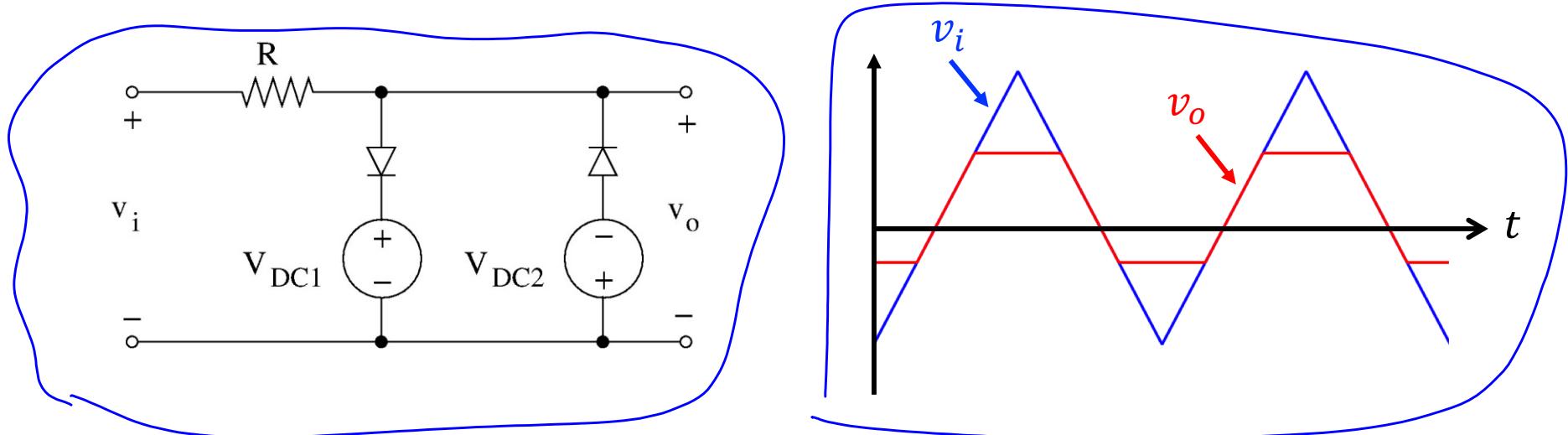v_o limited to $\leq V_{D0} + V_{DC1}$ and $\geq -V_{D0} - V_{DC2}$





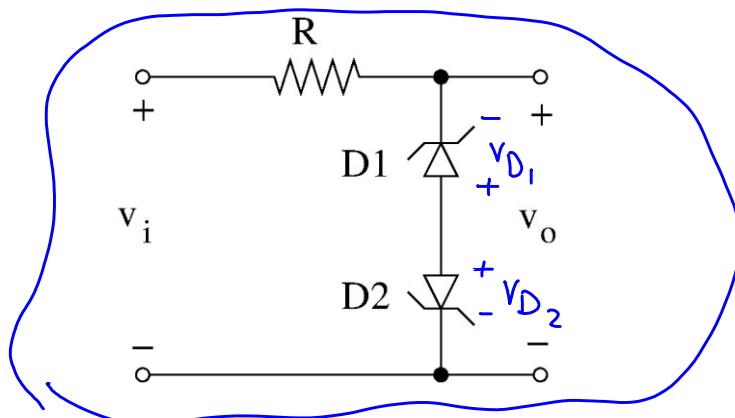v_o limited to $\leq V_{D0} + V_{Z1}$ and $\geq -V_{D0} - V_{Z2}$







Lecture 7 reading quiz

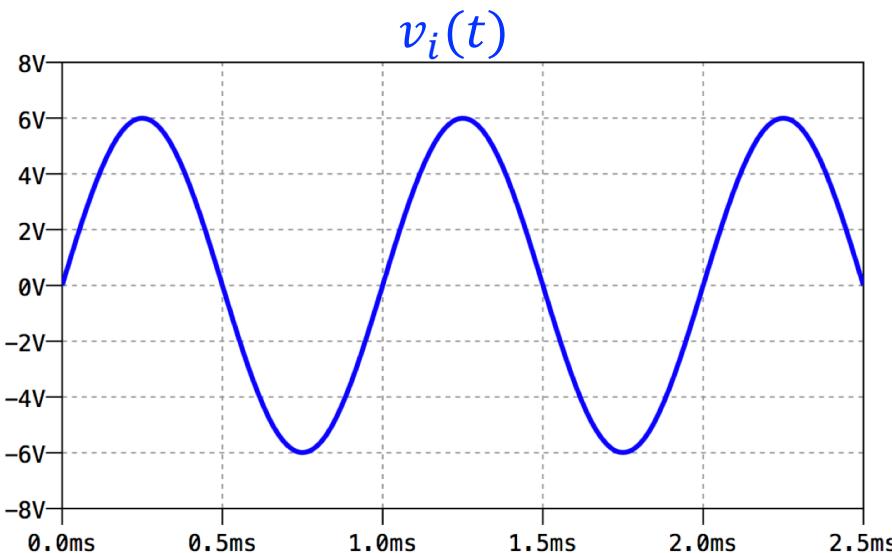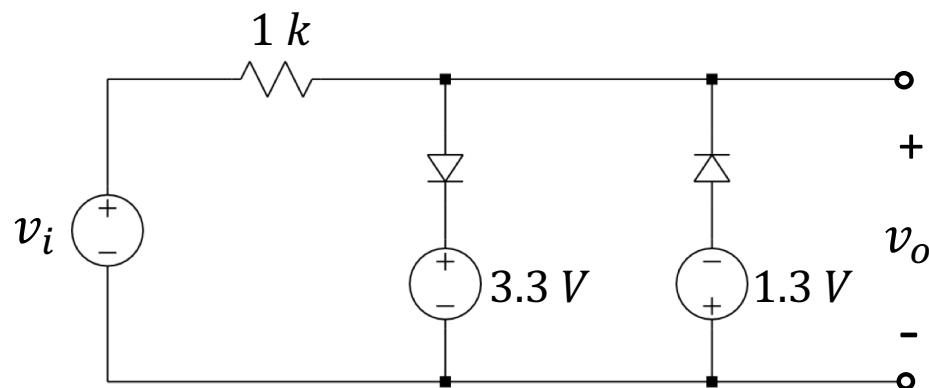Calculate and draw the output of the following two-port network for the given input signal.



Clicker question 1

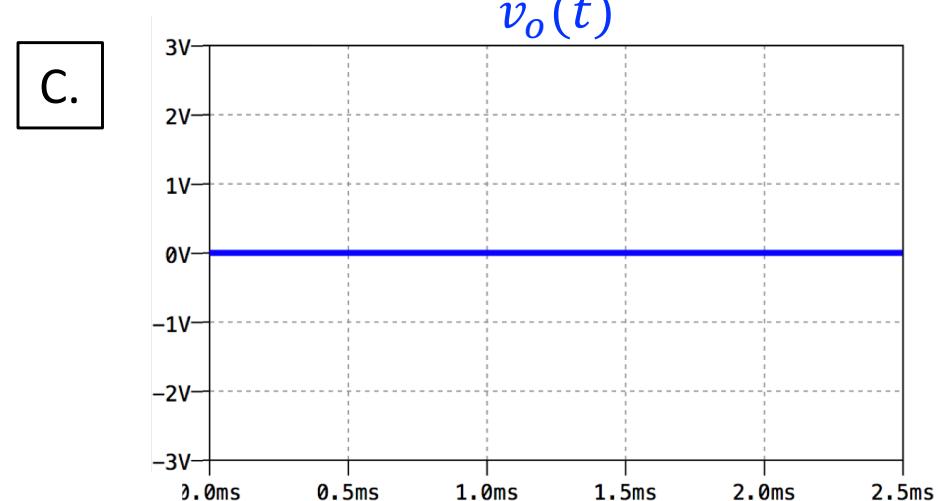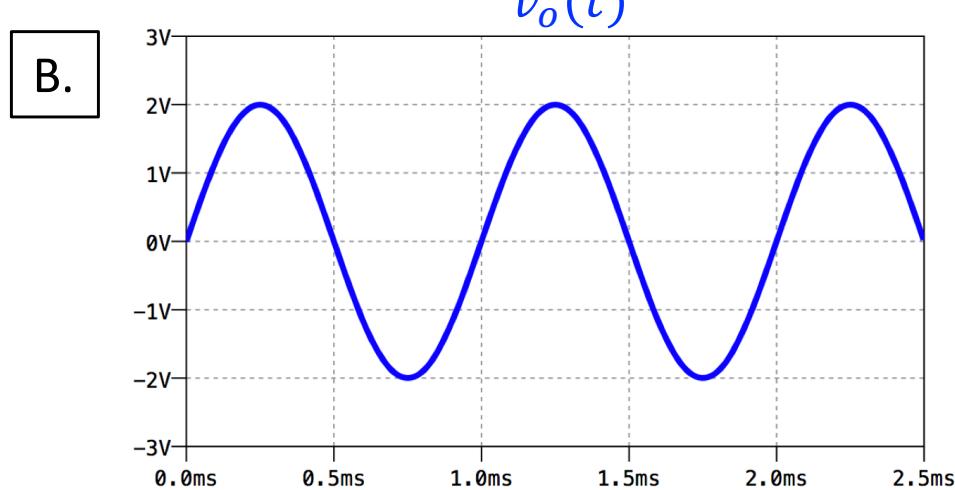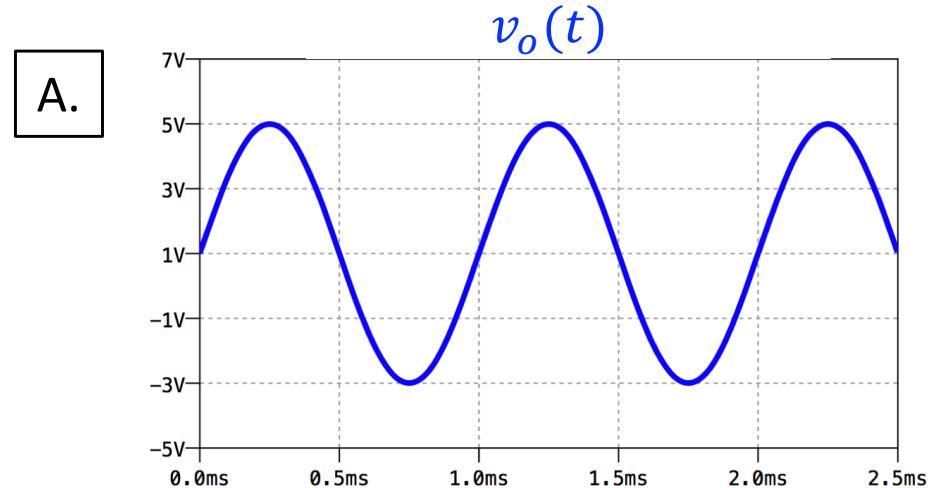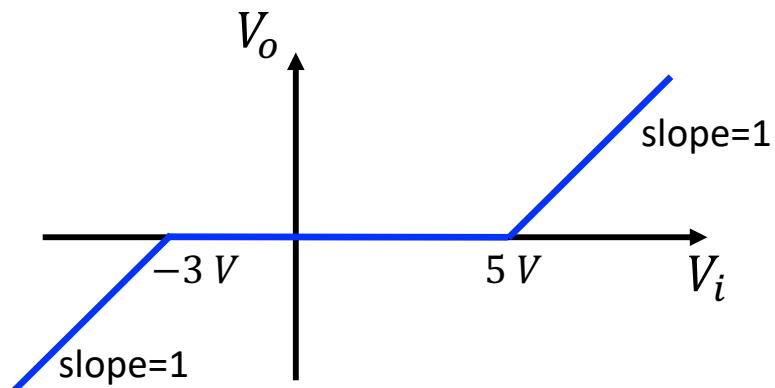
Which one of the waveforms could be the output of a two-port network with the below transfer function for the input $v_i(t) = 2\sin(\omega t)$?



Hints:

Clicker question 1


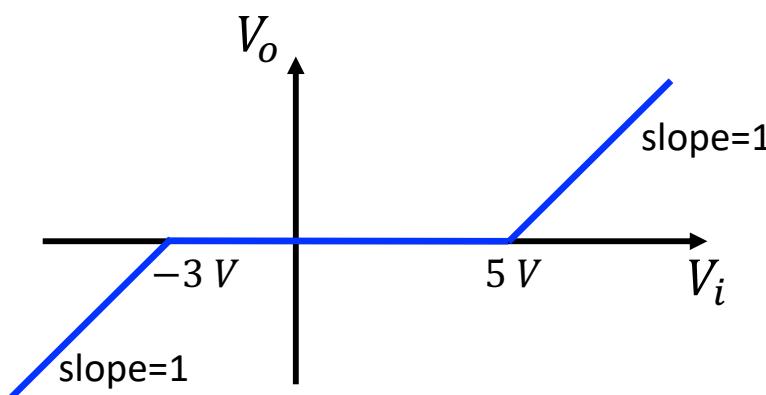
Which one of the waveforms could be the output of a two-port network with the below transfer function for the input $v_i(t) = 2\sin(\omega t)$?



- Looking at the transfer characteristic graph, for what range of V_i values, will the output be equal to zero?
- What is the range of V_i values for the given input signal?

Discussion question 1.

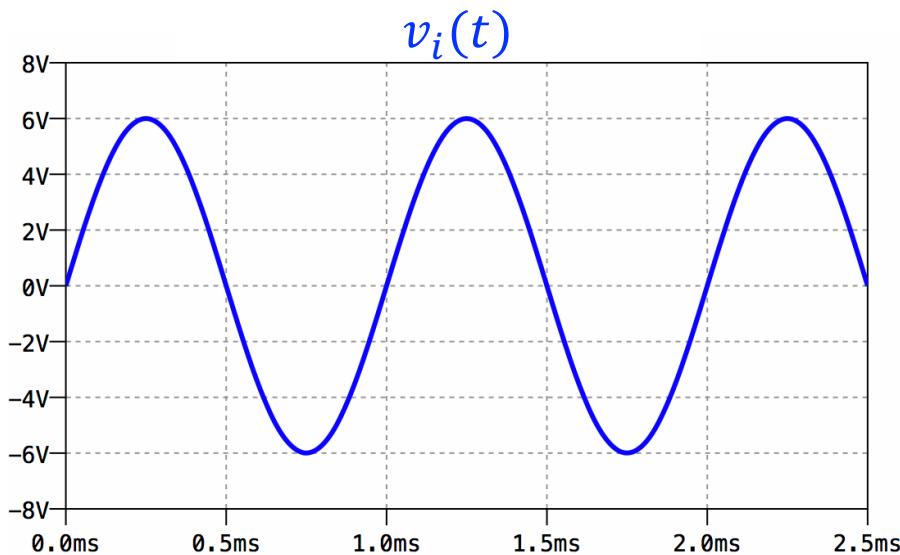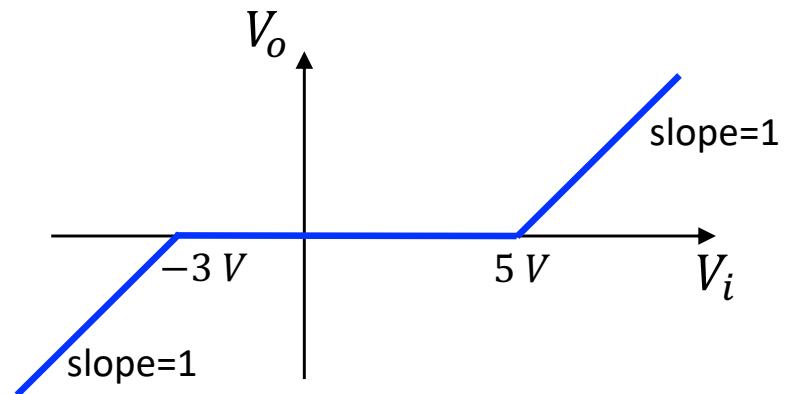Draw the output of a two-port network with the shown transfer function to the below input signal.





Hints:

Discussion question 1.


Draw the output of a two-port network with the shown transfer function to the below input signal.

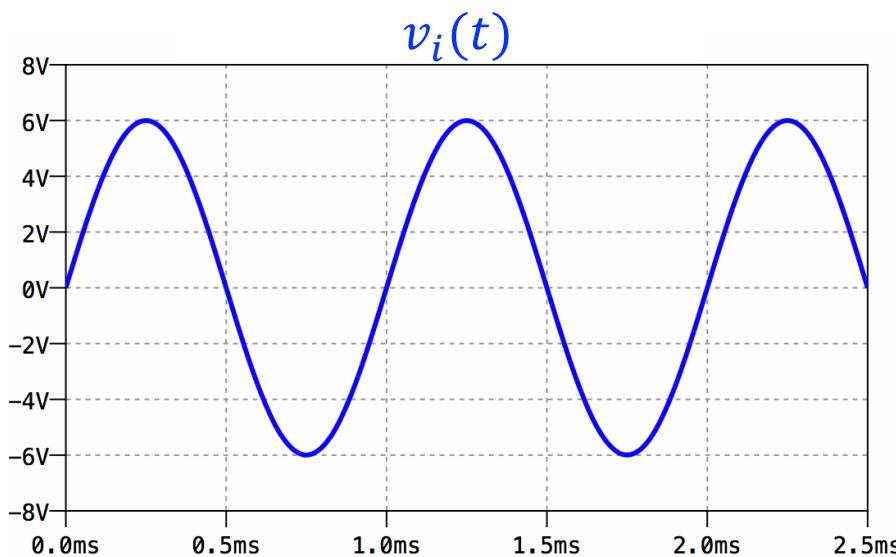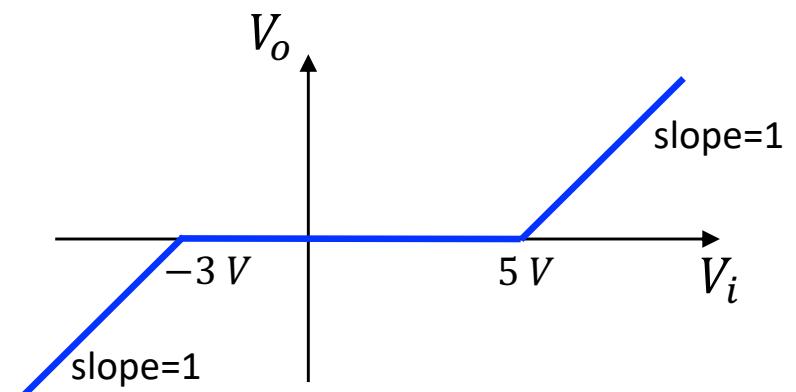- Write the equation of a line that relates V_o to V_i when V_i is greater than 5V?
- Write the equation of a line that relates V_o to V_i when V_i is less than -3V?
- On the graph of $v_i(t)$, find and label when v_i is less than -3, greater than 5, and in between. Follow the V_i vs. V_o equations that you found and draw $v_o(t)$.



Discussion question 2

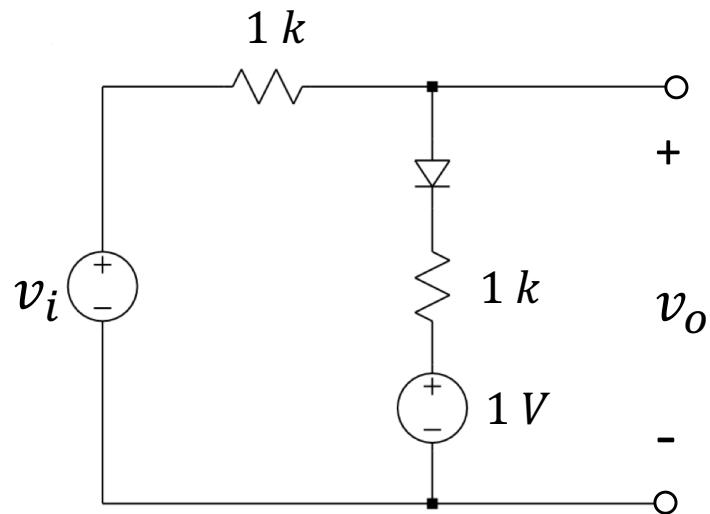Calculate and draw the transfer function for the following two-port network.
 $(V_{D0} = 0.7V)$




Hints:

Discussion question 2

Calculate and draw the transfer function for the following two-port network.

$$(V_{D0} = 0.7V)$$

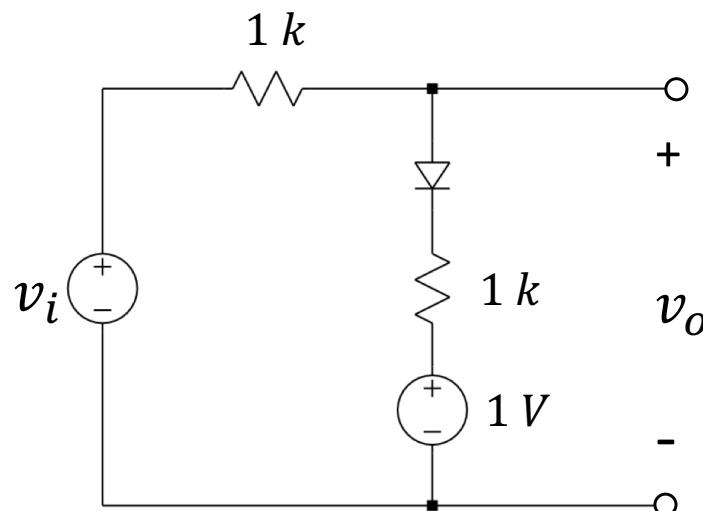

- Label the diode voltage and current.
- List the cases of operation of the diode. You have two cases in this circuit.
- You need to find the range of v_i values for each case and the relationship between v_i and v_o for each case.
- Use KVL to complete the above task.
- Using the ranges of v_i and the relationship between V_i and V_o for each range, draw the transfer function or transfer characteristic graph, which is a graph showing the relationship between V_o and V_i .

ECE 65: Components & Circuits Lab

Lecture 8

Diode waveform shaping circuits

Peak detector circuits


Reference notes: sections 2.9

Sedra & Smith (7th Ed): sections 4.4-4.6


Saharnaz Baghdadchi

Course map


2. Diodes

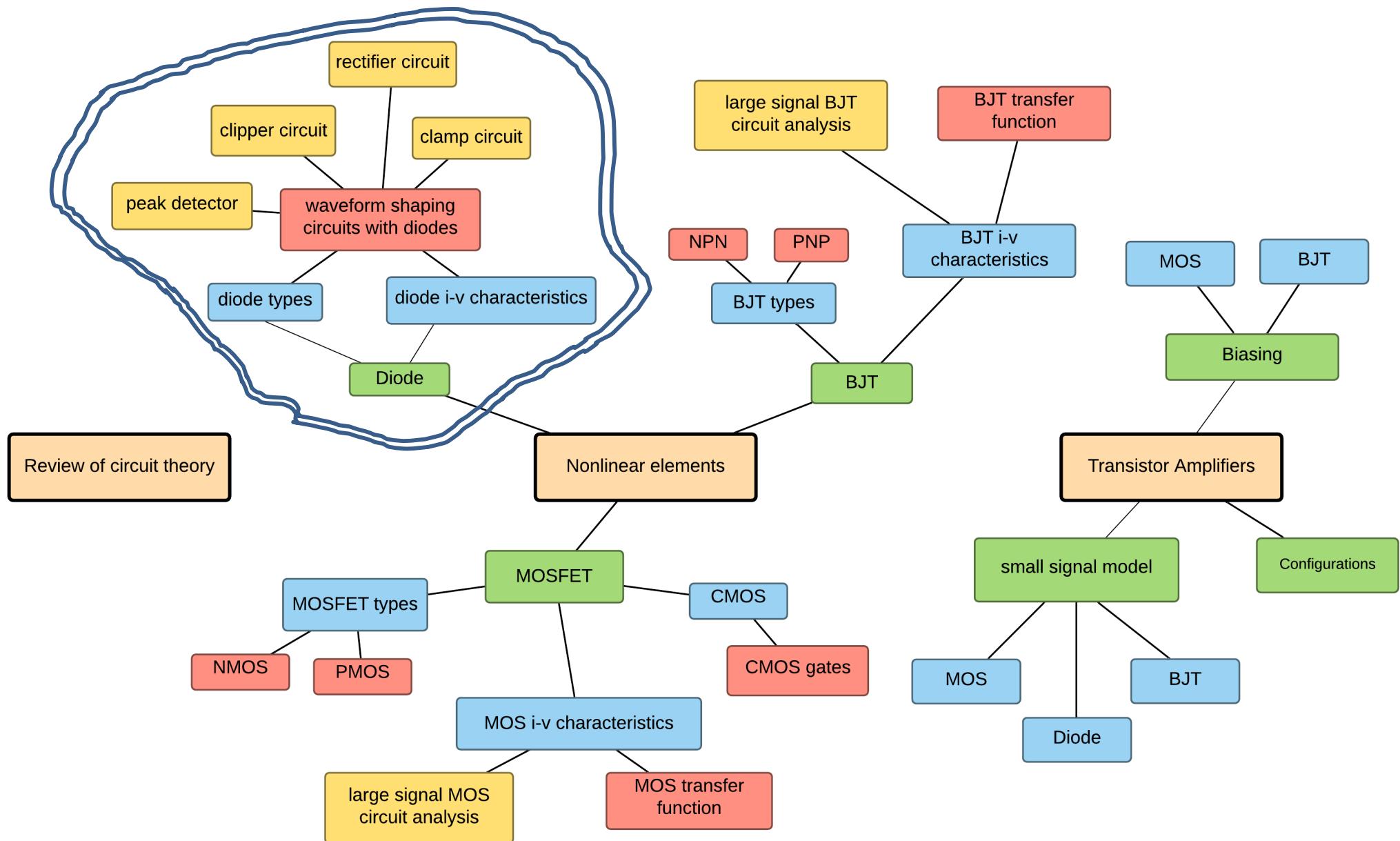


Ideal Peak Detector Circuit

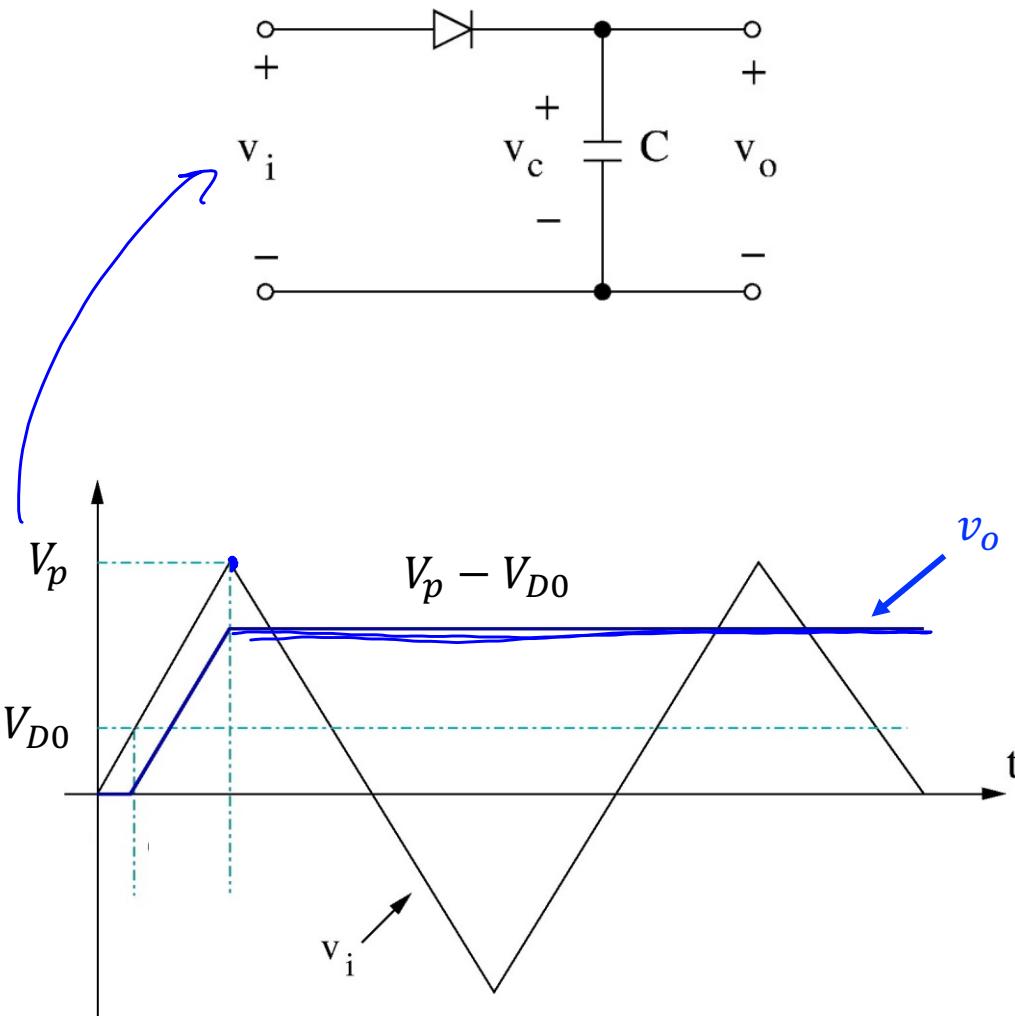

Ideal Peak Detector Circuit

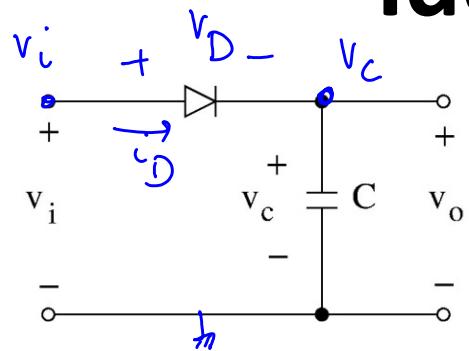


When the Diode is initially OFF:

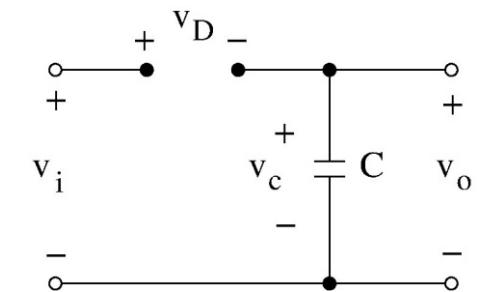


$$v_D = v_i - v_c = v_i$$

$$i_D = 0, \quad v_D < v_{D0}$$


$$\Rightarrow v_i < v_{D0}$$

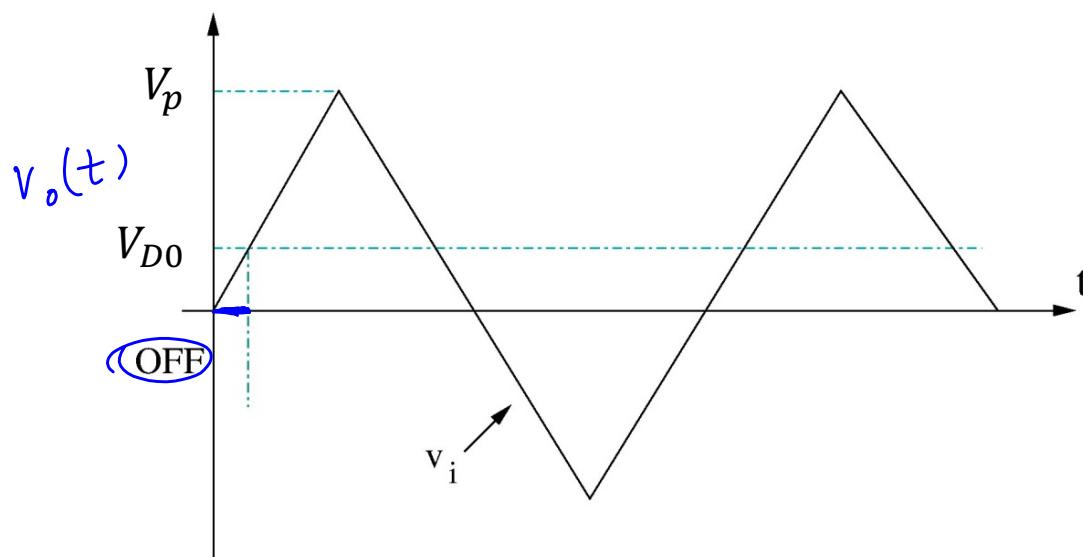

Ideal Peak Detector Circuit

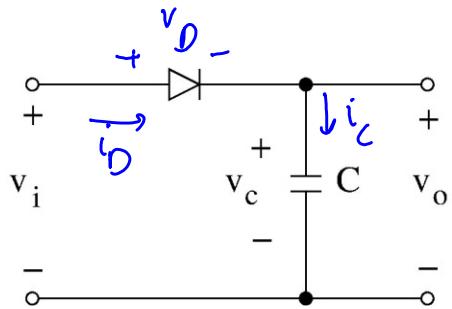

When the Diode is ON:

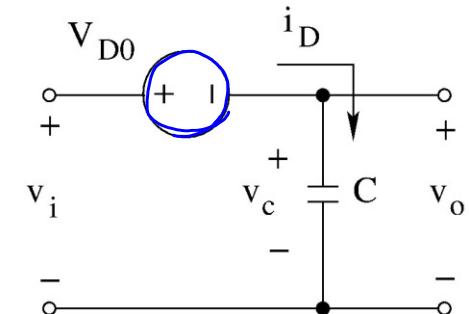


$$V_D = V_{D_0}$$

$$\dot{i}_D > 0$$

$$V_o = -V_D + V_i = -V_{D_0} + V_i$$


$$, \dot{i}_D = \dot{i}_C = C \frac{d v_C}{d t} = C \frac{d (V_i - V_{D_0})}{d t}$$

$$= C \frac{d V_i}{d t}$$


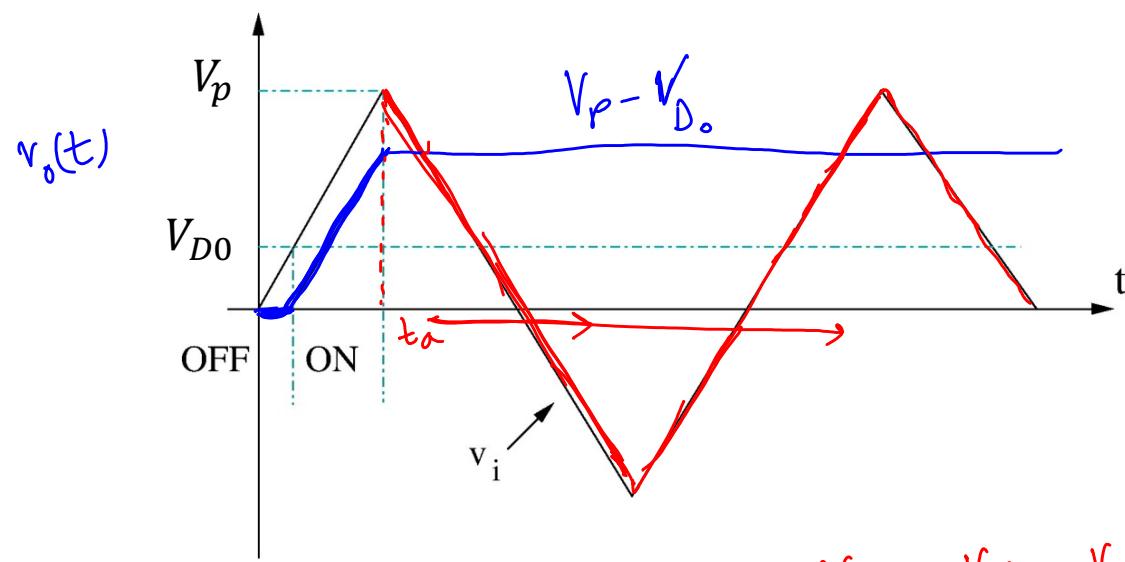


$$\text{at } t=t_a, V_i = V_p, V_C = V_p - V_{D_0}, V_o = V_i - V_C = V_i - (V_p - V_{D_0})$$


Ideal Peak Detector Circuit

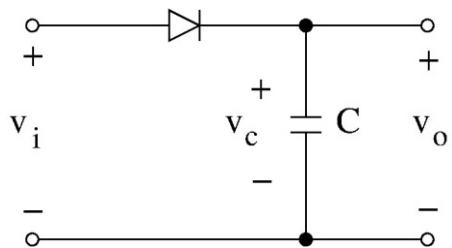

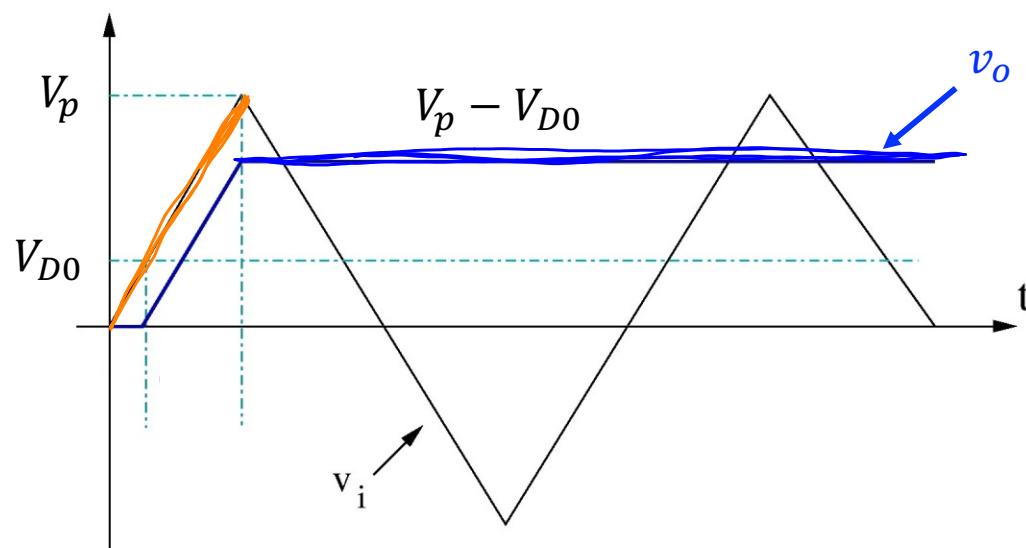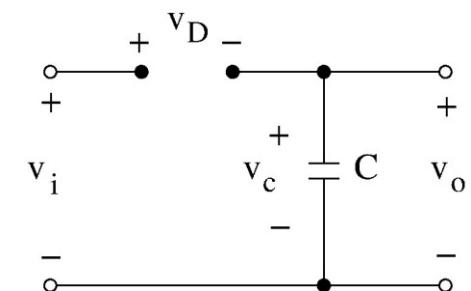After v_i reached its peak value, the diode does not turn ON anymore.




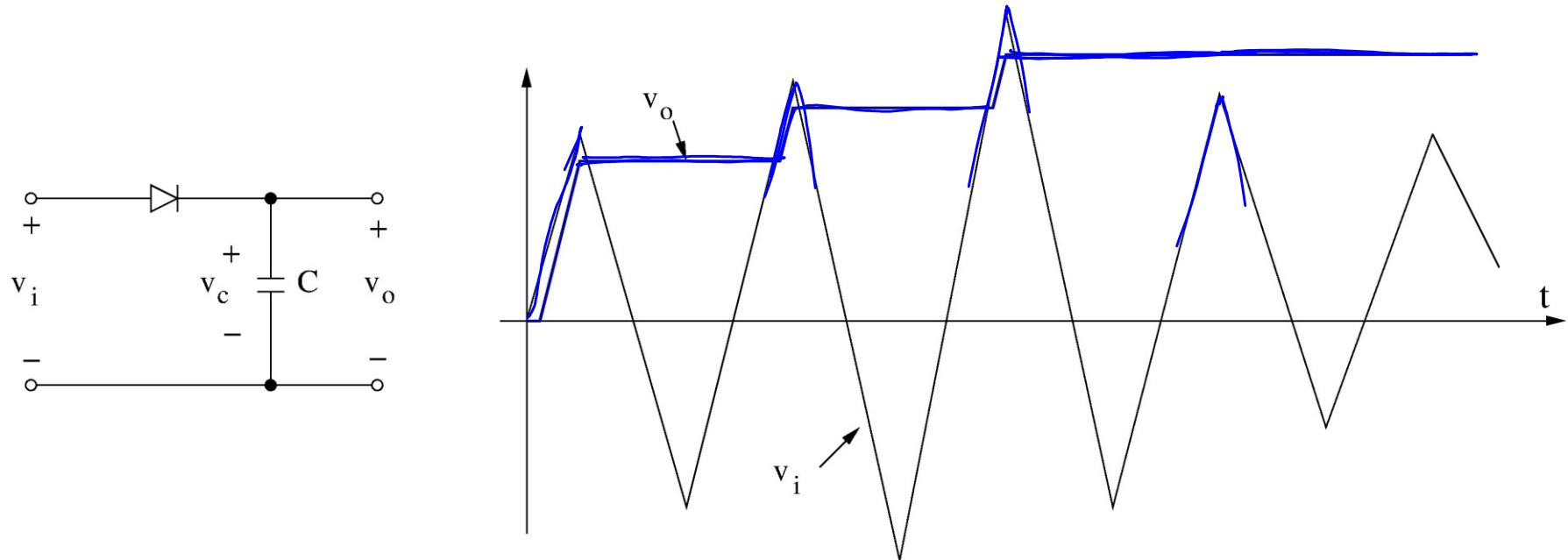
Response of the Ideal Peak Detector (v_i amplitude changes)



v_o is the “peak” value of input waveform ($V_p - V_{D0}$):


Note v_o did not “drop” after the peak was decreased in the 3rd cycle.

Practical Peak Detector Circuit

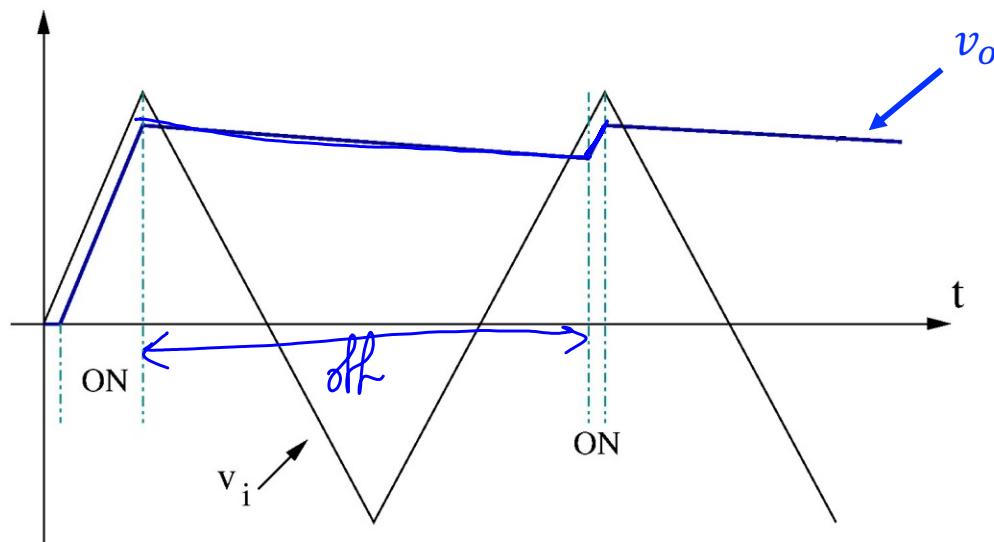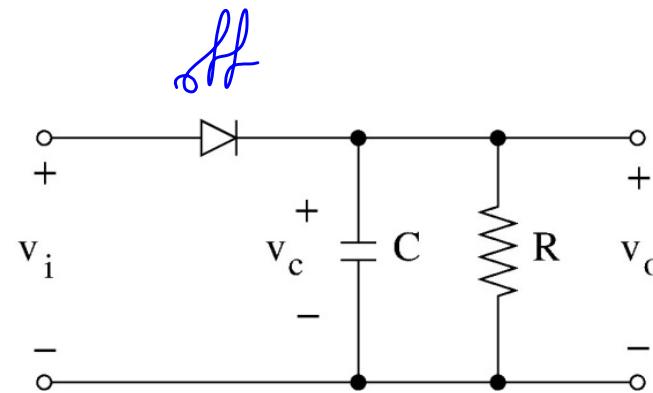

Practical Peak Detector Circuit

Diode OFF: $i_D = 0$ and $v_D < V_{D0}$


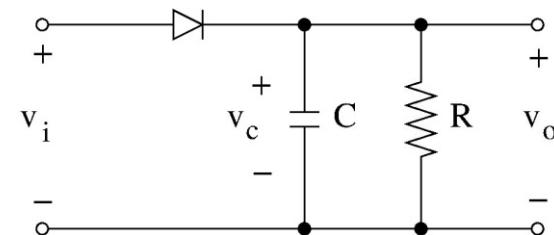


Capacitor discharges into the resistor with a time constant of $\tau = RC$

$$v_o = v_c(t) = v_{c0} e^{-(t-t_0)/\tau}$$

$$v_D = v_i - v_c < V_{D0}$$

$$\rightarrow v_i < v_c(t) + V_{D0}$$


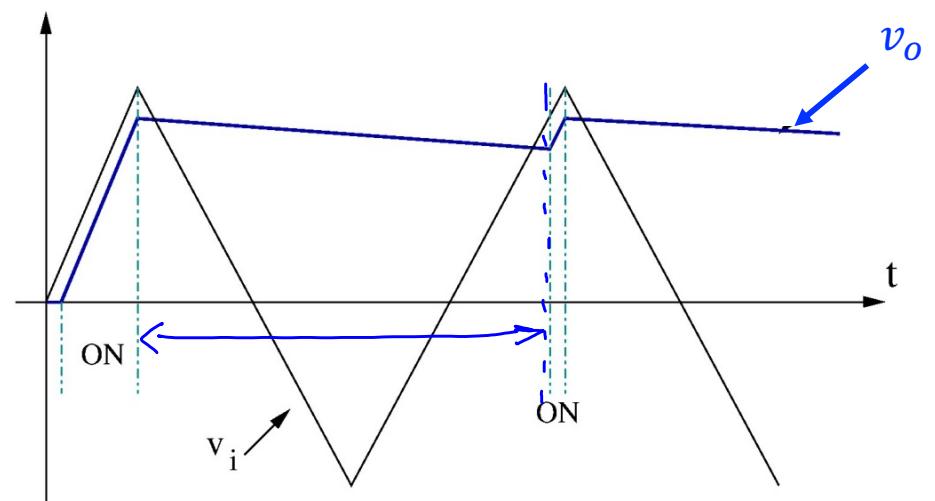
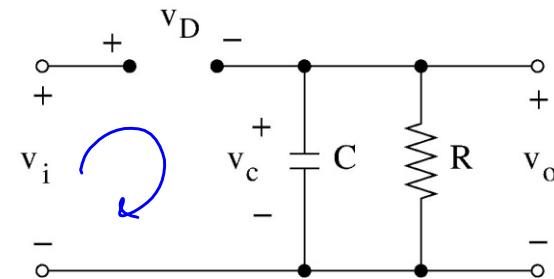


Practical Peak Detector Circuit

Diode ON: $v_D = V_{D0}$ and $i_D \geq 0$

$$v_o = v_c = v_i - V_{D0}$$
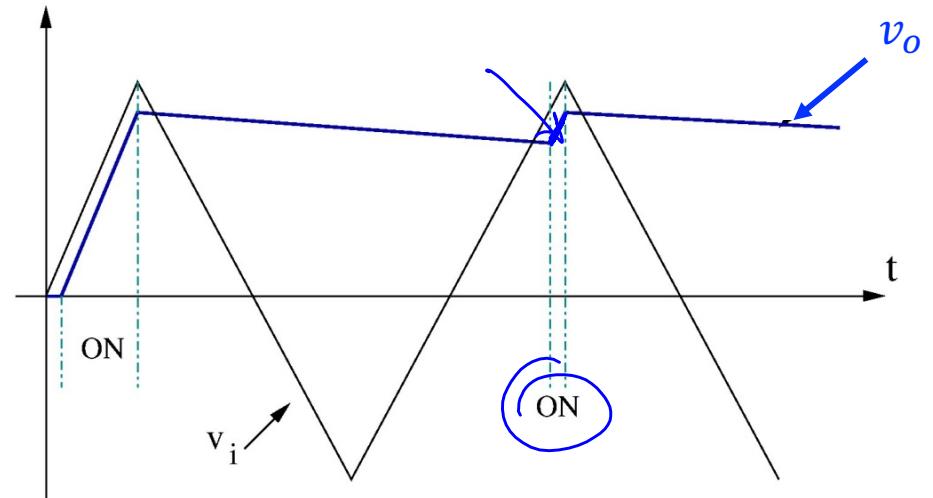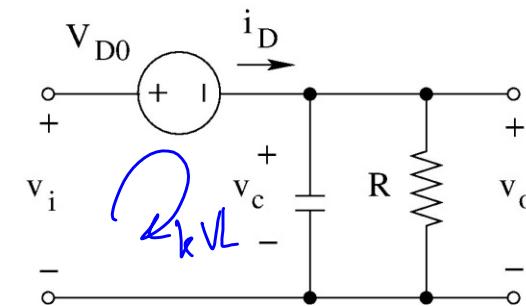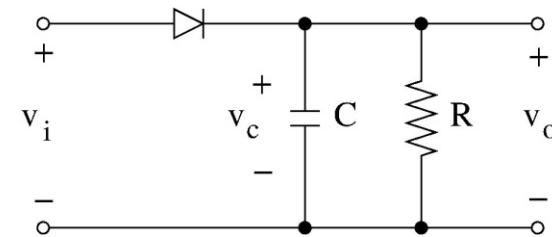
$$i_C = C \frac{dv_C}{dt} = C \frac{d(v_i - V_{D0})}{dt} = C \frac{dv_i}{dt}$$



Response of the Practical Peak Detector

Shape of output signal depends on the ratio of τ/T



“ideal” peak detector: $\tau/T \rightarrow \infty$

“Good” peak detector: $\tau/T \gg 1$

As τ/T decreases, the circuit departs from a peak detector.


For $\tau/T \ll 1$, capacitor discharges very fast and circuit resembles a rectifier circuit

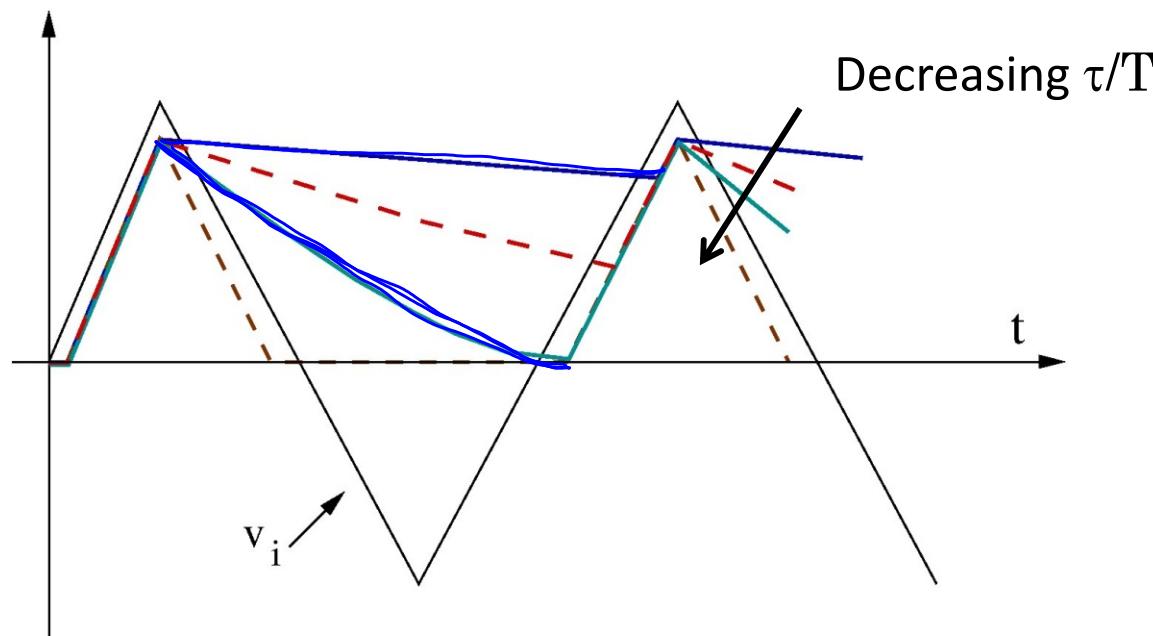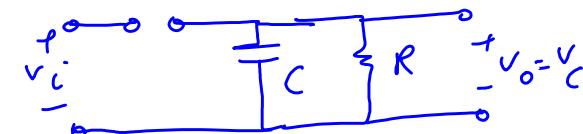τ : time constant = RC
 T : period of $v_i(t)$




Lecture 8 reading quiz.

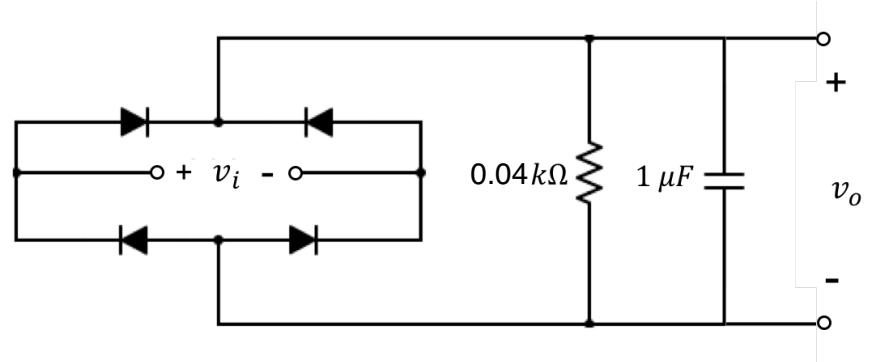
In the following diode circuit, which one of the options could be the input and output voltages for this circuit? $V_{D0} = 0.7 \text{ V}$.




A.

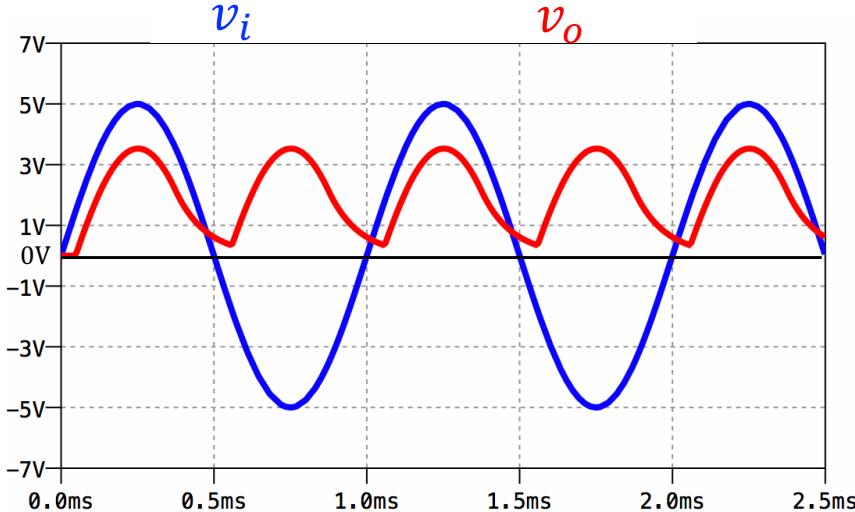


C.

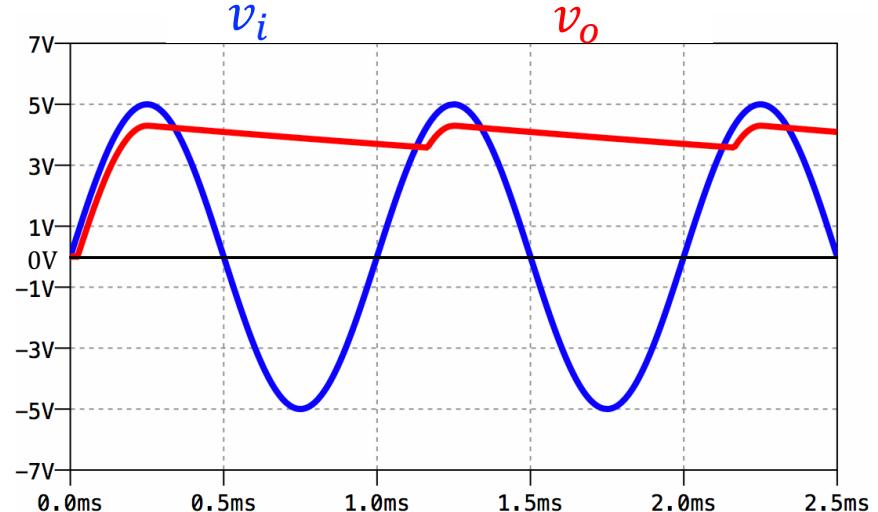

B.

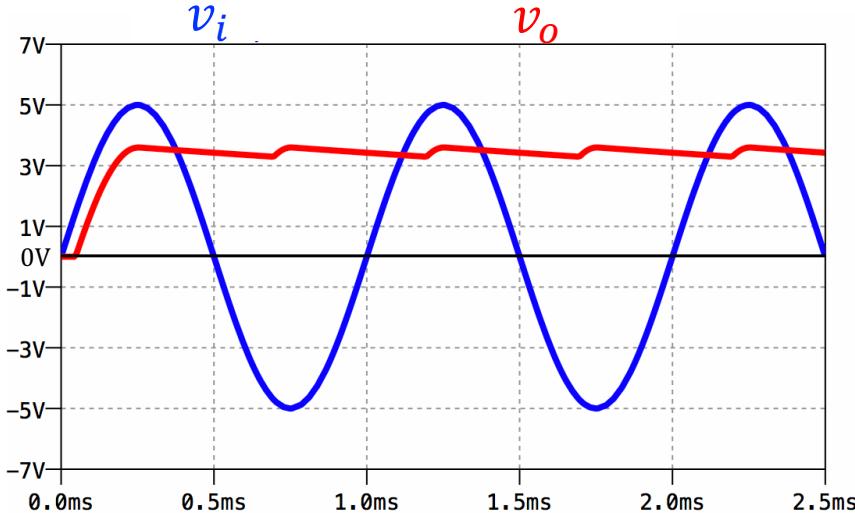


D.

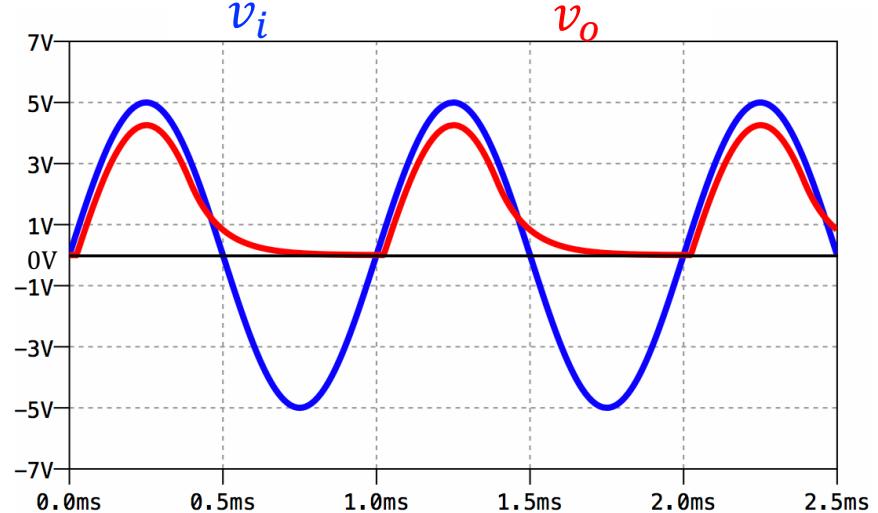

Discussion question 1.

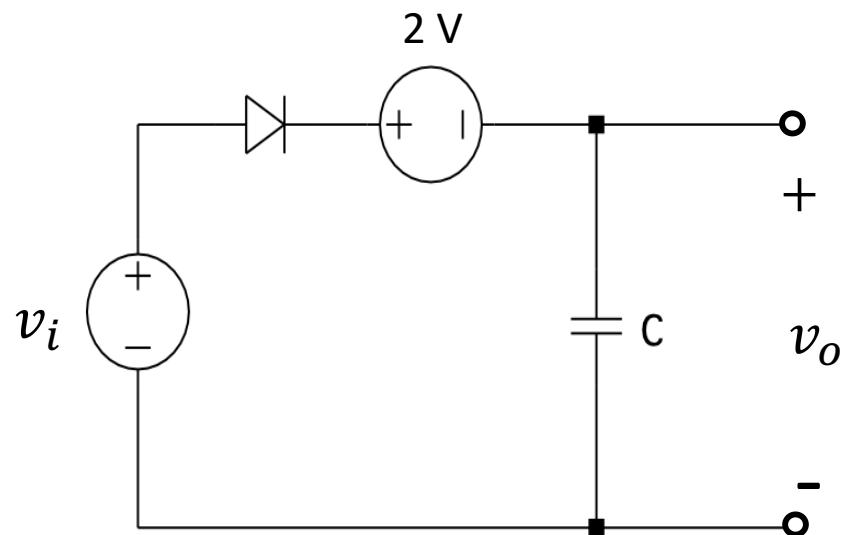In the circuit below, $v_i(t) = 10 \sin(\omega t)$ where $\omega=1000 \text{ rad/s}$, $v_c(0) = 0$. $V_{D0} = 0.7 \text{ V}$. What is the value of $v_o(t)$ at $t = 1\text{ms}$ and $t=2 \text{ ms}$? Draw one cycle of the input and output waveforms.




Hints:

Discussion question 1.

In the circuit below, $v_i(t) = 10 \sin(\omega t)$ where $\omega=1000 \text{ rad/s}$, $v_c(0) = 0$.

$V_{D0} = 0.7 \text{ V}$. What is the value of $v_o(t)$ at $t = 1\text{ms}$ and $t=2 \text{ ms}$? Draw one cycle of the input and output waveforms.

- Find the period of the input sinusoidal waveform.
 $T = 2\pi/\omega$
- Find the minimum amplitude of v_i to turn the diode ON. You should write a KVL in the circuit to get the answer. Note that $V_c(0)=0$
- The diode will conduct until v_i reaches its peak amplitude. Then, it will disconnect.
- Find the time point at which v_i reaches its peak amplitude and compare it with the given time points, $t = 1\text{ms}$ and 2ms . The relationship between v_{out} and v_i will be different at different time points.

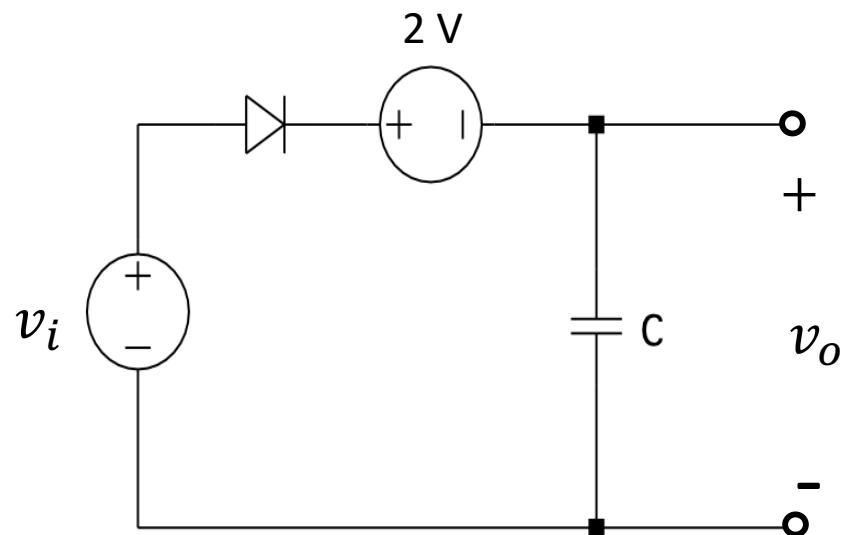


Discussion question 2.

Design a clipper circuit that limits voltages above 6 V. You can use any combination of regular PN junction diodes, Zener diodes or DC sources.

Extra problem for practice

Find v_R and i in the below circuit for $-5 \text{ V} \leq v_i \leq 5 \text{ V}$.

(Assume Si diodes with $V_{D0} = 0.7 \text{ V}$)

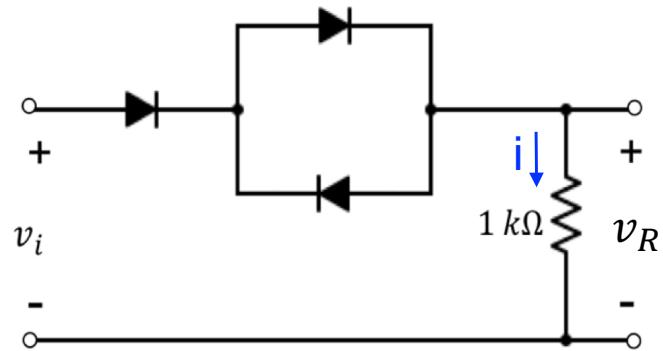

ECE 65: Components & Circuits Lab

Lecture 9

Diode waveform shaping circuits

Clamp circuits


Reference notes: sections 2.9

Sedra & Smith (7th Ed): sections 4.4-4.6

Saharnaz Baghdadchi



Course map

2. Diodes


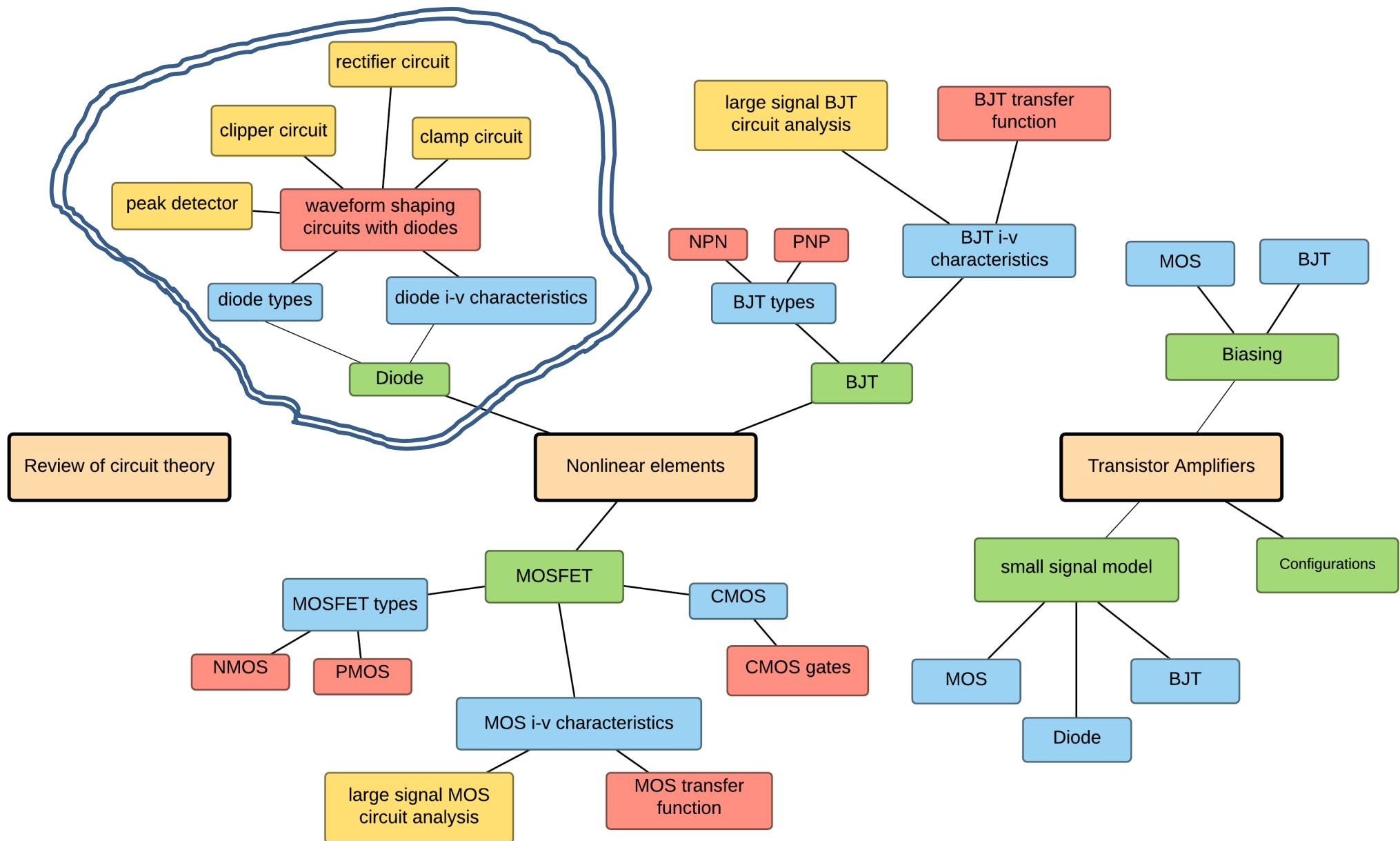


Clamp circuit and peak detector circuit

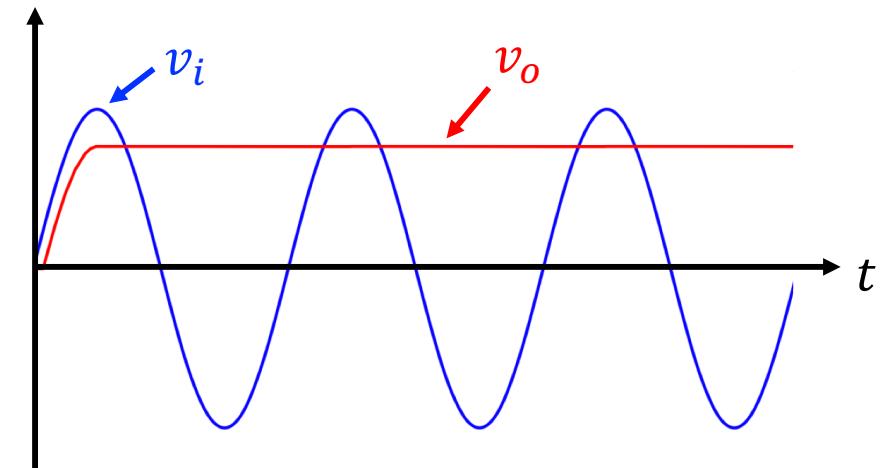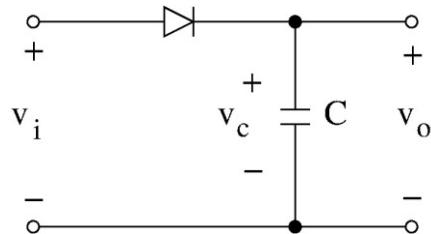Ideal peak detector:
 $v_o = V_p - V_{D0}$




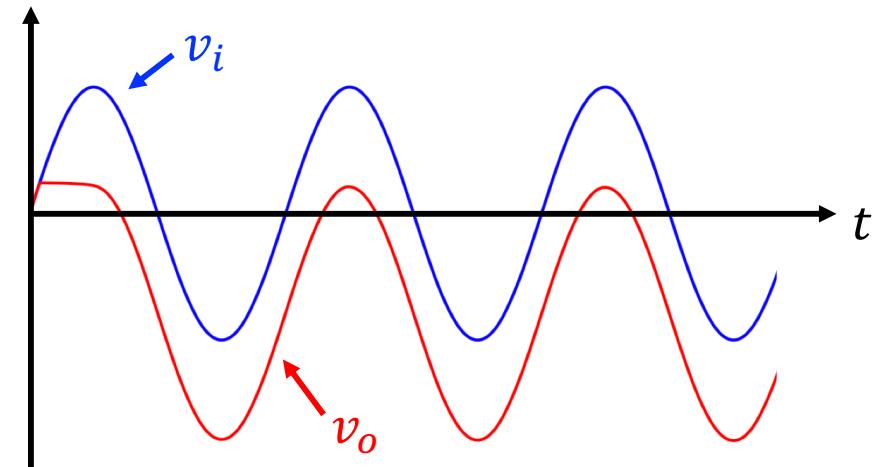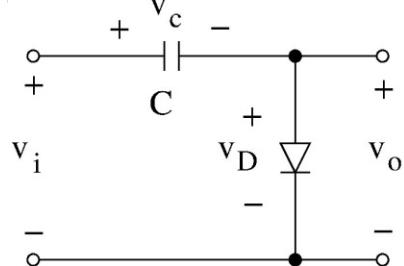Clamp circuit:
 $v_o = v_i - (V_p - V_{D0})$




Clamp Circuit

$$v_D = -v_c + v_i$$

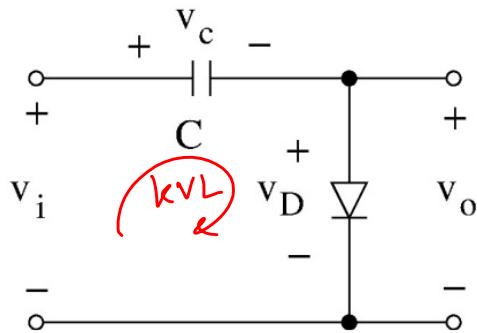

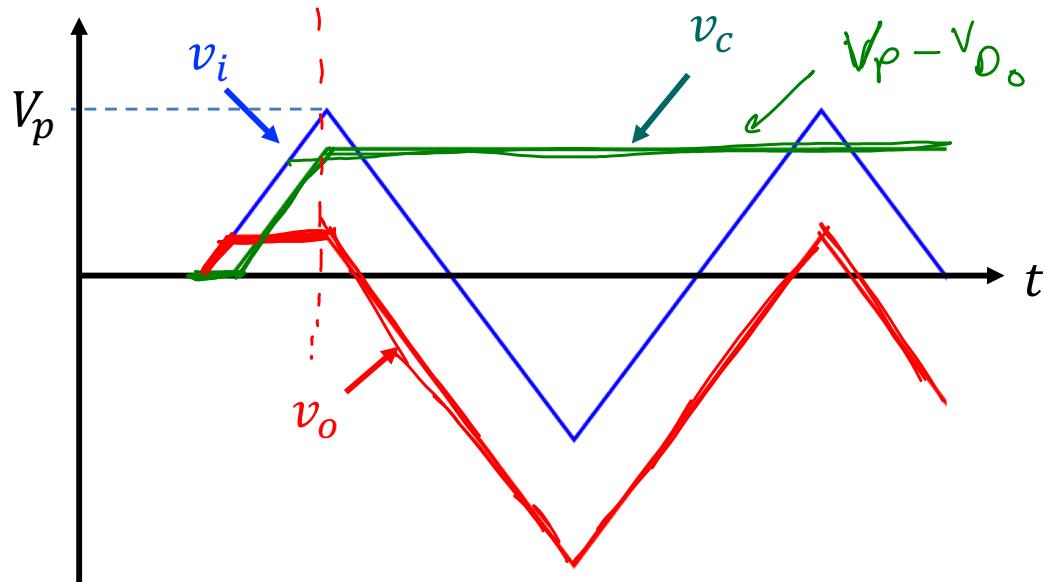The diode turns OFF when the capacitor is charged to $v_c = V_p - V_{D0}$







$$v_o = v_D = v_i - v_c$$

Diode off:


$$v_o = \underline{v_i} - (V_p - V_{D0})$$

Clamp Circuit with a Load

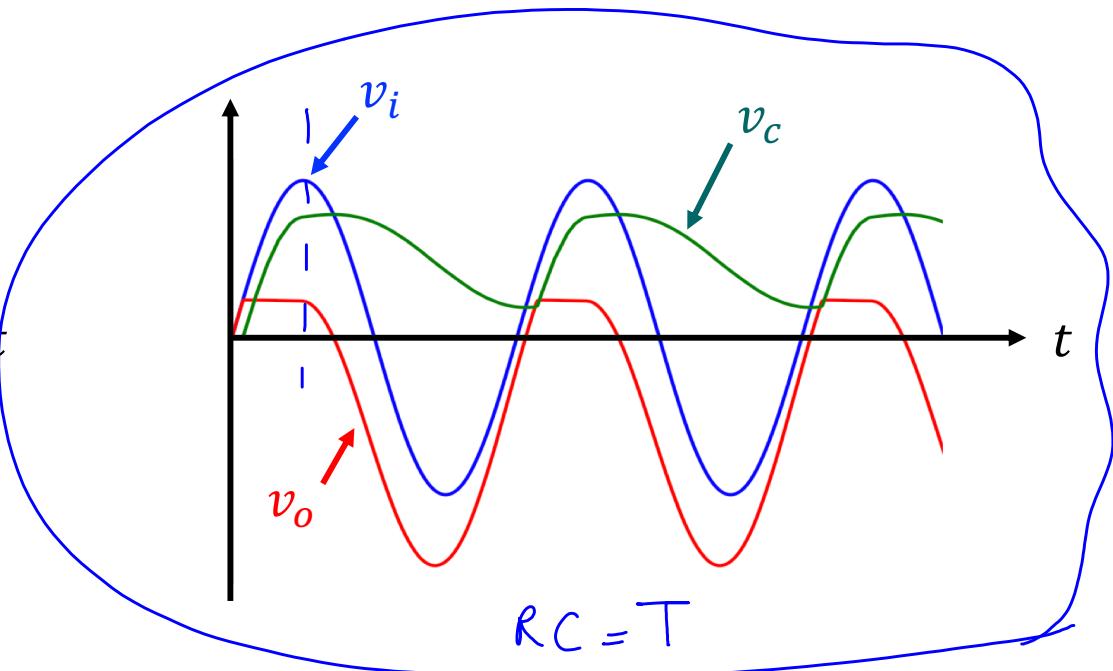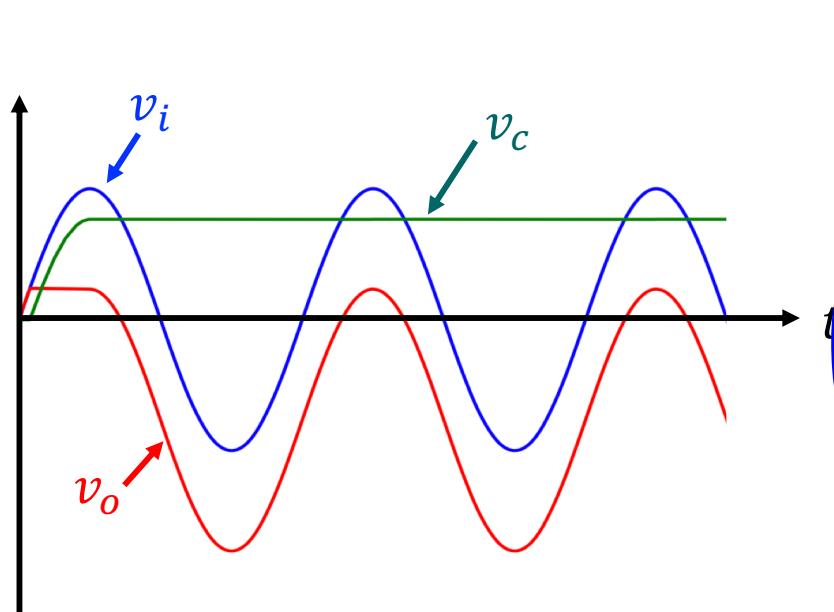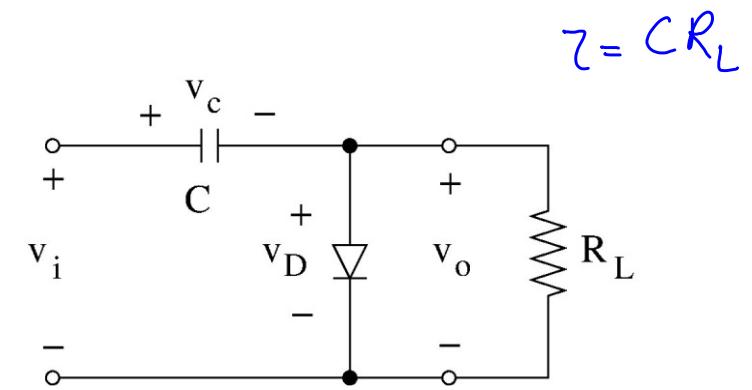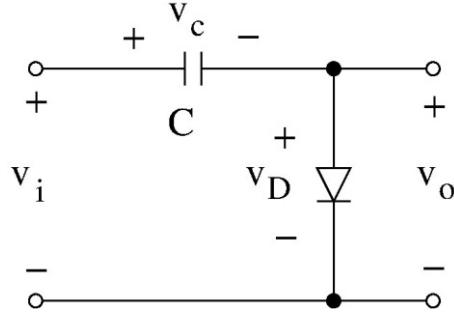

If $\tau = R_L C \gg T$ capacitor does not discharge substantially and clamp circuits works fine

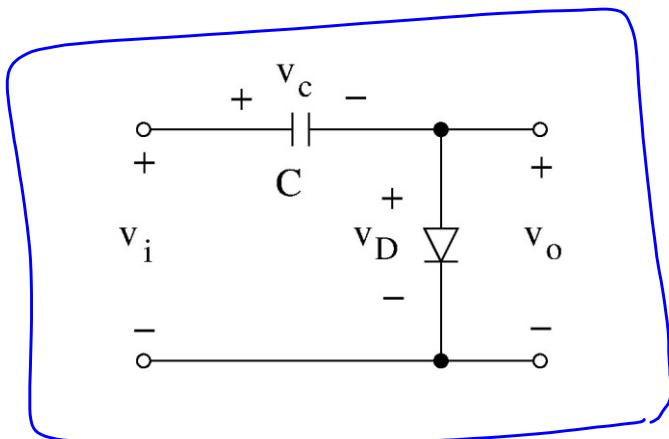
Voltage shift in a clamp circuit can be adjusted



$$V_C = V_P - V_{D_0}$$

$$V_o = -V_C + V_i$$


$$V_o = V_i - \boxed{(V_P - V_{D_0})}$$

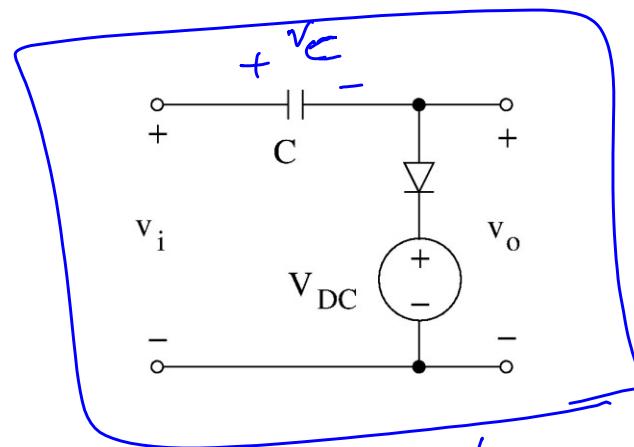

$$V_C = V_P - (V_{D_0} + V_{DC})$$

$$V_o = -V_C + V_i$$
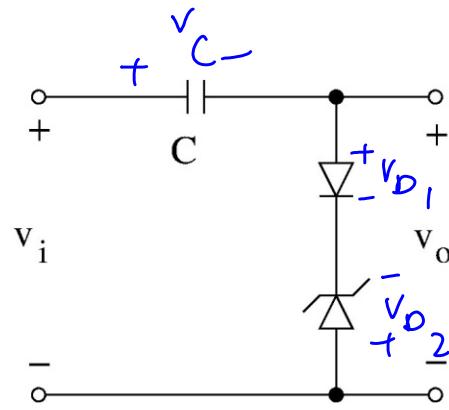
$$= V_i - \boxed{(V_P - V_{D_0} - V_{DC})}$$




$$V_o = -V_C + V_i$$


$$= V_i - (V_P - V_{D_0} - V_Z)$$

Clamp circuit can introduce a “positive” shift by reversing the diode terminals


Peak detector (diode is reversed):

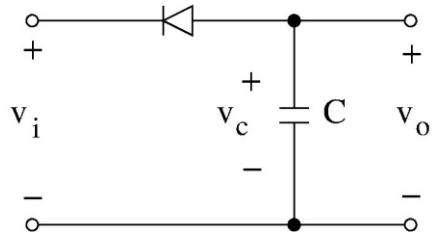

$$V_o = -V_c + V_i$$

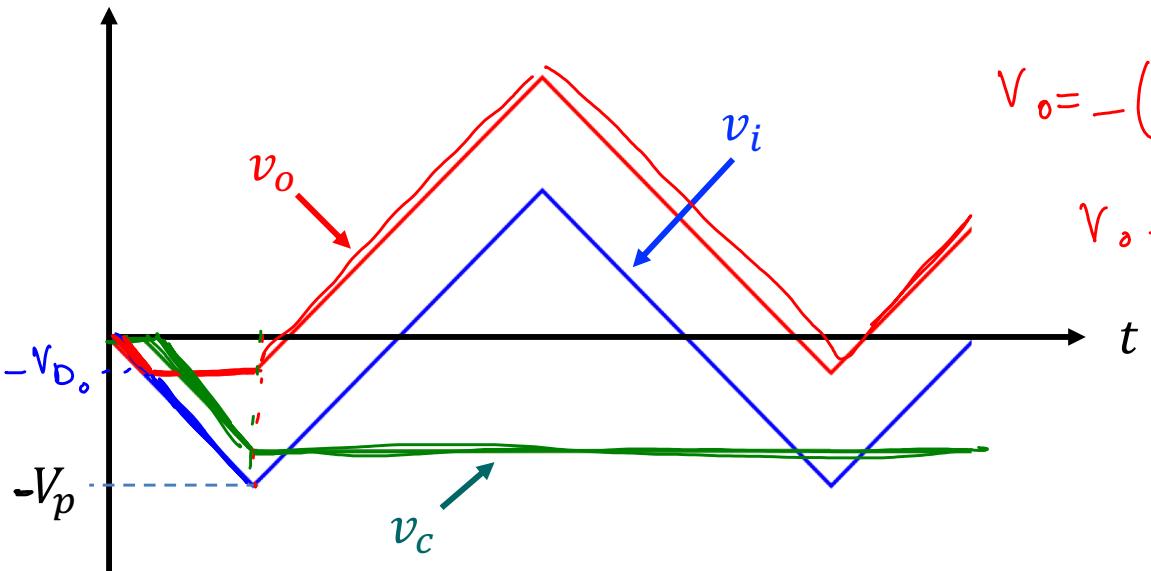

Clamp circuit (diode reversed):

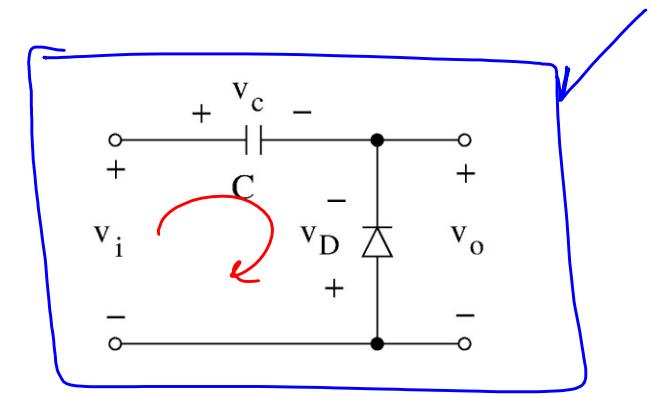

$$V_D = -V_i + V_c = -V_i$$

$$V_o = -(-V_p + V_{D_0}) + V_i$$

$$V_o = V_i + (V_p - V_{D_0})$$

$$V_o = -V_D$$

$$\Rightarrow V_o = +V_i$$


$$V_o = -V_{D_0}$$

$$V_c = V_i + V_{D_0}$$

After the diode turned off


$$V_c = -V_p + V_{D_0}$$

The positive shift can also be adjusted.

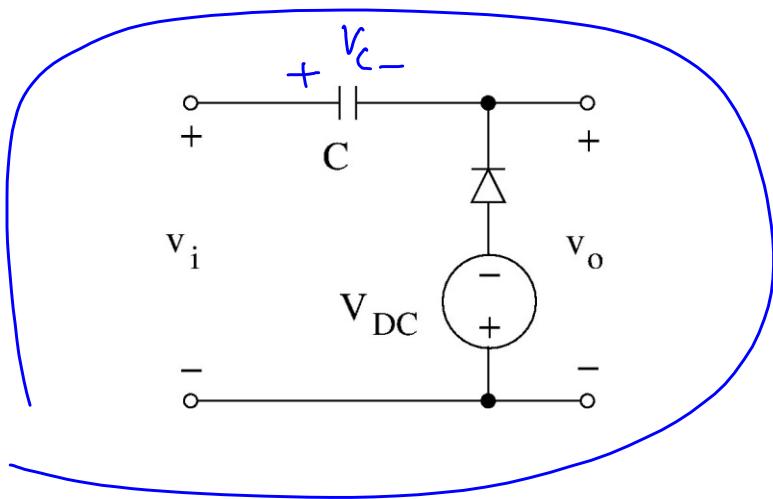

$$v_c = -v_p + V_{DC} + v_{D_o}$$


$$v_o = v_i + (v_p - V_{DC} - v_{D_o})$$

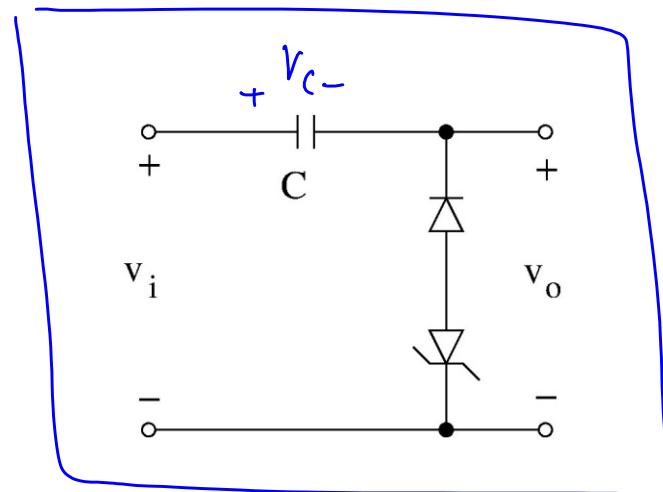

$$v_o = v_i + (v_p - v_z - v_{D_o})$$

Lecture 9 reading quiz

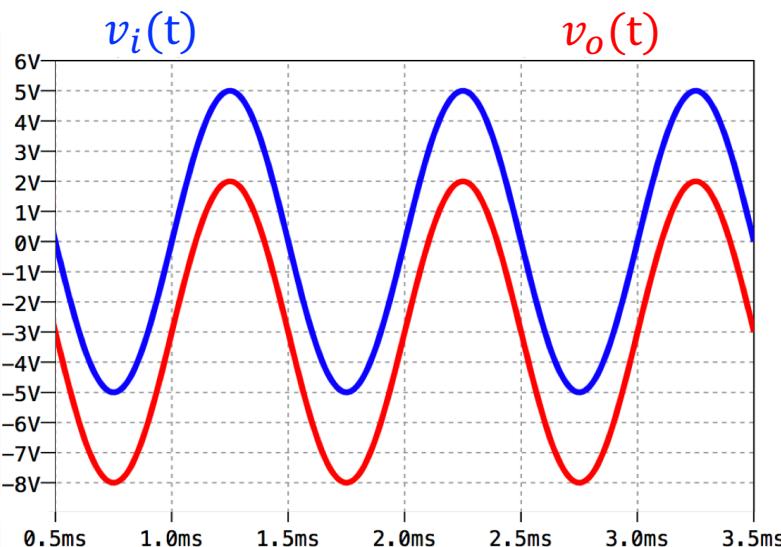Which one of the circuits in the provided options could produce the shown output waveform for the given input signal?



Discussion question 1

Consider a sinusoidal source $v_i(t) = 10 \sin(\omega t)$ V. Using a DC power supply, design a clamp circuit that adds a DC offset of 5V to $v_i(t)$. Draw two cycles of the input and output voltage waveforms.

Hints:

Discussion question 1

Consider a sinusoidal source $v_i(t) = 10 \sin(\omega t)$ V. Using a DC power supply, design a clamp circuit that adds a DC offset of 5V to $v_i(t)$. Draw two cycles of the input and output voltage waveforms.

- Check the lecture notes to see the structure of the clamp circuit that can add a positive DC shift to input signals.
 - You can use the equations included in the lecture notes to find the required amplitude of VDC to have the +5V DC shift.
 - After drawing the circuit structure, solve the circuit to find v_{out} as a function of v_i for different time intervals.
 - You need to find the minimum value of v_i to turn on the diode. You also need to find out for how long the diode can stay on and what happens when the diode turns off.
 - Draw $v_i(t)$ and $v_{out}(t)$ on the same graph.
-
- You can also draw the clamp circuit structure with a DC source with an unknown amplitude and solve the circuit to find the amplitude of the DC source.

Clicker question 1.

In the circuit below, $v_i(t) = 10 \sin(\omega t)$ where $\omega=1000\text{rad/s}$, $v_o(0) = 0$. $V_{D0} = 0.7 \text{ V}$

What is the value of $v_o(t)$ at $t = 2 \text{ ms}$?

- A. $v_o(t = 2 \text{ ms}) = 1.8 \text{ V}$
- B. $v_o(t = 2 \text{ ms}) = 6.4 \text{ V}$
- C. $v_o(t = 2 \text{ ms}) = 2.7 \text{ V}$

