

ECE 65: Components & Circuits Lab

Lecture 5

Zener Diode


Reference notes: sections 2.1-2.8

Sedra & Smith (7th Ed): sections 4.3-4.4

Saharnaz Baghdadchi


Course map

2. Diodes

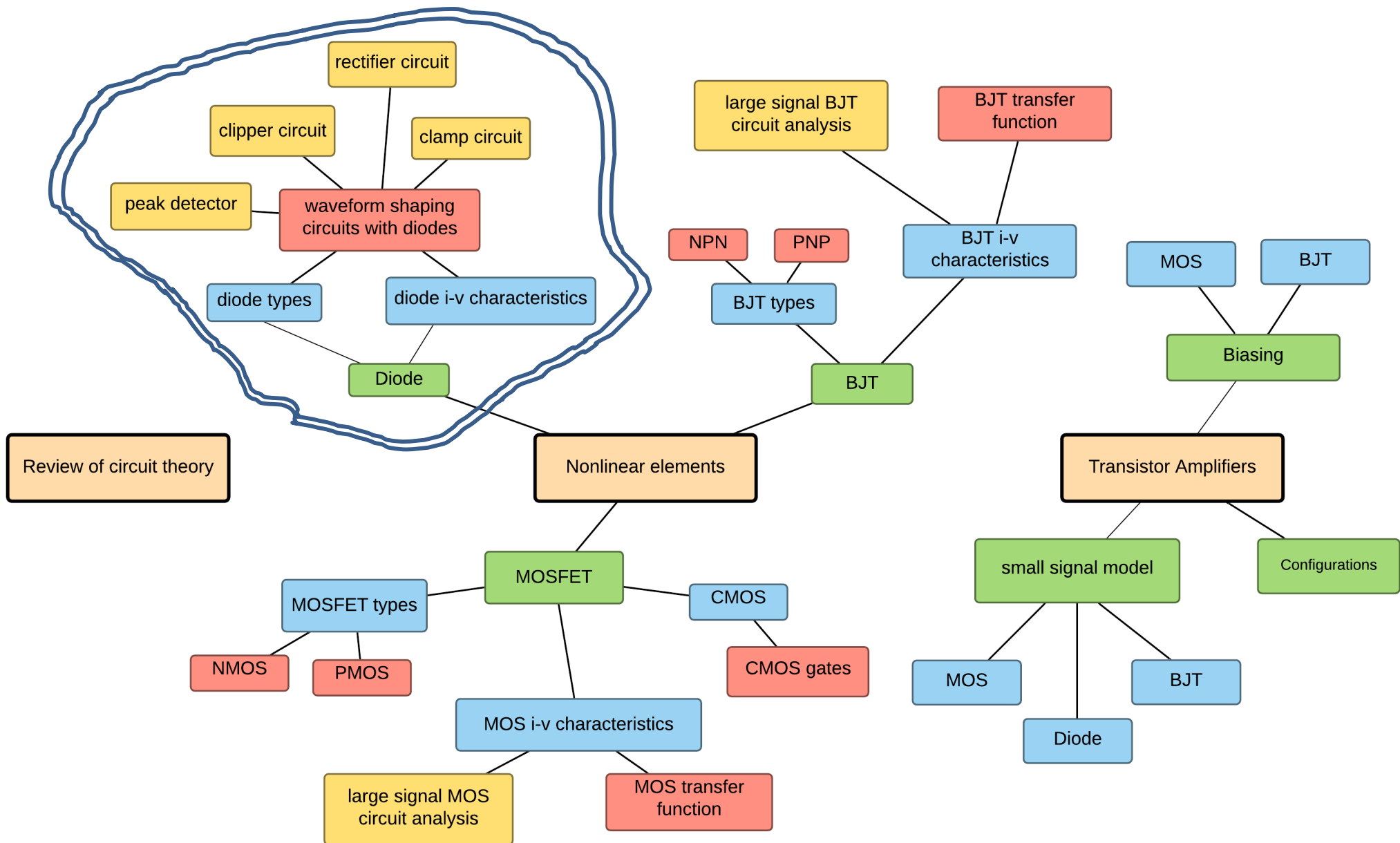


Other types of diodes

Light-emitting diode (LED)

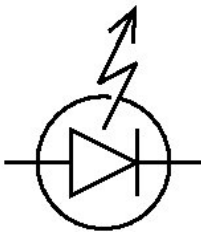

$$V_{D0} = 1.7 - 1.9 \text{ V}$$


Zener Diode

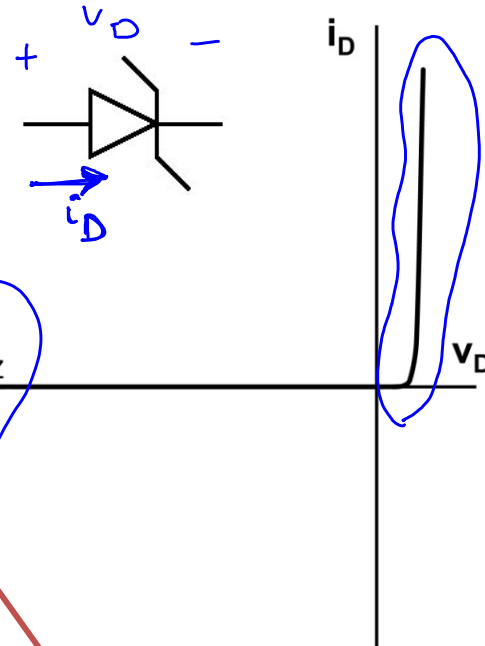

Made specially to operate in the reverse breakdown region.

Useful as a “reference” voltage in many circuits.

Zener Diode piecewise-linear model


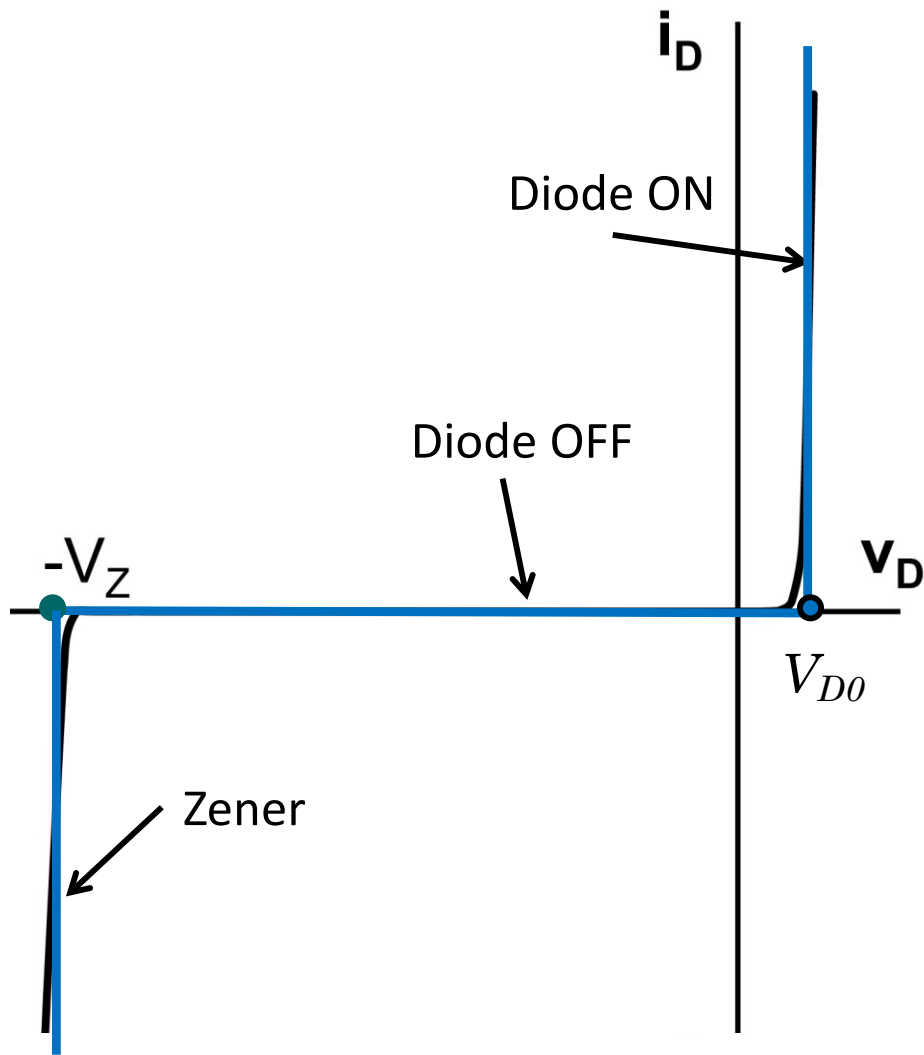


Diode ON: $v_D = V_{D0}$ and $i_D \geq 0$

Diode OFF: $i_D = 0$ and $-V_Z < v_D < V_{D0}$


Zener: $v_D = -V_Z$ and $i_D \leq 0$

Circuit Models:

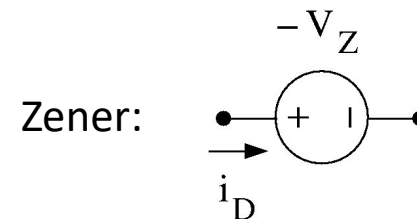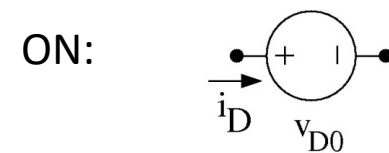

Zener Diode piecewise-linear model

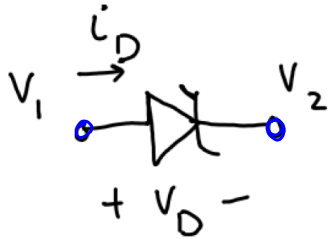Assume Zener diode with $V_D = 0.7\text{ V}$ and $V_Z = 5\text{ V}$.



- Ⓐ When $0 < V_1 - V_2 < 0.7$, diode is forward-biased, but it's not on, yet. $\Rightarrow i_D = 0$
- Ⓑ When $-5 < V_1 - V_2 < 0$, diode is reverse-biased, but it's not in the Zener region, so it's off. $\Rightarrow i_D = 0$
- Ⓒ When $V_1 - V_2 = 0.7$, diode is forward-biased and it's on $\Rightarrow i_D \geq 0$ and $V_D = V_{D_0} = 0.7\text{ V}$.
- Ⓓ When $V_1 - V_2 = -5\text{ V}$, diode is in Zener region, it conducts, $\Rightarrow i_D \leq 0$ and $V_D = -V_Z = -5\text{ V}$

Example:

In the following circuit, find i_L and v_L for $v_s = 10\text{ V}$. For what range of v_s and R_L the Zener diode will be in the Zener region and the circuit can operate as a voltage regulator? ($V_Z = 3\text{ V}$, $V_{D0} = 0.7\text{ V}$)


KCL:

$$\{ i_s + i_D - i_L = 0$$

KVL:

$$\{ v_s = R_s i_s - v_D$$
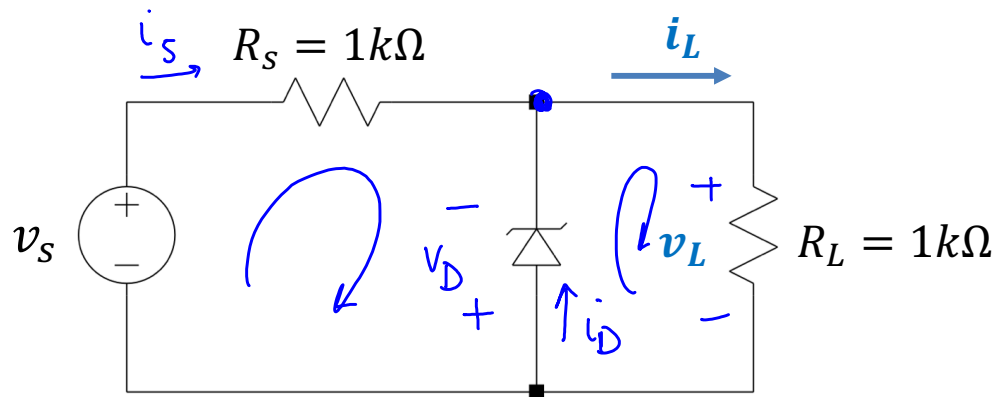
$$\{ v_D + v_L = 0 \rightarrow v_L = -v_D$$



Assume the diode is in the Zener region:

$$v_D = -V_Z, \quad i_D \leq 0$$

$$v_L = V_Z = 3\text{ V}$$

$$i_L = \frac{v_L}{R_L} = \frac{3\text{ V}}{1\text{ k}} = 3\text{ mA}, \quad i_L = 3\text{ mA}$$

$$i_s = \frac{v_s + v_D}{R_s} = \frac{10\text{ V} - 3\text{ V}}{1\text{ k}}$$

$$i_s = 7\text{ mA}$$

$$i_D = i_L - i_s = 3\text{ mA} - 7\text{ mA} = -4\text{ mA} < 0$$

when the diode is in the Zener region, $i_D \leq 0$.

$$i_D = i_L - i_S \leq 0 \longrightarrow i_S \geq i_L$$

$$V_L = V_Z, \quad i_L = \frac{V_L}{R_L} = \frac{V_Z}{R_L}$$

$$i_S = \frac{V_S - V_Z}{R_S}$$


$$\frac{V_S - V_Z}{R_S} \geq \frac{V_Z}{R_L}$$

$$\frac{V_S}{R_S} \geq V_Z \left(\frac{1}{R_L} + \frac{1}{R_S} \right) \longrightarrow V_S \geq \underline{\underline{V_Z \left(1 + \frac{R_S}{R_L} \right)}}$$

$$\frac{V_S/V_Z - 1}{R_S} \geq \frac{1}{R_L} \longrightarrow R_L \geq \frac{R_S}{V_S/V_Z - 1}$$

Lecture 3 reading quiz

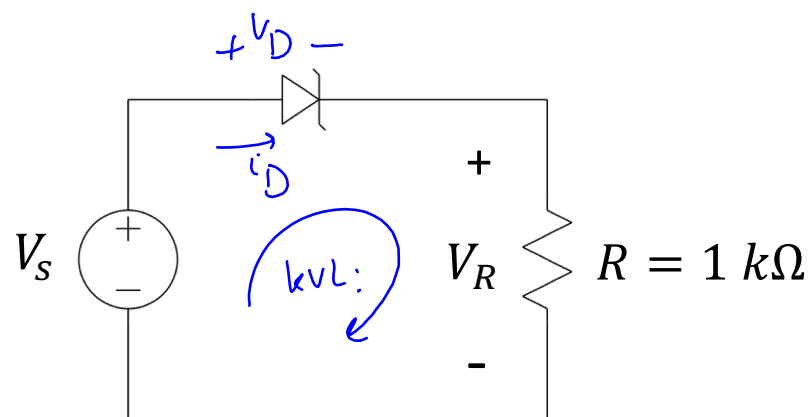In the following circuit, find V_R for $V_S = +5\text{ V}$ and $V_S = -5\text{ V}$. Assume $V_Z = 3\text{ V}$ and $V_{D0} = 0.7\text{ V}$.



$$V_S = 5\text{ V}$$

Assume diode is in Zener

$$V_D = -V_Z, \quad i_D \leq 0$$

$$\text{kVL: } V_S = V_D + R i_D$$


$$5 = -3 + 1\text{ k}\Omega \times i_D \rightarrow i_D = 8\text{ mA} > 0$$

Assumption was wrong.

Lecture 3 reading quiz

In the following circuit, find V_R for $V_S = +5\text{ V}$ and $V_S = -5\text{ V}$. Assume $V_Z = 3\text{ V}$ and $V_{D0} = 0.7\text{ V}$.

$$V_S = 5\text{ V}$$

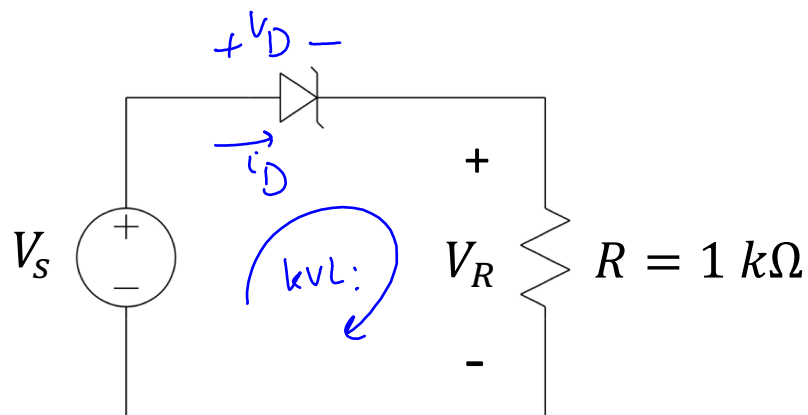

Assume the diode is ON,

$$V_D = V_{D0} \text{ and } i_D \geq 0$$

Assumption was correct

$$\text{KVL: } V_S = V_D + R i_D \longrightarrow 5 = 0.7 + 1\text{ k}\Omega \times i_D \longrightarrow i_D = 4.3\text{ mA} > 0$$
$$V_R = 1\text{ k}\Omega \times i_D = 4.3\text{ V}$$

For $V_S = -5V$,

Assume diode is in Zener region:


$$V_D = -V_Z, \quad i_D \leq 0$$

$$\text{KVL: } V_S = V_D + 1k\Omega \times i_D$$

$$-5V = -3V + 1k\Omega \times i_D \rightarrow i_D = -2mA < 0$$

Assumption was correct and the diode is in the Zener region.

$$V_R = 1k\Omega \times i_D = -2V$$

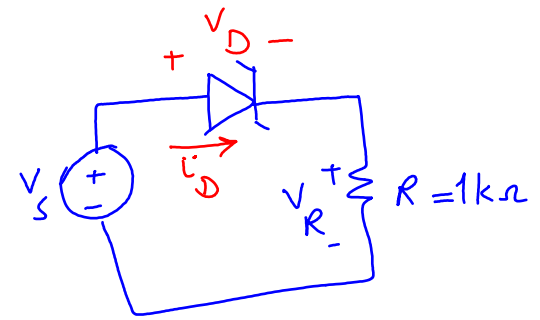

What if we assumed the diode was off for $V_S = -5V$


$$\text{Diode off: } i_D = 0, -3V < V_D < 0.7V$$

$$V_S = V_D + R i_D \rightarrow V_S = V_D = -5V < -3V \Rightarrow \text{Assumption was wrong.}$$

Discussion question 1.

In the below circuit find the range of v_i for which D_1 is ON and D_2 is in the Zener region. Calculate v_{out} .

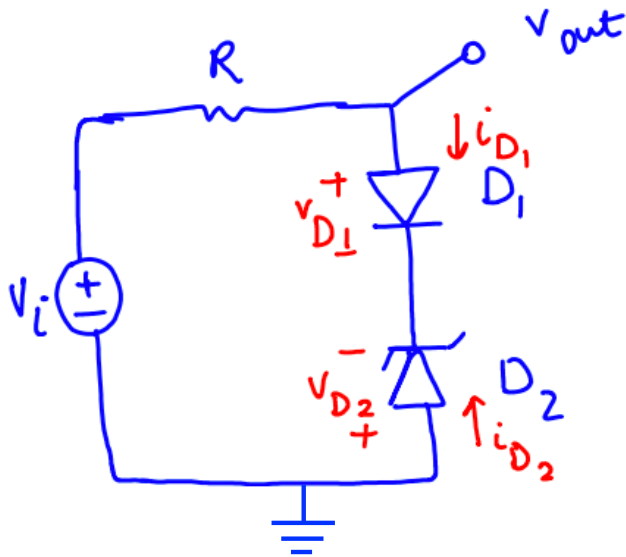Are there any other possible states at which D_1 and D_2 can operate?
Assume $V_{D0} = 0.7\text{ V}$ and $V_Z = 5\text{ V}$.




Extra activity: find v_{out} for all ranges of v_i (solve the circuit parametrically).

Discussion question 1.

$$V_{D_0} = 0.7V, \quad V_Z = 5V$$

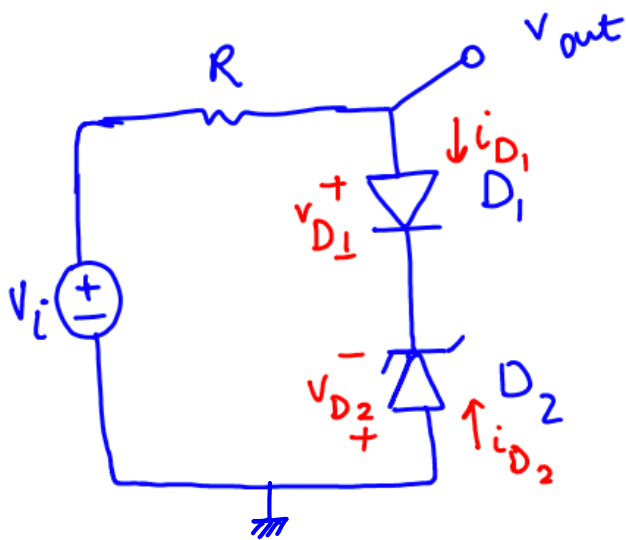Solve the following circuit parametrically.



D_1	D_2	
ON	ON	X
ON	OFF	X Diodes are in series
ON	Zener	✓
OFF	ON	X Diodes are in series
OFF	OFF	✓
OFF	Zener	X Diode are in series

D_1 and D_2 cannot be forward biased and ON, because:

$$D_1 \text{ ON} \rightarrow i_{D_1} \geq 0, \quad V_{D_1} = 0.7V$$


$$D_2 \text{ ON} \rightarrow i_{D_2} \geq 0, \quad V_{D_2} = 0.7V$$

KCL: $i_{D_1} = -i_{D_2} \Rightarrow$ both can't be ON at the same time.

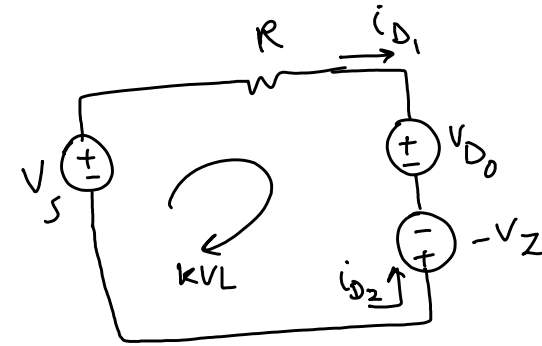(A) When D_1 is ON & D_2 is in Zener:

$$D_1 \text{ ON} \rightarrow i_{D_1} \geq 0 \text{ \& } V_{D_1} = V_{D_0} = 0.7 \text{ V}$$

$$D_2 \text{ Zener} \rightarrow i_{D_2} \leq 0 \text{ \& } V_{D_2} = -V_Z = -5 \text{ V}$$




$$\text{KVL: } i_{D_1} = \frac{V_S - V_{D_0} - V_Z}{R} \geq 0 \rightarrow V_S \geq V_Z + V_{D_0} \rightarrow V_S \geq 5.7 \text{ V}$$


For $V_S \geq 5.7 \text{ V} \rightarrow D_1$ is ON and D_2 is in Zener region

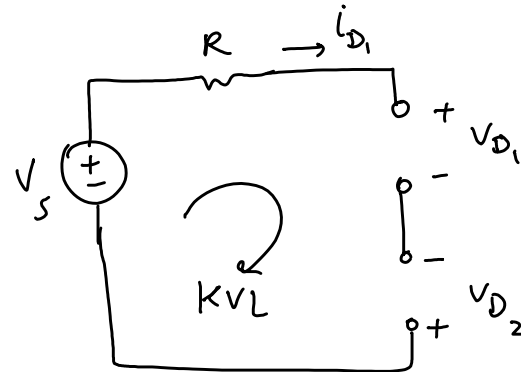(B) When D_1 and D_2 are off:

$$D_1 \text{ off} \rightarrow i_{D_1} = 0 \text{ \& } V_{D_1} < V_{D_0}$$

$$D_2 \text{ off} \rightarrow i_{D_2} = 0 \text{ \& } -V_Z < V_{D_2} < V_{D_0}$$



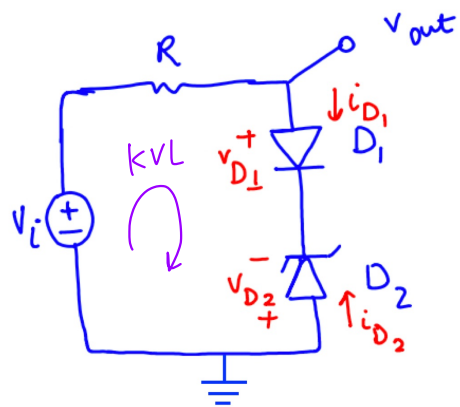

When D_1 and D_2 are off:

$$D_1 \text{ off} \rightarrow i_{D_1} = 0 \text{ \& } v_{D_1} < V_{D_0}$$

$$D_2 \text{ off} \rightarrow i_{D_2} = 0 \text{ \& } -V_Z < V_{D_2} < V_{D_0}$$

$$\text{KVL: } v_i = R \times i_{D_1} + v_{D_1} - v_{D_2} \Rightarrow v_i = v_{D_1} - v_{D_2}$$

$$-V_Z < V_{D_2} < V_{D_0} \rightarrow -V_{D_0} < -V_{D_2} < V_Z$$


also $v_{D_1} < V_{D_0}$. v_{D_1} in this range can have any value from $-\infty$ up to V_{D_0} .

As a result, we can write $-\infty < v_{D_1} < V_{D_0}$ * note: this is a theoretical range. There is a limit on negative v_D values.

$$\Rightarrow \begin{aligned} -V_{D_0} < -V_{D_2} < V_Z \\ -\infty < v_{D_1} < V_{D_0} \end{aligned} \rightarrow -\infty < \boxed{v_{D_1} - v_{D_2}} < V_Z + V_{D_0} \text{ or } v_i < V_Z + V_{D_0}$$

Clicker question 1:

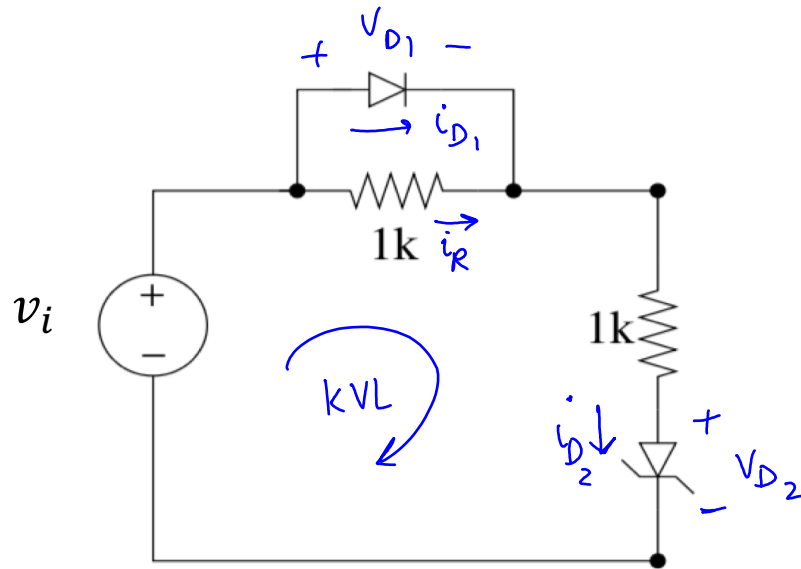What is the range of v_i for which both diodes are ON? Assume $V_Z = 4\text{ V}$ and $V_{D0} = 0.7\text{ V}$.



$$D_1 \text{ ON} : \begin{aligned} i_{D1} &\geq 0 \\ v_{D1} &= V_{D0} \end{aligned}$$


$$D_2 \text{ ON} : \begin{aligned} i_{D2} &\geq 0 \\ v_{D2} &= V_{D0} \end{aligned}$$

A. $v_i \geq 2.1\text{ V}$

B. $v_i \geq 1.4\text{ V}$

C. $v_i \geq 0.7\text{ V}$

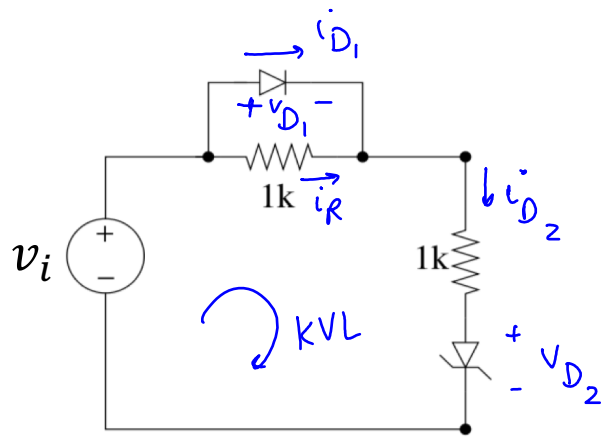D. Both diodes cannot be ON simultaneously.



KCL: $i_{D_2} = i_{D_1} + i_R$, $i_{D_1} \geq 0$ and $i_{D_2} \geq 0$

Both current inequalities must be true when D_1 and D_2 are ON.

$$i_R = \frac{v_{D_1}}{1k} = \frac{0.7V}{1k\Omega} = 0.7mA$$

$$i_{D_2} = i_{D_1} + 0.7mA$$

KVL: $v_i = v_{D_1} + 1k \times i_{D_2} + v_{D_2} \rightarrow v_i = 0.7V + 1k\Omega \times (i_{D_1} + 0.7mA) + 0.7V$

$$v_i = 2.1V + 1k\Omega \times i_{D_1} \rightarrow i_{D_1} = \frac{v_i - 2.1V}{1k\Omega} \geq 0 \rightarrow v_i \geq 2.1V$$