

PP Phasors 022


Unlimited Attempts.

$$i_S(t) = -15 \cdot \sin(10^6 t) \text{ A}$$

Find the Norton equivalent model
between a and b, in phasor notation:

$$\mathbf{I}_N = a + jb$$

$$\mathbf{Z}_N = c + jd$$

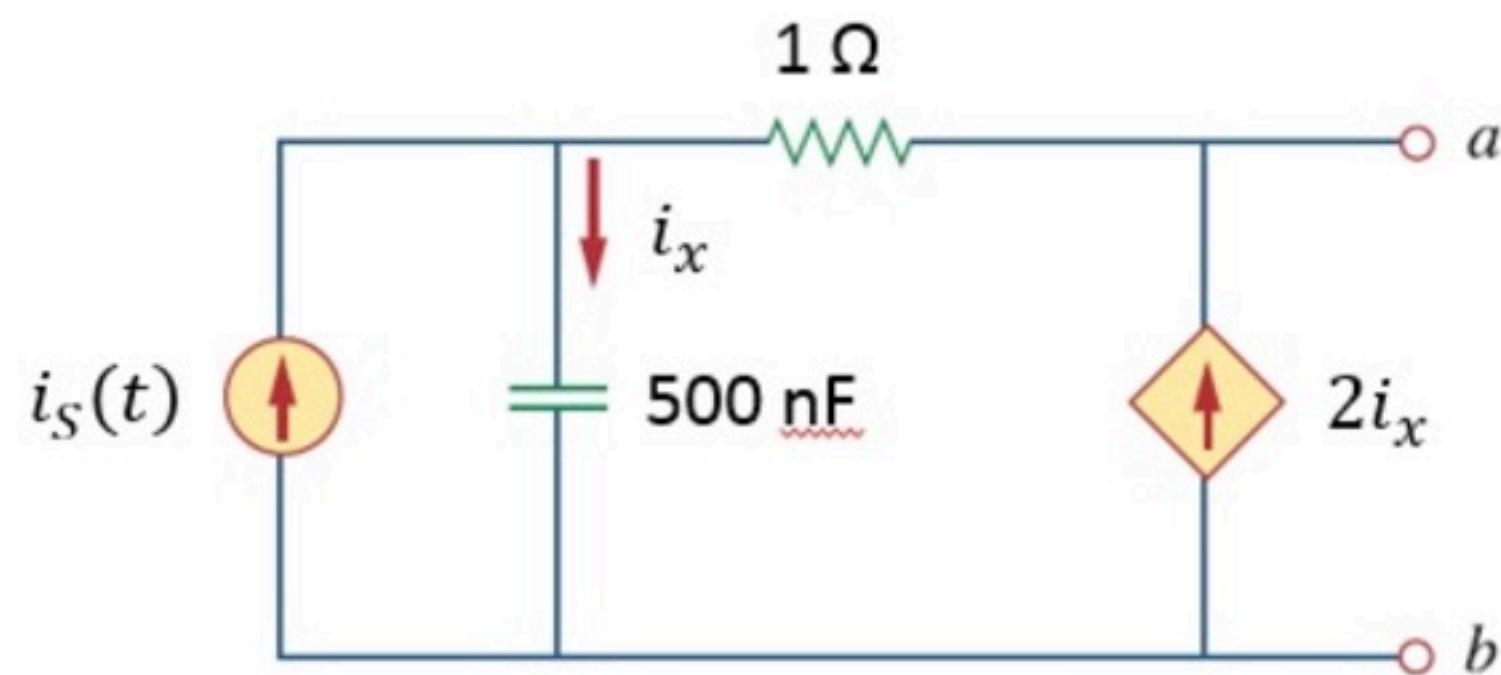

Note: This phasor Norton model is only valid for the particular frequency of the source (in this case, $\omega = 10^6 \text{ rad/s}$).

Given Variables:

...

Calculate the following:

a (A) :

-6



b (A) :

18



c (ohm) :

-1



d (ohm) :

2



Hint: Use a test voltage or current to find \mathbf{Z}_N .