

ECE 65: Components & Circuits Lab

Lecture 3

Operational Amplifier limitations


Reference notes: sections 7.5

Sedra & Smith (7th Ed): sections 2-2.3

Saharnaz Baghdadchi

Course map

7. Operational amplifiers

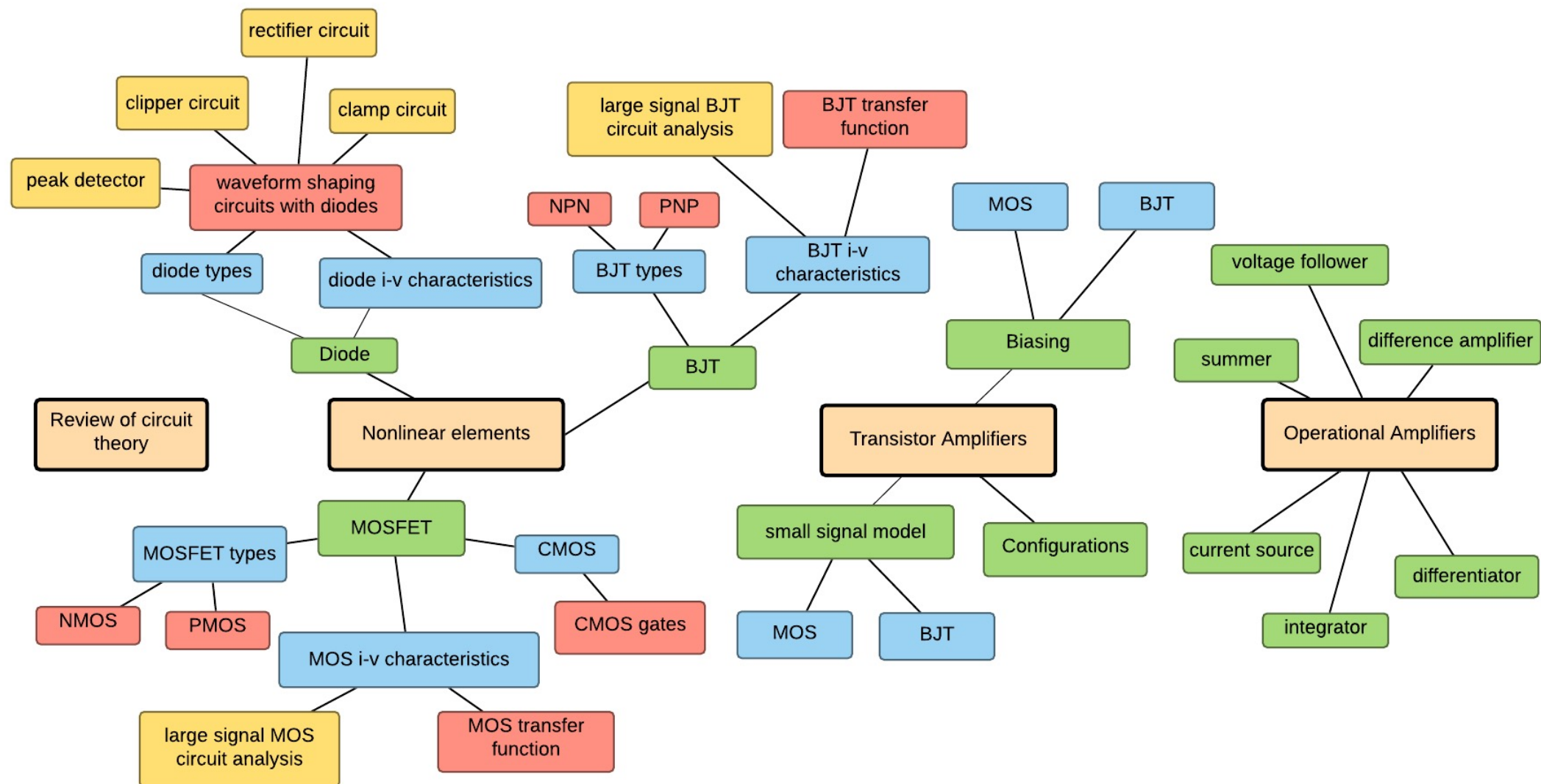

Voltage-supply limit or Saturation

As we saw before, the maximum output voltage of op-amps is limited by the positive and negative voltage sources (V_{S+} and V_{S-}) used to power up the op-amp chip.

$$V_{S-} < V_o < V_{S+}$$

$$V_{sat-} \leq V_o \leq V_{sat+}$$


$$V_{sat+} = 14V$$

$$V_{sat-} = -14V$$

Assume an ideal op-amp $\Rightarrow i_+ = i_- = 0$

Because of negative feedback: $v_+ = v_-$
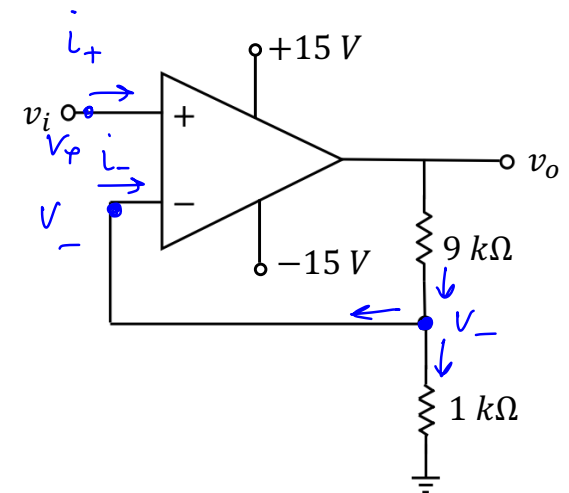
$$\text{here, } v_+ = v_i, \quad \frac{v_-}{1k\Omega} = \frac{v_o - v_-}{9k\Omega} \Rightarrow v_o = 10 v_- \Rightarrow \boxed{v_o = 10 v_i}$$



Voltage-supply limit or Saturation

As we saw before, the maximum output voltage of op-amps is limited by the positive and negative voltage sources (V_{S+} and V_{S-}) used to power up the op-amp chip.


$$V_{S-} < V_o < V_{S+}$$

$$V_{sat-} \leq V_o \leq V_{sat+}$$

$$V_{sat+} = 14V$$



$$V_{sat-} = -14V$$
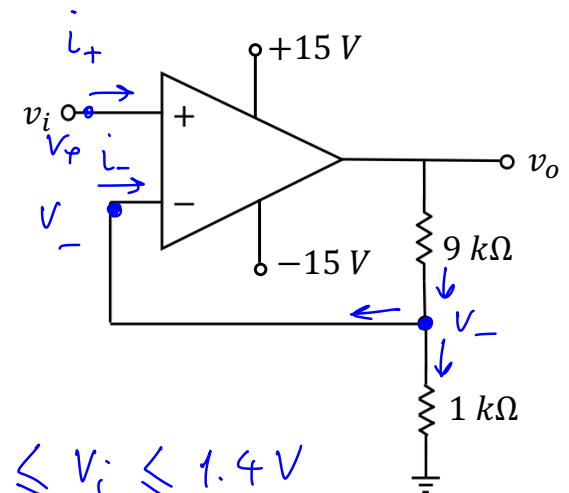
$$V_o = 10 V_i \Rightarrow -\frac{14V}{10} \leq V_i \leq \frac{14}{10} V \Rightarrow -1.4V \leq V_i \leq 1.4V$$





Voltage-supply limit or Saturation

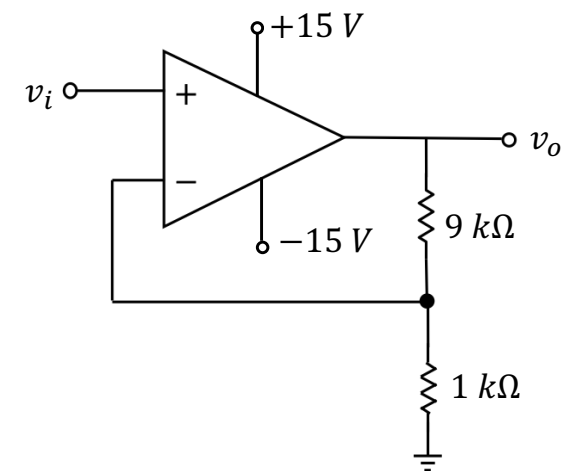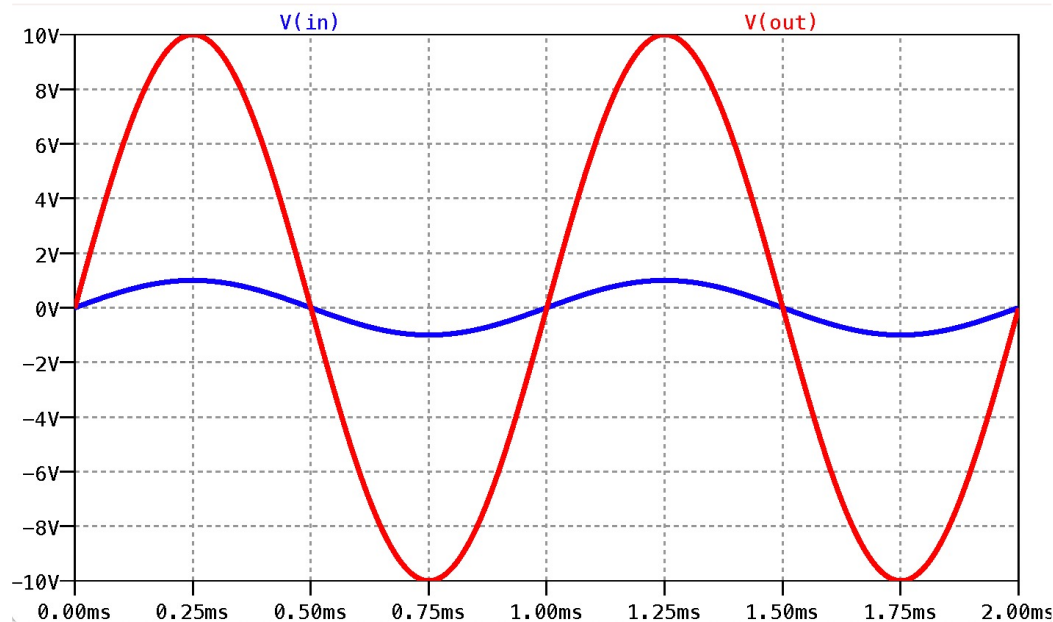As we saw before, the maximum output voltage of op-amps is limited by the positive and negative voltage sources (V_{S+} and V_{S-}) used to power up the op-amp chip.



Voltage-supply limit or Saturation

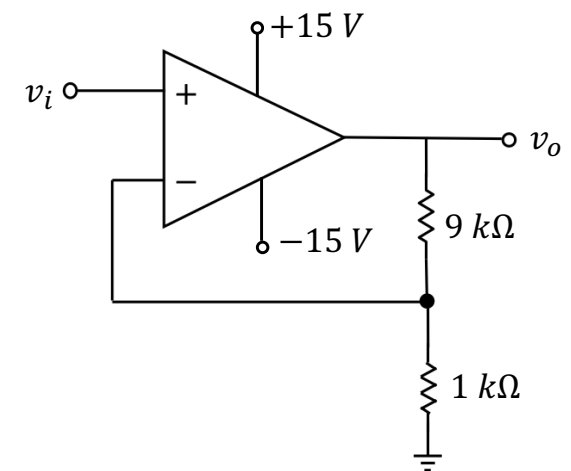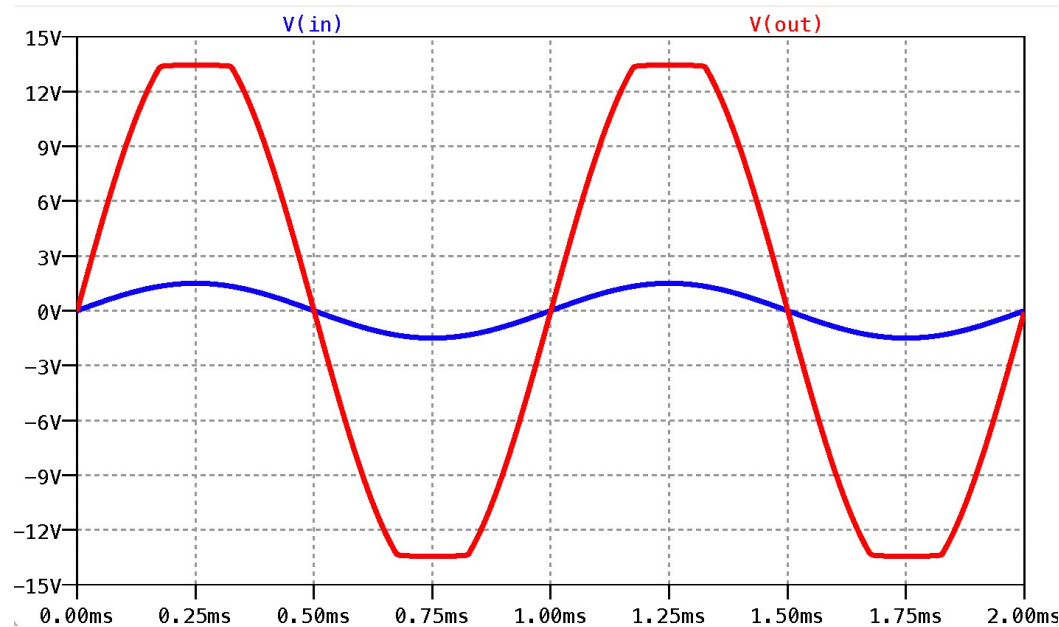
As we saw before, the maximum output voltage of op-amps is limited by the positive and negative voltage sources (V_{S+} and V_{S-}) used to power up the op-amp chip.



Maximum Output Current



The output current of an op-amp is limited to a specified maximum value.

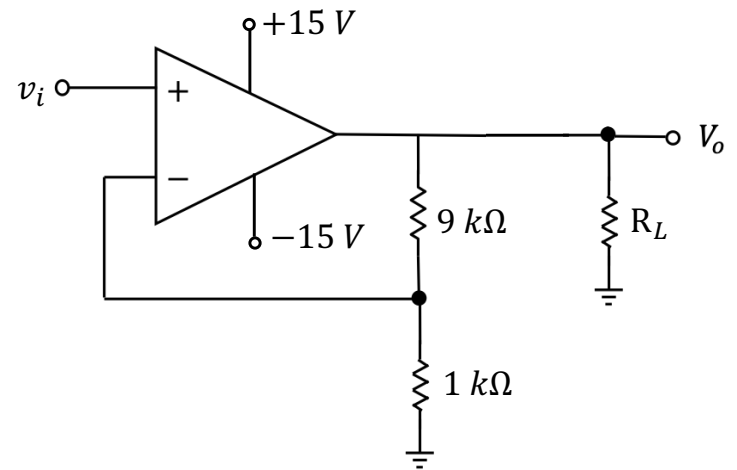For example, in the 741 op-amp, the maximum output current is $\pm 20\text{mA}$.



Maximum Output Current

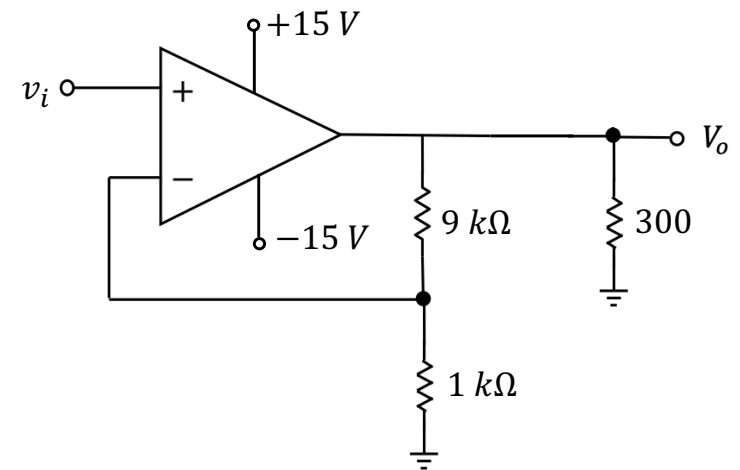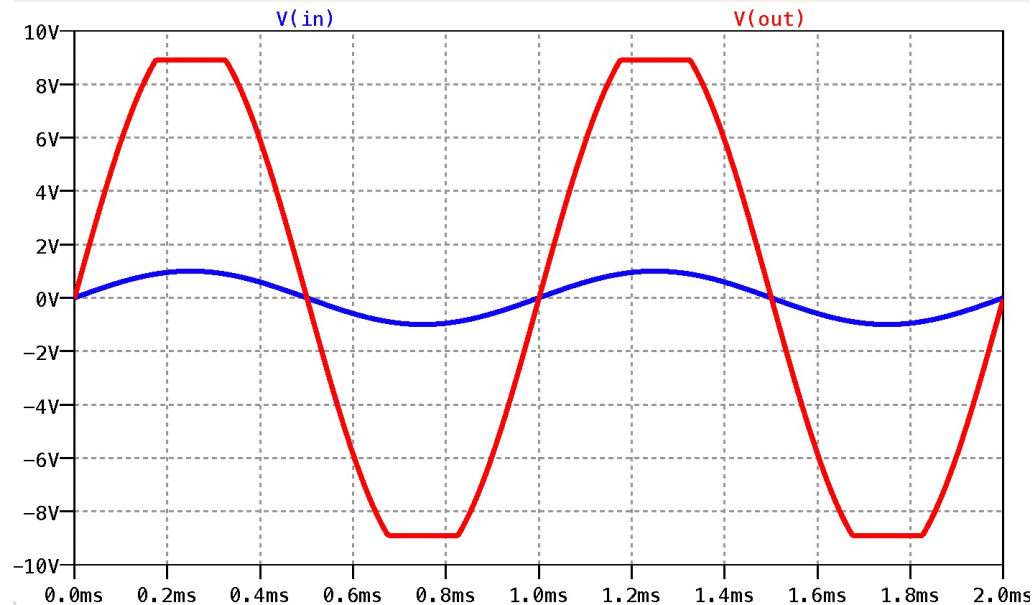If the circuit requires a current larger than the maximum output current, in either direction, the output voltage will saturate at a level corresponding to the maximum allowed output current.



Maximum Output Current - Example


The following op-amp circuit is fed with a low-frequency sinusoidal signal with peak amplitude of 1 V . The maximum output current is $\pm 20\text{ mA}$. If $R_L = 1\text{ k}\Omega$, specify and sketch the output voltage.

assume an ideal op-amp: $i_+ = i_- = 0 \Rightarrow i_1 = i_2$

KCL: $i_o = i_1 + i_L$

$$i_o = \frac{V_o}{9\text{ k}\Omega + 1\text{ k}\Omega} + \frac{V_o}{R_L}$$
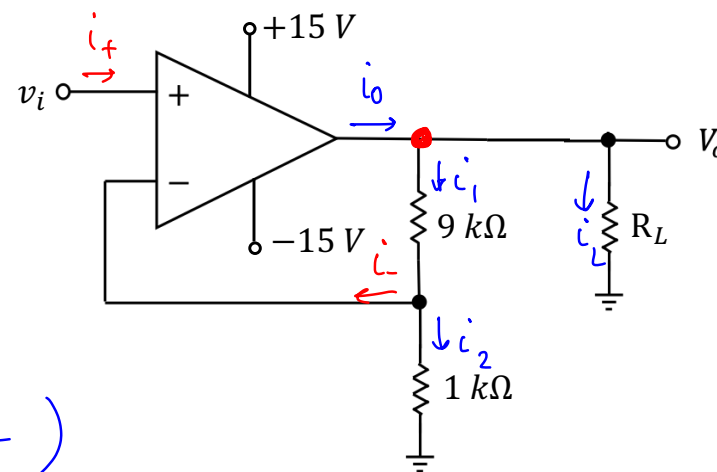
$$i_o = \frac{V_o}{10\text{ k}\Omega} + \frac{V_o}{1\text{ k}\Omega} = V_o \left(\frac{1}{10\text{ k}\Omega} + \frac{1}{1\text{ k}\Omega} \right)$$
$$= V_o \times 1.1$$



Maximum Output Current - Example

The following op-amp circuit is fed with a low-frequency sinusoidal signal with peak amplitude of 1 V . The maximum output current is $\pm 20\text{ mA}$. If $R_L = 1\text{ k}\Omega$, specify and sketch the output voltage.

assume an ideal op-amp: $i_+ = i_- = 0 \Rightarrow i_1 = i_2$



$$i_o = V_o \times 1.1$$

Assume linear amplification:

$$\frac{V_o}{V_i} = 10 \text{ V/V} \Rightarrow \text{if } V_{i_{\max}} = 1\text{ V} \Rightarrow V_{o_{\max}} = 10\text{ V}$$


$$\Rightarrow i_{o_{\max}} = 10 \times 1.1 = 11\text{ mA} < +20\text{ mA}$$

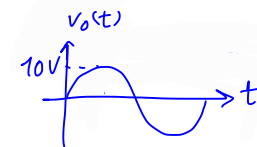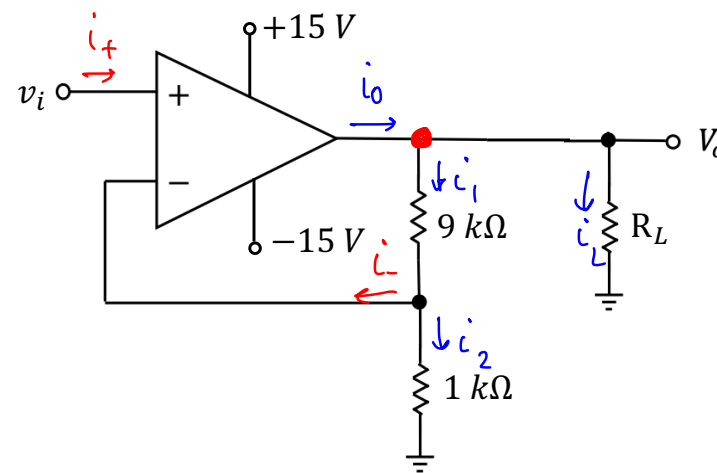\Rightarrow We are not limited by the maximum output current $\Rightarrow V_{o_{\max}} = 10\text{ V}$




Lecture 3 reading quiz.

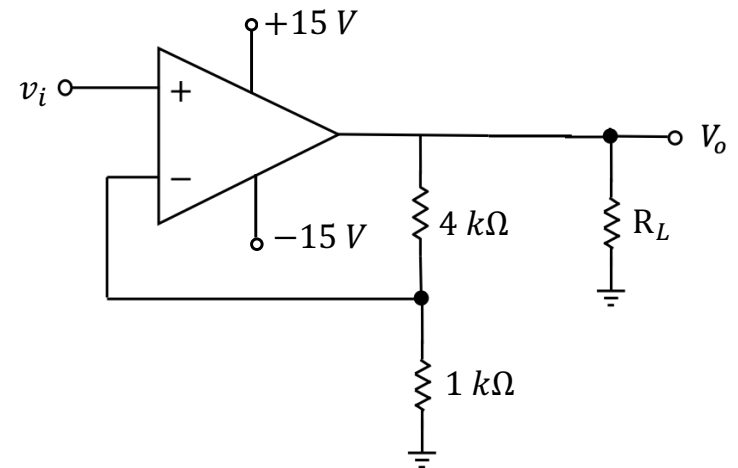The following op-amp circuit is fed with a low-frequency sinusoidal signal with the peak amplitude of V_P . The output saturation voltage is $\pm 13\text{ V}$, and the maximum output current is $\pm 20\text{ mA}$. If $R_L = 0.5\text{ k}\Omega$, find the maximum value of V_P for which an undistorted sinusoidal signal is obtained at the output?



Discussion question 1.

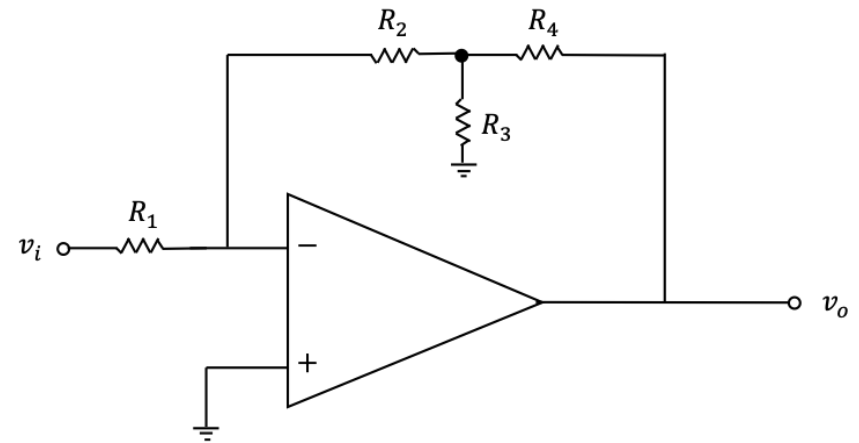What is v_o/v_i in this op-amp circuit? Assume an ideal op-amp.




Discussion question 2.

The following circuit uses a $10\text{ k}\Omega$ potentiometer to obtain an adjustable gain amplifier.

- a) Derive an expression for the gain as a function of the potentiometer setting x .
- b) What is the range of the gain obtained?
- c) Show how to add a fixed resistor so that the gain range can be 1 to 11 V/V. What is the value of that resistor?


Assume an ideal op-amp.

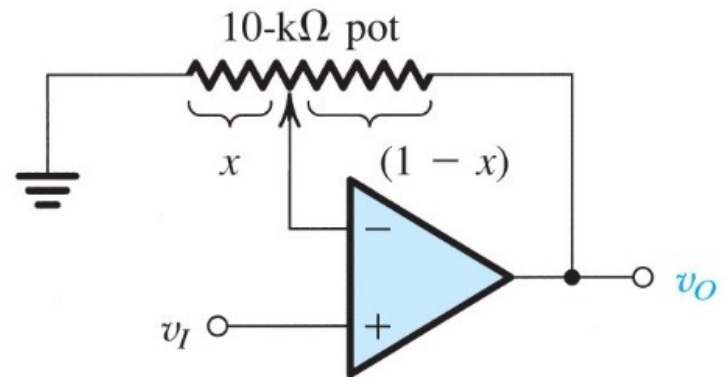

Discussion question 2.


- a) Derive an expression for the gain as a function of the potentiometer setting x .

Assume an ideal op-amp.

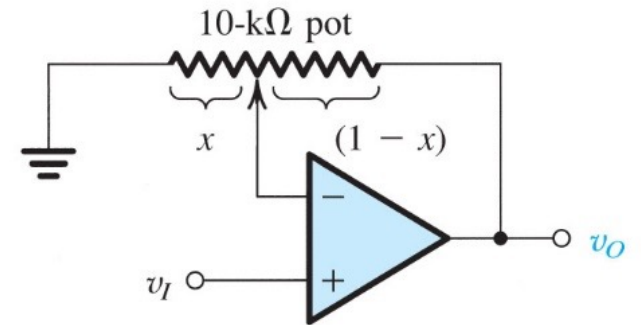

Discussion question 2.

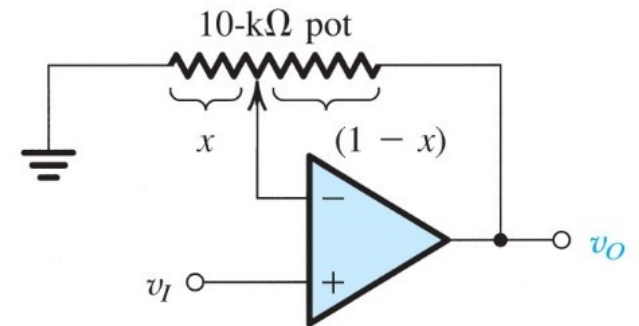- a) What is the range of the gain obtained?
Assume an ideal op-amp.



Discussion question 2.

- a) Show how to add a fixed resistor so that the gain range can be 1 to 11 V/V. What is the value of that resistor?

Assume an ideal op-amp.

