

ECE 35, Spring 2020

Quiz 1

/ 10

Last name


First + middle
name(s)

PID

(1) (5 points)

In the problem below, both the volt meter and the ammeter are ideal.

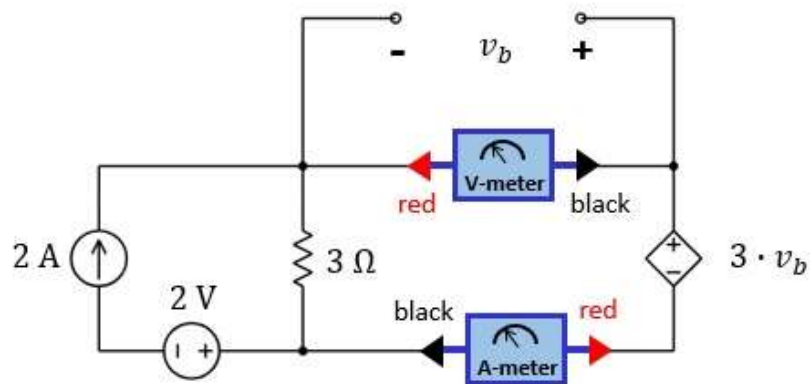- (a) What is the reading X of the ammeter?
- (b) What is the reading Y of the volt meter?
- (c) What is the power P_1 supplied by the current source?



(2) (5 points)

Consider the circuit below.

- (a) Find v_x .
- (b) What is the total power P_1 received by all resistors combined?
- (c) If we flip the direction of the voltage source, what is the power P_2 received by resistor R_1 ?

